

ECE 321 - Quiz #2 - Name _____

Sensors & Filters

Calculators, internet, Matlab permitted.

1) A thermistor has a temperature-resistance relationship of (Digikey part number 495-75201-ND) where T is the temperature in degrees C.

$$R = 10,000 \cdot \exp\left(\frac{3980}{T+273} - \frac{3980}{298}\right) \Omega$$

Design a circuit which outputs

- 0V at 25C and
- 10V at 100C

Note: A linearizing circuit isn't required.

Let $R = 2500$

25C ($Y = 0V$)

- $R = 10k$ Ohms
- $X = 8.000V$

100C: ($Y = 10V$)


- $R = 681.9$ Ohms
- $X = 2.168V$

As X goes down, Y goes up. Connect to the minus input

$$gain = \left(\frac{10V-0V}{8V-2.168V}\right) = 1.715$$

$Y = 0V$ when $X = 8.00V$

Offset = 8.00V

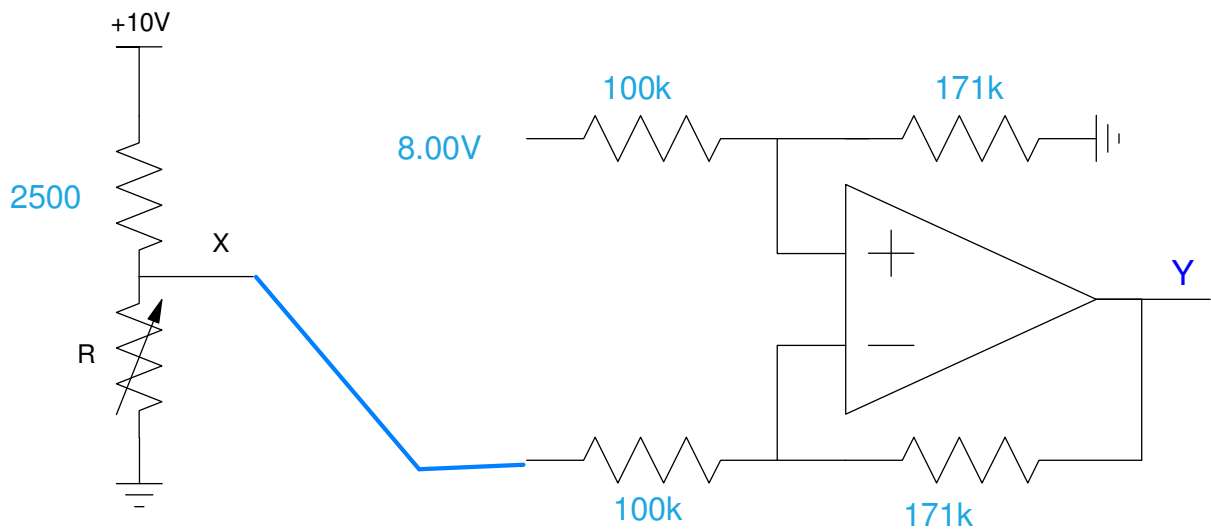

2) A thermistor has a temperature-resistance relationship of

$$R = 10,000 \cdot \exp\left(\frac{3980}{T+273} - \frac{3980}{298}\right) \Omega$$

where T is the temperature in degrees C. Assume the thermistor is used with a voltage divider so that

$$X = \left(\frac{R}{R+400}\right) 10V$$

2a) Determine the least squares curve fit for temperature as

$$T = aX + b$$



Assume the same temperature range as problem #1 (your answers will vary depending upon what temperature range you choose)

```
T = [25:0.1:100]';
R = 10000 * exp(3980 ./ (T+273) - 3980/298);
X = R ./ (R+400) * 10;
B = [X, X.^0];
A = inv(B'*B) * B'*T
```

```
-21.7887
243.4206
```

```
plot(X, T, X, B*A, 'r')
```

$$T = -21.7887X + 243.42$$

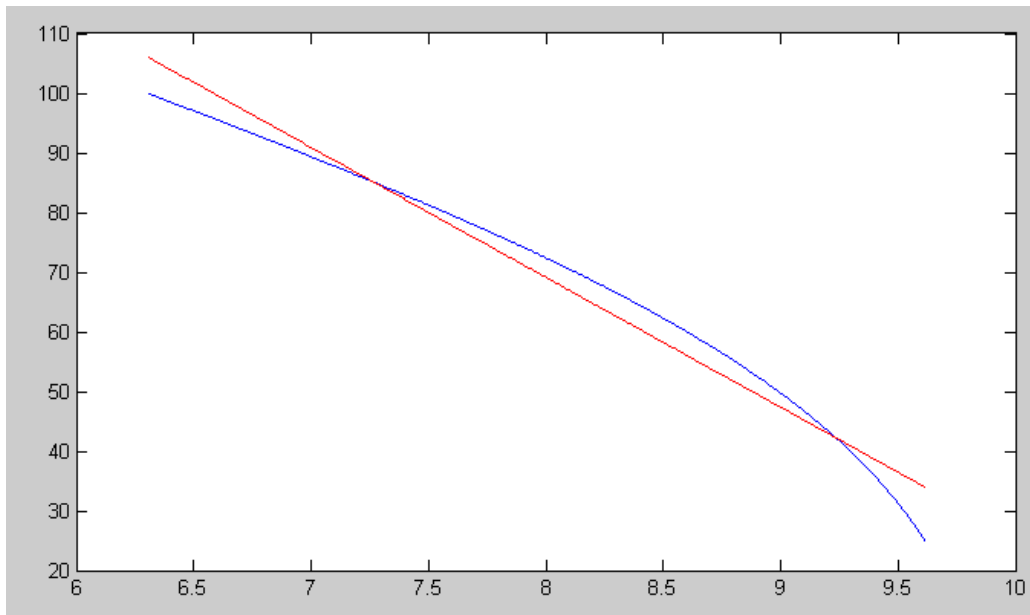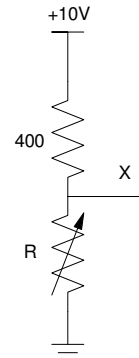

2b) Determine the least squares curve fit for temperature as

$$T = aX^3 + bX^2 + cX + d$$


Again, assuming (25C, 100C), (answers vary depending upon the temperature range)

```
>> B = [X.^3, X.^2, X, X.^0];  
>> A = inv(B'*B)*B'*T
```

```
-1.7333  
37.8345  
-290.5995  
863.6654
```

```
>> plot(X,T,X,B*A,'r')
```
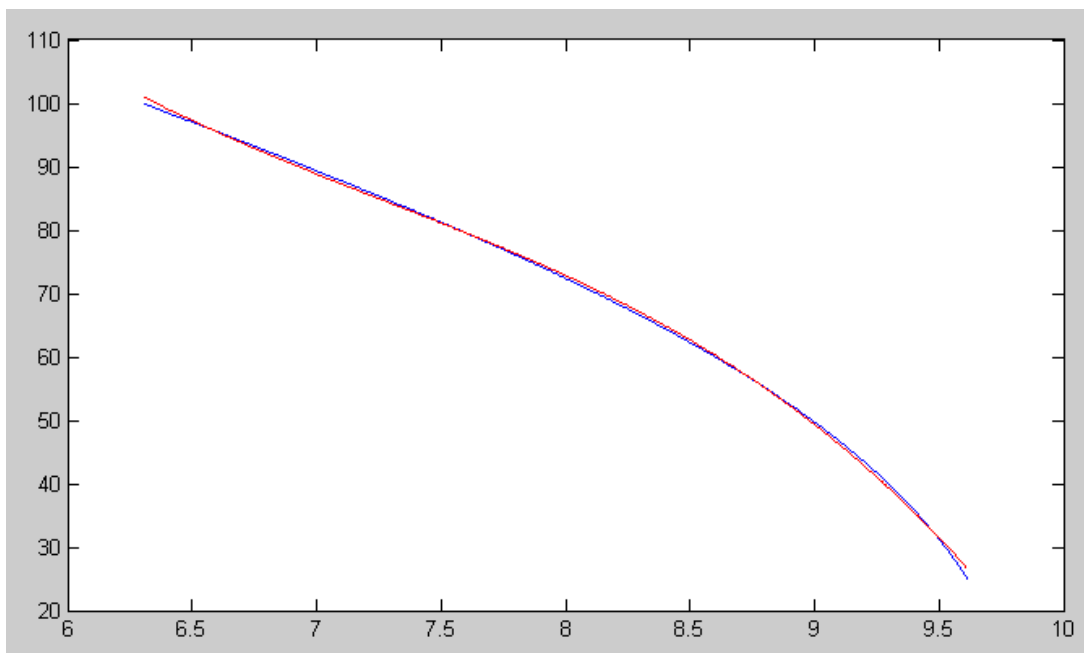
$$T \approx -1.733X^3 + 37.82X^2 - 280.599X + 863.66$$



3) X and Y are related by the following transfer function

$$Y = \left(\frac{50}{(s+5)(s+7)} \right) X$$

3a) What is the differential equation relating X and Y?

$$(s+5)(s+7)Y = (50)X$$

$$(s^2 + 12s + 35)Y = 50X$$

$$y'' + 12y' + 35y = 50x$$

3b) Determine y(t) assuming

$$x(t) = 4 + 5 \cos(6t) + 7 \sin(6t)$$

Use superposition and phasor analysis

$$x(t) = 4$$

$$s = 0$$

$$X = 4 + j0$$

$$Y = \left(\frac{50}{(s+5)(s+7)} \right)_{s=0} (4 + j0)$$

$$Y = 5.714$$

$$y(t) = 5.714$$

$$x(t) = 5 \cos(6t) + 7 \sin(6t)$$

$$s = j6$$

$$X = 5 - j7$$

$$Y = \left(\frac{50}{(s+5)(s+7)} \right)_{s=j6} (5 - j7)$$

$$Y = -4.908 - j3.404$$

$$y(t) = -4.908 \cos(6t) + 3.404 \sin(6t)$$

The total answer is DC + AC

$$y(t) = 5.714 - 4.908 \cos(6t) + 3.404 \sin(6t)$$

4) Design a circuit to implement the following filter:

$$Y = \left(\frac{500}{(s+2)(s+10)(s+20)} \right) X$$


Use a 3-stage RC filter with a gain

$$\frac{1}{R_1 C_1} = 2 \quad R_1 = 10k \quad C_1 = 50\mu F$$

$$\frac{1}{R_2 C_2} = 10 \quad R_2 = 100k \quad C_2 = 1\mu F$$

$$\frac{1}{R_3 C_3} = 20 \quad R_3 = 1M \quad C_3 = 50nF$$

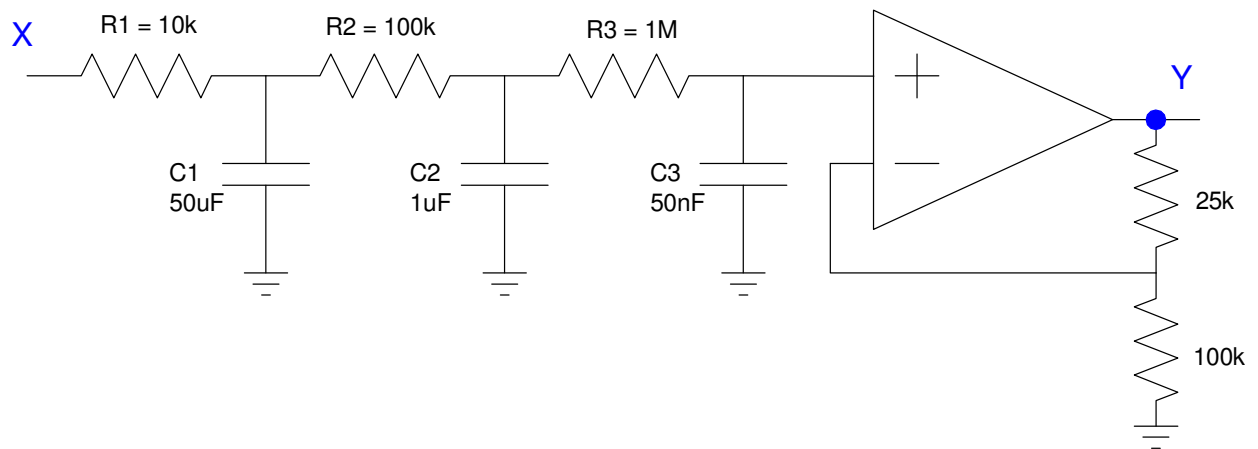The DC gain is 1.25. Add an amplifier with a gain of 1.25



5) Design a circuit to implement the following filter:

$$Y = \left(\frac{500}{(s+2)(s+3+j10)(s+3-j10)} \right) X$$

Express as

$$Y = \left(\frac{2}{s+2} \right) \left(\frac{250}{s+10.44 \angle \pm 73.3^\circ} \right)$$

$$\frac{1}{R_1 C_1} = 2 \quad \text{Let } R_1 = 10\text{k} \quad C_1 = 50\mu\text{F}$$

$$\frac{1}{R_2 C_2} = 10.44 \quad \text{Let } R_2 = 100\text{k} \quad C_2 = 958\text{nF}$$


$$3 - k = 2 \cos(73.3^\circ)$$

$$k = 2.425$$

The resulting DC gain is 2.45

The DC gain is supposed to be 2.294

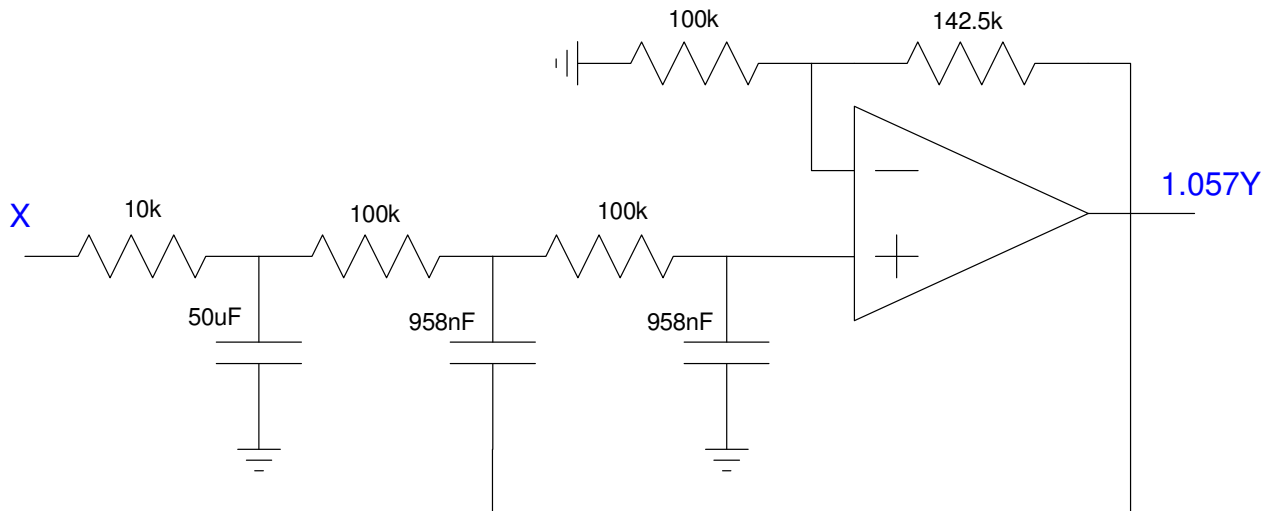Call the output 1.057Y (or reduce it by 5.7%)



6) Give the transfer function for a 6th order Butterworth filter with

- A DC gain of 1.000
- A corner at 20 rads/c

The amplitude of the poles is 20 rad/sec

The angle between poles is

$$\theta = \frac{180^\circ}{6} = 30^\circ$$

$$G(s) = \left(\frac{20^6}{(s+20\angle\pm 15^\circ)(s+20\angle\pm 45^\circ)(s+20\angle\pm 75^\circ)} \right)$$