

ECE 321 - Quiz #1 - Name _____

Op-Amp Amplifiers, Push-Pull amplifiers.

Calculators, internet, Matlab permitted.

1) Determine the voltages V1..V4

V1	V2	V3	V4
0.99995V	0.999935V	4.999875V	2.99905V
1.000V	1.000V	5.000V	3.000V

$$\left(\frac{V_1-1}{100}\right) + \left(\frac{V_1}{2,000,000}\right) = 0$$

$$\left(\frac{V_2-V_4}{200}\right) + \left(\frac{V_2}{100}\right) + \left(\frac{V_2}{2,000,000}\right) = 0$$

$$V_3 = 333333(V_1 - V_2)$$

$$\left(\frac{V_4-V_3}{200}\right) + \left(\frac{V_4-V_2}{200}\right) = 0$$

Solving in Matlab

```
-->A = [1/100+1/2e6, 0, 0, 0 ;
-->0, 1/200+1/100+1/2e6, 0, -1/200;
-->333333, -333333, -1, 0;
-->0, -1/200, -1/200, 1/200+1/200]
A =
```


```
0.0100005    0.    0.    0.
0.    0.0150005    0.    - 0.005
333333.    - 333333.    - 1.    0.
0.    - 0.005    - 0.005    0.01
```

```
-->B = [1/100;0;0;0]
B =
```

```
0.01
0.
0.
0.
```

```
-->V = inv(A) * B
V =
```
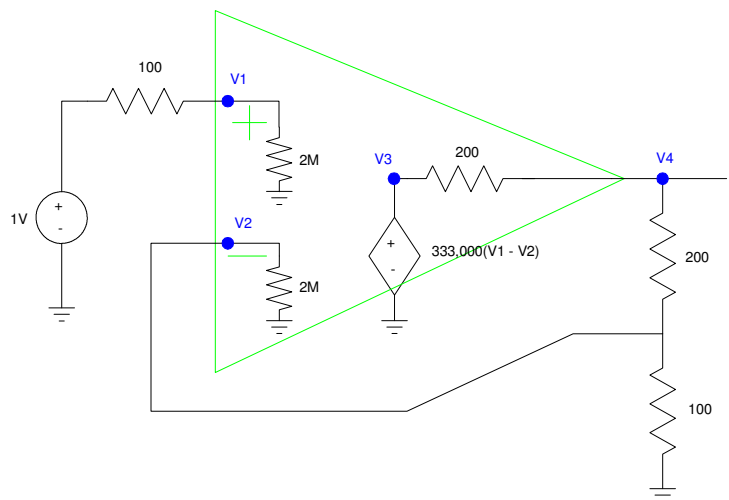
```
0.99995
0.999935
4.999875
2.999905
```




2) Assume signals A, B, C are 1Vpp signals in the range of 20-1000 Hz, capable of driving 1mA. Design an amplifier so that the output is

$$Y = 3A + 10B + 2C$$


There are many solutions. This is one

$$X = \left(\frac{3A + 10B + 2C}{15} \right)$$

$$Y = 15X$$

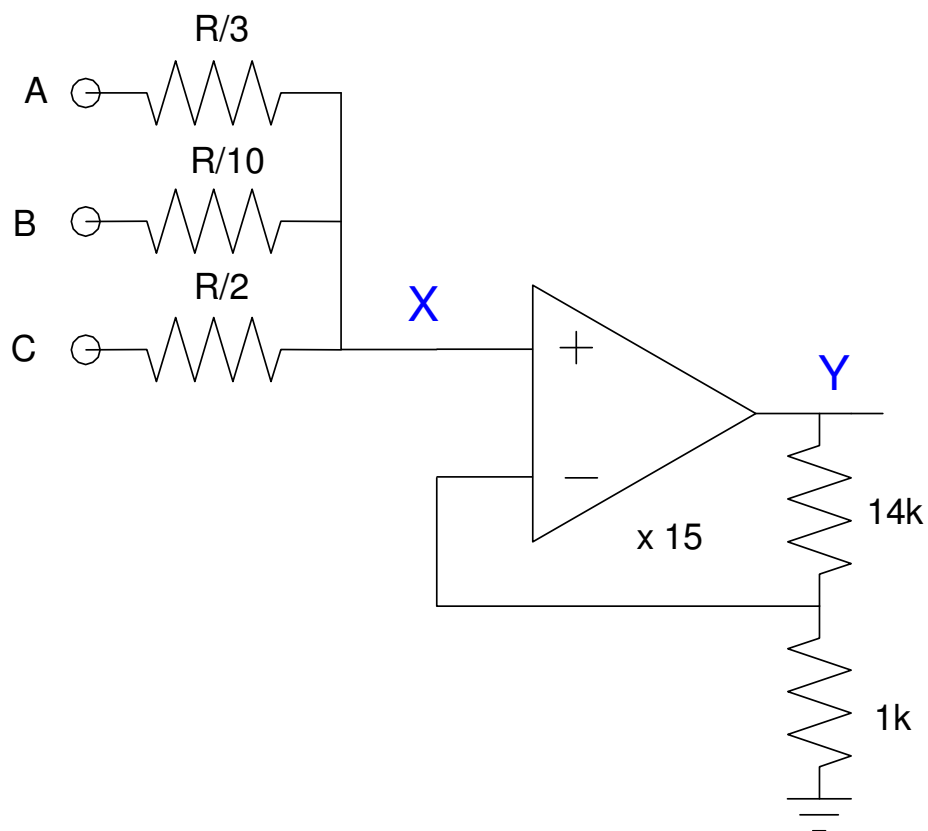

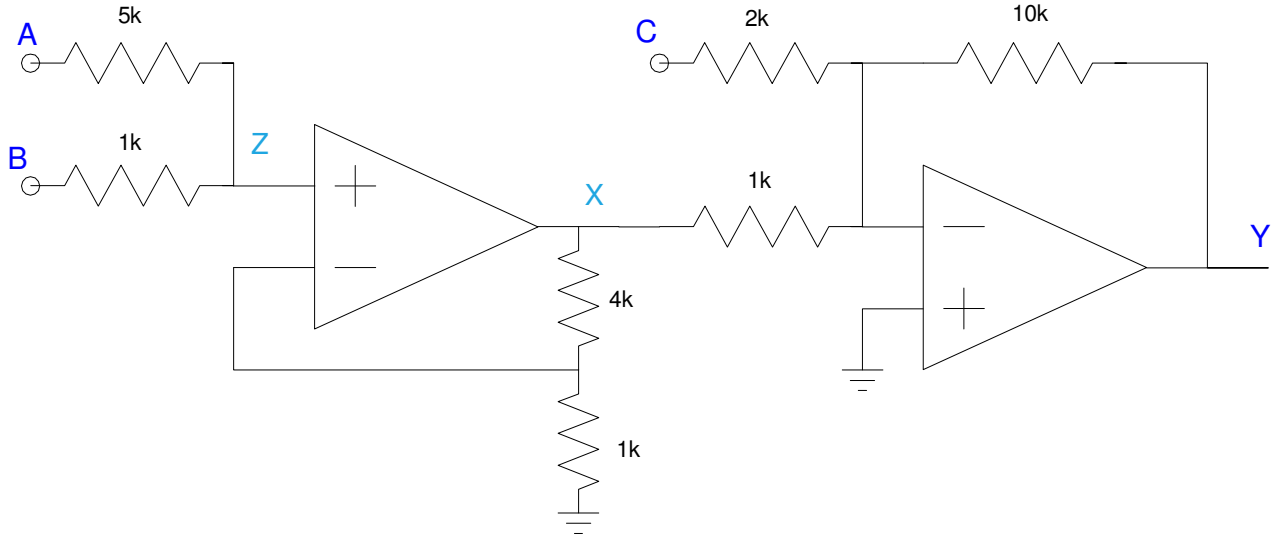3) Determine Y as a function of A, B, and C. Assume ideal op-amps



$$Z = \left(\frac{A+5B}{6} \right)$$

$$X = 5Z = \left(\frac{5}{6} \right) A + \left(\frac{25}{6} \right) B$$


$$Y = -\left(\frac{10k}{1k} \right) X - \left(\frac{10k}{2k} \right) C$$

$$Y = -\left(\frac{50}{6} \right) A - \left(\frac{250}{6} \right) B - 5C$$

$$Y = -8.333A - 41.667B - 5.00C$$

4) Determine the voltages for the following op-amp circuit. Assume ideal op-amps


V1	V2	V3	V4	V5	V6	V7
8V	6V	4V	2V	6.4V	6.4V	24V

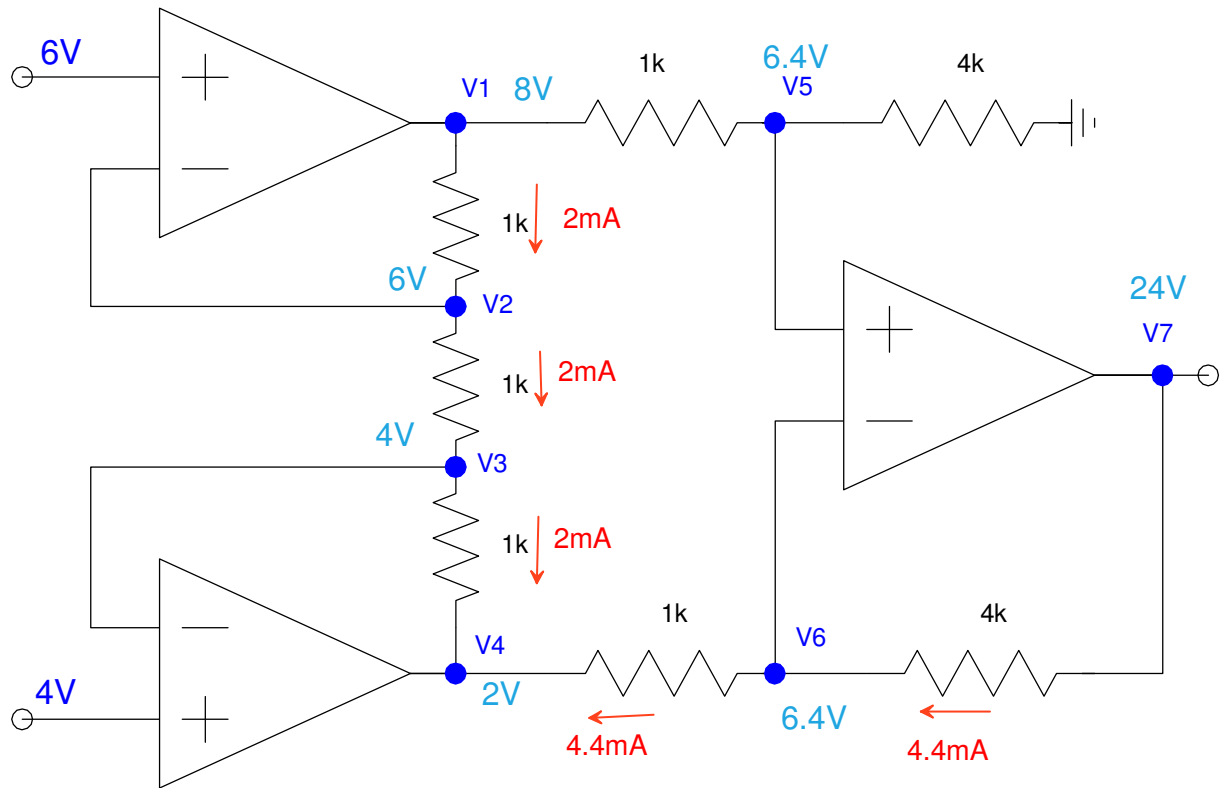

5) Determine the voltages for the following push-pull amplifier. Assume

- $|V_{be}| = 0.7V$
- $\beta = 100$

V1	V2	V3	I4	I5
8.7V	8.00V	2.00V	9.92mA	1.002A

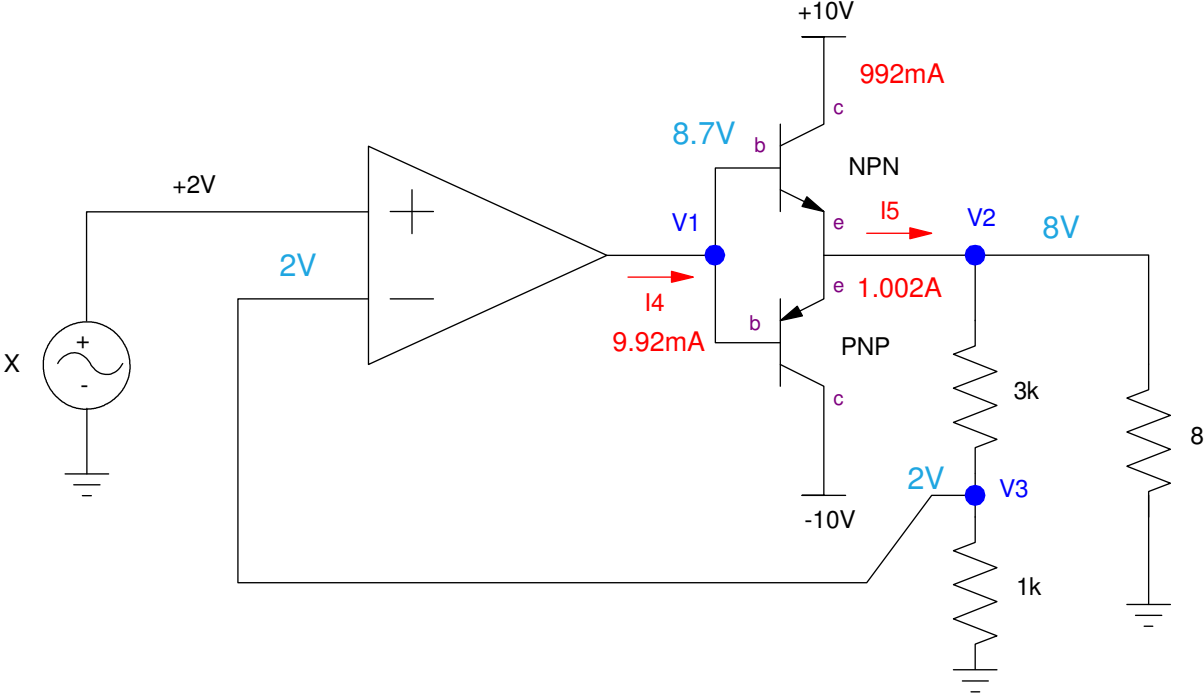

6) Determine the voltages for the following push-pull amplifier. Assume

- $|V_{be}| = 0.7V$
- $\beta = 100$

V1	V2	V3	I4	I5
5.70V	5.00V	2.00V	1.98mA	200mA

