



ECE 321 - Quiz #3 - Name _____

CE Amplifiers & 2-Port Models. Open-Book, Open Notes. Calculators and Matlab permitted.

1) Determine the Thevenin equivalent for R1 and R2 and Q-point for the following transistor circuit. Assume ideal 3904 transistors

- $\beta = 200$
- $|V_{be}| = 0.7V$



Vb (Vth)	Rb (Rth)	Vce	Ic
3.429V	2857 Ohms	1.425V	5.281mA

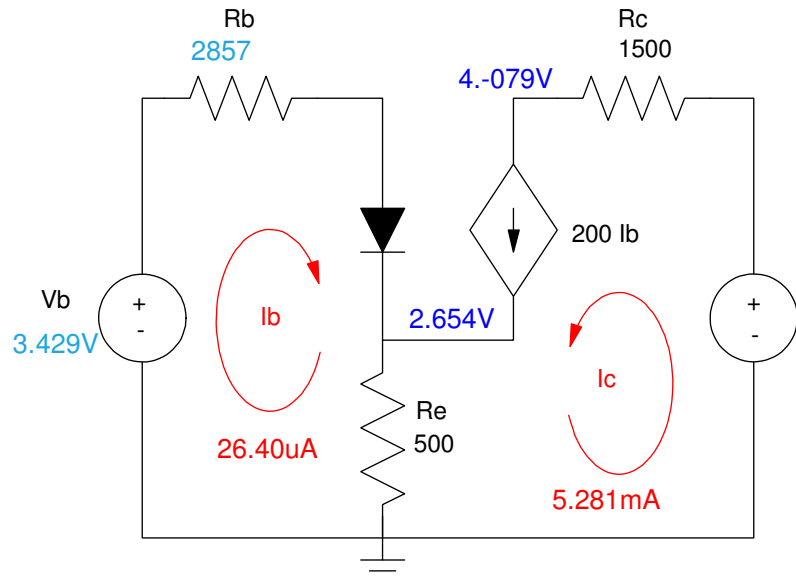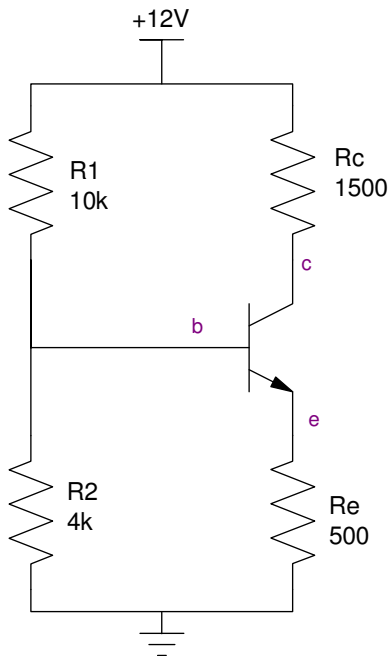

2) Determine R1 and R2 as well as Vb and Rb so that

- The Q-point is stabilized for variations in β (meaning $(1 + \beta)R_e \gg R_b$), and
- $V_{ce} = 6.00V$



R1	R2	Vb (Vth)	Rb (Rth)
12.44k	50.95k	2.355V	10k
Rb << 100.5k			

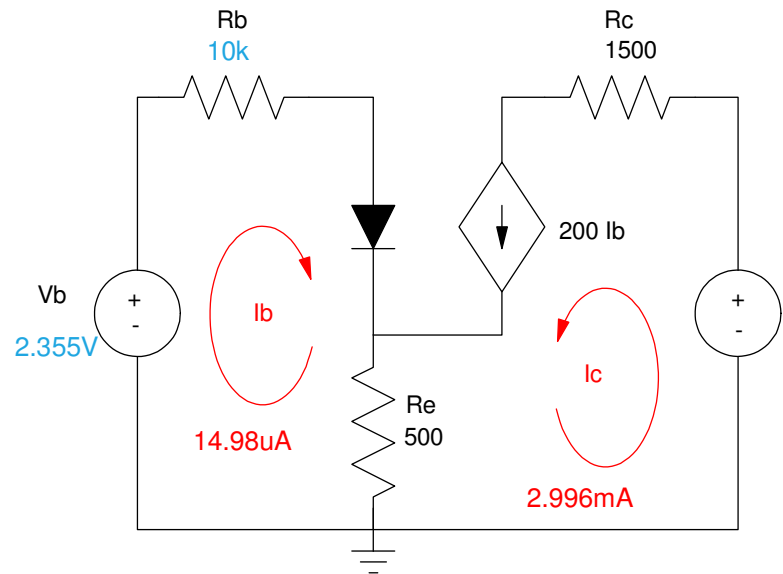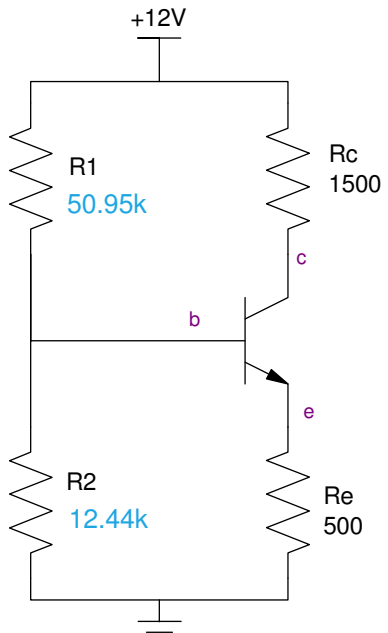

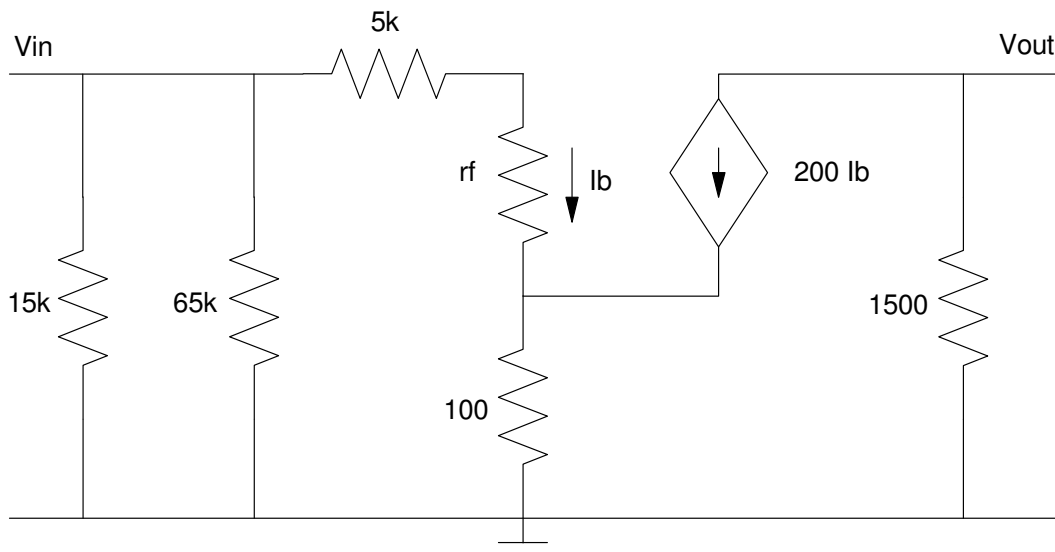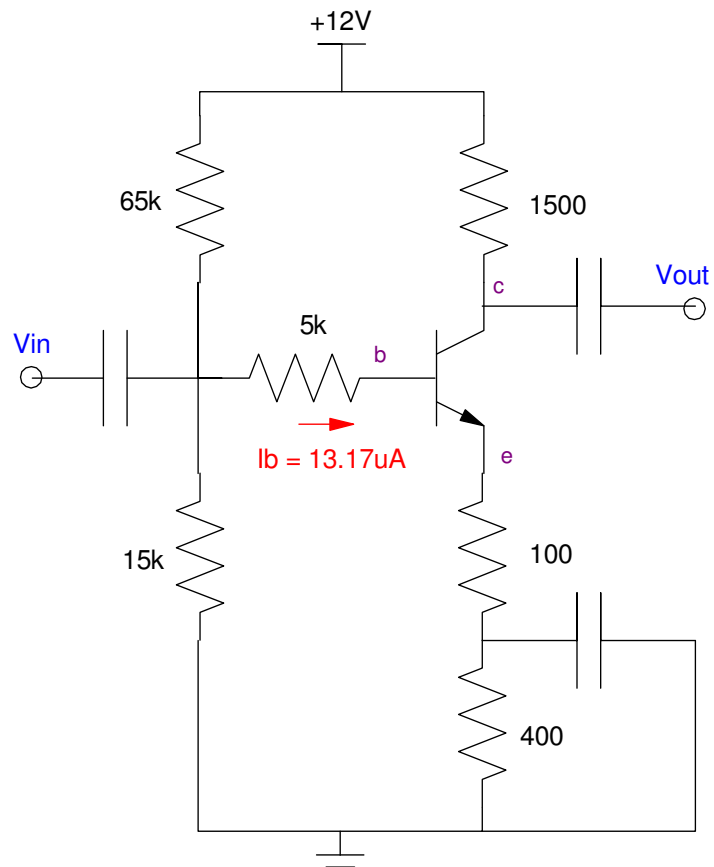3) Draw the small-signal model for the following amplifier. Assume


- $\beta = 200$
- $I_b(DC) = 13.17\mu A$

note: you don't need to find the 2-port model. That's a later quiz problem.



4) Determine the 2-port model for the following circuit

R _{in}	A _i	R _{out}	A _o
942	0.3684	1492	0.5833

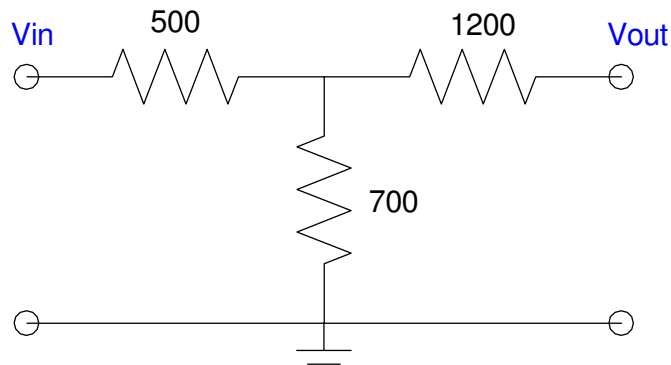

R_{in}:

- Short V_{out}
- $R_{in} = 500 + 1200 \parallel 700$

A_i:

- apply 1V at V_{out} . Measure V_{in}
- $V_{in} = 700 / (700 + 1200)$

R_{out}:


- Short V_{in}
- $R_{out} = 1200 + 500 \parallel 700$

A_o:

- Apply 1V to V_{in}
- $V_{out} = 700 / (700 + 500)$

5) Determine the 2-port model for the following circuit

R_{in}	A_i	R_{out}	A_o
24.62 Ohms	0	3733 Ohms	149.3

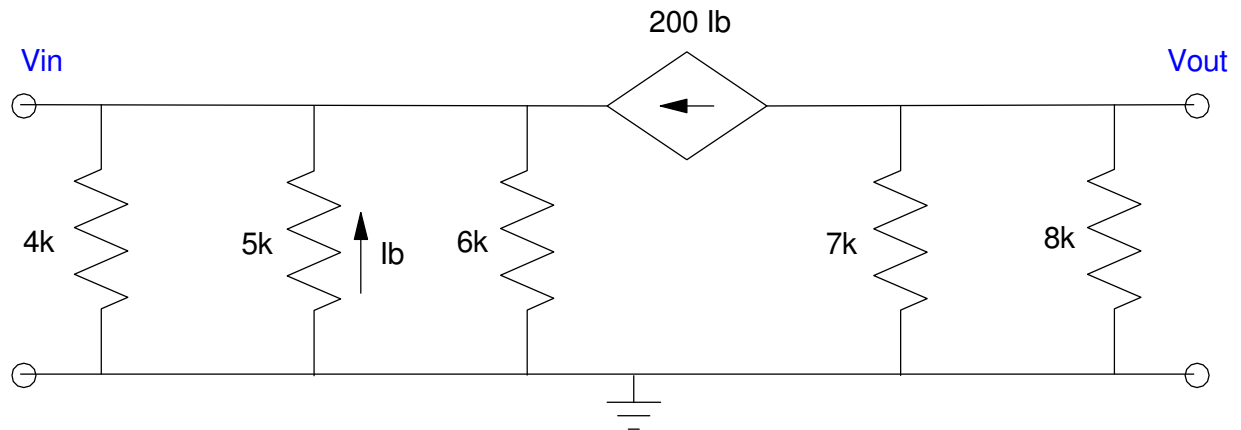

R_{in} :

- Short V_{out}
- Apply 1V to V_{in} . Compute the current

$$I = \frac{1}{4k} + \frac{1}{5k} + \frac{1}{6k} + 200\left(\frac{1}{5k}\right) = 40.62mA$$

$$R_{in} = \frac{1V}{40.62mA} = 24.62\Omega$$

$A_i = 0$

R_{out}

- Short V_{in}
- $R_{out} = 7k \parallel 8k = 3733$

A_o :

- Apply 1V to V_{in}

$$I_b = -\frac{1V}{5k} = -200\mu A$$

$$200I_b = -40mA$$

$$V_{out} = 40mA \cdot 7k \parallel 8k = 149.3$$

6) Determine the 2-port model for the following amplifier

Rin	Ai	Rout	Ao
2k	0	1000 3k 1500	+1333

