


ECE 321 - Final Exam - Name _____

Fall 2021

1. OpAmp Circuits: Determine y as a function of A , B , and C . Assume

- Ideal op-amps
- $R = 1100 + 100 * (\text{your birth month}) + (\text{your birth day})$. May 14th would give $R = 1614$ Ohms


R $1100 + 100 * \text{mo} + \text{day}$	$Y = aA + bB + cC$

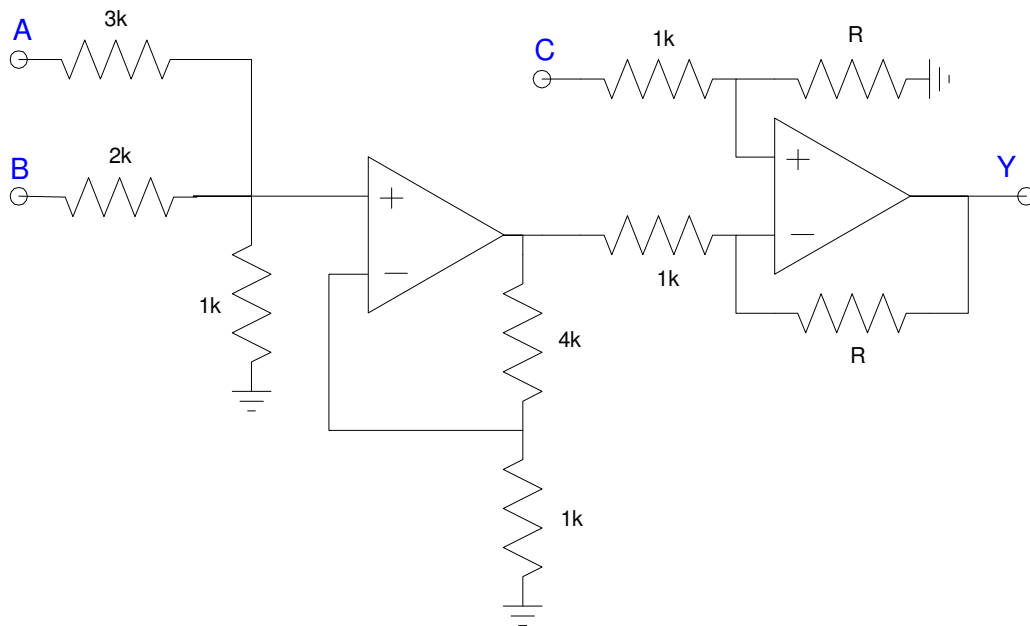

2. Push-Pull: Determine the voltages and currents for the following push-pull amplifier. Assume

- $R = 1100 + 100 * (\text{birth month}) + (\text{birth day})$. May 14th gives $R = 1614$ Ohms
- $|V_{ce}| = 0.7V$ (ideal silicon diodes)
- $\beta = 30$

R	V1	V2	V3	I4	I5
$1100 + 100 * \text{mo} + \text{day}$					

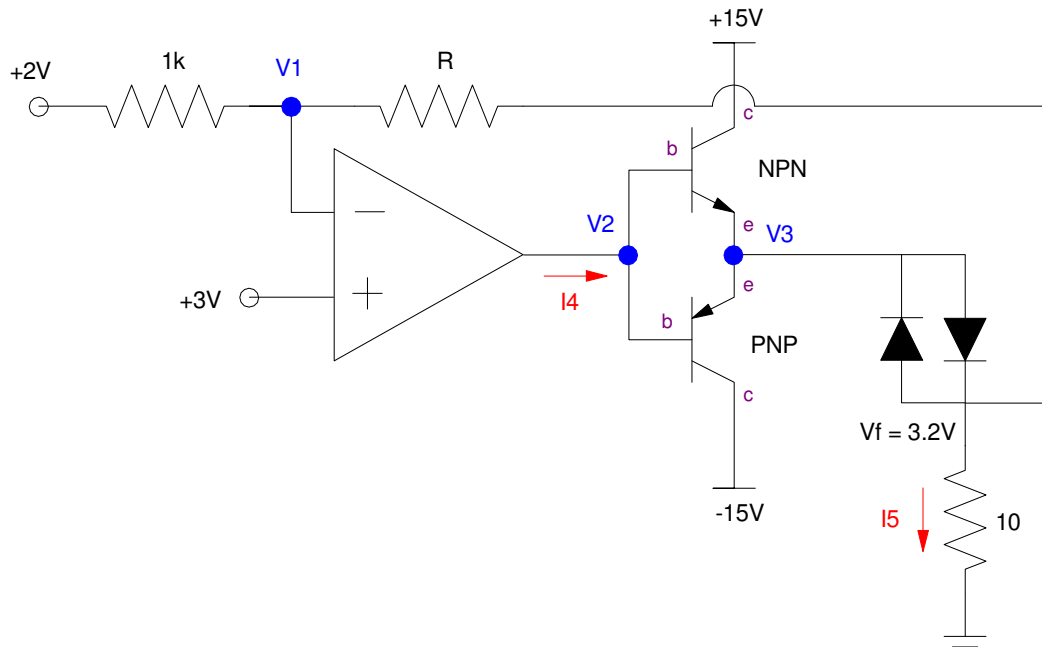

3. Instrumentation Amplifier: Assume a thermistor has the temperature - resistance relationship of


$$R_t = 3000 \cdot \exp\left(\frac{4000}{T+273} - \frac{4000}{298}\right) \Omega$$

Design a circuit which outputs

- +20V at +20C, and
- -10V at -10C

Assume

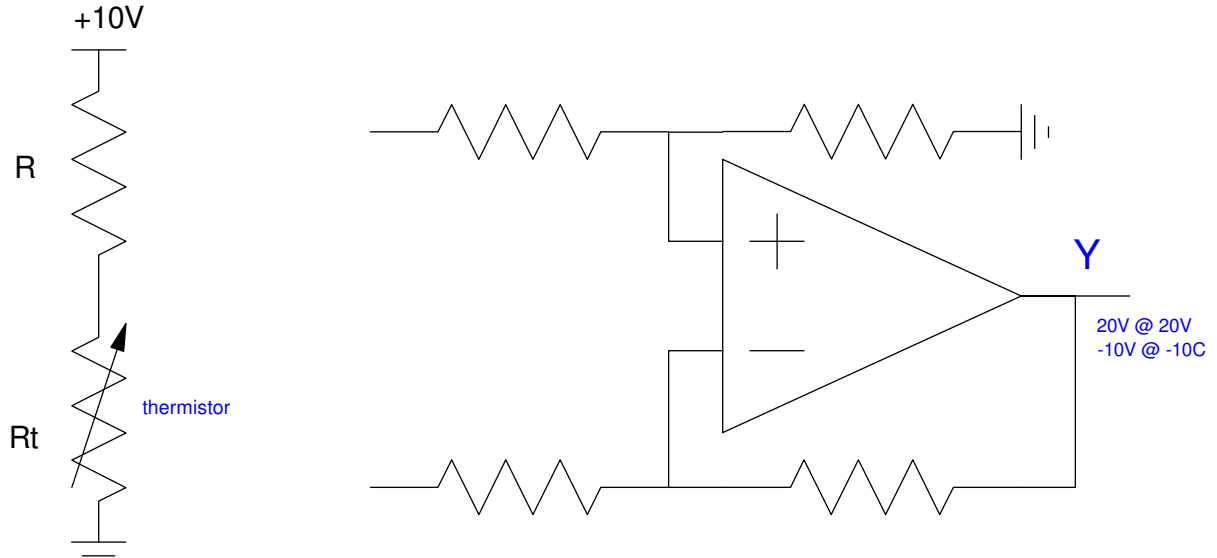- $R = 1100 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$




4. Filters: Let

- $R = 1100 + 100 * (\text{your birth month}) + (\text{your birth day})$. May 14th would give $R = 1614$ Ohms

Find the transfer function from X to Y



R $1100 + 100 * mo + day$	Transfer Function $Y = G(s) * X$

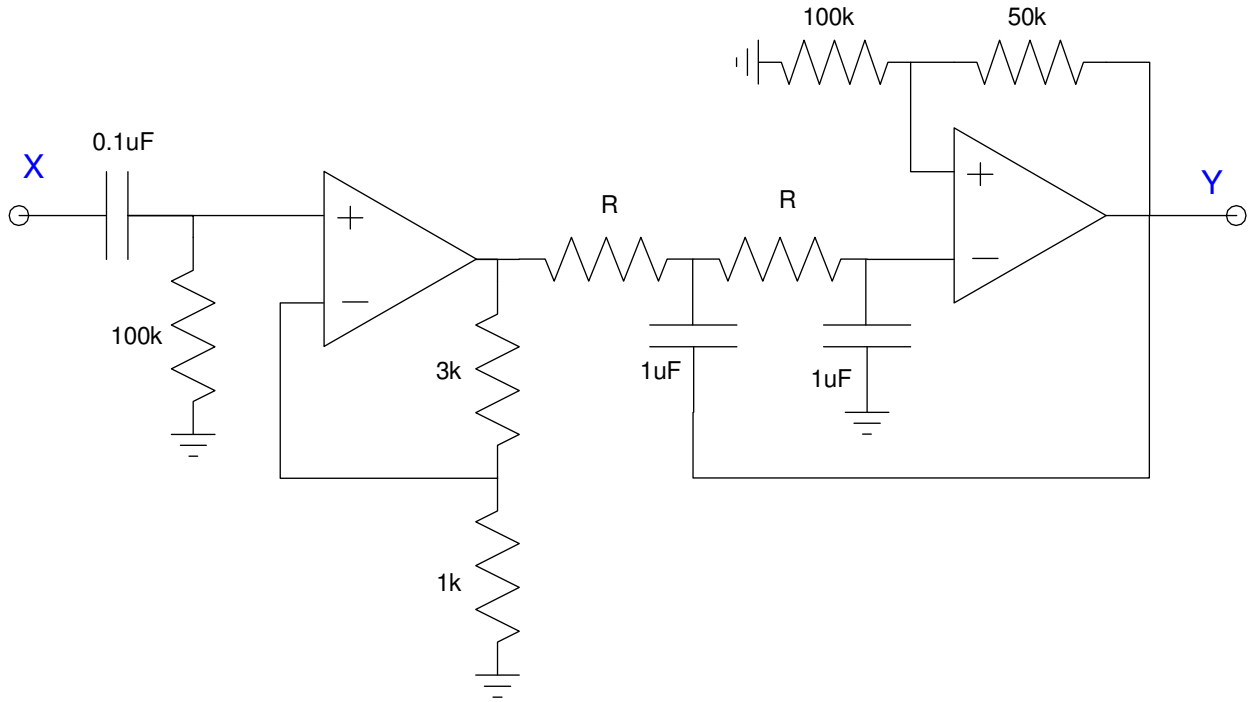

5. CE Amplifiers (DC analysis): Determine the Thevenin equivalent of R1 and R2 as well as the operating point for the following transistor circuit. Assume

- $R = 1100 + 100 * (\text{your birth month}) + (\text{your birth date})$
- $\beta = 30$
- $|V_{ce}| = 0.7V$



R	Vb	Rb	Vce	Ic
1100 + 100*mo + day				

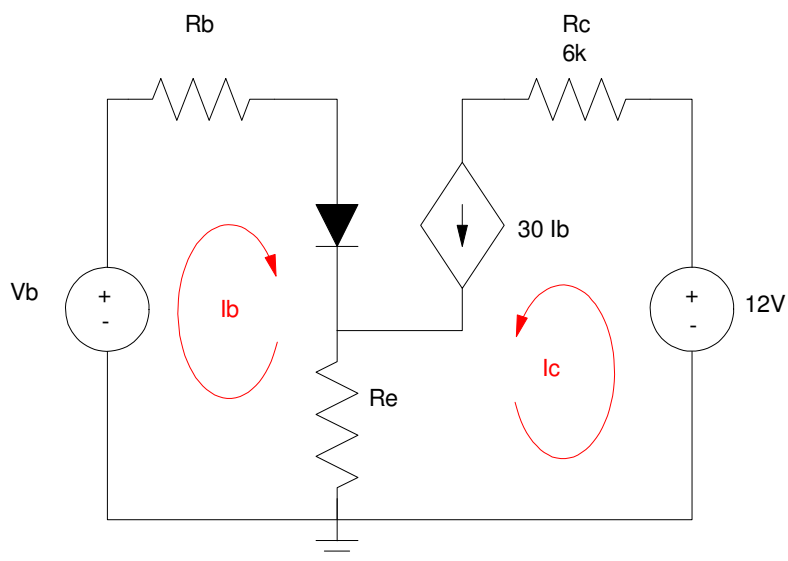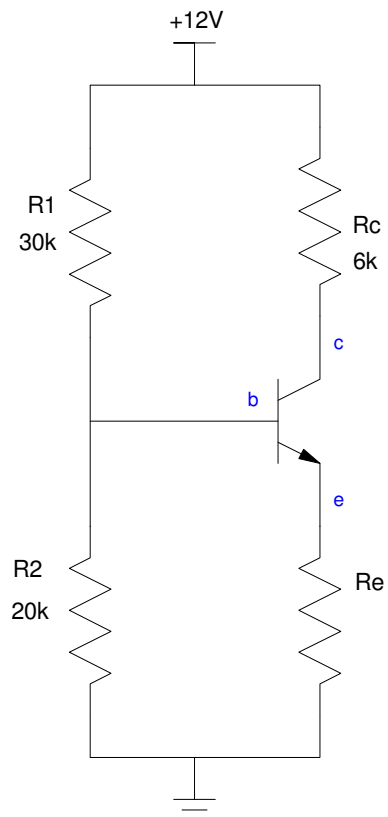

6. 2-Port model: Determine the 2-port parameters for the following circuit. Assume

- $R = 1100 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ Ohms

R	R _{in}	A _i	R _{out}	A _o
1100 + 100*mo + day				

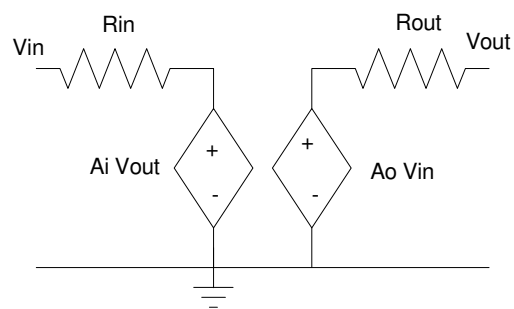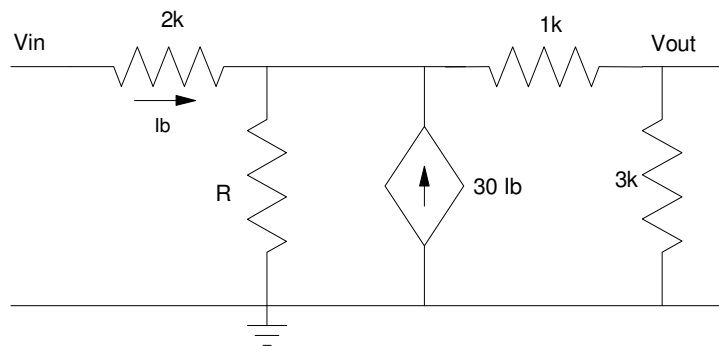

7. 2-Port model: Determine the 2-port parameters for the following circuit. Assume

$$R = 1100 + 100 * (\text{your birth month}) + (\text{your birth date}) \text{ Ohms}$$

R	R _{in}	A _i	R _{out}	A _o
1100 + 100*mo + day				

