# ECE 321 - Homework #1

Op Amp Amplifiers, Push-Pull Amplifiers. Due Monday, November 8th

Please make the subject "ECE 321 HW#1" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

For all problems, assume you are using


- MCP602 Op Amps (max current = 50mA)
- 2SC6144 transistors ( $\beta = 200, 10$  max, |Vbel = 0.7V

## Amplfier:

Design a circuit to implement

1a) Y = +3X


1b) Y = -3X

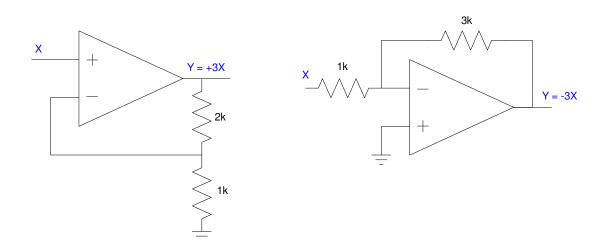

1c) Y = 12 - 4X

#### Rewrite as

Y = 4(3 - X)

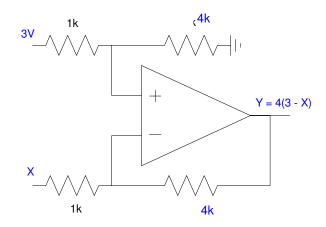


# Mixer

2) Design a circuit to mix three signals together:


• Y = 6A + 1B + 3C

Option 1: Rewrite as

$$Y = 10 \left(\frac{6A + B + 3C}{10}\right)$$

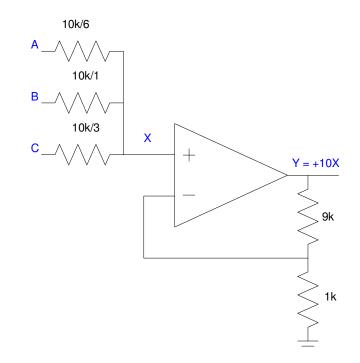


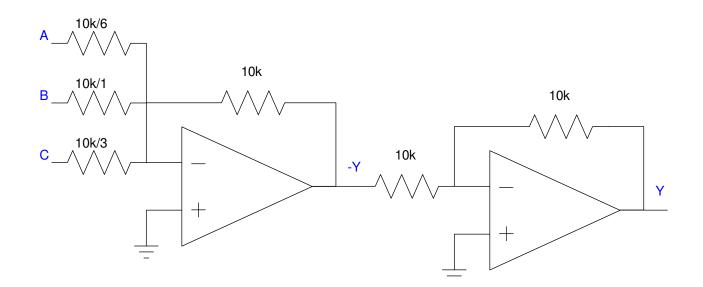Option 2: Use inverting summing amplifiers




# **Push-Pull Amplifier**

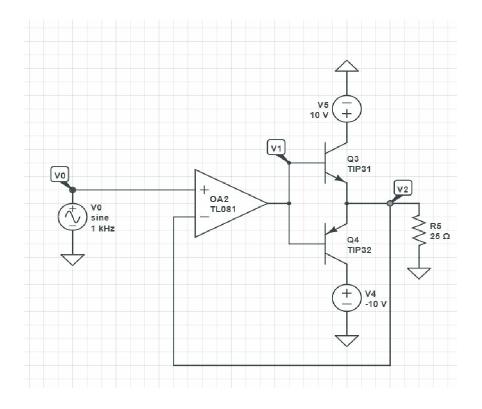- 3) Design a circuit so that Y = X
  - X = -5V to +5V, 10mA max
  - Y = -5V to +5V, 200mA (25 ohm speaker (net))



### 4) Simulate in CircuitLab

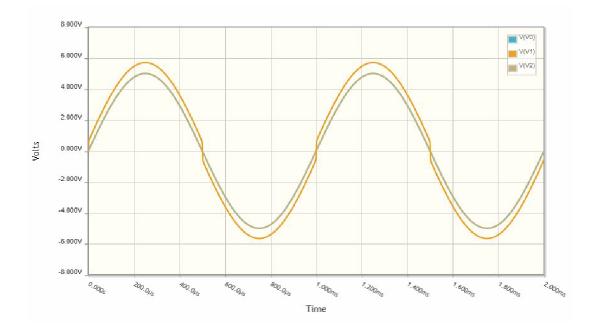



## Lab (Hardware)

The following circuit


- Creates a 2.5V power supply from a single +5V supply (V0). This 2.5V supply then acts like circuit ground
- Amplifies the output of a cell phone (or computer or 555 timer) (V2), and
- Drives an 8 Ohm speaker (V3)
- 5) Calculate the voltages and currens when

V1 = 2.0V

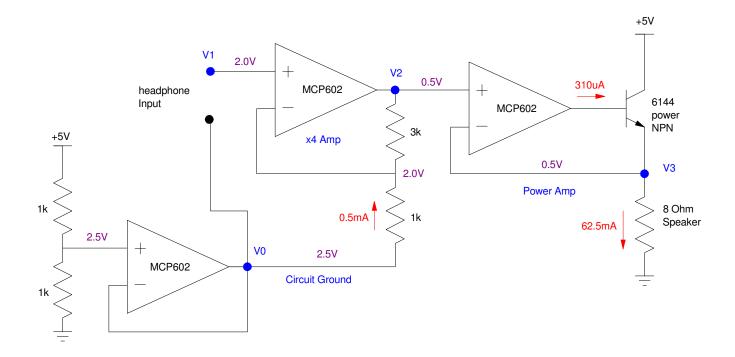

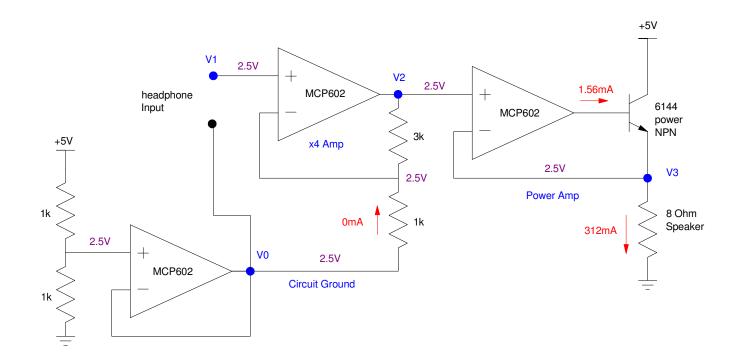



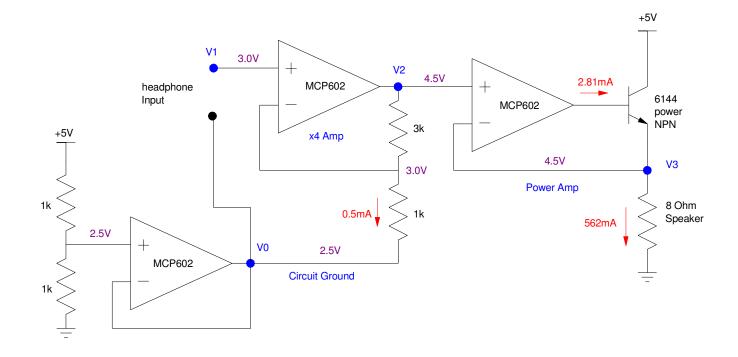



6) Simulate this curcuit in CircuitLab with

• V1 = 1Vpp, 1kHz sine wave

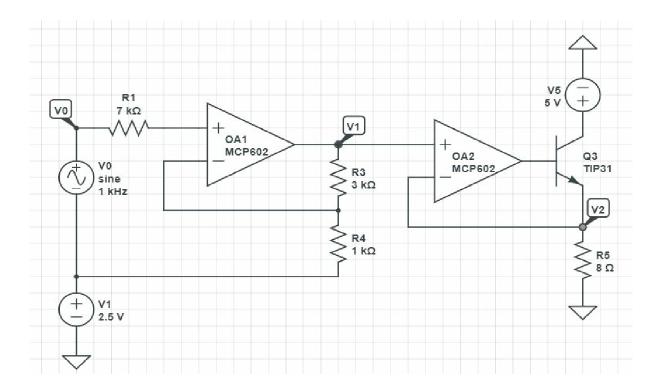
#### Note:

- V1 = 4\*V0, centered at 2.5V (circuit ground)
- V2 = V1



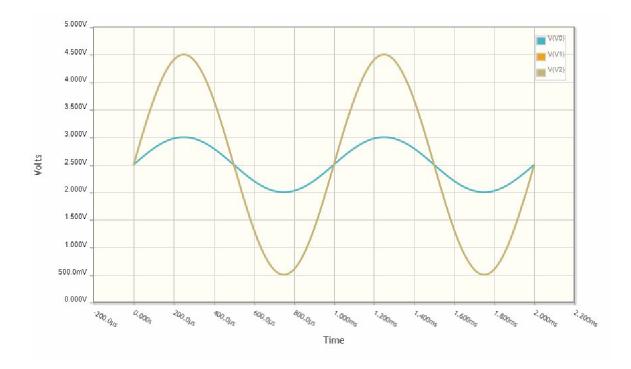


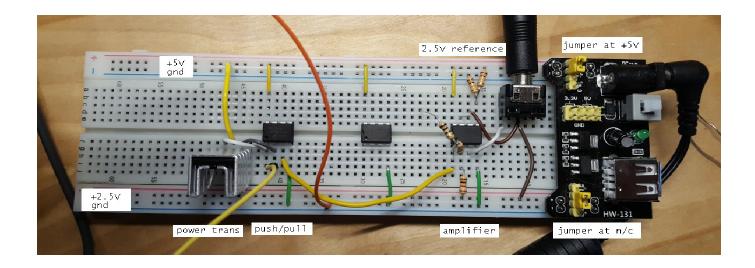- 7) Build this circuit in hardware. With a sine wave input, (1kHz) verufy that that
  - V2 = 4\*V1 (relative to circuit ground)
  - V3 = V2 (relative to circuit ground)



Using OnLineToneGenerator.com, a 440Hz sine wave was applied to the input

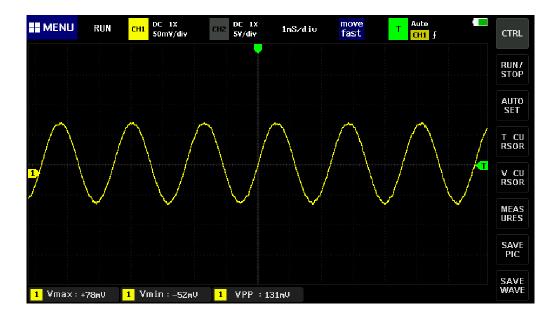- V1 = 44mVrms
- V2 = 131Vrms sine wave
- V3 = 131 Vrms sine wave



### 8) Demo

• Replace V1 with an audio signal and verify the song plays on the speaker

Playing "Hot and Cold" by Elmo and Ms. Perry

