

ECE 321 - Homework #2


Push-Pull Amplifiers - Phasors - Due Monday, April 13th

1) Design a circuit with a push-pull amplifier to amplify the output of an iPhone

- Input: 1Vpp sine wave, < 10mA
- Output: 8 Ohm 20W speaker
- Relationship: $V_o = 10 \cdot V_{in}$, $\approx 1V$

There are several solutions. The following lets you build it in sections:


- x10
- push-pull amplifier

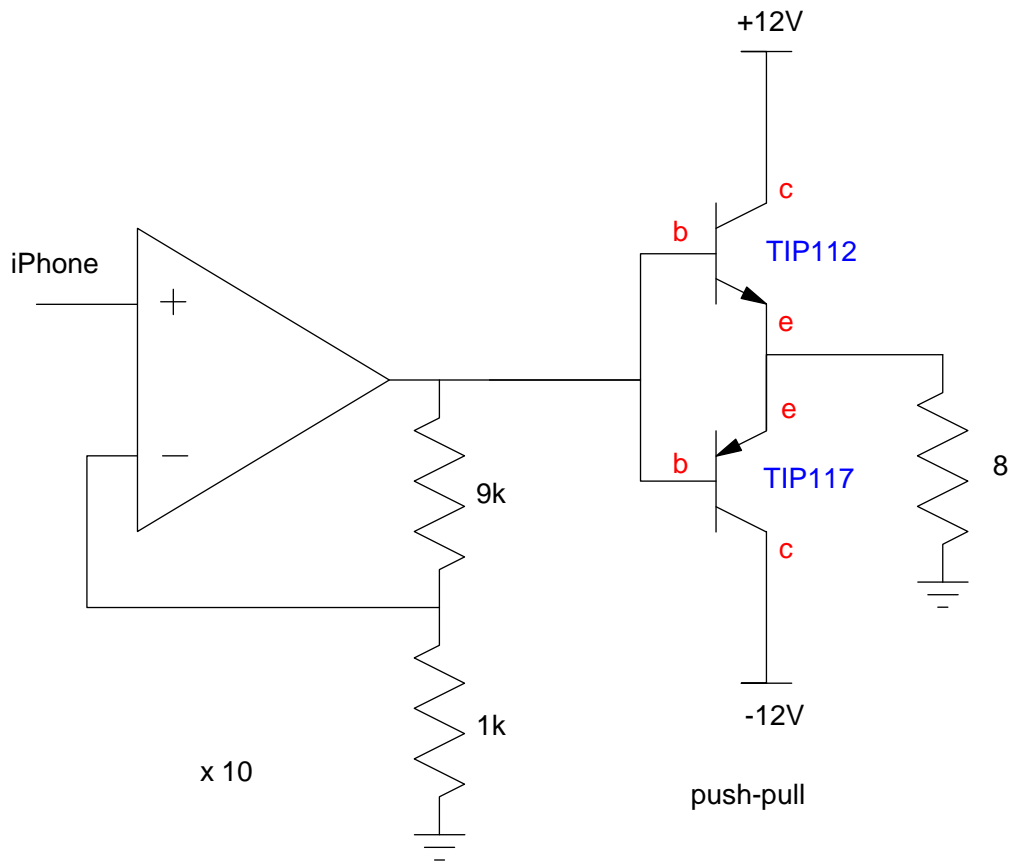

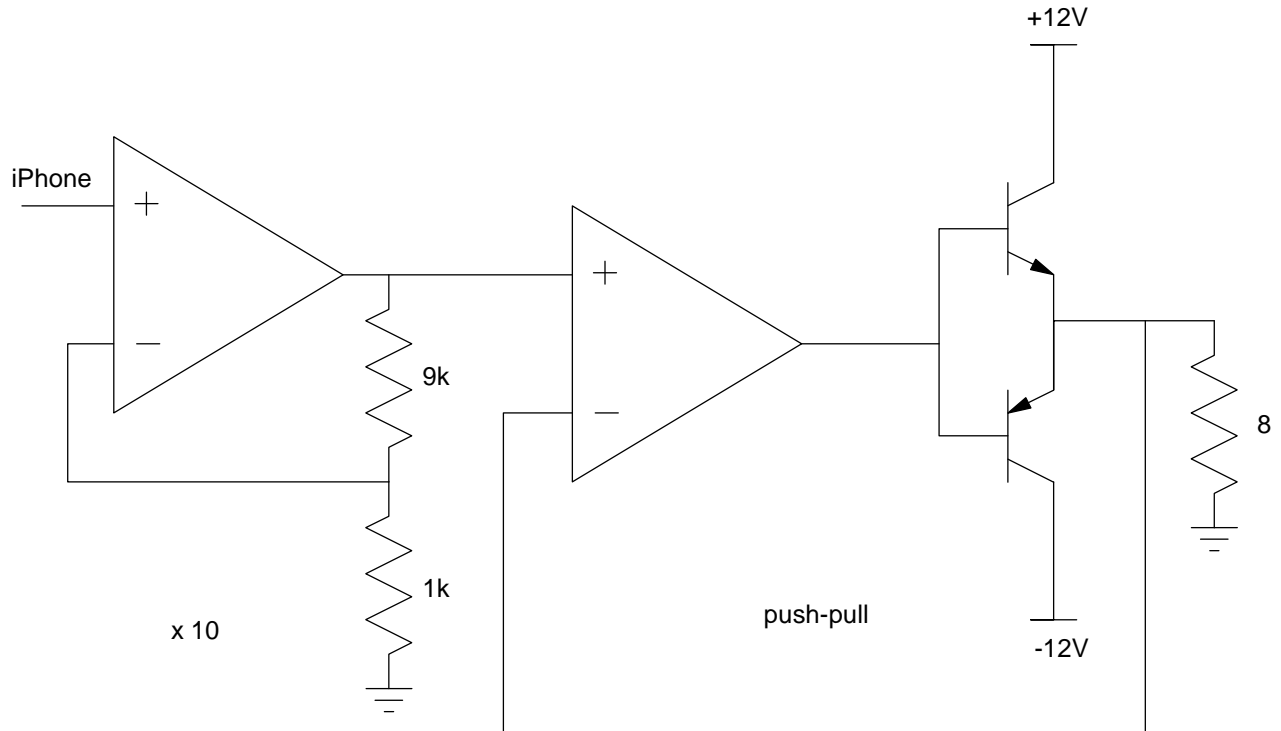2) Design a push-pull amplifier without crossover distortion to amplify the output of an iPhone

- Input: 1Vpp sine wave, < 10mA
- Output: 8 Ohm 20W speaker
- Relationship: $V_o = 10 \cdot V_{in}$, $\approx 100\text{mV}$

Same circuit as before, but add an op-amp to force the voltage at the speaker to match the voltage at the output of the first op-amp



3) For the following filter:

$$Y = \left(\frac{20}{s^2 + 5s + 20} \right) X$$

3a) What is the differential equation relating X and Y?

Cross multiply

$$(s^2 + 5s + 20)Y = 20X$$

'sY' means "the derivative of Y"

$$\frac{d^2y}{dt^2} + 5\frac{dy}{dt} + 20y = 20x$$

3b) Find y(t) if x(t) = 2 + 3 sin(4t)

Use superposition:

$$x(t) = 2$$

$$s = 0$$

$$\left(\frac{20}{s^2 + 5s + 20} \right)_{s=0} = 1$$

$$y(t) = (1) * 2 = 2$$

$$x(t) = 3 \sin(4t)$$

$$s = j4$$

$$\left(\frac{20}{s^2 + 5s + 20} \right)_{s=j4} = 0.9806 \angle -76.7^\circ$$

$$y(t) = (0.9806 \angle -76.7^\circ) \cdot 3 \sin(4t)$$

$$y(t) = 2.9417 \sin(4t - 76.7^\circ)$$

$$x(t) = 2 + 3 \sin(4t)$$

$$y(t) = 2 + 2.9417 \sin(4t - 76.7^\circ)$$

4) For the following filter: $Y = \left(\frac{300}{(s+10)(s+20)} \right) X$

4a) What is the differential equation relating X and Y?

Cross multiply

$$(s + 1)(s + 2)Y = 300X$$

$$(s^2 + 3s + 2)Y = 300X$$

'sY' means 'the derivative of Y'

$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = 300x$$

4b) Find y(t) if x(t) = 2 + 3 sin(4t)

Use superposition:

$$x(t) = 2$$

$$s = 0$$

$$\left(\frac{300}{(s+10)(s+20)} \right)_{s=0} = 1.5$$

$$y = (1.5) \cdot 2$$

$$y(t) = 3$$

$$x(t) = 3 \sin(4t)$$

$$s = j4$$

$$\left(\frac{300}{(s+10)(s+20)} \right)_{s=j4} = 1.3657 \angle -33.1^\circ$$

$$y(t) = (1.3657 \angle -33.1^\circ) \cdot 3 \sin(4t)$$

$$y(t) = 4.0970 \sin(4t - 33.1^\circ)$$

$$x(t) = 2 + 3 \sin(4t)$$

$$y(t) = 3 + 4.0970 \sin(4t - 33.1^\circ)$$

Term Project

5) Specify the requirements for your ECE 321 term project in terms of

- Input
- Output
- Relationship.

For ECE 321, the output must be an analog signal (i.e. able to take on any voltage between a range, such as -10V to +10V).