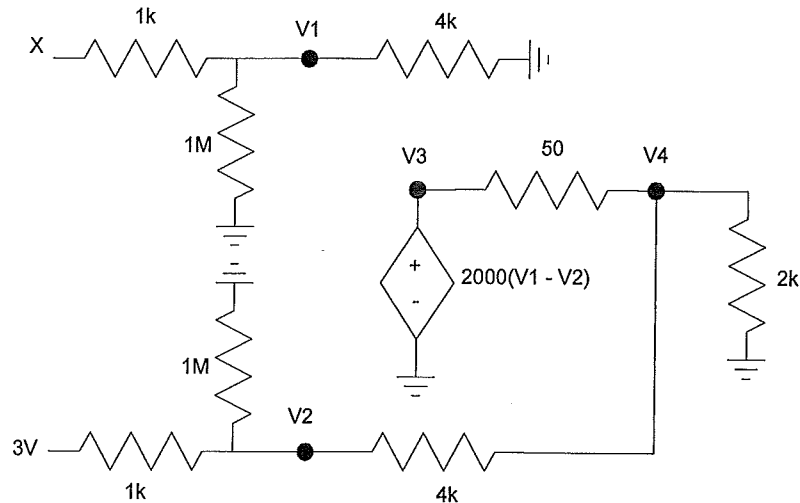


ECE 321 - Quiz 1: Name _____

Op-Amps. April 8, 2015

1) Write the voltage node equations for the following op-amp circuit:



Node V1:

$$\frac{V_1 - X}{1k} + \frac{V_1}{4k} + \frac{V_1}{1m} = 0$$

Node V2:

$$\frac{V_2 - 3}{1k} + \frac{V_2}{1m} + \frac{V_2 - V_4}{4k} = 0$$


Node V3:

$$V_3 = 2000(V_1 - V_2)$$

Node V4:

$$\frac{V_4 - V_2}{4k} + \frac{V_4 - V_3}{50} + \frac{V_4}{2k} = 0$$

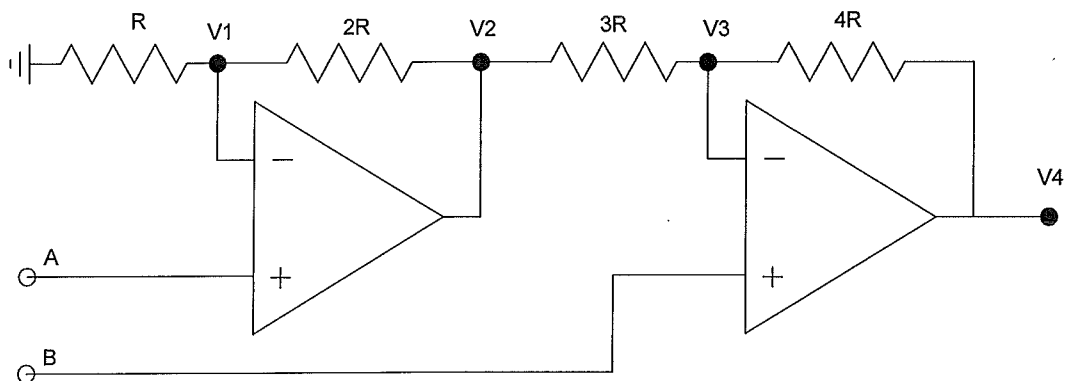2) Assume ideal op-amps. Write the voltage node equations for the following circuit.



Node V1:

$$\frac{V_1}{R} + \frac{V_1 - V_2}{2R} = 0$$

Node V2:

$$V_1 = A$$


Node V3:

$$\frac{V_3 - V_2}{3R} + \frac{V_3 - V_4}{4R} = 0$$

Node V4:

$$V_3 = B$$

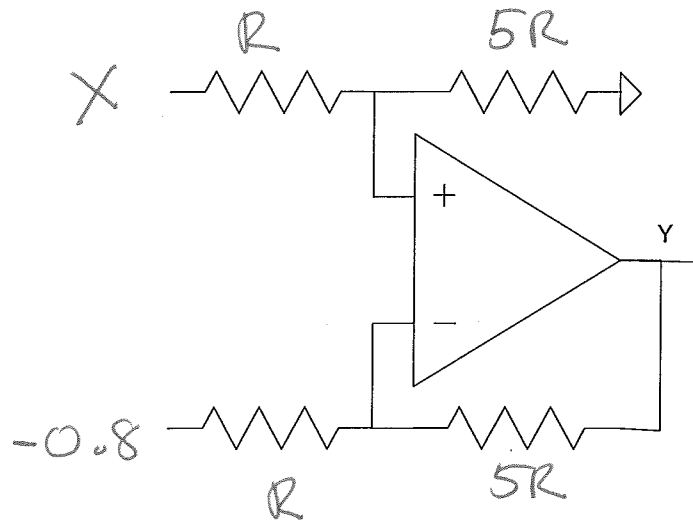3) Specify the resistors and voltages so that the following circuit implements the function
 $y = 5x + 4$



$$y = 5(x + 0.8)$$


$$y = 5(x - (-0.8))$$

$R = \text{anything}$ ($1k, 10k, \dots$)

4) Specify the resistors and voltages so that the following circuit outputs

0V when R = 300 Ohms, and

+10V when R = 400 Ohms

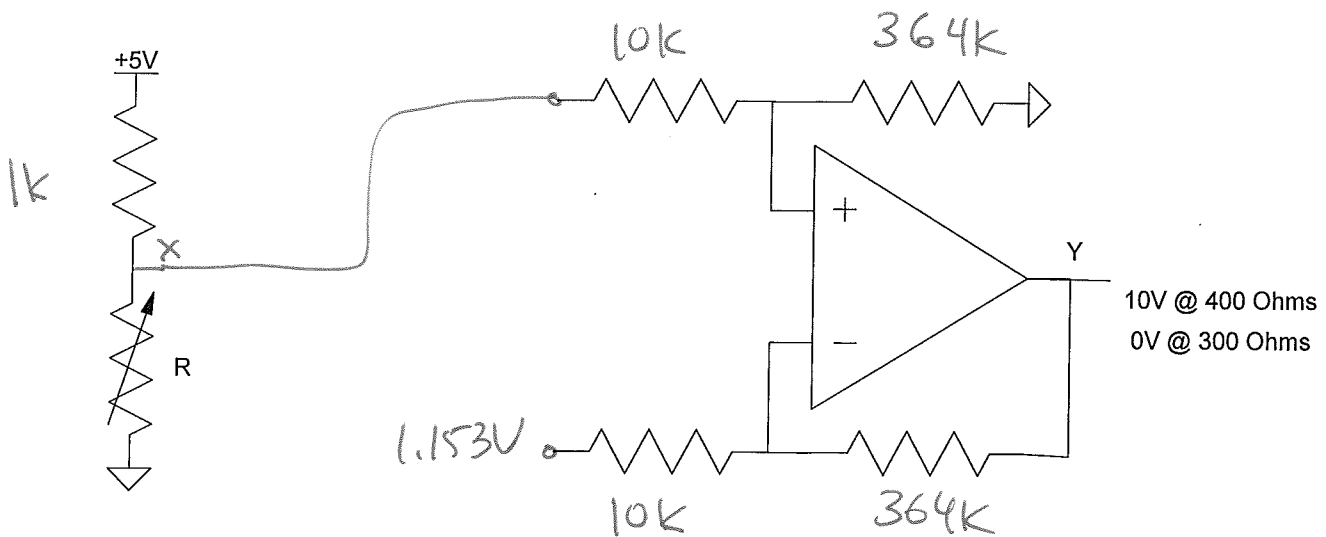

$$300\Omega$$

$$x = 1.1538V$$

$$400\Omega$$

$$x = 1.4286V$$

$$\text{gain} = 36.4$$

many solutions


$$- \text{gain} = \frac{10V}{V_{400} - V_{300}}$$

$$- \text{offset} = V_{300}$$

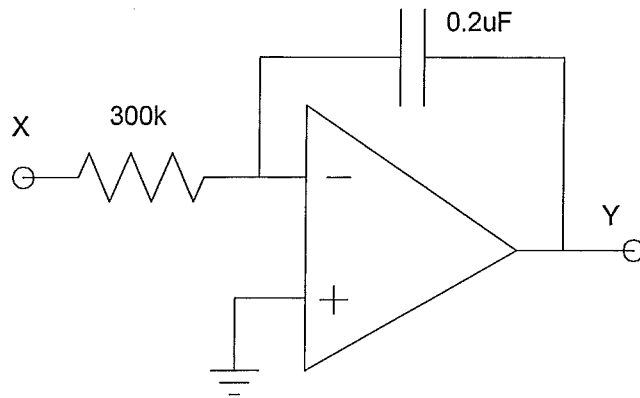5) For the following circuit,

- Find the differential equation relating X and Y.
- Find $y(t)$ assuming $x(t) = 2 \sin(3t) + 4 \cos(200t)$

Differential equation relating X and Y
$y = -16.67 \int x dt \quad \underline{\underline{\text{or}}} \quad \frac{dy}{dt} = -16.67x$
$y(t)$
$11.11 \cos(3t) - 333 \sin(200t)$



$$y = -\frac{1}{Rf} \frac{1}{s} x$$

$$y = -16.67 \int x dt$$

$$y = -16.67 \left[-\frac{2}{3} \cos(3t) + \frac{4}{200} \sin(200t) \right]$$

Bonus: There is some concern about railways carrying oil and other flammable material through cities. When can a railway refuse to carry cargo if the railway engineers feel it is unsafe?

no - railways cannot refuse any cargo as long as it meets federal regulations

