



ECE 321 - Quiz #4: Name _____

CE Amplifiers and 2-Port Models - April 30, 2015

1) DC Analysis: Determine the Q-point for the following circuit. Assume

- Current gain = 200 ($\beta = 200$)
- $V_{be} = 0.7V$ when on

V_{bb} Thevenin voltage for $R_1:R_2$	R_{bb} Thevenin resistance for $R_1:R_2$	V_c	I_c
4V	66.67k	4.95V	1.4mA

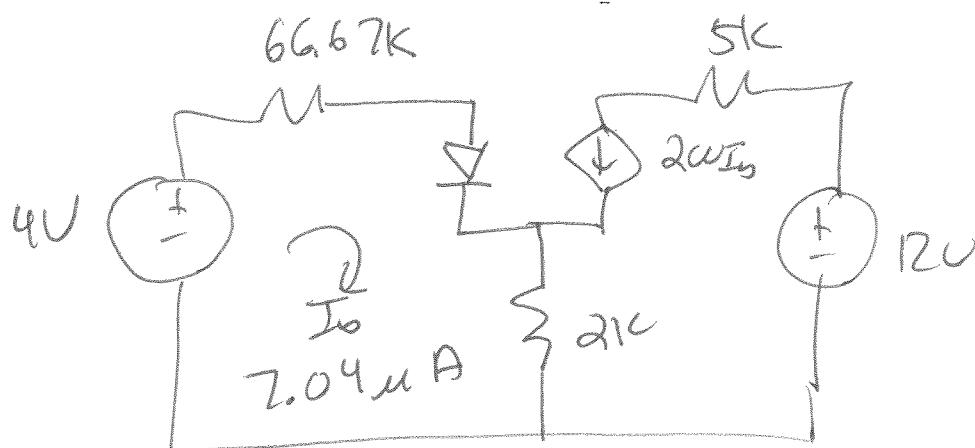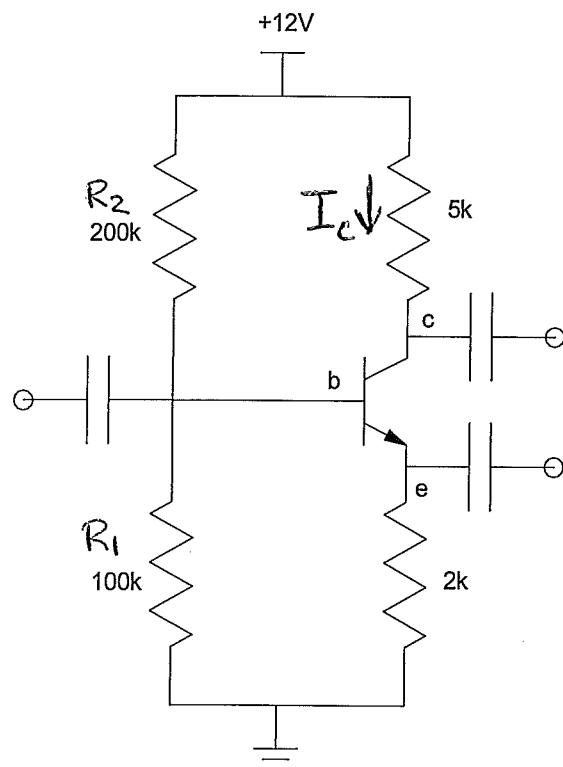


2) DC Analysis: Specify the parameters V_{bb} and R_{bb} along with R_1 and R_2 so that

- The Q-point is stabilized ($R_e \gg R_b$), and
- The Q-point is $I_c = 1\text{mA}$
- $\beta = 200$

V_{bb} Thevenin voltage for $R_1:R_2$	R_{bb} Thevenin resistance for $R_1:R_2$	R_1	R_2
2.91V	40k	52.8k	165k

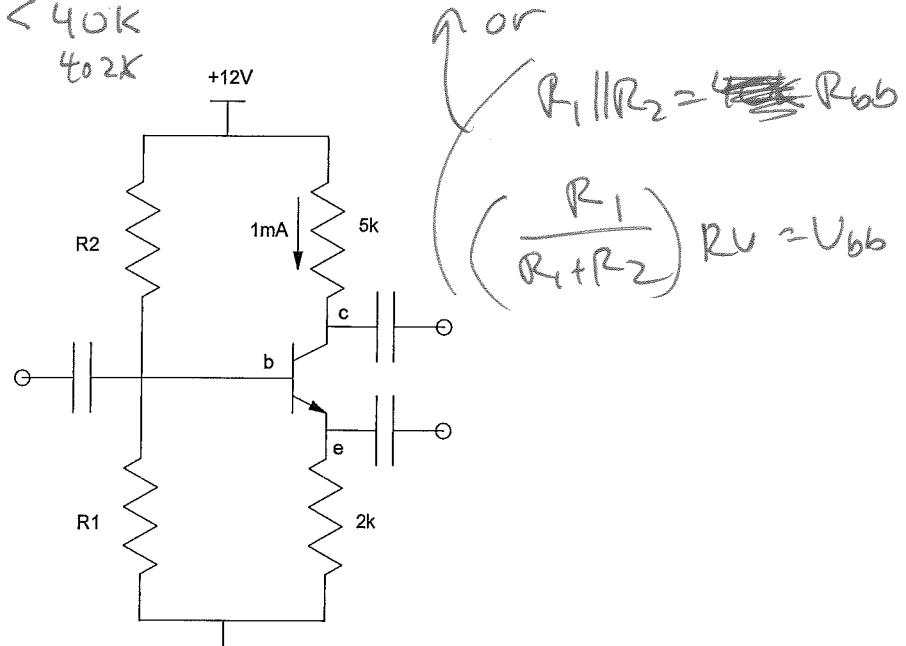
$$f(R_{bb}) \rightarrow \text{any } < 40\text{k} \text{ to } 2\text{k}$$



$$\frac{R_1 \cdot R_2}{R_1 + R_2} > R_{bb}$$



$$(R_{bb} \ll 40\text{k} \Omega)$$

v_{in}

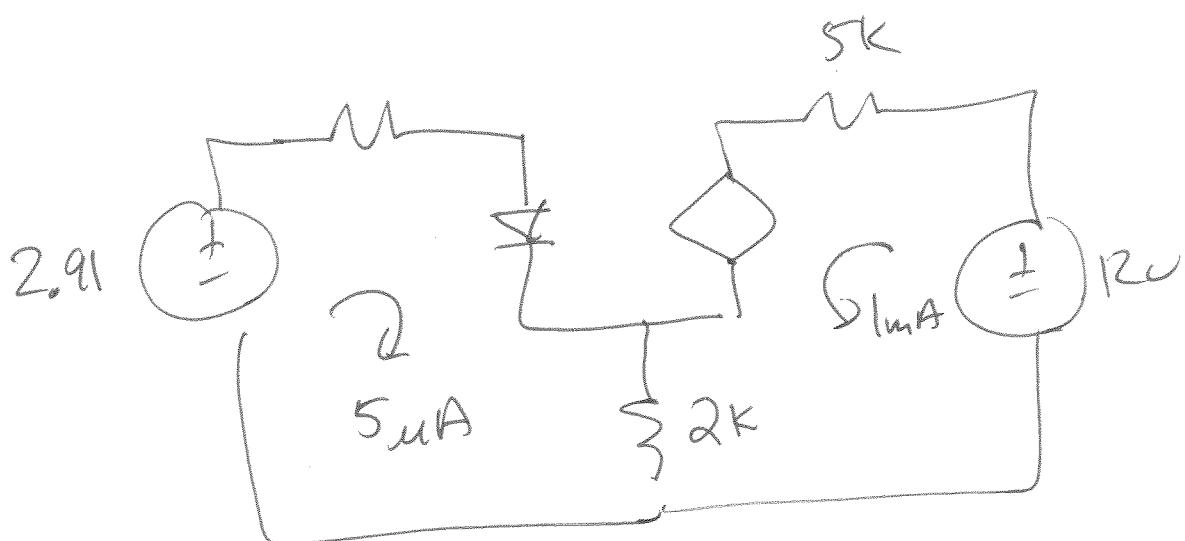

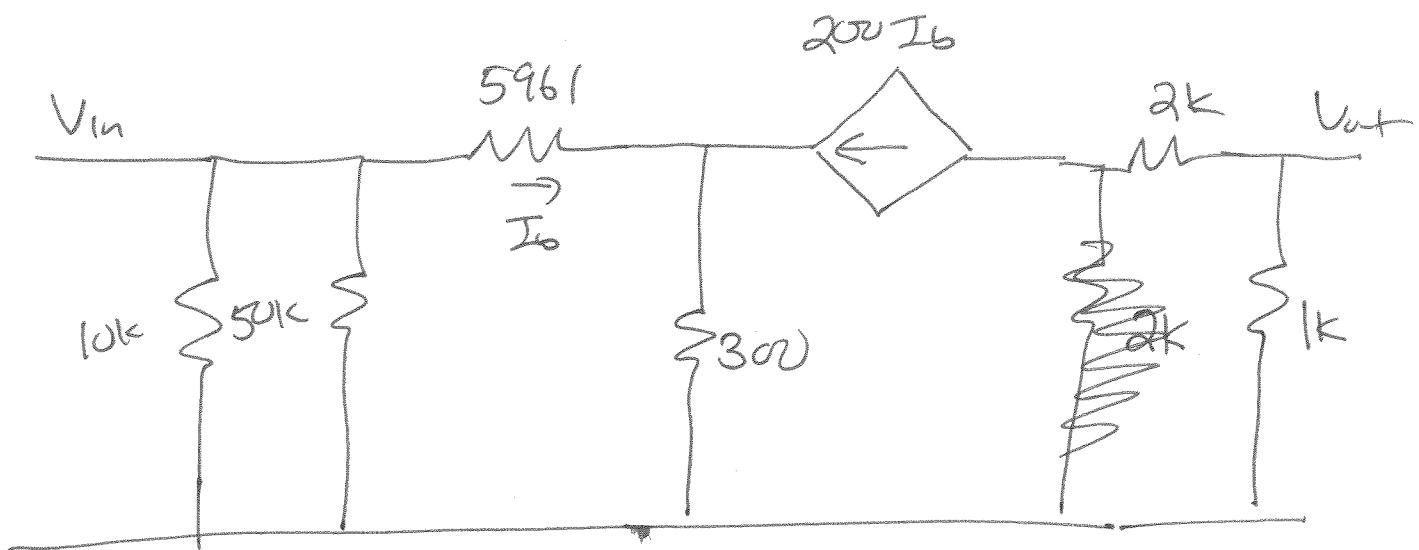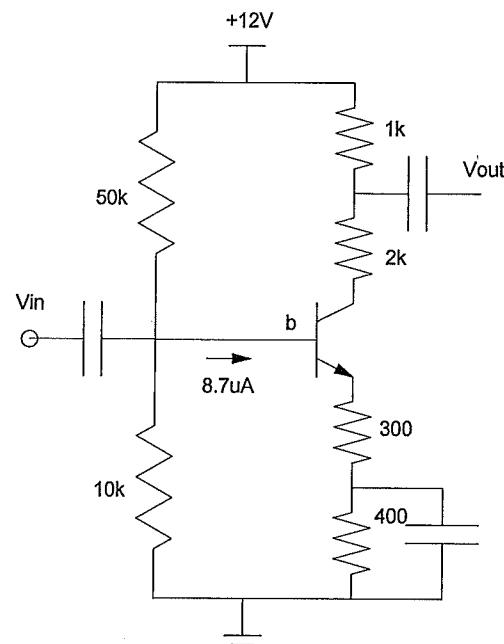3) AC Analysis: Draw the small-signal model for the following circuit. Assume



- $\beta = 200$
- The Q-point is $I_{be} = 8.72\mu A$
- $r_f = \frac{0.052}{I_{be}} = 5961\Omega$



- 1 pt for each missing term


4) Find the 2-port model for the following circuit:

Rin	Ain	Rout	Aout
2.67k	0.833	14.40	.904

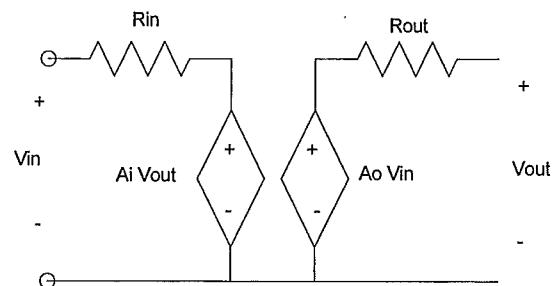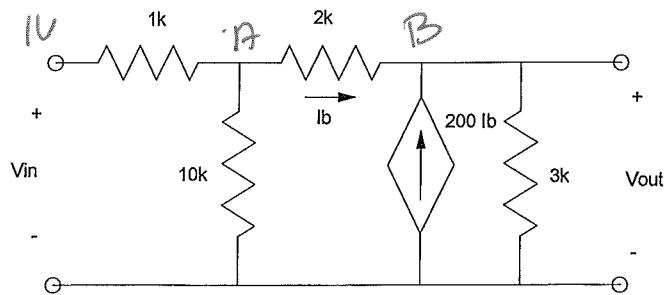

$$R_{in} = 1k + 2k \parallel 10k$$
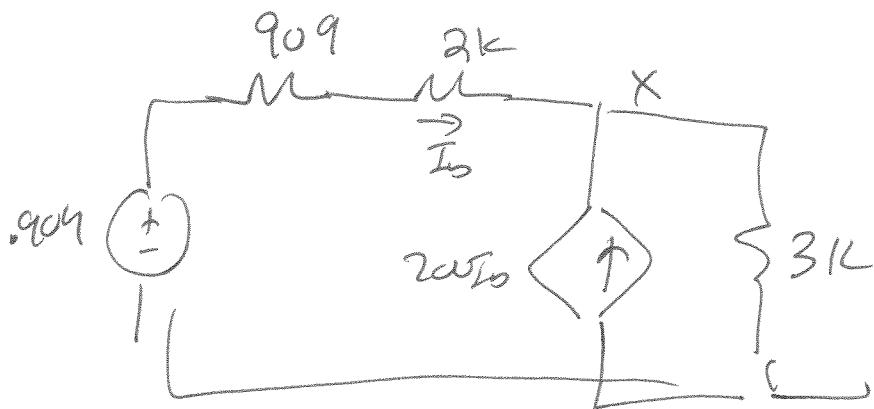
$$R_{out} = 2909 \parallel 3k \parallel 14.55$$




$$(201) \frac{X - .909}{2909} + \frac{X}{3k} = 0 \quad \left(\frac{\frac{201}{2909}}{\frac{21}{2909} + \frac{1}{3k}} \right) .909$$

$$X = .904$$

5) Determine the 2-port simplified model for this circuit:

Rin	Ain	Rout	Aout
3k	0	7k	-11250

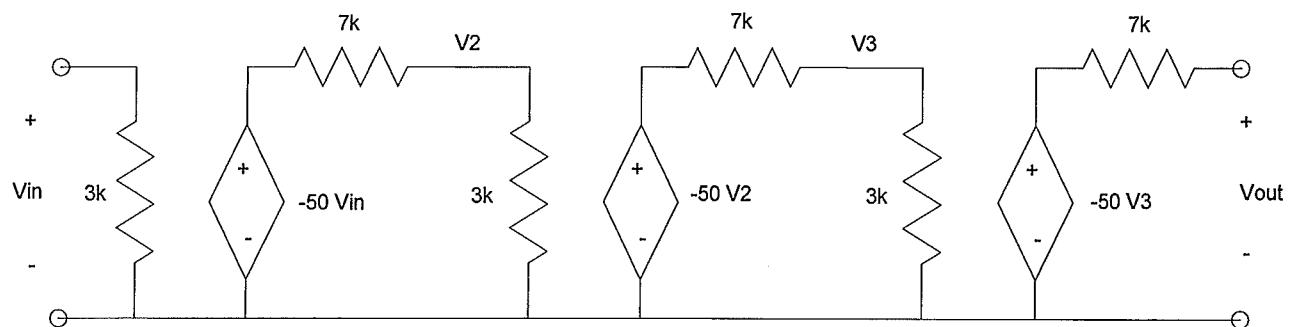

Bonus! Chernobyl was the worst disaster in history for the nuclear power industry. What is the

- The official death toll to date, and
- The estimated death toll (to date) according to Greenpeace:

31

100,000

