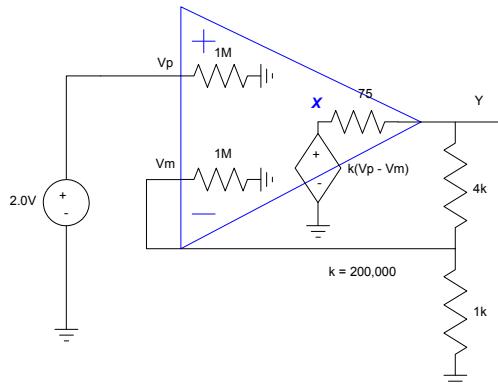


ECE 321 - Homework #1

Op-Amps - Due Wednesday April 8th

- 1) Write the voltage node equations for the following circuit using a non-ideal op-amp model:



You need four equations for four voltage nodes: Vp, Vm, Y, X,


$$Y: \quad V_p = V_m$$

$$X: \quad X = 200,000(V_p - V_m)$$

$$V_p: \quad V_p = 2$$

$$V_m: \quad \left(\frac{V_m}{2M} \right) + \left(\frac{V_m - Y}{4k} \right) + \left(\frac{V_m}{1k} \right) = 0$$

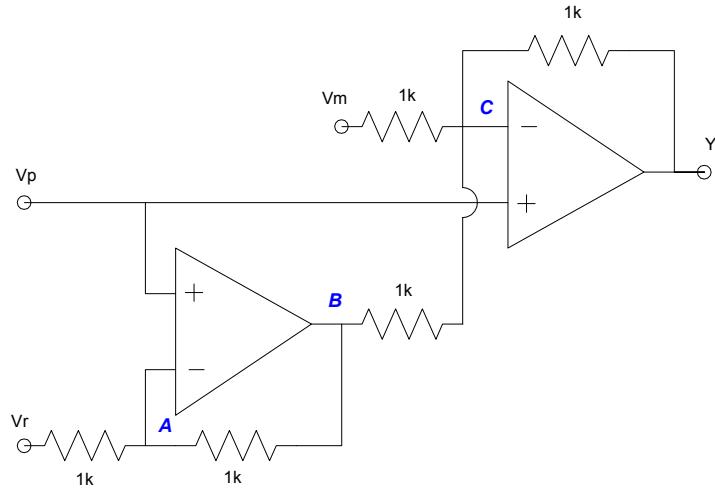2) Write the voltage node equations for the following circuit assuming ideal op-amps:



You need to write four equations for the four unknown voltage nodes (A, B, C, Y)

$$B: \quad V_A = V_p$$

$$Y: \quad V_c = V_p$$

$$A: \quad \left(\frac{V_A - V_r}{1k} \right) + \left(\frac{V_A - V_b}{1k} \right) = 0$$

$$C: \quad \left(\frac{V_c - V_m}{1k} \right) + \left(\frac{V_c - V_b}{1k} \right) + \left(\frac{V_c - V_y}{1k} \right) = 0$$

3) Mixer: Design an op-amp circuit which will add together two audio signals

Input:

- A: $\pm 1V$ signal, capable of driving 10mA, 0-20kHz
- B: same

Output

- $Y = \pm 10V$ signal, capable of driving 10mA, 0-20kHz


Relationship:

- $Y = 8A + 2B$


1V capable of driving 10mA means the input resistance is 100 Ohms (or more). Let the feedback resistor be 100k

For a gain of 8, use an 8:1 ratio for resistors

For a gain of 2, use a 2:1 ratio for resistors

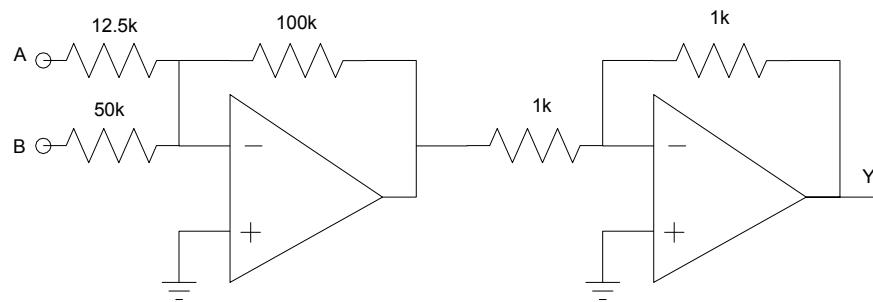

Option 2:

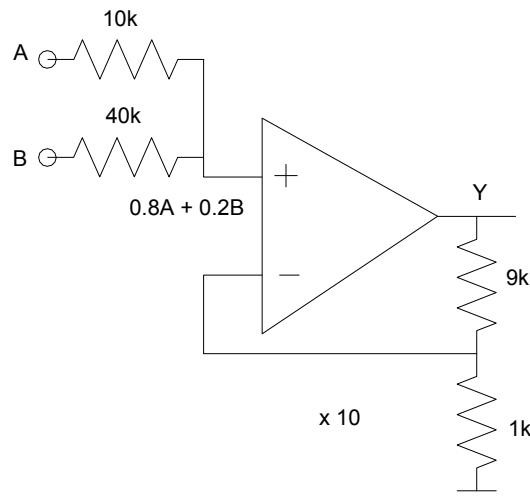

4) Instrumentation Amplifier. Design a circuit to implement the following:

Input:

- $X = 3..4V$ signal, capable of driving 10mA, 0-20kHz

Output:


- $Y = 0..10V$ signal, capable of driving 10mA, 0-20kHz

Relationship:

- $Y = 10X - 30$

Rewrite this as

$$Y = 10(X - 3)$$

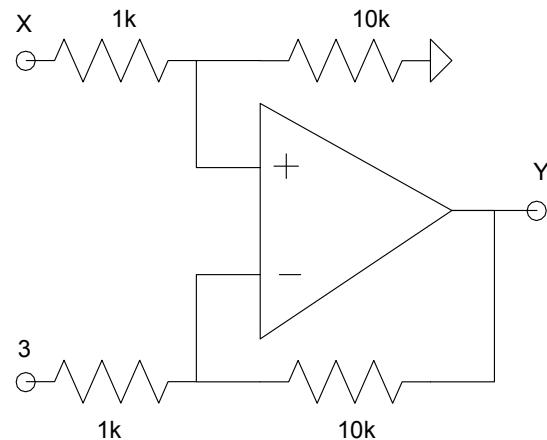

5) Instrumentation Amplifier (take 2). Design a circuit to implement the following:

Input:

- Thermistor from 0 to 20C.
- $R = 1000 \cdot e^{-0.04(T-25)} \Omega$

Output:


- Y = 0..10V signal, capable of driving 10mA, 0-20kHz

Relationship:

- 0C = 0V
- 20C = 10V
- $Y = T/2$

Assume a 1k resistor for a voltage divider. In MATLAB
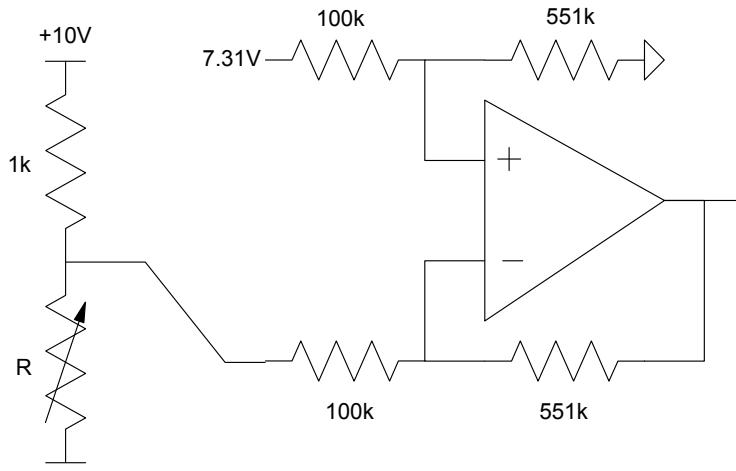
```
-->T = [0, 20]'  
0.  
20.  
  
-->R = 1000*exp(-0.04*(T-25))  
2718.2818  
1221.4028  
  
-->X = R ./ (1000+R) * 10  
7.3105858  
5.49834  
  
-->gain = (10 - 0) / (X(2) - X(1))  
gain =  
- 5.5180152  
  
-->offset = X(1)  
7.3105858
```



6) Integrators and Differentiators: Design an op-amp circuit to implement the following function

Input:

- $X = \pm 10V$ sinusoid, capable of driving 10mA, 0..100Hz

Output:

- $Y = \pm 10V$ sinusoid, capable of driving 10mA, 0..100Hz


Relationship:

- $\frac{dY}{dt} + 6Y = 3x$

Rewriting this...

$$sY + 6Y = 3X$$

$$Y = \left(\frac{3}{s+6}\right)X$$

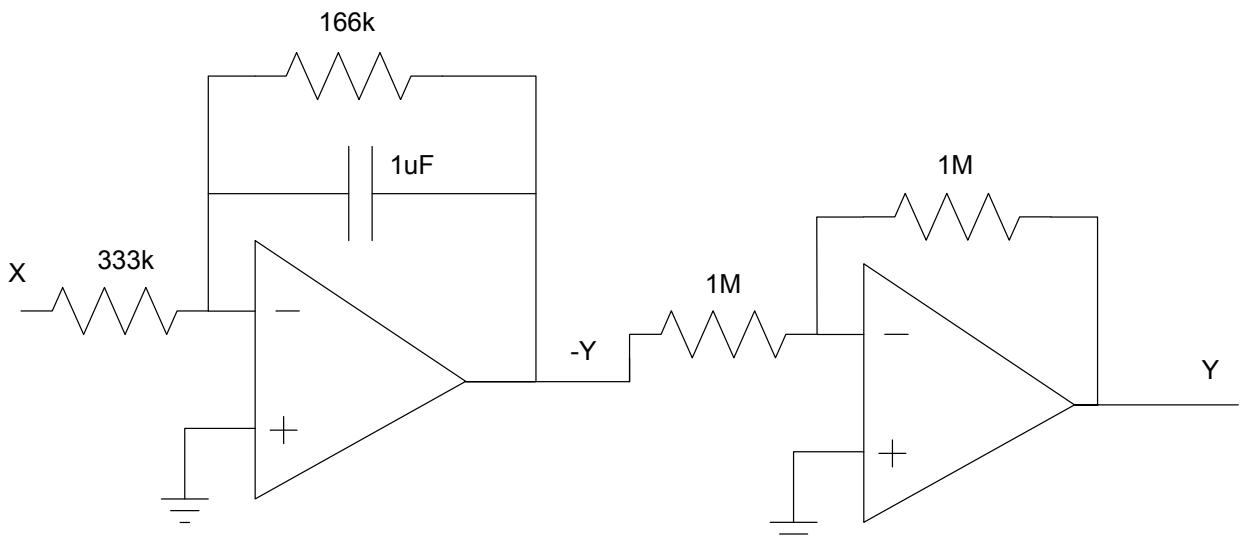

7) Integrators and Differentiators (take 2): Design an op-amp circuit to implement the following function

Input:

- $X = \pm 10V$ sinusoid, capable of driving 10mA, 0..100Hz

Output:

- $Y = 10V$ sinusoid, capable of driving 10mA, 0..100Hz

Relationship:

- $\frac{d^2y}{dt^2} + 6\frac{dy}{dt} + 5y = 2x$
-

Rewrite as

$$s^2 Y + 6s Y + 5Y = 2X$$

$$Y = \left(\frac{2}{s^2 + 6s + 5} \right) X$$

$$Y = \left(\frac{2}{(s+1)(s+5)} \right) X$$

$$Y = \left(\frac{1}{s+1} \right) \left(\frac{2}{s+5} \right) X$$

