
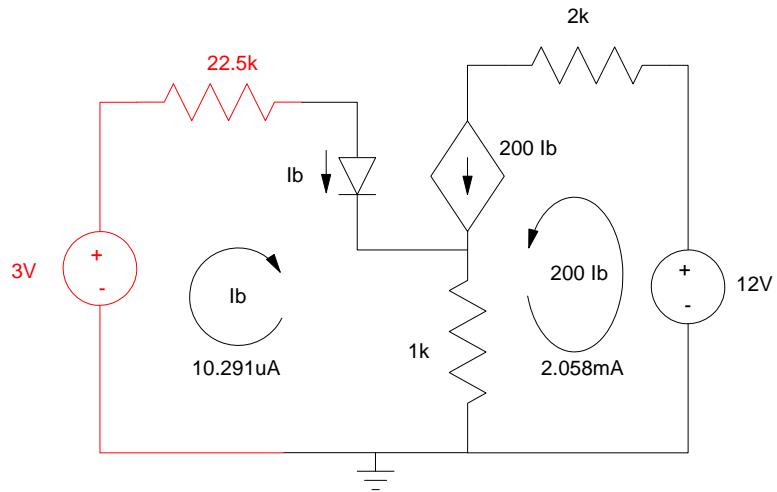


# ECE 321 - Solution to Homework #5

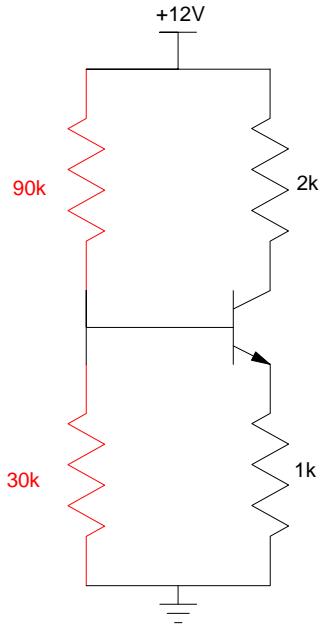1) Find the Q-point for the following circuit



First, redraw the circuit using the Thevenin equivalent for R<sub>1</sub> and R<sub>2</sub>

- $V_{th} = 3.00V$
- $R_{th} = 22.5k$

Next, analyze the circuit

$$-3V + 22500I_b + 0.7 + 1000(1 + \beta)I_b = 0$$

$$I_b = 10.291\mu A$$

$$I_c = \beta I_b = 2.058mA$$

$$V_c = 12 - 2000I_c = 7.884V$$

$$V_e = (I_b + I_c)1000 = 2.068V$$



$$V_{ce} = 5.815V$$

Q-Point:

$$I_c = 1.058mA$$


$$V_{ce} = 5.815V$$

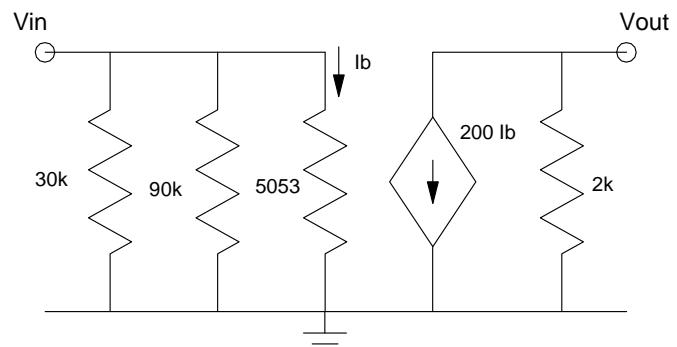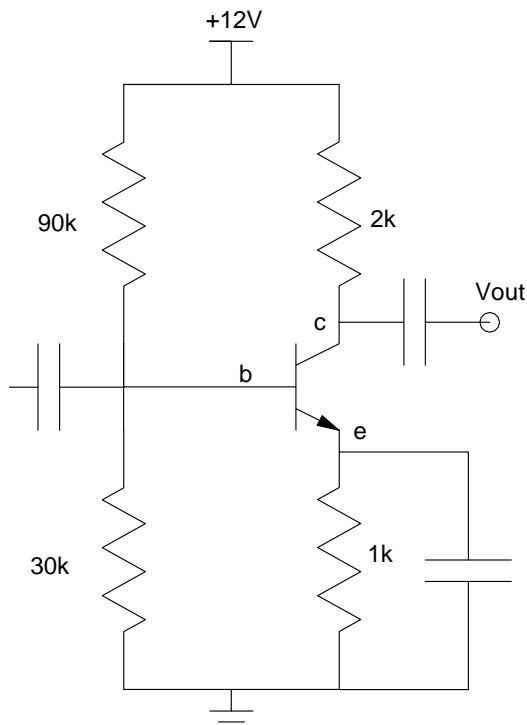2) Find the 2-port model when connected as a common-emitter amplifier





2-Port Model:

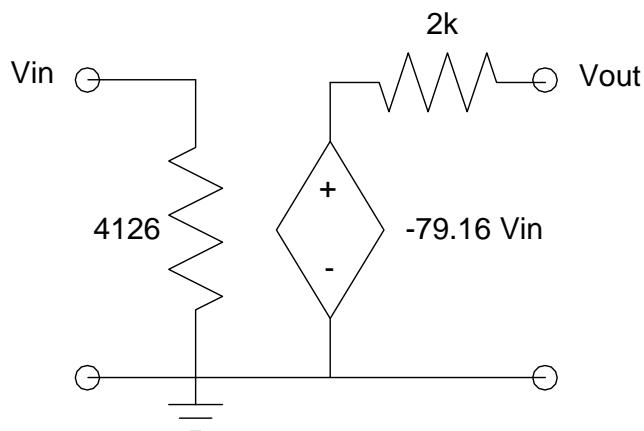- $R_{in} = 30k \parallel 90k \parallel 5053 = 4126$
- $A_i = 0$
- $R_{out} = 2k$
- $A_o = -\left(\frac{\beta R_c}{r_f}\right) = -79.16$



3) Find the 2-port model as a common-base configuration

3a) Draw the small-signal model

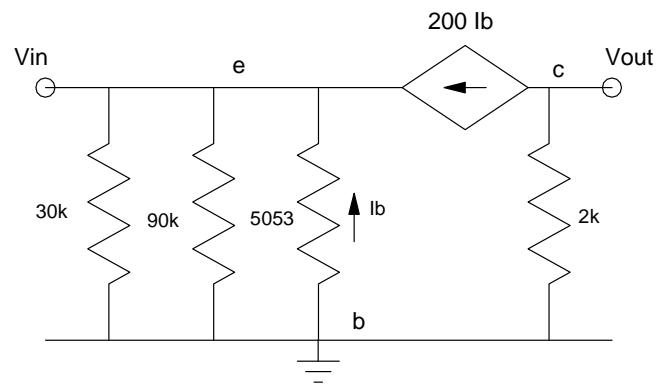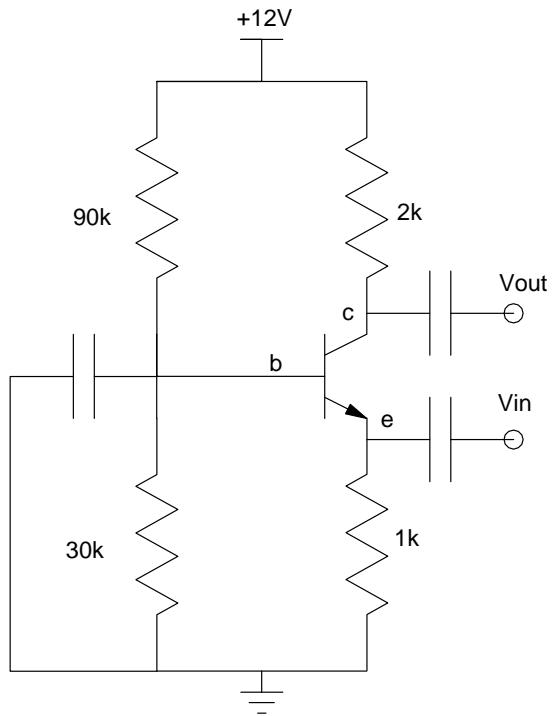


3b) Find the 2-port model

$$R_{in} = 30k \parallel 90k \parallel 5053 \parallel \frac{5053}{200} = 25.11\Omega$$

$$A_{in} = 0$$



$$R_{out} = 2k$$
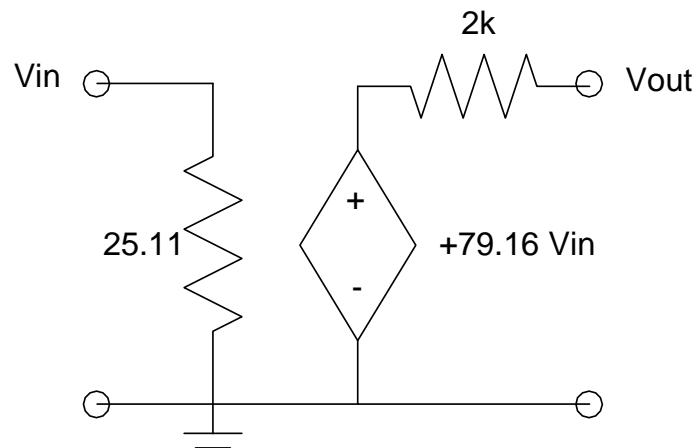
$$A_{out} = +\frac{\beta R_c}{r_f} = +79.61$$




4) Find the 2-port model as a common-collector configuration

4a) Draw the small-signal model

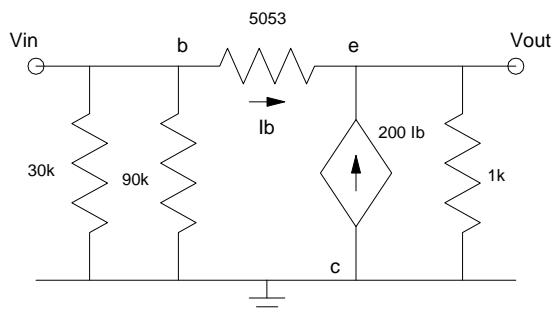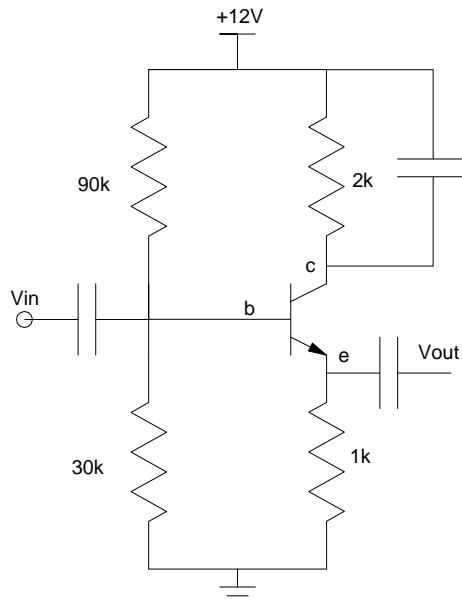

4b) Find the 2-port model

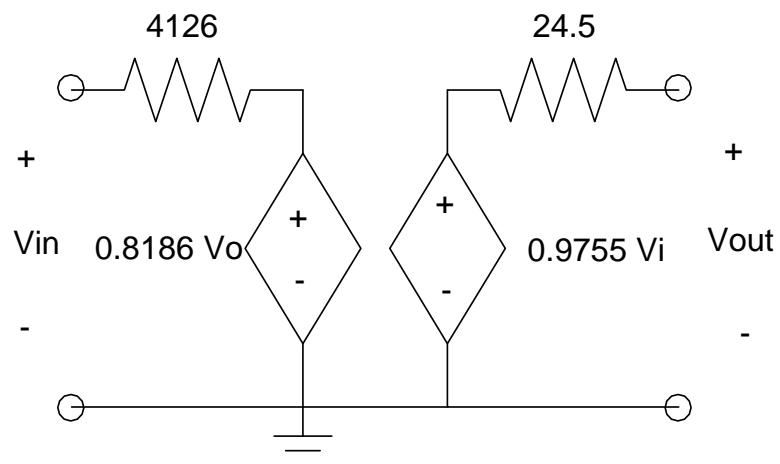- $R_{in} = 30k \parallel 90k \parallel 5053 = 4126$
- $A_{in} = \left( \frac{30k \parallel 90k}{30k \parallel 90k + 5053} \right) = 0.8166$
- $R_{out} = 1k \parallel 5053 \parallel \frac{5053}{200} = 24.5\Omega$
- $A_{out} = \left( \frac{1k}{1k + \frac{5053}{\beta+1}} \right) = 0.9755$



5) Design a multi-stage amplifier for

- Input:  $V_{in} = 1\text{uV}$ ,  $R_{th} = 1\text{k}$
- Output: 8 Ohm speaker
- Relationship:  $V_o = 1e6 V_{in}$

First stage = CE (high input impedance)

Last stage = push-pull amp

Each stage adds a gain of 53.33

$$79.16 \cdot \left( \frac{4126}{4126+2000} \right) = 53$$

To get a gain of 1,000,000

$$\left( \frac{4126}{4126+1000} \right) \cdot 53 \cdot 53 \cdot 53 \cdot 53 \cdot k = 1,000,000$$

So, 4 CE stages is enough. To trim the gain, add a resistor to reduce the gain by 5.2

