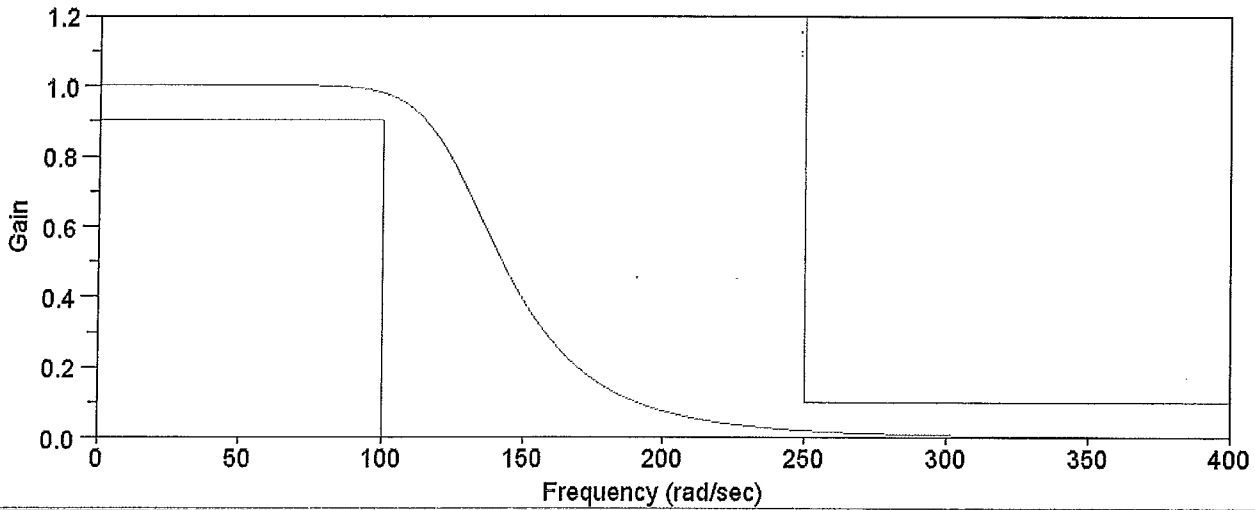


# ECE 321 - Quiz #3: Name \_\_\_\_\_

Active Filters - April 23, 2015

1) Give the pole location for a 6th-order Butterworth low-pass filter which meets the following design specifications:

- $0 < \omega < 100$  rad/sec      gain  $> 0.9$
- $\omega > 250$  rad/sec      gain  $< 0.1$



Location of 1st pair of complex poles $s = a + jb$	Location of 2nd pair of complex poles $s = c + jd$	Location of 3rd pair of complex poles $s = e + jf$
X $\angle \pm 15^\circ$	X $\angle \pm 45^\circ$	X $\angle \pm 75^\circ$


$$\frac{180^\circ}{6} = 30^\circ$$

$$100 < \omega < 150$$

anything in  
this range

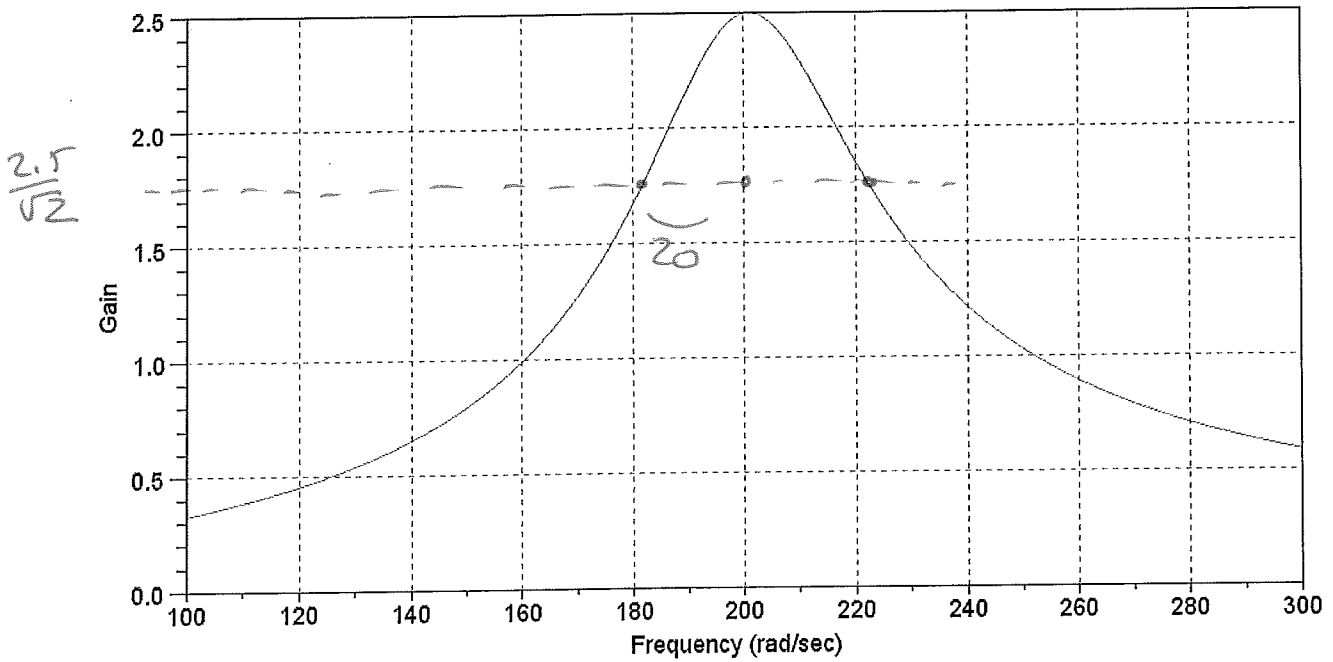2) Give the transfer function for a band-pass filter with the following gain vs. frequency

$$\frac{200\omega \text{ -or- } 100s}{(s+20+j20\omega)(s+20-j20\omega)}$$



gain at  $s=j200 = 2.5$


3) The transfer function for a 5th-order Chebychev low-pass filter with a corner at 2 rad/sec is as follows:

$$G = \left( \frac{1.81}{(s+0.327)(s^2+0.53s+1.489)(s^2+0.202s+3.72)} \right)$$

Let all capacitors be 1uF. Specify the resistors so that this filter implements the above transfer function where

$$k = 1 + \frac{R_2}{R_1}$$

Stage 1	Stage 2			Stage 3		
R	R	R1	R2	R	R1	R2
3.05m	819K	100K	256K	518K	100K	189K

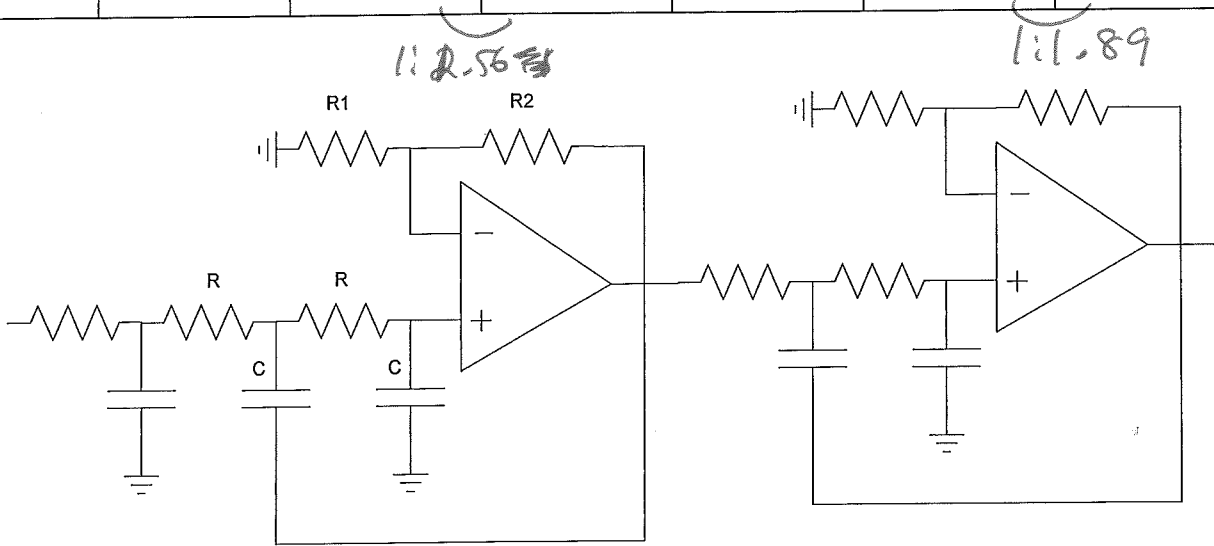

(All capacitors = 1uF)

$$\left( \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \right)$$

$$\left( \frac{k \left( \frac{1}{RC} \right)^2}{s^2 + \left( \frac{3-k}{RC} \right) s + \left( \frac{1}{RC} \right)^2} \right)$$

↑  
1.489  
gain = 2.56

$$\left( \frac{k \left( \frac{1}{RC} \right)^2}{s^2 + \left( \frac{3-k}{RC} \right) s + \left( \frac{1}{RC} \right)^2} \right)$$

gain = 2.89


4) The transfer function for a band-pass filter which passes 50 rad/sec with 3dB down frequencies of 45 and 55 rad/sec is

$$Y = \left( \frac{-20s}{s^2 + 10s + 2500} \right) X = Y = \left( \frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2}\right)\left(\frac{1}{R_3 C^2}\right)} \right) X$$

Find R and C to implement this filter. The transfer function for this filter is

R1	R2	R3	C
50k	2k	200k	1μF

↑  
given C  
find R

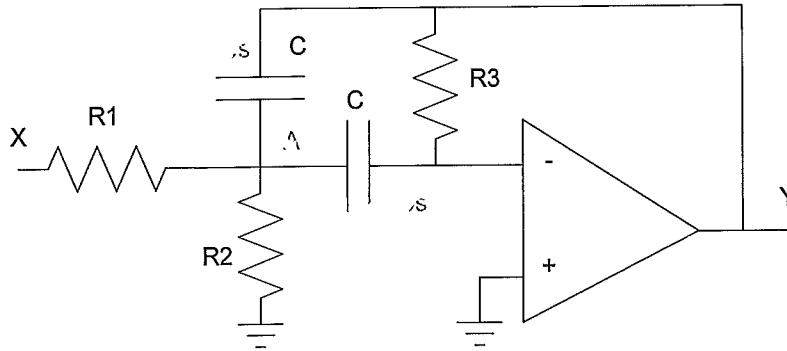

$$\frac{2}{R_3 C} = 10$$

$$R_3 = \frac{2}{10}$$

$$\frac{R_1 + R_2}{R_1 R_2} \left( \frac{1}{R_3 C^2} \right) = 2500$$

$$(R_1 || R_2) = 2000$$

5) Square waves are easy to produce. Sine waves are hard. In order to approximate a sine wave, a square wave is passed through a filter. Assume the square wave can be expressed as:

$$x(t) = 5 + 6.36 \sin(t) + 2.12 \sin(3t) + 1.27 \sin(5t) + 0.91 \sin(7t) + \dots$$

$$y(t) \approx 6.36 \sin(t)$$

Give the transfer function for a filter which passes the  $\sin(t)$  term and rejects the remaining terms:

$G(s)$ :


- Gain  $> 0.9$
- Gain  $< 0.1$

$\omega = 1$  rad/sec  
 $\omega = 0, 3, 5, 7, 9, \text{ etc}$

gain at  $s=j1$   
 $= 1$  (70.9)

$$\frac{0.2s}{(s + 0.1 + j)(s + 0.1 - j)}$$

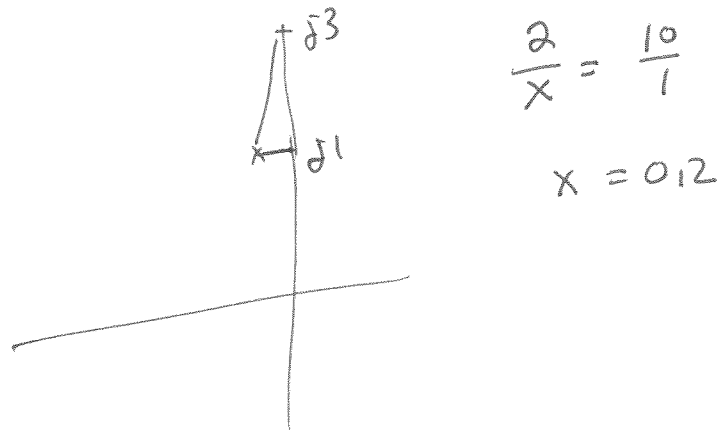Complex part =  $j1$   
 real part  $\leq 0.2$



Bonus! The mission statement of the U.S. Environmental Protection Agency (EPA) is to protect human health and the environment. Within 20%, how many EPA field offices are there in North Dakota?

Zero

