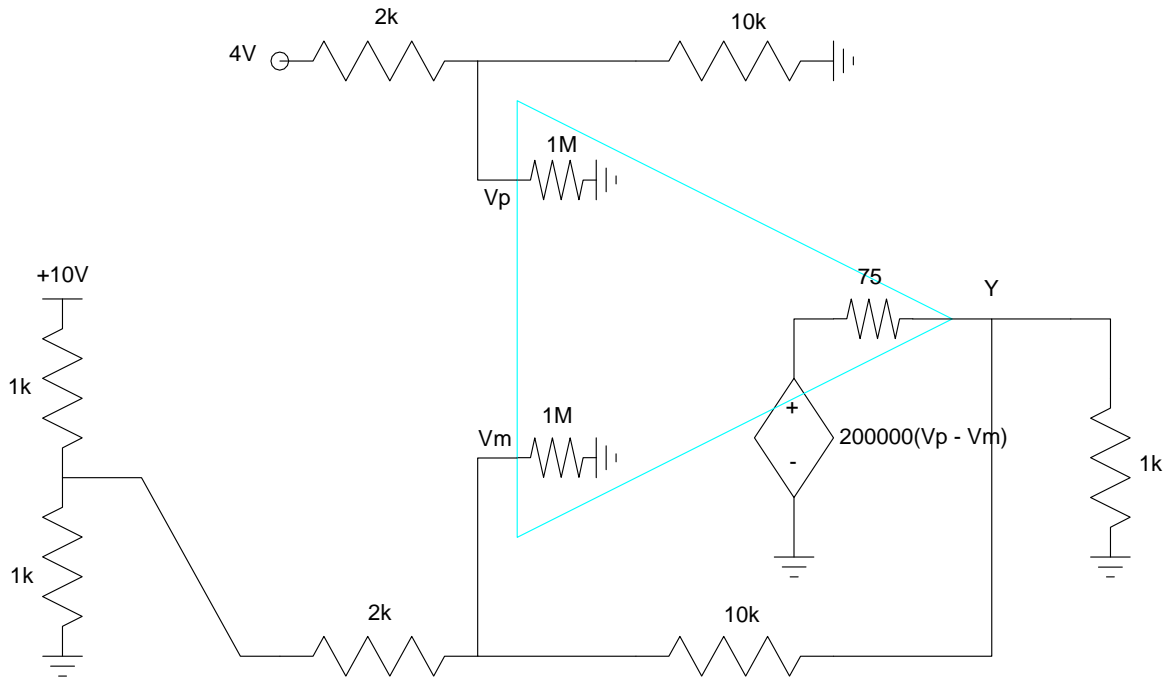


ECE 321 - Homework #1


Op-Amps, Instrumentation Amplifiers, Push-Pull Amplifiers. Due Monday, April 4th

- 1) Assume non-ideal op-amps. Write the voltage node equations for the following circuit.
- 2) Find the nodal voltages.



Problem 1 - 2

- 3) Assume ideal op-amps. Write the voltage node equations for the following circuit.
- 4) Find the nodal voltages.

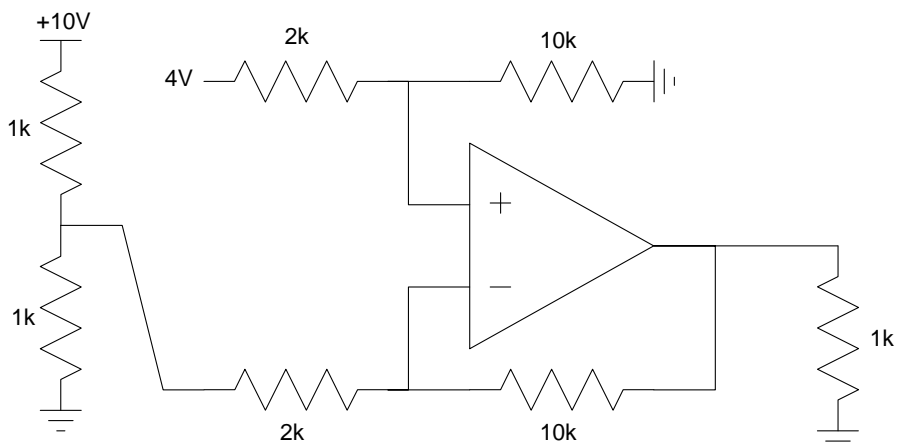

Problem 3 - 4

5) Assume a thermistor has the following resistance - temperature relationship.

$$R \approx 1000 \cdot \exp(-0.04(T - 25)) \Omega$$

Design a circuit which outputs

- -10V for $T = -20\text{C}$
- +10V for $T = +20\text{C}$
- Voltage proportional for $-20\text{C} < T < +20\text{C}$

6) Design a circuit with a push-pull amplifier

Input: -10V to +10V, capable of driving 10mA

Output: Red LED ($I > 0$) and Blue LED ($I < 0$)

Relationship:

$I = -100\text{mA}$ to $+100\text{mA}$, proportional to V :

$$I = V/100$$