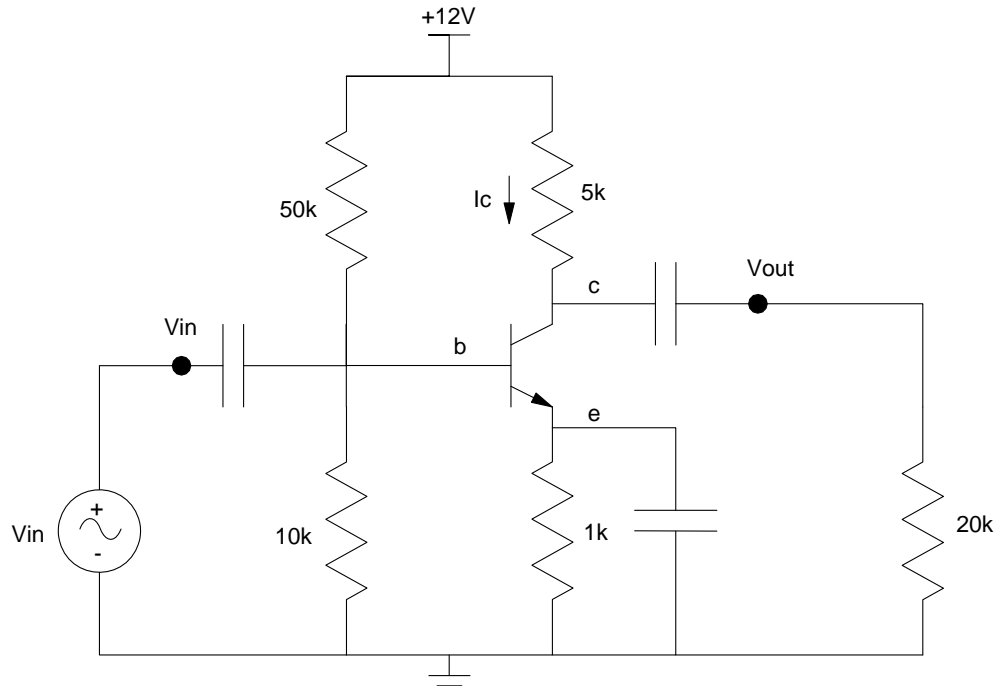


# ECE 321 - Homework #4

BJT Amplifier Design. Due Monday, April 25th

For each problem, use the following circuit. Assume an ideal silicon diode with  $\beta = 100$




Problem 1-3: BJT Amplifier in Common Base or Common Collector Configuration

- 1a) Draw the small-signal model for this circuit in common base configuration.
- 1b) Determine the 2-port model for this circuit in common base configuration.
  
- 2a) Draw the small-signal model for this circuit in common collector configuration.
- 2b) Determine the 2-port model for this circuit in common collector configuration.
  
- 3) Determine the 2-port model for a common emitter : common collector amplifier.

MOSFET Amplifier: Assume for the MOSFET amplifier (next page) that

- $V_{tn} = 2V$
  - $k_n = 0.001 \frac{A}{V^2}$
- 4) Determine R1 and R2 so that the Q point is  $V_{ds} = 6V$  and  $R1 \parallel R2 = 100k$  Ohms
  - 5) Determine the 2-port model for this MOSFET amplifier in common source configuration.

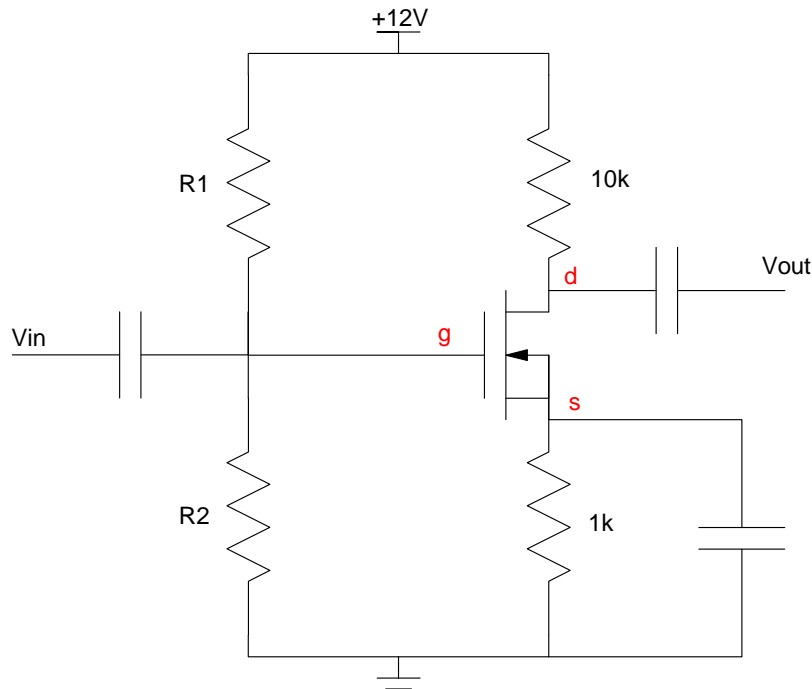

Problem 4-5: Common Source Amplifier

6) Use CE / CC / CB / CD amplifiers to design a multi-stage amplifier to meet the following requirements:

Input:

- 1uVpp sine wave at 1kHz, output impedance = 100k Ohms

Output:

- 8 Ohm Speaker

Relationship:

- 1uVpp sine wave at the input drives the 8 Ohm speaker at 4 Watts at 1kHz, +/- 1 Watt

## Problem 7-10) Term Project

Design, build, and test one section of your term project. Include

- 7) Requirements. What are the inputs, output, and how they relate.
- 8) Analysis: Give computations for resistors, etc. so that your circuit meets your requirements.
- 9) Test: Simulate in PartSim (or like program) to verify your analysis
- 10) Validation: Build your circuit in lab and collect data to verify it meets your requirements.