

ECE 321 - Quiz #4: Name _____


BJT Amplifiers. April 28, 2016

1) BJT DC Analysis:

1a) Convert R1 and R2 to its Thevenin equivalent to find V_b and R_b.

1b) Determine the Q-point for the following BJT circuit:


V _b	R _b	I _c	V _{ce}
2V	16.67K	1.105mA	6.456V

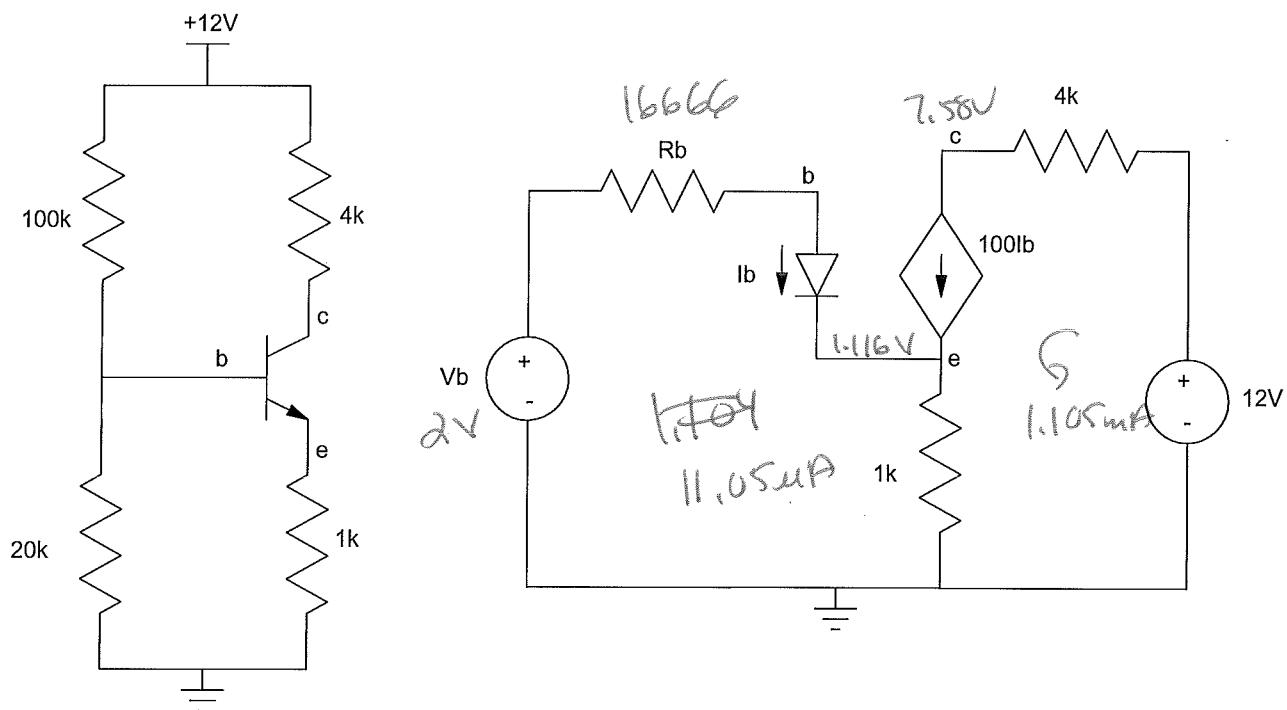

2) Find R₁ and R₂ so that

- The Q-point is stabilized for variations in β , and
- $V_{ce} = 4V$

R ₁	R ₂	V _b	R _b
48.53k	12.60k	2.472V	10k

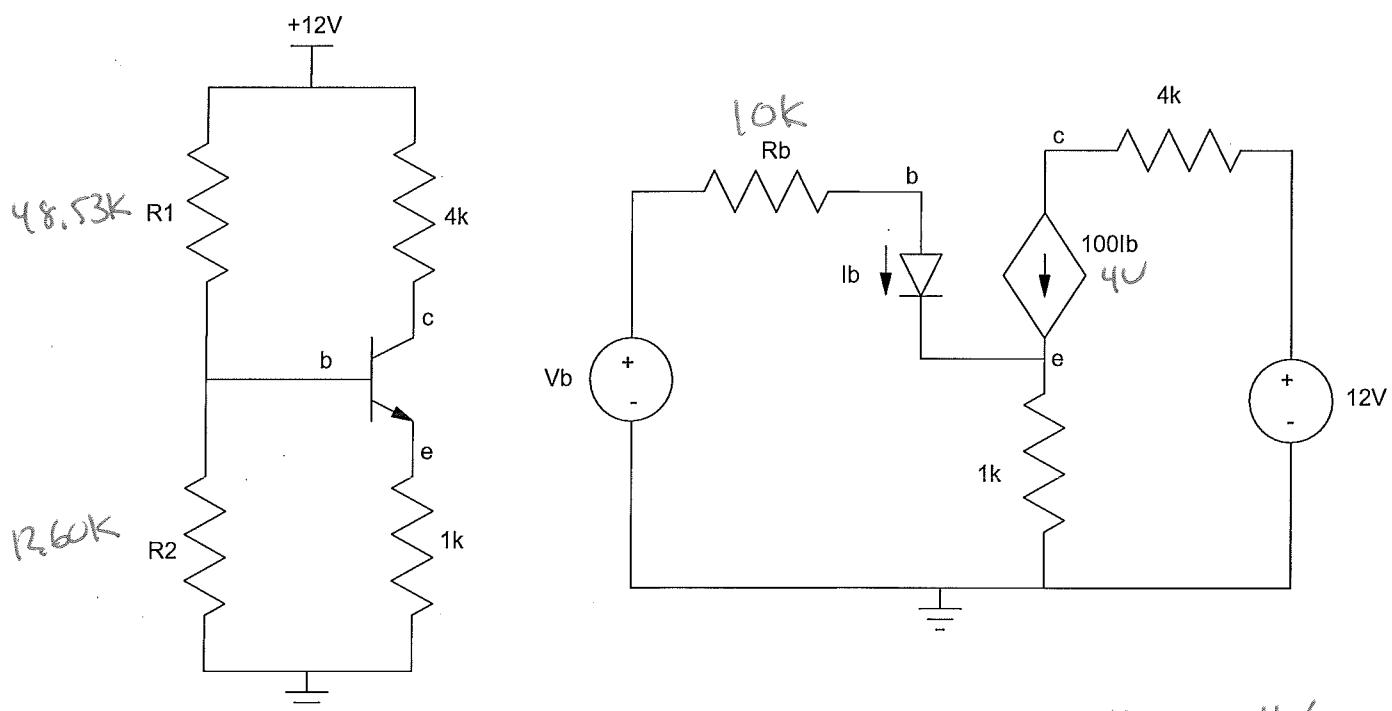

$$8V = 4k \cdot I_c + 1k(I_c + I_b)$$

$$I_c = 1.597 \mu A$$

$$I_b = 15.97 \mu A$$



$$V_b = 2.472V$$

A_{1u}

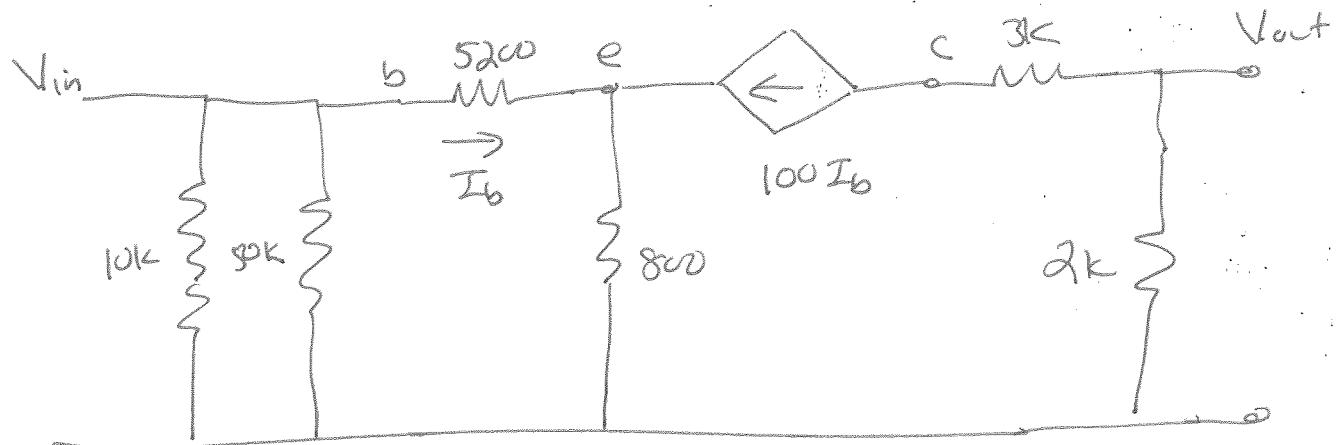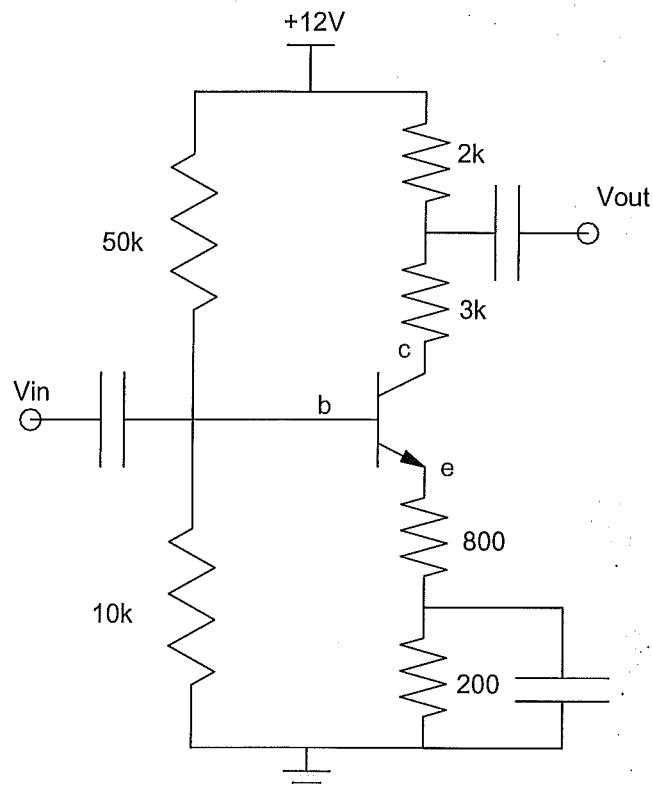3) Assume the Q-point for the BJT amplifier is


- $I_{bq} = 10\mu A$
- $r_f = 5200\Omega$

Draw the small-signal model (AC model) of the following circuit connected in common-emitter configuration:



4) Find the 2-port model for the following circuit:

Rin	Ai	Rout	Ao
49,35	0	2k	+40

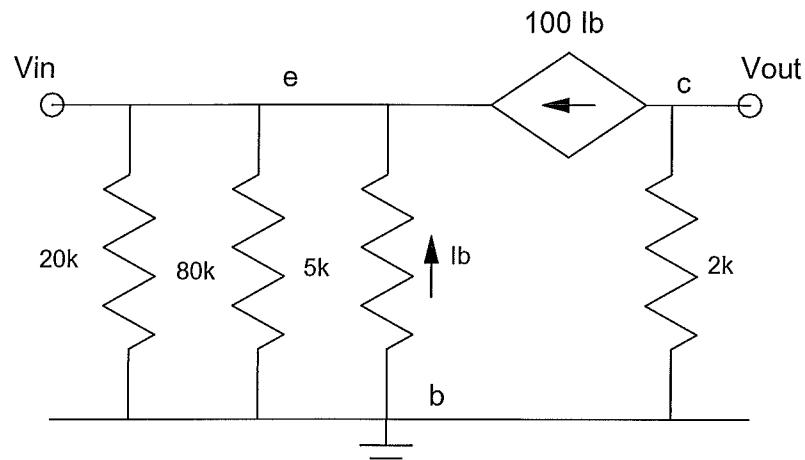


$$R_{in} = 20k \parallel 80k \parallel 5k \parallel \frac{5k}{100} = 49,35$$

$$A_{o^2} = \frac{\beta \cdot 2k}{r_f} = \frac{100 \cdot 2000}{5000} = 40$$

5) Find the 2-port model for the following CE : CE amplifier

Rin	Ai	Rout	Ao
1k	○	$\frac{3k}{2k}$	+3333

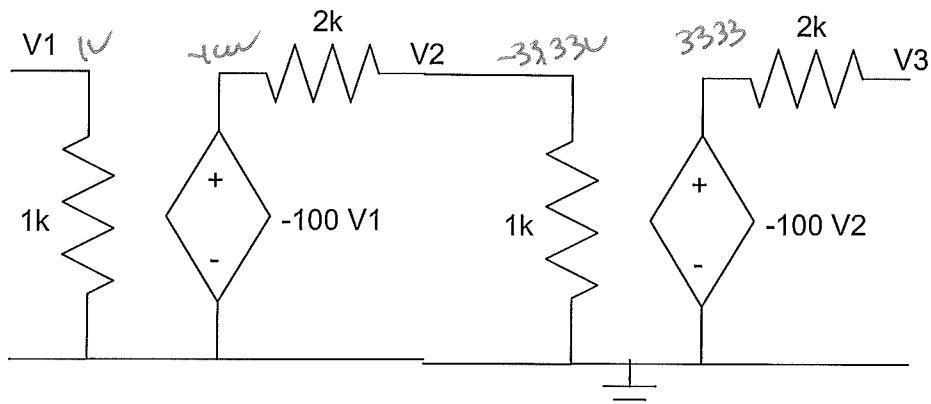

Bonus: Godzilla / Bernie Sanders Trivia! Which is older:

- Godzilla (based upon the first movie release) or
- Bernie Sanders?