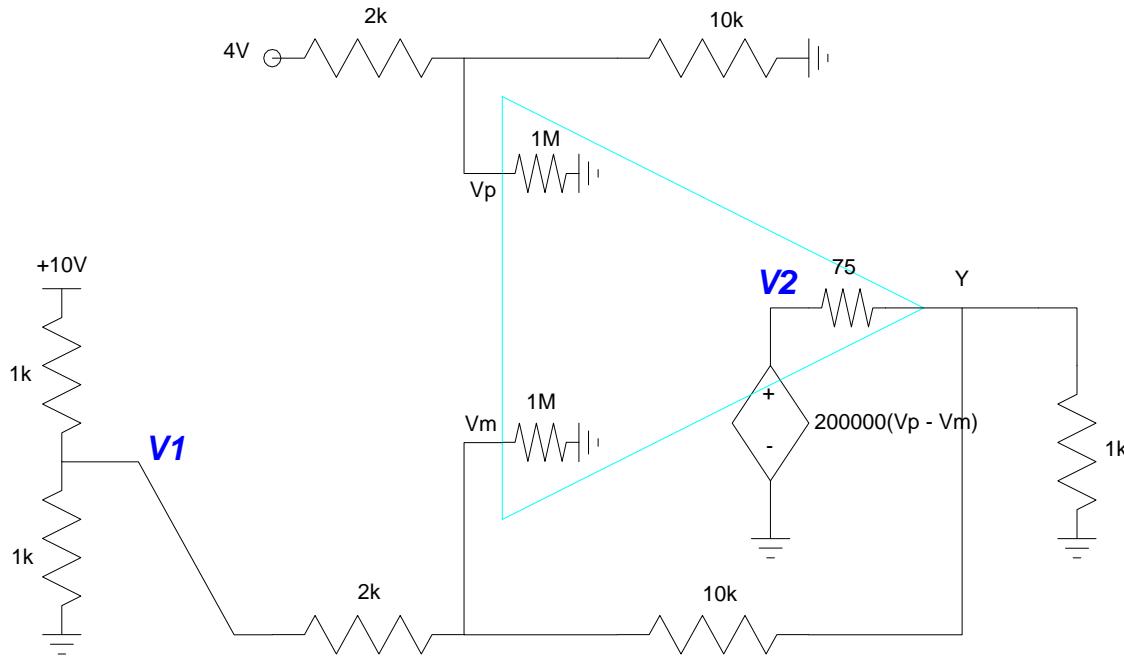


ECE 321 - Homework #1

Op-Amps, Instrumentation Amplifiers, Push-Pull Amplifiers. Due Monday, April 4th

- 1) Assume non-ideal op-amps. Write the voltage node equations for the following circuit.
- 2) Find the nodal voltages.



Problem 1 - 2

$$V1: \left(\frac{V_1 - 10}{1k} \right) + \left(\frac{V_1}{1k} \right) + \left(\frac{V_1 - V_m}{2k} \right) = 0$$

$$V2: V_2 = 200000(V_p - V_m)$$

$$Vp: \left(\frac{V_p - 4}{2k} \right) + \left(\frac{V_p}{10k} \right) + \left(\frac{V_p}{1M} \right) = 0$$

$$Vm: \left(\frac{V_m - V_1}{2k} \right) + \left(\frac{V_m - Y}{10k} \right) + \left(\frac{V_m}{1M} \right) = 0$$

$$Y: \left(\frac{Y - V_2}{75} \right) + \left(\frac{Y - V_m}{10k} \right) + \left(\frac{Y}{1k} \right) = 0$$

2) Solve. First rewrite, grouping terms:

$$2.5V_1 - 0.5V_m = 10$$

$$V_2 - 200000V_p + 200000V_m = 0$$

$$1.202V_p = 4$$

$$1.202V_m - V_1 - 0.2Y = 0$$

$$1.0825Y - V_2 - 0.0075V_m = 0$$

Put in matrix form:

$$\begin{bmatrix} 2.5 & 0 & 0 & -0.5 & 0 \\ 0 & 1 & -200k & 200k & 0 \\ 0 & 0 & 1.202 & 0 & 0 \\ -1 & 0 & 0 & 1.202 & -0.2 \\ 0 & -1 & 0 & -0.0075 & 1.0825 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_p \\ V_m \\ Y \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 4 \\ 0 \\ 0 \end{bmatrix}$$

```
>> A=[ 2.5,0,0,-0.5,0;
       0,1,-200000,200000,0;
       0,0,1.202,0,0;
       -1,0,0,1.202,-0.2;
       0,-1,0,-0.0075,1.0825]
```

$$1.0e+005 *$$

$$\begin{bmatrix} 0.0000 & 0 & 0 & -0.0000 & 0 \\ 0 & 0.0000 & -2.0000 & 2.0000 & 0 \\ 0 & 0 & 0.0000 & 0 & 0 \\ -0.0000 & 0 & 0 & 0.0000 & -0.0000 \\ 0 & -0.0000 & 0 & -0.0000 & 0.0000 \end{bmatrix}$$


```
>> B = [10;0;4;0;0]
```

$$\begin{bmatrix} 10 \\ 0 \\ 4 \\ 0 \\ 0 \end{bmatrix}$$

```
>> V = inv(A)*B
```

V1	4.6656
V2	-3.6272
Y	3.3278
Vp	3.3278
Vm	-3.3277

3) Assume ideal op-amps. Write the voltage node equations for the following circuit.

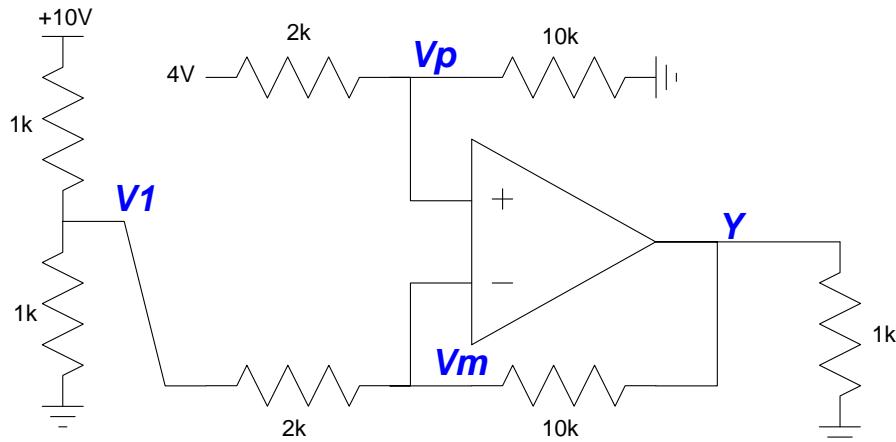

Problem 3 - 4

$$V1: \left(\frac{V_1 - 10}{1k} \right) + \left(\frac{V_1}{1k} \right) + \left(\frac{V_1 - V_m}{2k} \right) = 0$$

$$Y: \quad V_p = V_m$$

$$Vp: \left(\frac{V_p - 4}{2k} \right) + \left(\frac{V_p}{10k} \right) = 0$$

$$Vm: \left(\frac{V_m - V_1}{2k} \right) + \left(\frac{V_m - Y}{10k} \right) = 0$$

4) Find the nodal voltages.

Rewrite:

$$2.5V_1 - 0.5V_m = 10$$

$$V_p - V_m = 0$$

$$1.2V_p = 4$$

$$1.2V_m - V_1 - 0.2Y = 0$$

Put in matrix form:

$$\begin{bmatrix} 2.5 & 0 & -0.5 & 0 \\ 0 & 1 & -1 & 0 \\ 0 & 1.2 & 0 & 0 \\ -1 & 0 & 1.2 & -0.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_p \\ V_m \\ Y \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 4 \\ 0 \end{bmatrix}$$

Solve in Matlab:

```
>> A = [2.5,0,-0.5,0;0,1,-1,0;0,1.2,0,0;-1,0,1.2,-0.2]
2.5000      0    -0.5000      0
      0    1.0000   -1.0000      0
      0    1.2000      0      0
    -1.0000      0    1.2000   -0.2000
>> B = [10;0;4;0]
10
0
4
0
>> V = inv(A)*B
v1    4.6667
vp    3.3333
vm    3.3333
y    -3.3333
```

Compare to the previous solution:

```
v1    4.6656
v2   -3.6272
y    3.3278
vp    3.3278
vm   -3.3277
```

5) Assume a thermistor has the following resistance - temperature relationship.

$$R \approx 1000 \cdot \exp(-0.04(T - 25)) \Omega$$

Design a circuit which outputs

- -10V for T = -20C
- +10V for T = +20C
- Voltage proportional for -20V < T < +20C

Assume a 3k resistor for a voltage divider:

At -20C: ($V_o = -10V$)

$$R = 6049 \text{ Ohms}$$

$$V_a = 6.685V$$

At +20C: ($V_o = +10V$)

$$R = 1221 \text{ Ohms}$$

$$V_a = 2.8934V$$

The output voltage increases as V_a decreases. Connect the divider to the - input

The gain is

$$gain = \frac{\delta V_{out}}{\delta V_{in}} = \frac{20V}{6.685V - 2.8934V} = 5.2748$$


Let $R_1 = 100k$, $R_2 = 527.48k$

The offset fixes a point. At +20C, the output is +10V

$$V_o = gain(V_p - V_m)$$

$$10V = 5.2748(V_p - 2.8934V)$$

$$V_p = 4.7892V$$

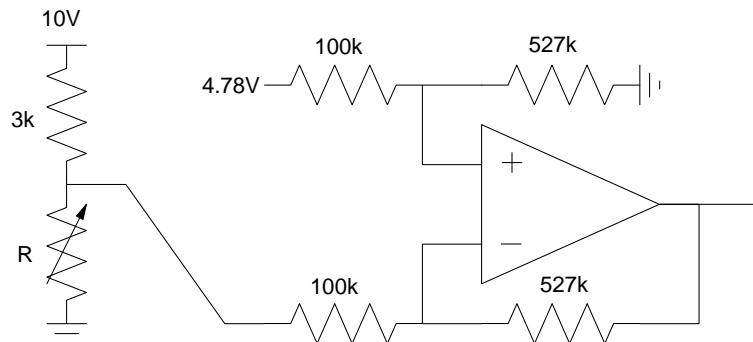

6) Design a circuit with a push-pull amplifier

Input: -10V to +10V, capable of driving 10mA

Output: Red LED ($I > 0$) and Blue LED ($I < 0$)

Relationship:

$I = -100\text{mA}$ to $+100\text{mA}$, proportional to V :

$$I = V/100$$

