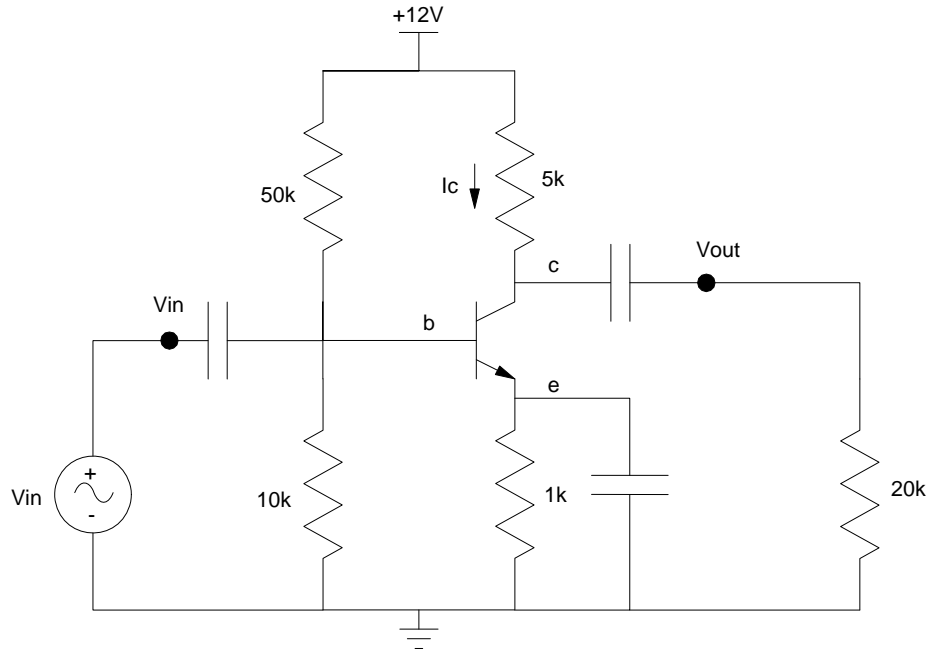


ECE 321 - Homework #5


BJT Amplifier Design. Due Monday, April 25th

For each problem, use the following circuit. Assume an ideal silicon diode with $\beta = 100$



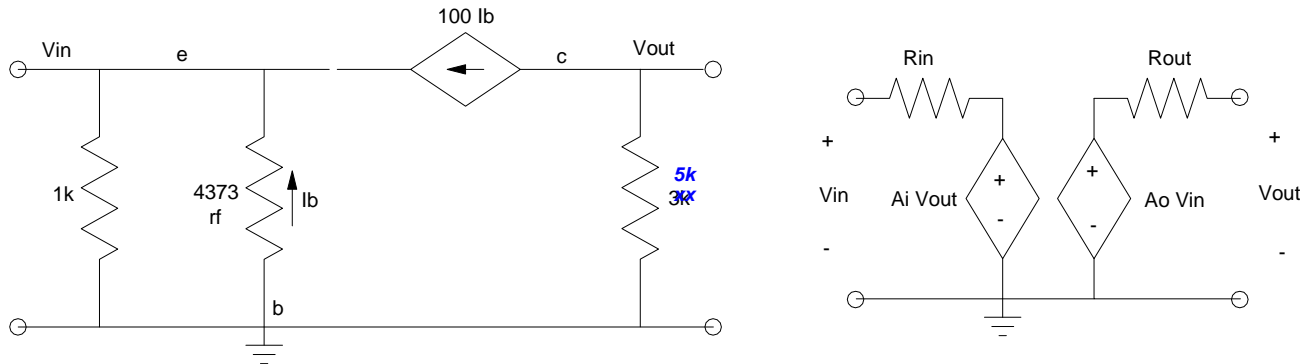Problem 1-3: BJT Amplifier in Common Base or Common Collector Configuration

1a) Draw the small-signal model for this circuit in common base configuration.



1b) Determine the 2-port model for this circuit in common base configuration.



$$R_{in}: 1k \parallel 4373 \parallel 4373/100 = 41.5 \text{ Ohms}$$

$$A_i: 0$$

$$R_{out}: 5k$$

$$A_o: \left(\frac{5k \cdot 100}{4373} \right) = +114$$

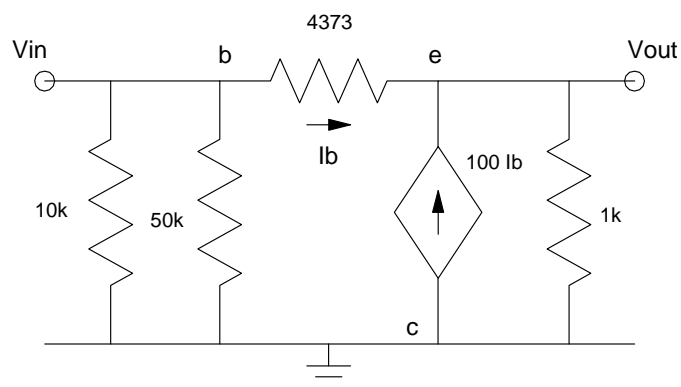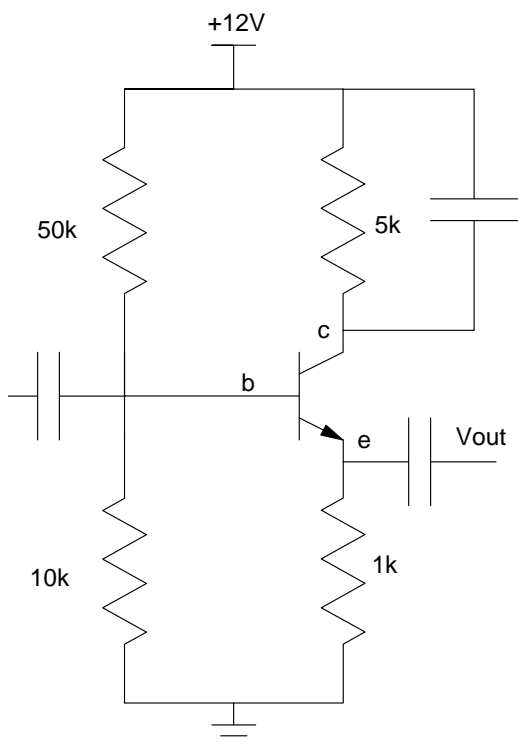2a) Draw the small-signal model for this circuit in common collector configuration.



2b) Determine the 2-port model for this circuit in common collector configuration.

$$R_{in}: 10k \parallel 50k \parallel 4373 = 2688$$


$$A_i: \left(\frac{10k \parallel 50k}{10k \parallel 50k + 4373} \right) = 0.6558$$

$$A_o: \left(\frac{X-1}{4373} \right) + 100 \left(\frac{X-1}{4373} \right) + \left(\frac{X}{1000} \right) = 0$$

$$X = A_o = 0.9585$$

$$R_o: 1k \parallel 4373 \parallel 4373/100 = 41.5$$

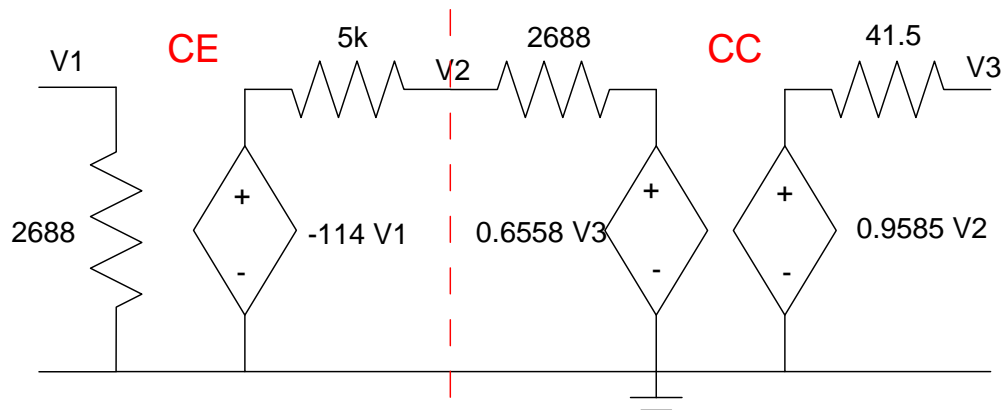3) Determine the 2-port model for a common emitter : common collector amplifier.



$R_{in} = 2688$ $A_i = 0$ R_{out} : Short V_1 . Apply 1V to V_3 . Compute the current

$$V_1 = 0$$

$$V_2 = \left(\frac{5k}{5k+2688} \right) 0.6558V = 0.4265V$$

$$0.9585V_2 = 0.4088V$$

$$I_{in} = \left(\frac{1V-0.4088V}{41.5\Omega} \right)$$

$$R_{out} = \frac{1}{I_{in}} = \left(\frac{41.5\Omega}{1V-0.4088V} \right) = 70.2\Omega$$

Ao: Apply 1V to V_1 . Compute V_3

$$V_2 = \left(\frac{2688}{2688+5000} \right) (-114V) + \left(\frac{5k}{5k+2688} \right) (0.6558V_3)$$

$$V_3 = 0.9585V_2$$

Solving 2 equations for 2 unknowns

$$V_2 = 67.42V$$

$$V_3 = A_o = 64.62$$

MOSFET Amplifier: Assume for the MOSFET amplifier (next page) that

- $V_{tn} = 2V$
- $k_n = 0.001 \frac{A}{V^2}$

4) Determine R_1 and R_2 so that the Q point is $V_{ds} = 6V$ and $R_1 \parallel R_2 = 100k$ Ohms

$$I_{ds} = \frac{12V-6V}{10k+1k} = 545.5\mu A$$

$$V_s = 1000I_{ds} = 545.5mV$$

$$I_{ds} = \frac{k_n}{2}(V_{gs} - V_{th})^2$$

$$V_{gs} = 3.044V$$


$$V_g = 3.590V$$

$$\left(\frac{R_2}{R_1+R_2}\right) 12V = 3.590V$$

$$R_1 \parallel R_2 = 100k$$

$$R_1 = 334k$$

$$R_2 = 143k$$

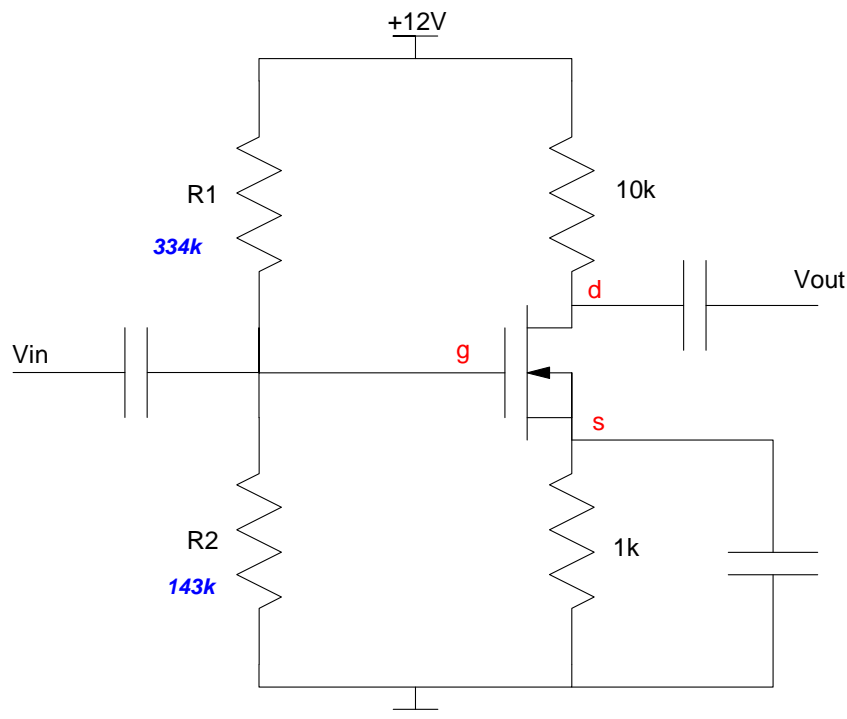



Problem 4-5: Common Source Amplifier

5) Determine the 2-port model for this MOSFET amplifier in common source configuration.

$$g_m = \frac{dI_{ds}}{dV_{gs}} = \frac{d}{dV_{gs}} \left(\frac{k_n}{2} (V_{gs} - V_{th})^2 \right)$$

$$g_m = (k_n (V_{gs} - V_{th}))$$

$$g_m = 0.003044 \frac{A}{V}$$

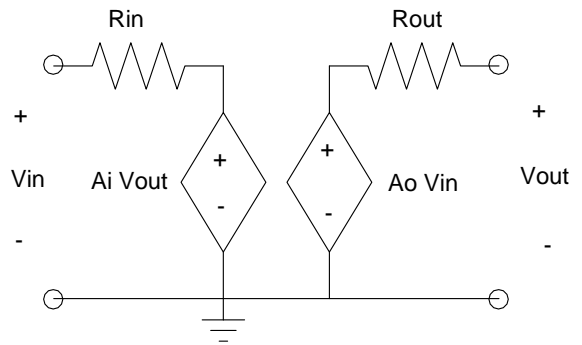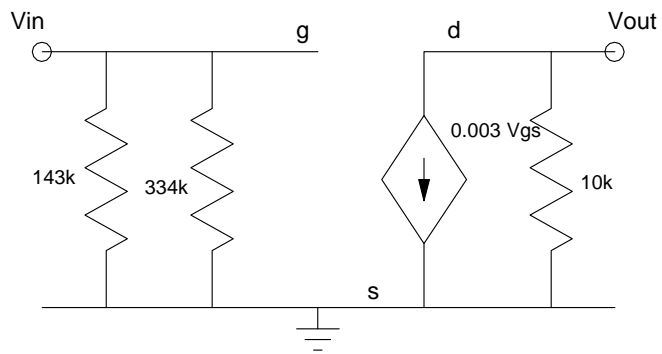

$$R_{in}: 143k \parallel 334k = 100k$$

$$A_i: 0$$

$$R_{out}: 10k$$

$$A_o: -10k \cdot g_m = -30.44$$

6) Use CE / CC / CB / CS amplifiers to design a multi-stage amplifier to meet the following requirements:

Input:


- 1 μ Vpp sine wave at 1kHz, output impedance = 100k Ohms

Output:

- 8 Ohm Speaker

Relationship:

- 1 μ Vpp sine wave at the input drives the 8 Ohm speaker at 4 Watts at 1kHz, \pm 1 Watt

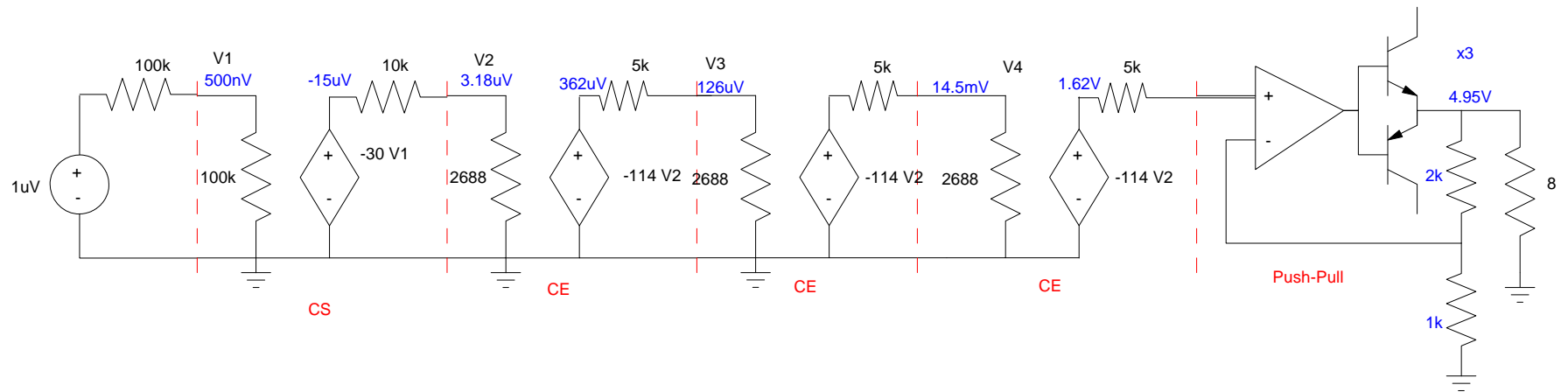

Problem 7-10) Term Project

Design, build, and test one section of your term project. Include

- 7) Requirements. What are the inputs, output, and how they relate.
- 8) Analysis: Give computations for resistors, etc. so that your circuit meets your requirements.
- 9) Test: Simulate in PartSim (or like program) to verify your analysis
- 10) Validation: Build your circuit in lab and collect data to verify it meets your requirements.