

ECE 321 Homework #5

Sound on a Light Beam. Due Friday, May 5th

- 1) LED Analysis: Assume the LED has the following characteristics
 - $V_f = 3.3V @ 100mA$
 - $1200 \text{ lux} @ 20mA @ 3cm$
- a) Calculate the DC current through the LED.
- b) Find the impedance of the $1\mu F$ capacitor at $1kHz$
- c) Compute the AC current through the LED assuming the input is $100mV_{pp}$ at $1kHz$.
- d) Compute the Lux produced by the LED (DC and AC terms)

- 2) CdS Analysis: Assume the CdS light sensor has the characteristic

$$R = \frac{280,000}{Lux}$$

- a) Determine the DC resistance of the CdS light sensor
- b) Determine the AC resistance of the CdS light sensor
- c) Determine the voltage at point B (DC and AC term). Assume the input is $1mV_{pp}$ at $1kHz$

- 3) Determine the gain of the non-inverting amplifier so that the output at point D is $2V_{pp}$ at $1kHz$

Bonus!: Build this circuit in lab and drive the filter - push pull amplifier from previous homework sets.

Collect data to verify your calculations for the LED and CdS sensor.

