

ECE 321: Quiz #2 Name _____

9:00 / 11:00

Op-Amp Filters - April 13, 2017

- 1) X and Y are related by the following low-pass filter with real poles:

$$Y = \left(\frac{30}{(s+2)(s+5)} \right) X = \left(\frac{30}{s^2 + 7s + 10} \right) X$$

What is the differential equation relating X and Y?

Differential Equation relating X and Y

$$y'' + 7y' + 10y = 30x$$

What is $y(t)$ assuming $x(t) = 2 + 3 \sin(4t)$

$y(t)$ assuming $x(t) = 2 + 3 \sin(4t)$

$$y = 6 + 3.14 \sin(4t - 102^\circ)$$

$$s=0$$

$$\text{gain} = 3$$

$$y = 3 \cdot 2 = 6$$

$$s=j4$$

$$\text{gain} = \left(\frac{30}{s^2 + 7s + 10} \right)_{s=j4}$$


$$\text{gain} = 1.04 \angle -102^\circ$$

$$y = 3.14 \sin(4t - 102^\circ)$$

2) Find R and C to implement the following transfer function

$$Y = \left(\frac{30}{(s+2)(s+5)} \right) X = \left(\frac{30}{s^2 + 7s + 10} \right) X$$

C1	C2	R3
50 μ F	2 μ F	30k 2k
20 μ F	5 μ F	

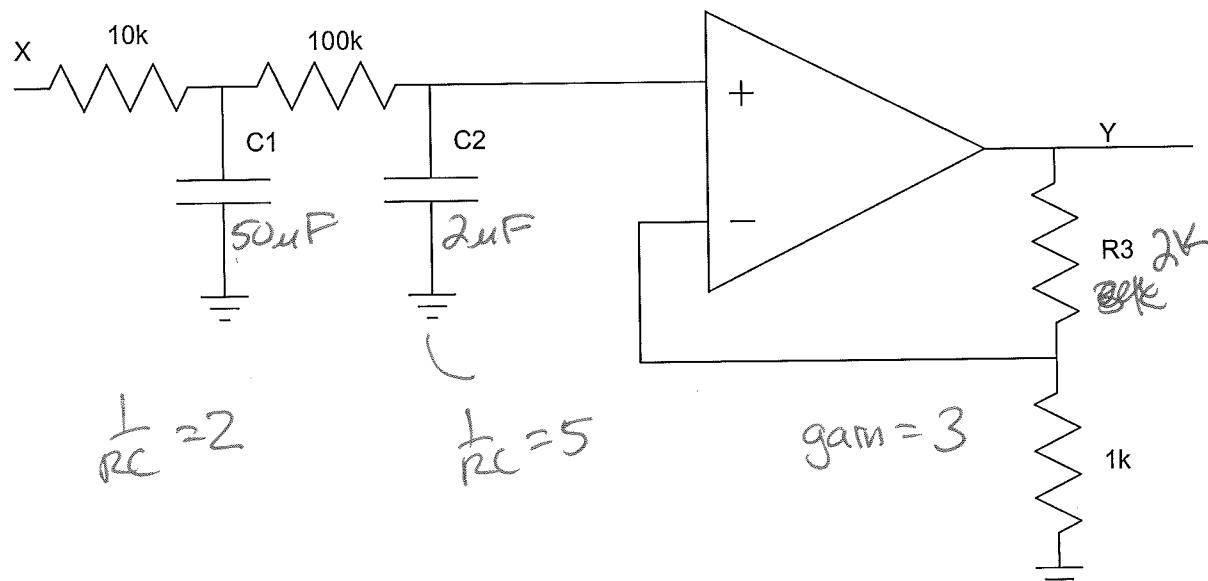

3) X and Y are related by the following low-pass filter with complex poles:

$$Y = \left(\frac{30}{(s+2+j5)(s+2-j5)} \right) X = \left(\frac{30}{s^2 + 4s + 29} \right) X$$

What is the differential equation relating X and Y?

Differential Equation relating X and Y

$$y'' + 4y' + 29y = 30x$$

What is y(t) assuming $x(t) = 2 + 3 \sin(4t)$

y(t) assuming $x(t) = 2 + 3 \sin(4t)$

$$y = 2.06 + 4.36 \sin(4t - 51^\circ)$$

$$s=0$$

$$\text{gain} = \frac{30}{29}$$

$$y = 2.06$$

$$s=j4$$

$$\text{gain} = \left(\frac{30}{s^2 + 4s + 29} \right)_{s=j4}$$

$$\text{gain} = 6.455 \angle -51^\circ$$

$$y = 4.36 \sin(4t - 51^\circ)$$

4) Find R and C to implement the following transfer function

$$Y = \left(\frac{300}{(s+2+j5)(s+2-j5)} \right) X = \left(\frac{300}{s^2 + 4s + 29} \right) X$$


note: The filter below has the transfer function of

$$Z = \left(\frac{k \left(\frac{1}{RC} \right)^2}{s^2 + \left(\frac{3-k}{RC} \right)s + \left(\frac{1}{RC} \right)^2} \right) X \quad k = 1 + \frac{R_1}{1k}$$

R	C	R1	R3
100k	1.85μF	1.2572k	3.58k

$$\frac{1}{RC} = 5.385$$
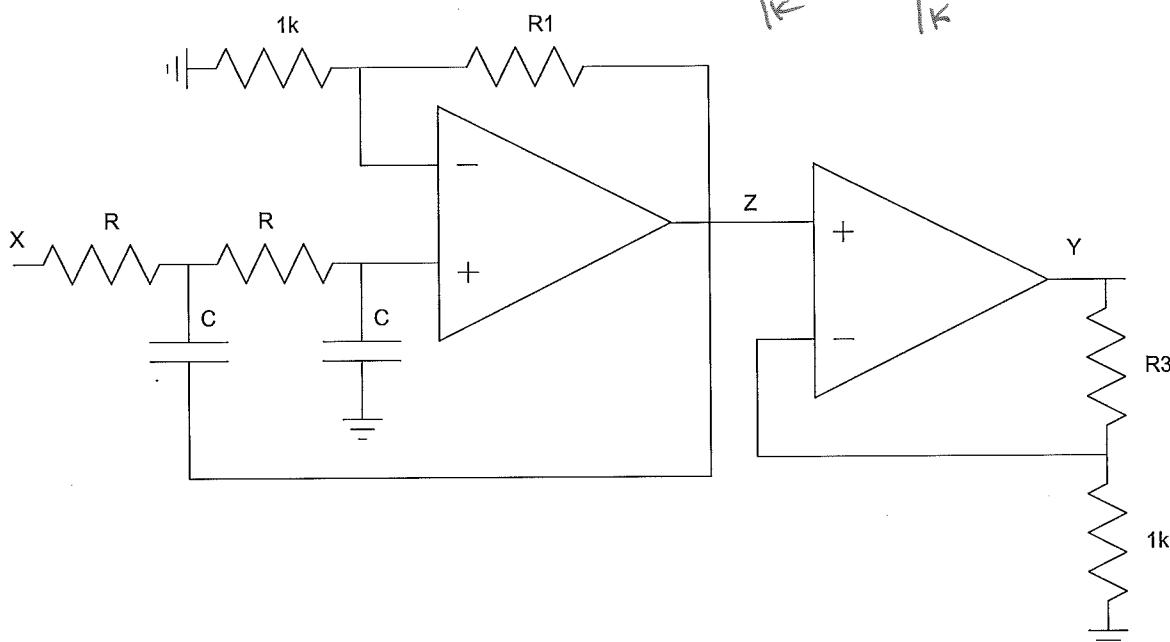
$$\frac{(1+R_1)}{1k} \cdot \frac{(1+R_3)}{1k} = \frac{300}{29}$$



$$\frac{1}{RC} = \sqrt{29} = 5.385$$

$$\text{total DC gain} = \frac{300}{29}$$

$$R = 100k$$

$$(2.2572)(k_2) = 10.34$$

$$C = 1.85\mu F$$

$$k_2 = 4.58$$

$$k_2 (3-k) (5.385) = 4$$

$$3-k = .7428$$

$$k = 2.2572$$

5) Find R and C so that the following band-pass filter has the transfer function of

$$Y = -\left(\frac{8s}{s^2 + 4s + 100}\right)X$$

$$\frac{R_1 + R_2}{R_1 R_2 R_3 C^2} = 100$$


The transfer function for this filter is

$$Y = \left(\frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}\right)} \right) X$$

$$(R_1 + R_2) = 100 R_1 R_2 R_3 C^2$$

$$R_2 = \frac{R_1}{100 R_1 R_3 C^2 - 1}$$

R1	R2	R3	C
125k	23.8k	500k	1uF

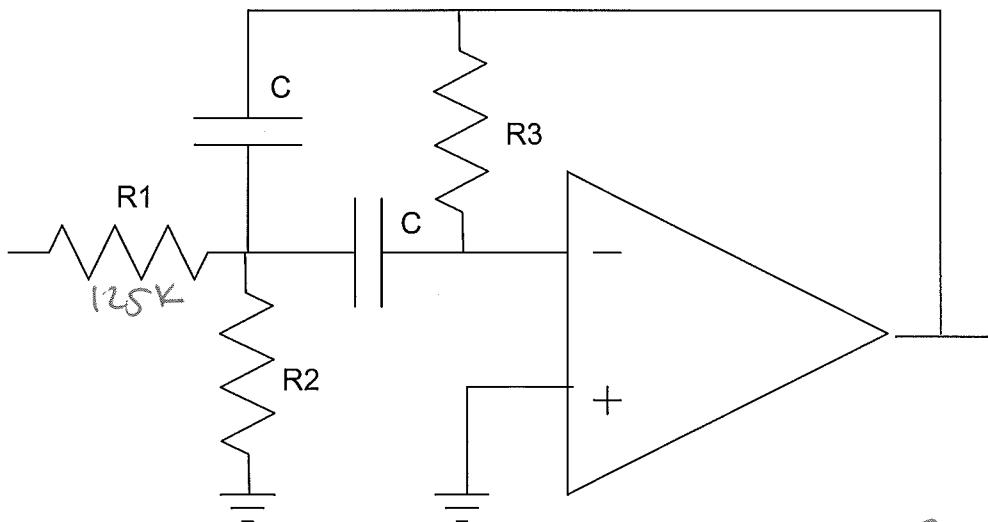

$$\frac{2}{R_3 C} = 4$$

$$\frac{1}{R_1 C} = 8$$

$$R_3 = 500k$$

$$R_1 = 125k$$

$$\frac{R_1 + R_2}{R_1 R_2 R_3 C^2} = 100$$

Bonus! Why is Easter held after the 1st full moon following the spring equinox?

~~Easter~~

$$R_1 + R_2 = R_2 \cdot 6.25$$

$$\Rightarrow R_2 (512.5) = R_1$$

$$R_2 = R_1 / 5.125$$

$$R_2 = 23.8k$$