

ECE 321 - Homework #2

Filters. Due Monday April 3, 2017

Problem 1) DC Block: For the following filter:

$$Y = \left(\frac{2s}{s+6} \right) X$$

a) Determine the differential equation relating X and Y

Cross multiply

$$(s + 6)Y = (2s)X$$

'sY' means 'the derivative of Y

$$\frac{dy}{dt} + 6y = 2\frac{dx}{dt}$$

or using dot notation

$$\dot{y} + 6y = 2\dot{x}$$

b) Determine y(t) assuming

$$x(t) = 2 + 3 \sin(10t) + 4 \sin(100t)$$

Use superposition

$x(t) = 2$ $s = 0$ $\left(\frac{2s}{s+6} \right)_{s=0} = 0$ $y = (0) \cdot 2$ $y(t) = 0$ block	$x(t) = 3 \sin(10t)$ $s = j10$ $\left(\frac{2s}{s+6} \right)_{s=j10} = 1.715 \angle 31^\circ$ $(1.715 \angle 31^\circ) \cdot 3 \sin(10t)$ $y(t) = 5.145 \sin(10t - 31^\circ)$ pass	$x(t) = 4 \sin(100t)$ $s = j100$ $\left(\frac{2s}{s+6} \right)_{s=j100} = 1.996 \angle 3^\circ$ $y = (1.996 \angle 3^\circ) \cdot 4 \sin(100t)$ $y(t) = 7.98 \sin(100t + 3^\circ)$ pass
--	--	---

This is a DC block

Add up the three inputs to get x(t). Add up the three outputs to get y(t)


$$y(t) = 0 + 5.145 \sin(10t - 31^\circ) + 7.98 \sin(100t + 3^\circ)$$

c) Design an op-amp circuit to implement this filter.

Gain = 2. Use two 100k resistors.

$1/RC = 6$. Let

- $R = 100k$
- $C = 1.667\mu F$

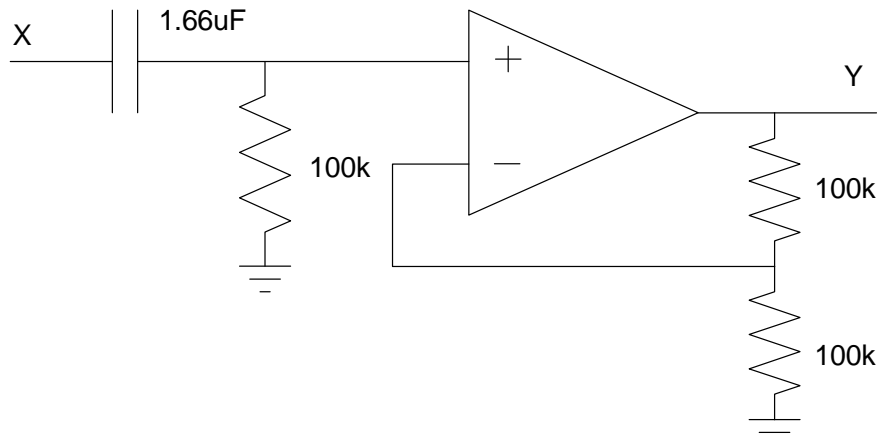

One possible implementation of a DC Block

Problem 2) Low Pass Filter with Real Poles: For the following filter:

$$Y = \left(\frac{400}{(s+10)(s+20)} \right) X$$

a) Determine the differential equation relating X and Y

Multiply out and cross multiply

$$(s^2 + 30s + 200)Y = 400X$$

which means

$$\frac{d^2y}{dt^2} + 30\frac{dy}{dt} + 200y = 400x$$

or

$$\ddot{y} + 30\dot{y} + 200y = 400x$$

b) Determine y(t) assuming

$$x(t) = 2 + 3 \sin(10t) + 4 \sin(100t)$$

Use superposition

$x(t) = 2$ $s = 0$ $\left(\frac{400}{(s+10)(s+20)} \right)_{s=0} = 2$ $y = (2) \cdot 2$ $y(t) = 4$ <p style="text-align: center;">pass</p>	$x(t) = 3 \sin(10t)$ $s = j10$ $\left(\frac{400}{(s+10)(s+20)} \right)_{s=j10} = 1.26 \angle -71.6^\circ$ $y = (1.26 \angle -71.6^\circ) \cdot 3 \sin(10t)$ $y(t) = 3.79 \sin(10t - 71.6^\circ)$ <p style="text-align: center;">mostly pass</p>	$x(t) = 4 \sin(100t)$ $s = j100$ $\left(\frac{400}{(s+10)(s+20)} \right)_{s=j100} = 0.039 \angle -163^\circ$ $y = (0.039 \angle -163^\circ) \cdot 4 \sin(100t)$ $y(t) = 0.156 \sin(100t - 163^\circ)$ <p style="text-align: center;">block</p>
--	---	--

This is a low-pass filter.

Add up the three outputs to get y(t)

$$y(t) = 4 + 3.79 \sin(10t - 71.6^\circ) + 0.156 \sin(100t - 163^\circ)$$

c) Design an op-amp circuit to implement this filter.

Use two RC filters with


$$1/RC = 10$$

- $R = 10k$
- $C = 10\mu F$


$$1/RC = 20$$

- $R = 100k$
- $C = 0.5\mu F$

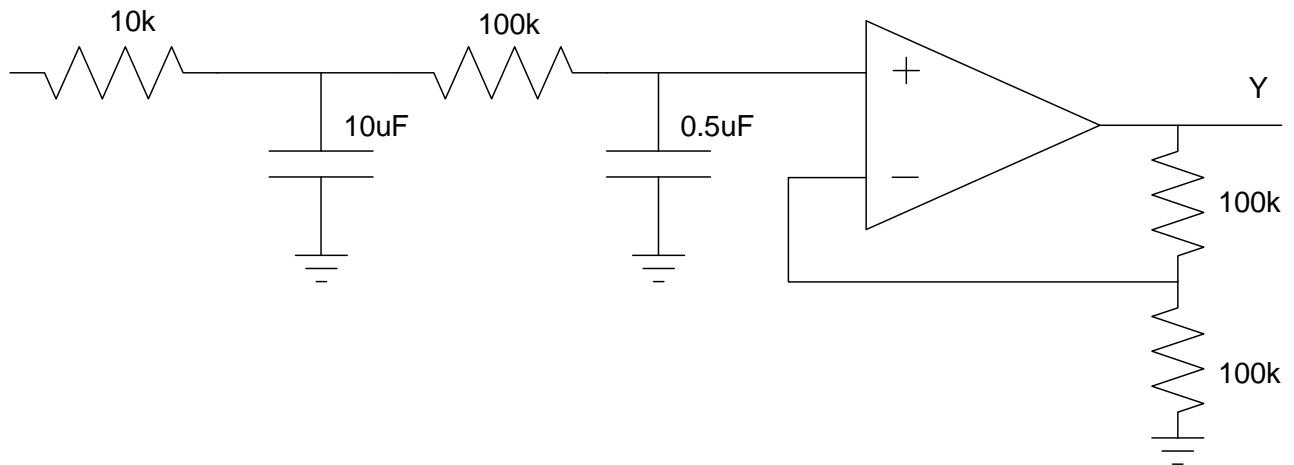Add a gain of two so that the DC gain is two



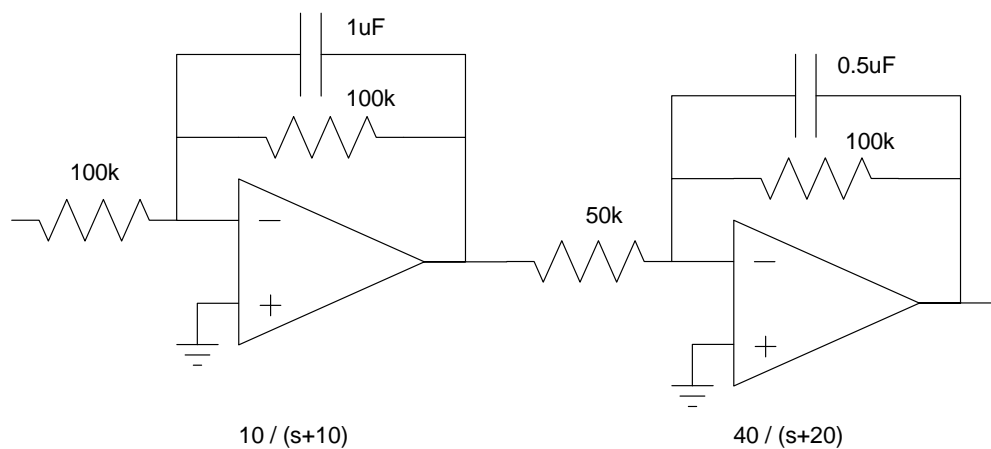One implementation of a low-pass filter with two real poles



Another implementation of a low-pass filter with two real poles

Problem 3) Low Pass Filter with Complex Poles: For the following filter:

$$Y = \left(\frac{225}{s^2 + 15s + 225} \right) X$$

a) Determine the differential equation relating X and Y

$$(s^2 + 15s + 225)Y = 225X$$

$$\frac{d^2y}{dt^2} + 15\frac{dy}{dt} + 225y = 225x$$

$$\ddot{y} + 15\dot{y} + 225y = 225x$$

b) Determine y(t) assuming

$$x(t) = 2 + 3 \sin(10t) + 4 \sin(100t)$$

$x(t) = 2$ $s = 0$ $\left(\frac{225}{s^2 + 15s + 225} \right)_{s=0} = 1$ $y = (1) \cdot 2$ $y(t) = 2$ <p style="text-align: center;">pass</p>	$x(t) = 3 \sin(10t)$ $s = j10$ $\left(\frac{225}{s^2 + 15s + 225} \right)_{s=j10} = 1.34 \angle -116^\circ$ $y = (1.34 \angle -116^\circ) \cdot 3 \sin(10t)$ $y(t) = 4.02 \sin(10t - 116^\circ)$ <p style="text-align: center;">pass</p>	$x(t) = 4 \sin(100t)$ $s = j100$ $\left(\frac{225}{s^2 + 15s + 225} \right)_{s=j100} = 0.022 \angle -171^\circ$ $y = (0.022 \angle -171^\circ) \cdot 4 \sin(100t)$ $y(t) = 0.089 \sin(100t - 171^\circ)$ <p style="text-align: center;">block</p>
---	--	---

This is a better low-pass filter. The gain at 10 is closer to the DC gain (1.00)

$$y(t) = 2 + 4.02 \sin(10t - 116^\circ) + 0.089 \sin(100t - 171^\circ)$$

c) Design an op-amp circuit to implement this filter.

$$\left(\frac{1}{RC}\right)^2 = 225$$

$$\left(\frac{1}{RC}\right) = 15$$


Let $R = 100k$, $C = 0.67\mu F$

$$\left(\frac{3-k}{RC}\right) = 15$$

$$3 - k = 1$$

$$k = 2$$

Let $R_1 = R_2 = 100k$

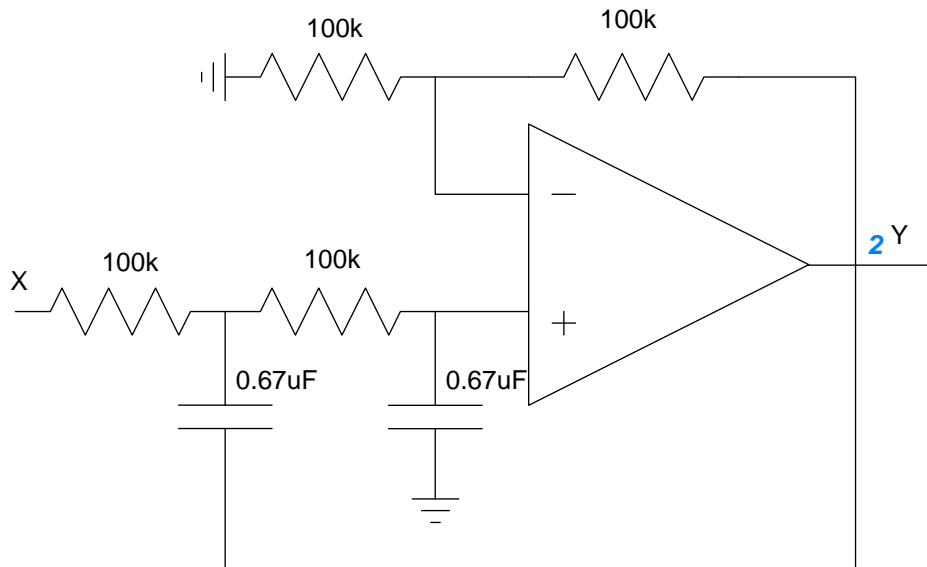

Problem 4) Band Pass Filter: For the following filter:

$$Y = \left(\frac{2s}{s^2 + 2s + 10} \right) X$$

a) Determine the differential equation relating X and Y

$$(s^2 + 2s + 10)Y = (2s)X$$

$$\frac{d^2y}{dt^2} + 2\frac{dy}{dt} + 10y = 2\frac{dx}{dt}$$

$$\ddot{y} + 2\dot{y} + 10y = 2\dot{x}$$

b) Determine y(t) assuming

$$x(t) = 2 + 3 \sin(10t) + 4 \sin(100t)$$

Use superposition:

$$x(t) = 2$$

$$s = 0$$

$$\left(\frac{2s}{s^2 + 2s + 10} \right)_{s=0} = 0$$

$$y = (0) \cdot 2$$

$$y(t) = 0$$

block

$$x(t) = 3 \sin(10t)$$

$$s = j10$$

$$\left(\frac{2s}{s^2 + 2s + 10} \right)_{s=j10} = 0.2169 \angle -77^\circ$$

$$y = (0.2169 \angle -77^\circ) \cdot 3 \sin(10t)$$

$$y = 0.6508 \sin(10t - 77^\circ)$$

pass

$$x(t) = 4 \sin(100t)$$

$$s = j100$$

$$\left(\frac{2s}{s^2 + 2s + 10} \right)_{s=j100} = 0.02 \angle -88^\circ$$

$$y = (0.02 \angle -88^\circ) \cdot 4 \sin(100t)$$

$$y(t) = 0.08 \sin(100t - 88^\circ)$$

block

This is a band-pass filter. Frequencies close to 3.16 rad/sec get passed, those far away get blocked.

Add up all the outputs to get y(t)

$$y(t) = 0 + 0.6508 \sin(10t - 77^\circ) + 0.08 \sin(100t - 88^\circ)$$

c) Design an op-amp circuit to implement this filter.

Use the band-pass filter:

$$\left(\frac{2s}{s^2 + 2s + 10} \right) = \left(\frac{\left(\frac{1}{R_1 C} \right) s}{s^2 + \left(\frac{2}{R_3 C} \right) s + \left(\frac{R_1 + R_2}{R_1 R_2} \right) \left(\frac{1}{R_3 C^2} \right)} \right)$$

Matching terms:

$$\left(\frac{1}{R_1 C} \right) = 2$$

Let $C = 1\mu\text{F}$

$$R_1 = 500k$$

$$\left(\frac{2}{R_3 C} \right) = 2$$

$$R_3 = 500k$$

$$\left(\frac{R_1 + R_2}{R_1 R_2} \right) \left(\frac{1}{R_3 C^2} \right) = 10$$

$$R_2 = 300k$$

