

ECE 321 - Final. Name _____

2-Port Models, Common Emitter Amplifiers. April 26, 2018


1) Determine the voltages and currents for the following push (pull) amplifier. Assume for the transistor

- $\beta = 1000$
- $V_{be} = 1.4V$

Assume for the LED

- $V_f = 3.0V$ @ $300mA$:

V1	I2	I3	V4

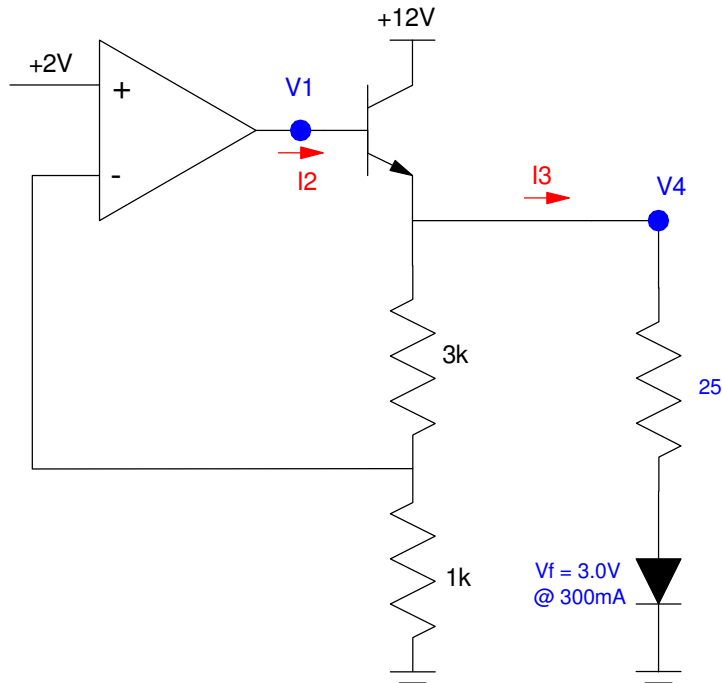


2) Determine the voltages and currents for the following push (pull) amplifier. Assume for the transistor

- $\beta = 1000$
- $V_{be} = 1.4V$

Assume for the LED

- $V_f = 3.0V @ 300mA$:

V1	I2	V3	I4


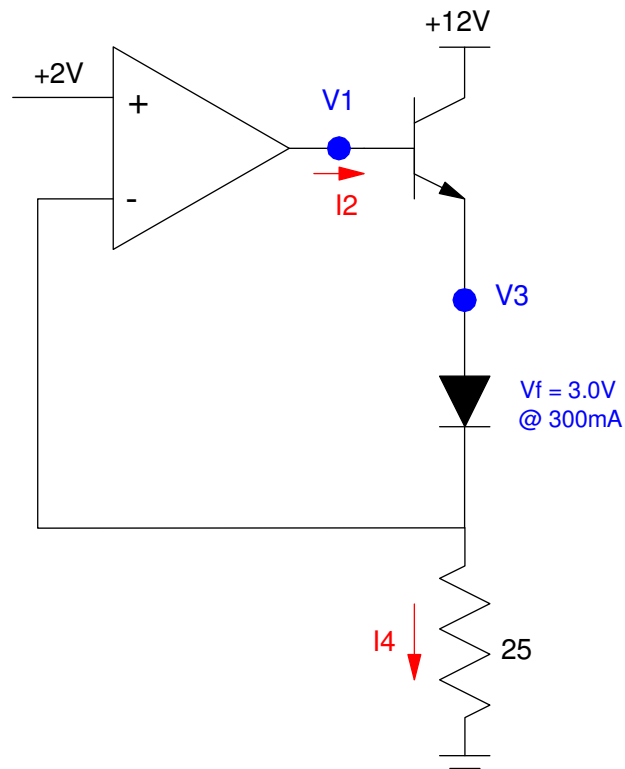


3) Design an instrumentation amplifier so that the output is

- -10V when $R = 1000$ Ohms
- +10V when $R = 1200$ Ohms

For your circuit, what is the output voltage (V_{out}) when $R = 1100$ Ohms?

V_{out} when $R = 1100$:

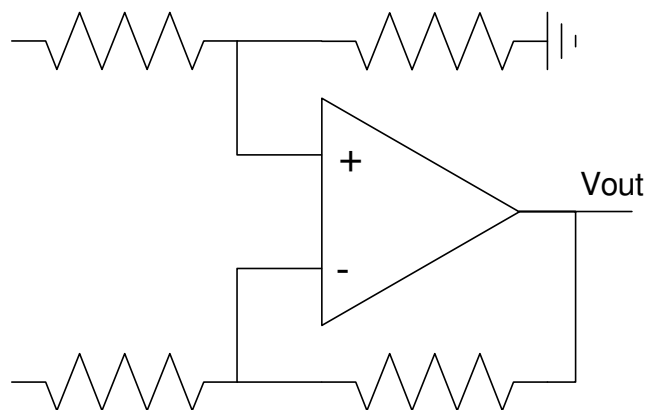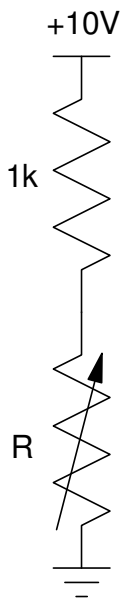

4) Give the transfer function for a low-pass filter which comes close to meeting the following requirements (fine tuning in Matlab might be required)

- $0.9 < \text{Gain} < 1.1$ frequencies less than 200 rad/sec
- $\text{Gain} < 0.1$ frequencies above 300 rad/sec

You are free to choose any type of filter you like (Chebychev, Butterworth, Elliptic, etc.)

5) A 3rd-order Butterworth low-pass filter has the following transfer function:

$$Y = \left(\frac{250}{(s+5)(s^2+5s+25)} \right) X = \left(\frac{250}{s^3+10s^2+50s+125} \right) X$$

a) What is the differential equation relating X and Y?



b) Determine y(t) assuming

$$x(t) = 3 \sin(4t) + 5 \cos(10t)$$

6) Find the Thevenin equivalent of R1, R2 (V_b , R_b), and the Q-point (I_c , V_{ce}) for the following transistor circuit. Assume a 3904 transistor:



- $\beta = 200$
- $V_{be} = 0.7V$

V_b	R_b	I_c	V_{ce}

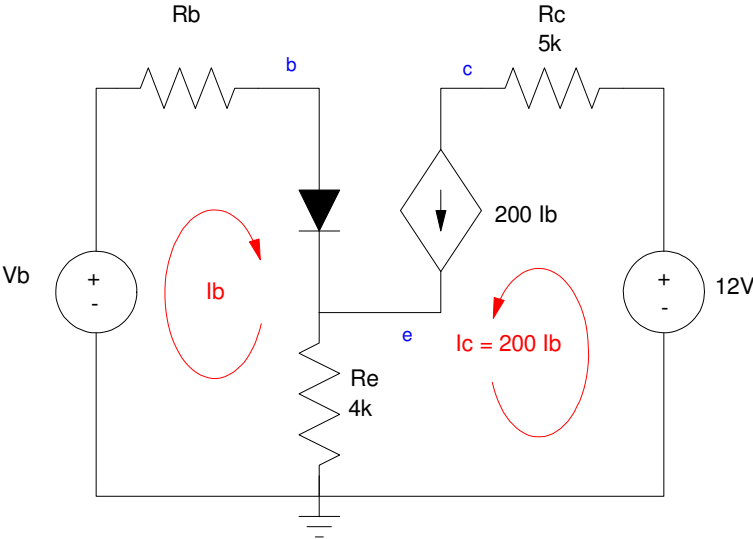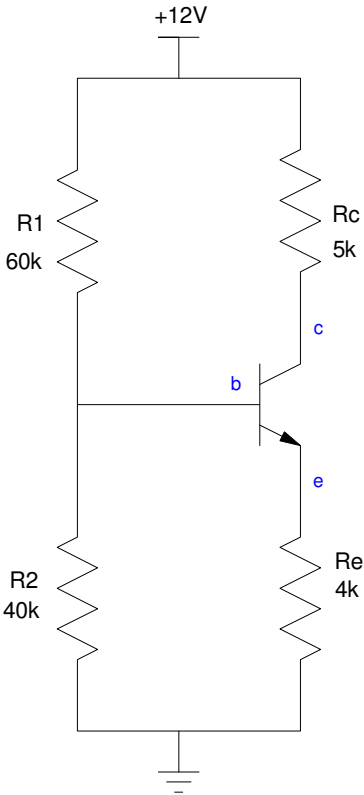

7) Find the 2-port model for the following circuit:


Rin	Ai	Ao	Rout

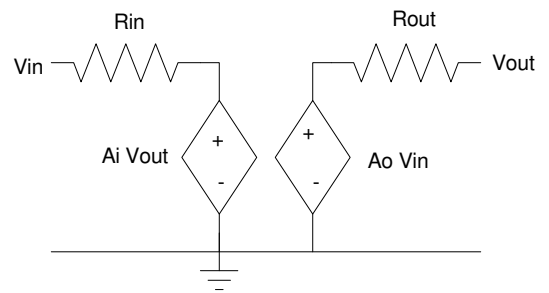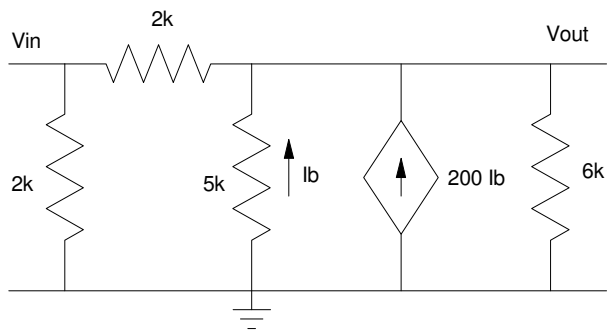

8) Determine the operating point for the following transistor circuit. Assume

- $\beta = 200$
- $V_{be} = 0.7V$
- $V_{ce:sat} = 0.2V$

Ib	Ic	Ve	Vc

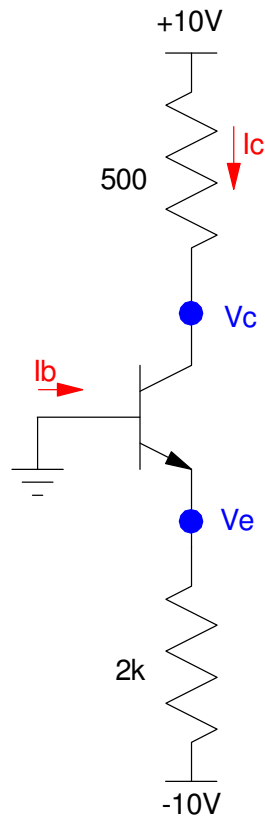

Bernie vs. Godzilla Bonus!! Three of the following are U.S. Senators. Three are Godzilla monsters. Which are the Senators?

Barrasso Ebirah Kiryu Minya Stabenow Wicker