

# ECE 321 - Homework #1

Push-Pull Amplifiers, Instrumentation Amplifiers, Active Filters. Due Wednesday, April 4th, 2018

For all circuits, assume TIP112 (NPN) and TIP117 (PNP) transistors

- $|V_{be}| = 1.4V$
- $|V_{ce(sat)}| = 0.9V$
- $\beta = 1000$

## Push-Pull Amplifiers


1) Determine the voltages and current for the following push-pull amplifier with

- $V_{in} = 2V$
- $V_{in} = -2V$


2) Verify your design in PartSim

3) Determine the voltages and current for the following push-pull amplifier with

- $V_{in} = 2V$
- $V_{in} = -2V$

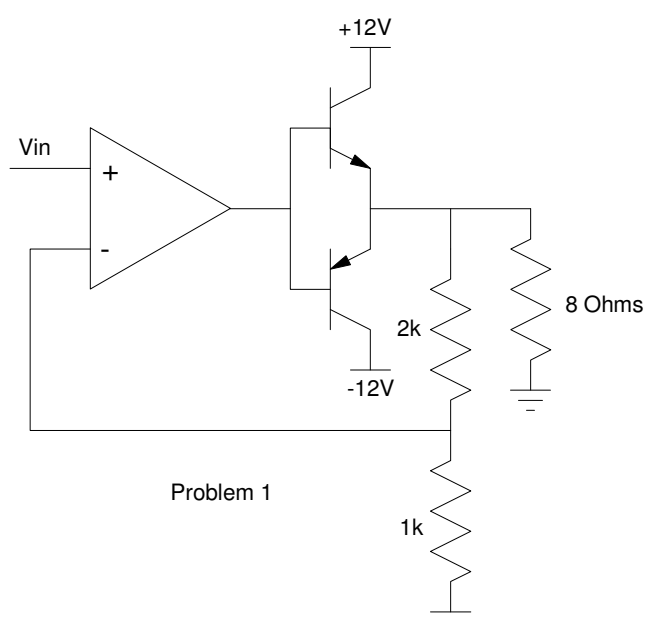

Problem 1

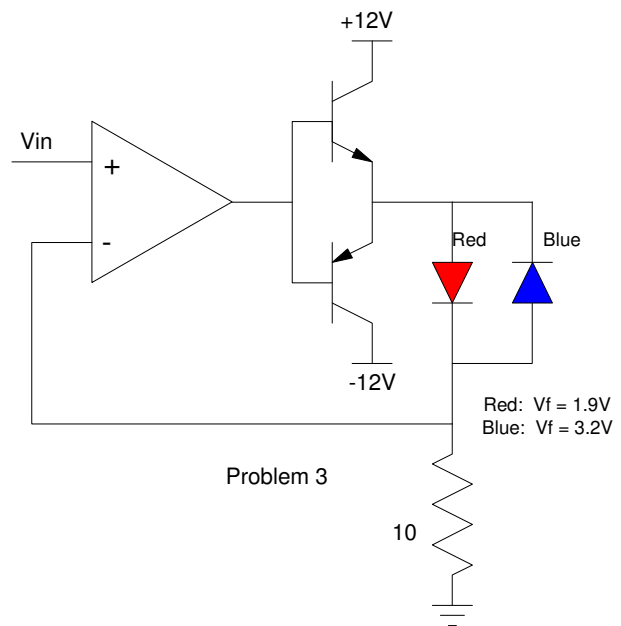

Problem 3

## Op-Amp Circuits:

4) Design an op-amp circuit to implement the functions

- $Y = 4X$
- $Y = -4X$
- $Y = 4X - 12$

A light sensor has the following light / resistance relationship:

$$R = \frac{100,000}{Lux} \Omega$$

5) Design an instrumentation amplifier whose output is

- 0V when the light level is 50 Lux
- 10V when the light level is 100 Lux

6) Design an instrumentation amplifier whose output is

- -10V when the light level is 50 Lux
- +10V when the light level is 100 Lux

## Op-Amp Circuits

7) Assume ideal op-amps

- Write the voltage node equations for the following op-amp circuits
- Solve for the voltages V1 .. V4

