

ECE 321 - Homework #3

Filter Design. Due Monday, April 16th, 2018

(Option 1): Design a filter to meet the following requirements

- Input: +/- 10V analog signal, 0 - 10kHz, capable of driving 10mA (1k resistor)
- Output: +/- 10V analog signal, 0 - 10kHz, capable of driving 10mA (1k resistor)
- Relationship

$$0.9 < \text{Gain} < 1.1 \quad 0 < f < 200 \text{ Hz}$$

$$\text{Gain} < 0.1 \quad f > 600 \text{ Hz}$$

(Option 2): Make up your own problem

- 1) (Analysis): Give the transfer function for a filter which meets these requirements
- 2) (Analysis): Design an op-amp circuit to implement this transfer function
- 3) (Simulation): Test your design in simulation with PartSim (or similar software)
- 4) (Validation): Build your circuit and test it in lab to verify it meets your requirements.