

# ECE 321 - Homework #5

Common Emitter / Base / Collector Amplifiers. Due Monday, April 30th, 2018

For the following transistor amplifiers, assume

- $\beta = 200$
- The Q-point (DC operating point) is
  - $V_{ce} = 6V$
  - $I_c = 2mA$
  - $I_b = 10\mu A$

1) Common Emitter:

- Draw the small signal model for the amplifier connected in a common-emitter configuration (note:  $C_e = 0$ )
- Determine the 2-port model

2) Common Base:

- Draw the small signal model for the amplifier connected in a common-base configuration
- Determine the 2-port model


3) Common Emitter:

- Draw the small signal model for the amplifier connected in a common-collector configuration
- Determine the 2-port model


4) Using your resulting 2-port models, find the 2-port model for a four-stage amplifier:

CB : CE : CE : CC

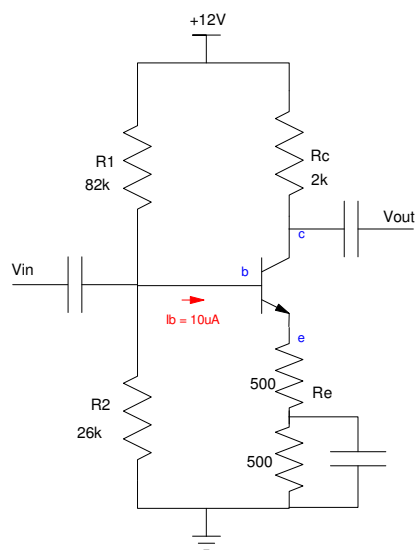
5) (Lab - 20pt) Build the three-stage circuit from homework #4 and collect data in lab to verify it meets the overall requirements.



Problem 1; CE Amplifier

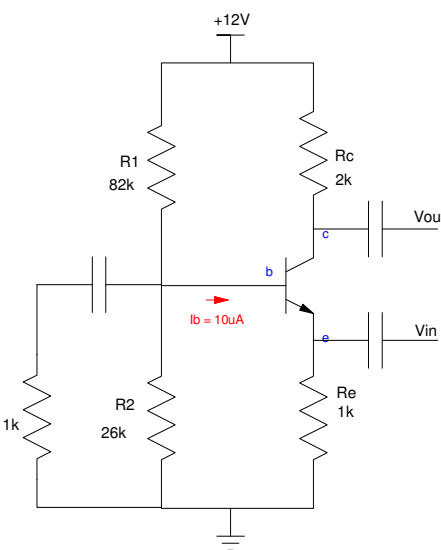

Problem 2: Common Base

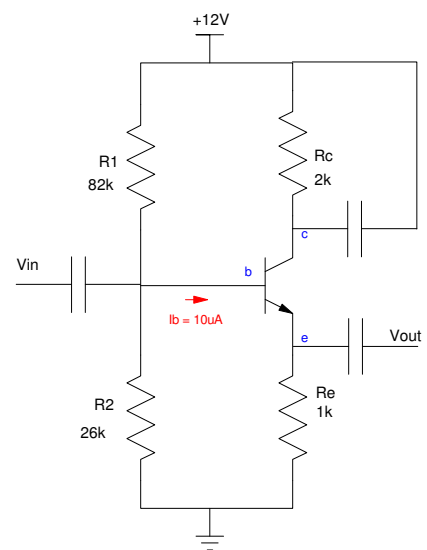

Problem 3) Common Collector