

ECE 321 - Quiz #1. Name _____


Push-Pull Amplifiers, Op-Amp Amplifiers. April 6, 2018

Push-Pull Amplifiers: Voltage Output

1) Determine the voltages and currents for the following push-pull amplifier. Assume TIP transistors with

- $\beta = 1000$
- $|V_{be}| = 1.4V$
- $|V_{ce:sat}| = 0.9V$

V1	V2	Ib	Ic
9.4V	8V	1.001mA	1.001A

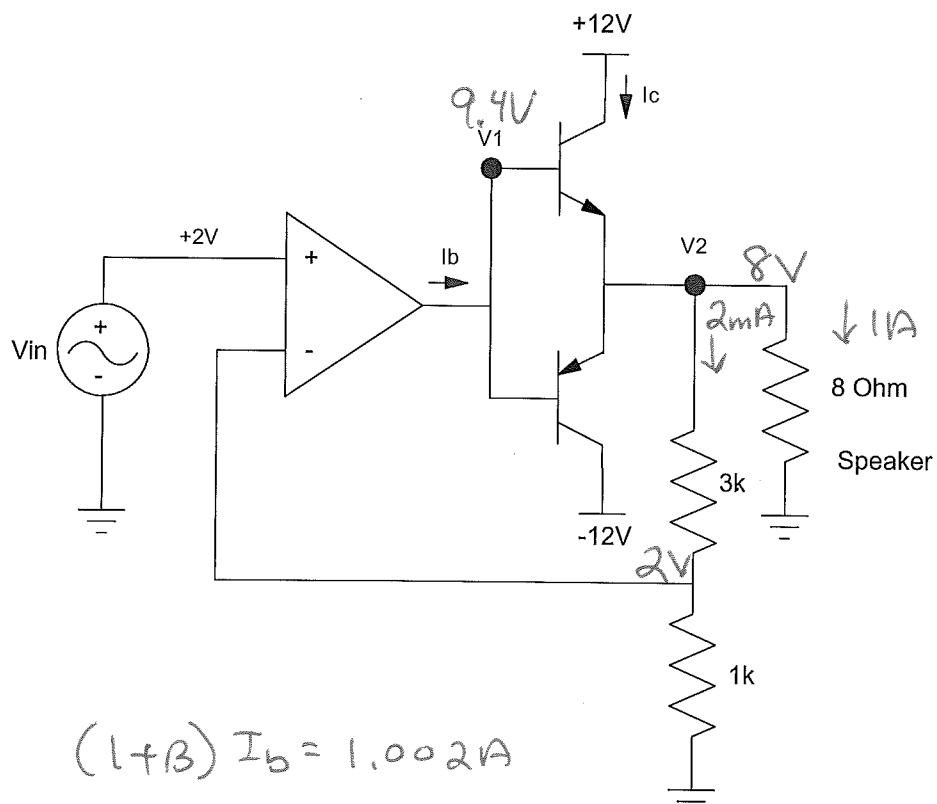

$$(1+\beta) I_b = 1.002A$$

$$I_b = \frac{1.002}{1001} = 1.001mA$$


$$I_c = 1000 I_b = 1.001A$$

Push-Pull Amplifiers: Current Output

2) Determine the voltages and currents for the following push-pull amplifier. Assume TIP transistors with

- $\beta = 1000$
- $|V_{be}| = 1.4V$
- $|V_{ce,sat}| = 0.9V$

V1	V2	Ib	Ic
7.3V	5.9V	199.8μA	199.8mA

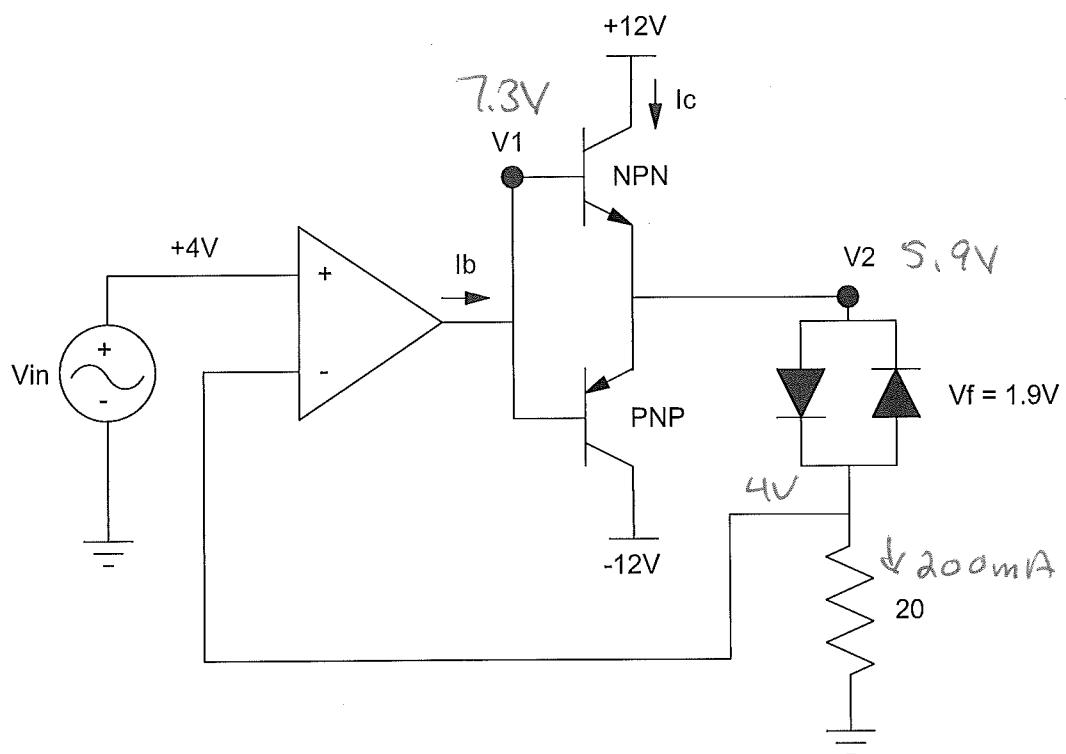


$$(1+\beta)I_b = 200\text{mA}$$

$$I_b = \frac{200\text{mA}}{1001} = 199.8\mu\text{A}$$

$$I_c = \beta I_b = 199.8\mu\text{A}$$


3) Design an op-amp circuit which has a gain of

$$Y = 3X - 12 \quad = 3(X - 4)$$

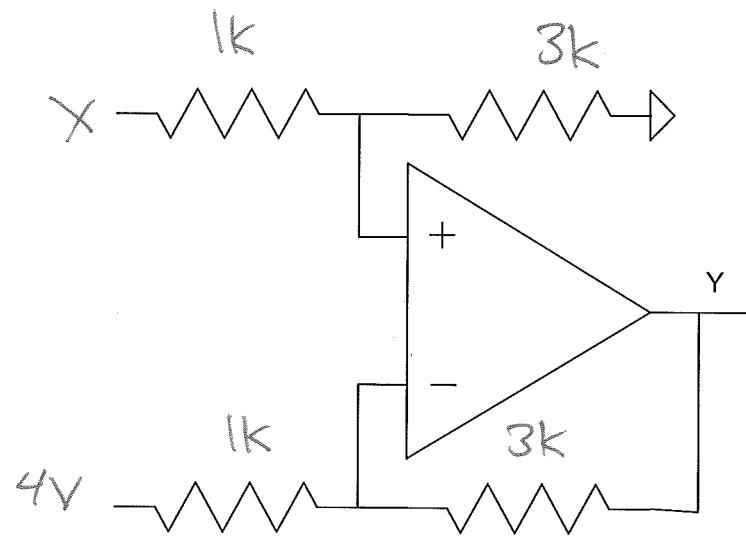

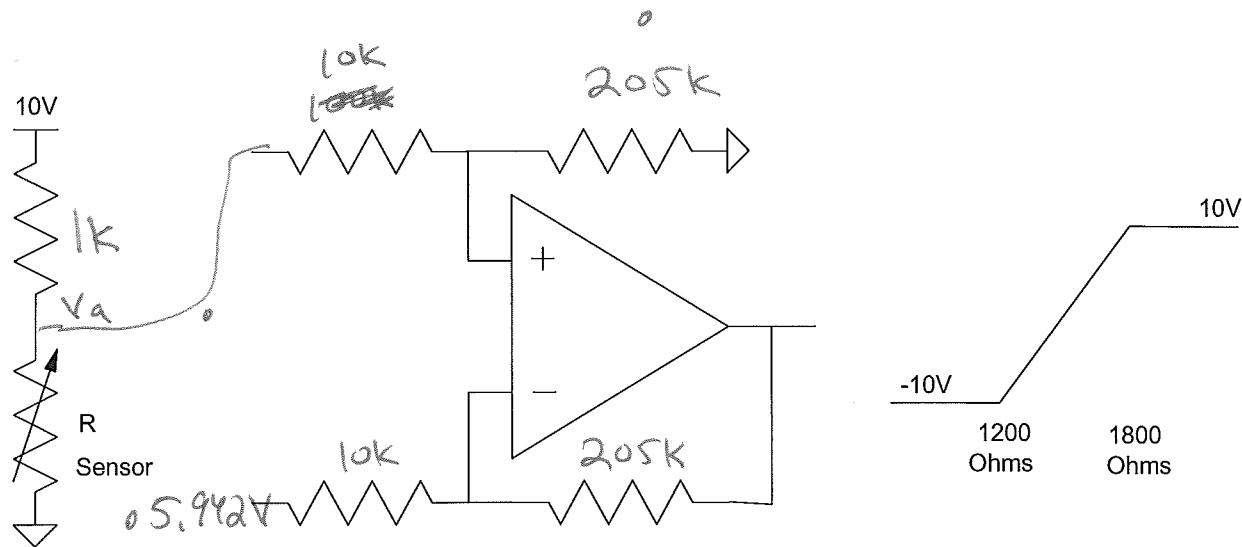4) Design a circuit which outputs

- 10V when $R = 1200$ Ohms
- +10V when $R = 1800$ Ohms
- Proportional for $1200 < R < 1800$ Ohms



1200Ω

$$V_a = 5.45V$$

$$V_o = -10V$$

1800Ω

$$V_a = 6.429V$$

$$V_o = +10V$$

$$\text{If } \text{ gain} = \frac{10 - (-10)}{6.429 - 5.45} = 20.53$$

$$y = 20.53(V_a - V_b)$$


at 1800Ω

$$10 = 20.53(6.429 - V_b)$$

$$V_b = 5.942V$$

gain > 20

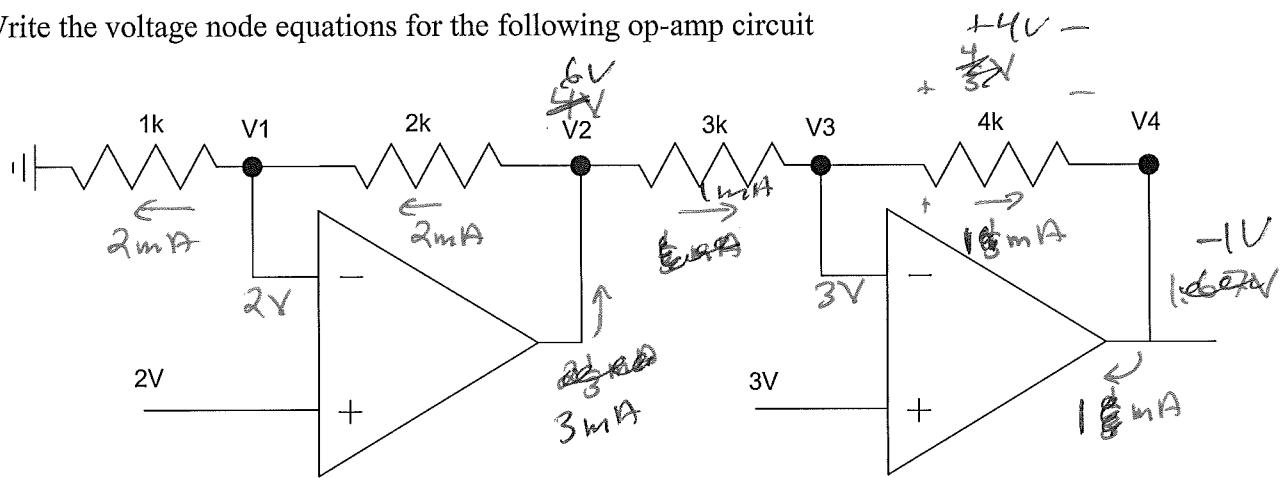5) Write the voltage node equations for the following op-amp circuit



$$Y_1 = 2$$

$$Y_3 = 3$$

$$\frac{Y_1}{1k} + \frac{Y_1 - Y_2}{2k} = 0$$

$$\frac{Y_3 - Y_2}{3k} + \frac{Y_3 - Y_4}{4k} = 0$$

born Sept 8, 1941

Godzilla, King of
the Monsters
(1933)

Bonus! Which is older: Bernie Sanders or Godzilla? (i.e. were any Godzilla movies made at the time Bernie Sanders was born?)