

CE 321 - Quiz #2. Name _____

Active Filters. April 12, 2018

1) X and Y are related by the following transfer function

$$Y = \left(\frac{150}{(s+2)(s+4)(s+10)} \right) X = \left(\frac{150}{s^3 + 16s^2 + 68s + 80} \right) X$$

1a) What is the differential equation relating X and Y?

$$y''' + 16y'' + 68y' + 80y = 150x$$

1b) Find y(t) assuming

$$x(t) = 5 + 6 \cos(7t)$$

$$x(t) = 5$$

$$s = 0$$

$$\left(\right)_{s=0} = 1.875$$

$$y = 1.875 \cdot 5$$

$$y = 9.375$$

$$x(t) = 6 \cdot \cos(7t)$$

$$s = j7$$

$$\left(\right)_{s=j7} = .209 \angle -169^\circ$$

$$y = 1.25 \angle -169^\circ = (.209 \angle -169^\circ)(6)$$

$$y = 1.25 \cos(7t - 169^\circ)$$


$$y = 9.375 + 1.25 \cos(7t - 169^\circ)$$

2) X and Y are related by the following transfer function:

$$Y = \left(\frac{150}{(s+2)(s+4)(s+10)} \right) X = \left(\frac{150}{s^3 + 16s^2 + 68s + 80} \right) X$$

Specify R and C values so that the following circuit implements this transfer function

| C1 | C2 | C3 | R4 |
|-------------|--------------|-----------|-------|
| 500 μ F | 12.5 μ F | 1 μ F | 87.5k |

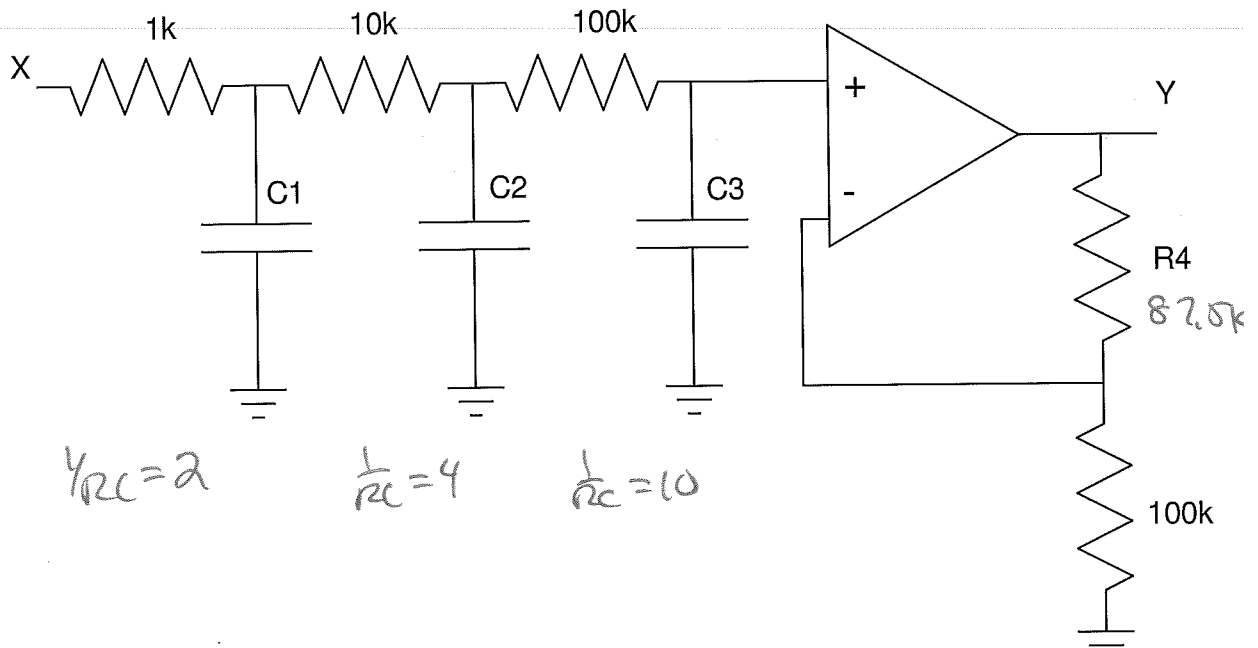

$$\frac{1}{RC} = 2$$

$$\frac{1}{RC} = 4$$

$$\frac{1}{RC} = 10$$

$$\text{DC gain} = 1.875$$

3) X and Y are related by the following transfer function:

$$Y = \left(\frac{2000}{(s+8.5)(s+12.1\angle 69.5^\circ)(s+12.1\angle -69.5^\circ)} \right) X$$

Find y(t) assuming

$$x(t) = 5 + 6 \cos(7t)$$

$$X(t) = 5$$

$$s=0$$

$$y = \cancel{(1.607)}(5)$$

$$\left(\right)_{s=0} = 1.607$$

$$y = 1.607 \cdot 5$$

$$y = 8.035$$

$$X(t) = 6 \cos(7t)$$

$$s = j7$$

$$\left(\right)_{s=j7} = 1.59 \angle -71^\circ$$

$$y = (1.59 \angle -71^\circ) \cdot 6$$

$$y = 9.55 \angle -71^\circ$$

$$y(t) = 9.55 \cos(7t - 71^\circ)$$

$$y = 8.035 + 9.55 \cos(7t - 71^\circ)$$


4) X and Y are related by the following transfer function:

$$Y = \left(\frac{2000}{(s+8.5)(s+12.1 \angle 69.5^\circ)(s+12.1 \angle -69.5^\circ)} \right) X$$

DC gain = 1.607

Specify R and C's so that the following filter implements this transfer function

| C1 | C2 | R3 | R4 |
|--------------|--------------|--------|-------------|
| 1.17 μ F | .826 μ F | 119.9k | gain = 0.69 |

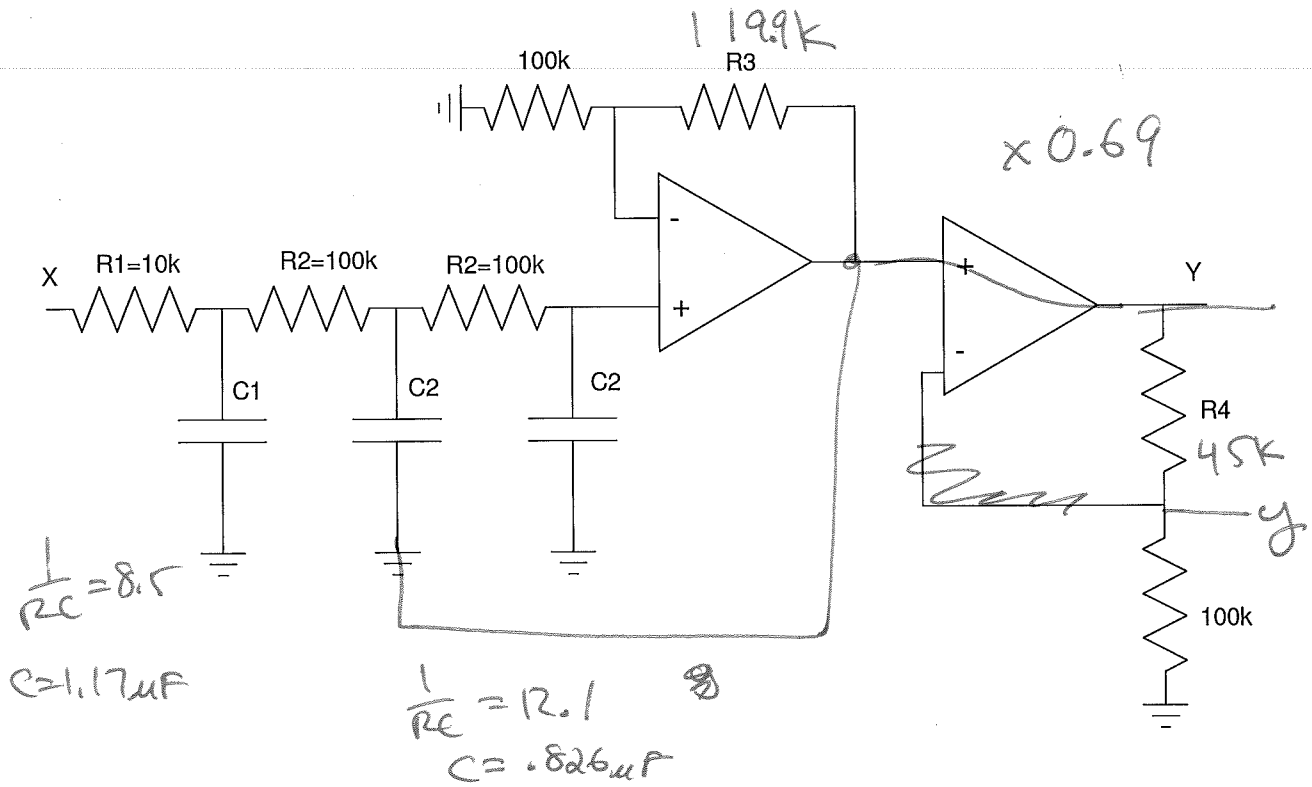

$\frac{1}{RC} = 8.5$
 $C = 1.17 \mu F$

$\frac{1}{RC} = 12.1$
 $C = .826 \mu F$

$$\left(\frac{\frac{1}{R_1 C_1}}{s + \frac{1}{R_1 C_1}} \right)$$

$$\left(\frac{k \left(\frac{1}{R_2 C_2} \right)^2}{s^2 + \left(\frac{3-k}{R_2 C_2} \right) s + \left(\frac{1}{R_2 C_2} \right)^2} \right)$$

$$\left(1 + \frac{R_4}{100,000} \right)$$

$$k = \left(1 + \frac{R_3}{100,000} \right)$$

3.1k

6.9k

DC gain = 2.299

~~$3-k = 2 \cos \theta$~~

$3-k = 2 \cos \theta$


$k = 2.299$

5) X and Y are related by the following transfer function:

$$Y = \left(\frac{5s}{s^2 + 15s + 200} \right) X = \left(\frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}\right)} \right) X$$

Specify R and C's so that the following filter implements this transfer function

| R1 | R2 | R3 | C |
|------|------|------|-----|
| 200k | 460k | 133k | 1uF |

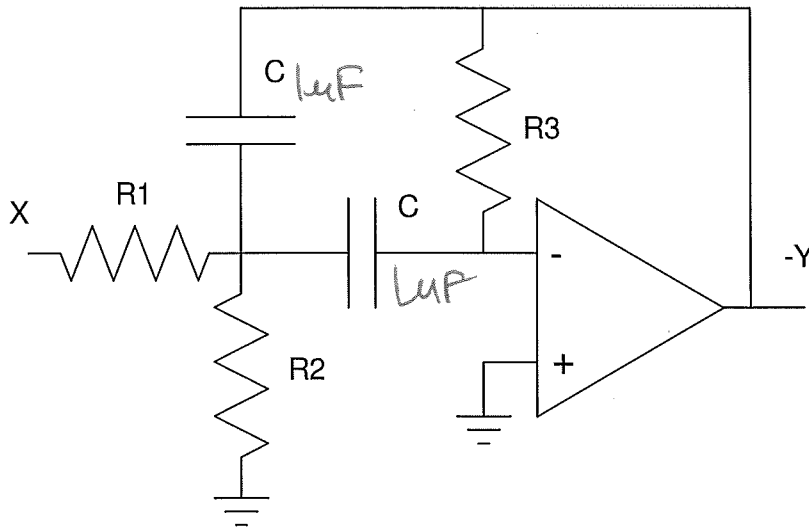

$$\frac{1}{R_1 C} = 5 \qquad \frac{2}{R_3 C} = 15$$

$$R_1 = 200k \qquad R_3 = 133k$$

$$\frac{R_1 + R_2}{R_1 R_2 R_3 C^2} = 200$$

Bernie Sanders vs. Godzilla Bonus! Which is more:

- The number of times Bernie Sanders has run for public office, or
- The number of Godzilla movies made?

$$\left(\frac{R_1 + R_2}{R_1 R_2} \right) = 266.6 \mu F$$

$$\frac{R_1 R_2}{R_1 + R_2} = 37.5k$$

$$R_1 || R_2 = 37.5k$$

$$R_2 = 46.1k$$