
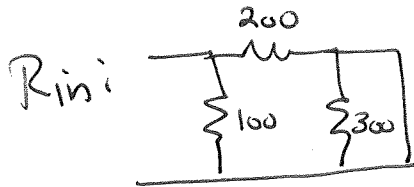


ECE 321 - Quiz #4. Name _____


2-Port Models, Common Emitter Amplifiers. April 26, 2018

1) Find the 2-port model for the following circuit:



R _{in}	A _i	R _{out}	A _o
66.67	1/3	120	3/5

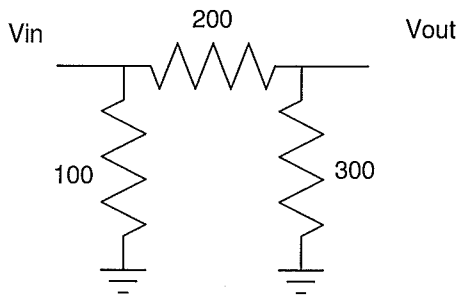


$$R_{in} = 100 \parallel 200 = 66.67$$

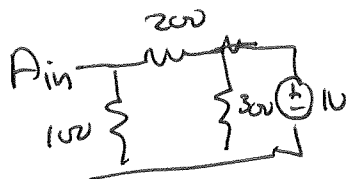

$$A_{in} = 1/3$$

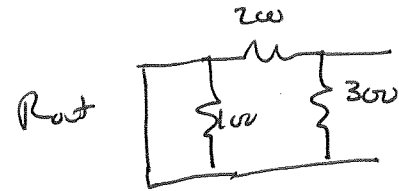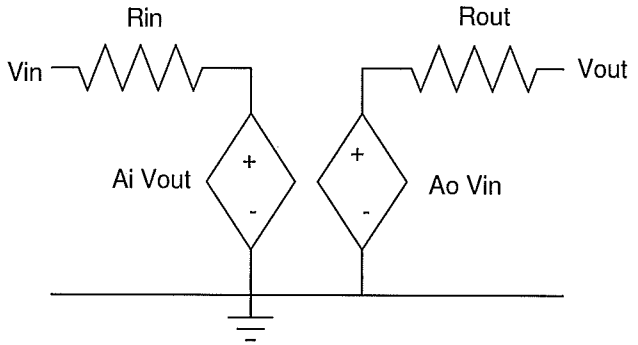



$$R_{out} = 200 \parallel 300 = 120$$

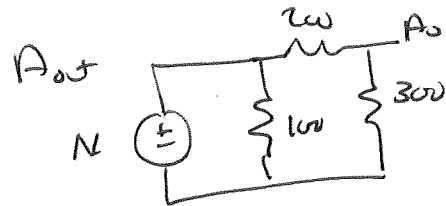

$$A_o = \left(\frac{3}{5} \right)$$

2) Find the 2-port parameters for the following circuit:

R_{in}	A_i	R_{out}	A_o
1754	0	2k	-200

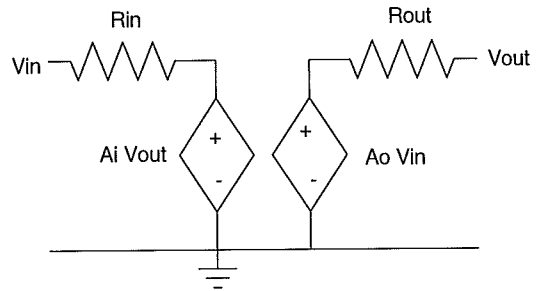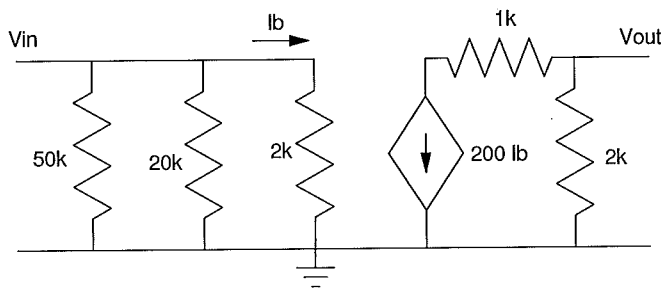

$$R_{in} = 50k \parallel 20k \parallel 2k$$

$$= 1754$$

$$A_i = 0$$


$$R_{out}: \text{set } V_{in} = 0$$

$$I_b = 0$$

$$\beta I_b = 0$$

$$R_{out} = 2k$$

A_o :

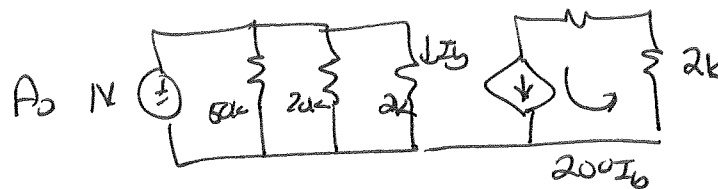

$$I_b = \frac{1}{2k}$$

$$V_o = -2k (200 I_b)$$



$$= -2k (200) \left(\frac{1}{2k} \right)$$

$$= -200$$

3) (Analysis) Determine the Thevenin equivalent for R1 / R2 / 12V source and the Q-point (V_{ce} , I_c) for the following circuit. Assume

- $\beta = 200$

V_b (V_{th})	R_b (R_{th})	V_{ce}	I_c
66.67k	4.00V	5.16V	758 μ A

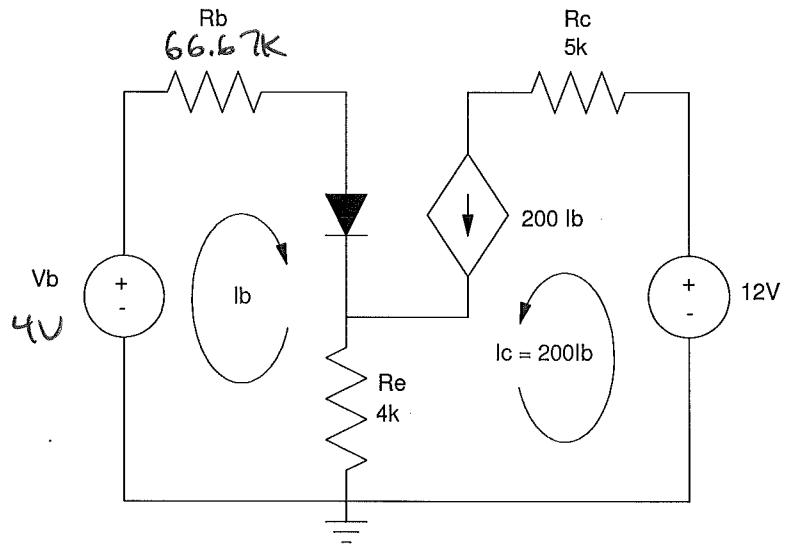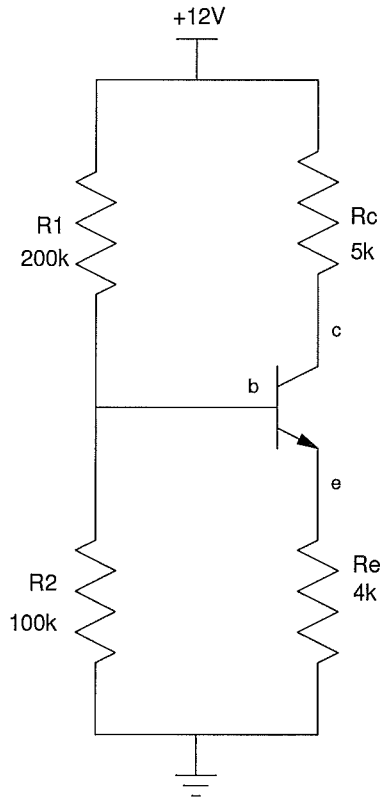

$$R_b = R_1 \parallel R_2 = 66.66k$$

$$V_b = \left(\frac{100k}{100k + 200k} \right) \cdot 12V$$

$$V_b = 4V$$

$$I_b = \frac{4 - 0.7}{66.67k + (1 + 200) \cdot 4k}$$

$$I_b = 3.79 \mu A$$

$$I_c = 200 I_b = 758 \mu A$$

$$V_c = 12 - 5k \cdot I_c = 8.21V$$


$$V_e = 4k (I_b + I_c) = 3.097V$$

$$V_{ce} = 5.16V$$

4) Find R1 and R2 so that

- The Q-point is stabilized for variations in β ($(1 + \beta)R_e \gg R_b$), and
- The Q-point is $V_{ce} = 6V$ ($I_c = 665.2\mu A$).

R1	R2	Vb	Rb
263k	114k	3.64	80k

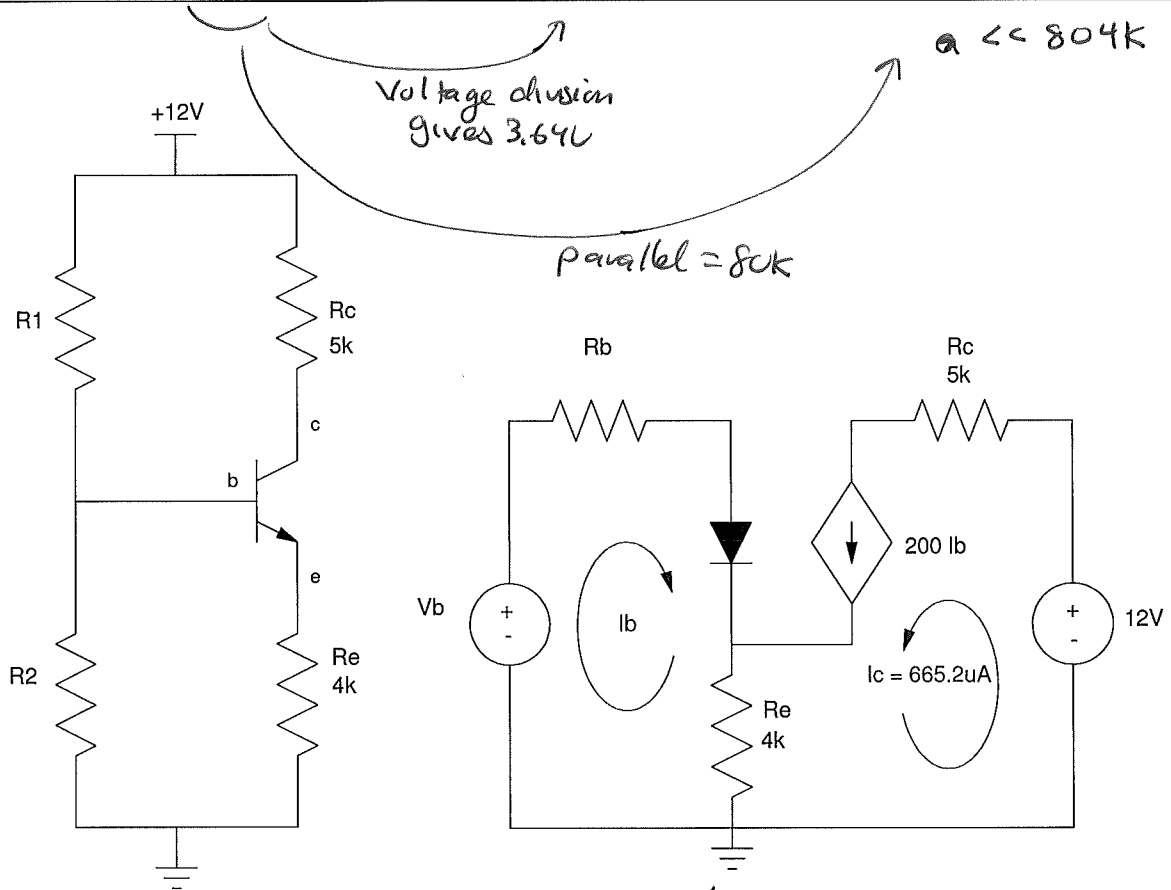

$$(1 + \beta)R_e \gg R_b$$

$$804k \gg R_b$$

$$\text{Let } R_b = 80k$$

$$V_b = R_b I_b + 0.7 + 4k(I_b + I_c)$$

$$V_b = 3.64$$

$$R_1 \parallel R_2 = 80k$$

$$\left(\frac{R_2}{R_1 + R_2} \right) 12V = 3.64V$$



$$R_1 = \left(\frac{12V}{3.64V} \right) \cdot 80k$$

$$R_1 = 263k$$

$$R_2 = 114k$$

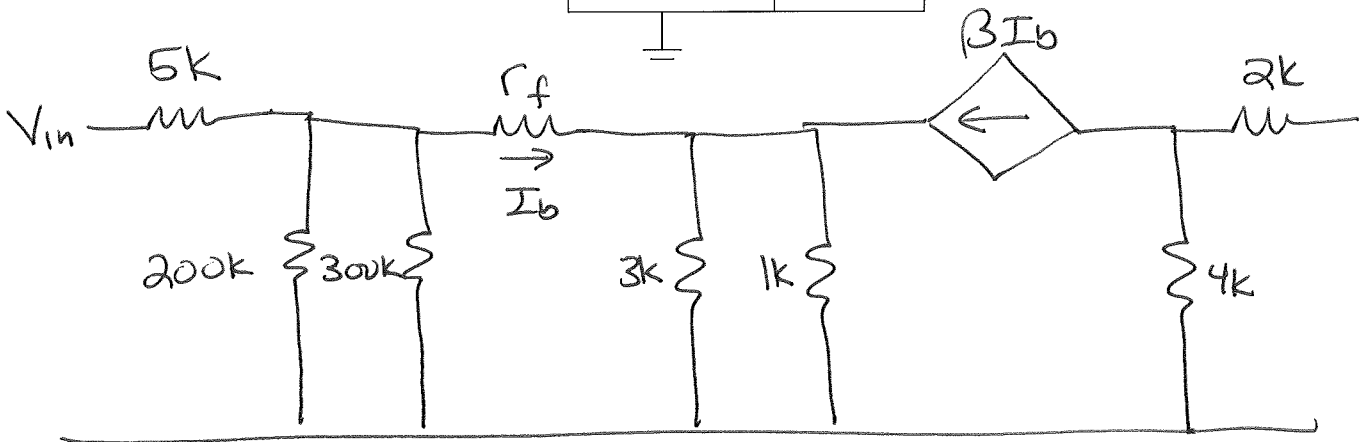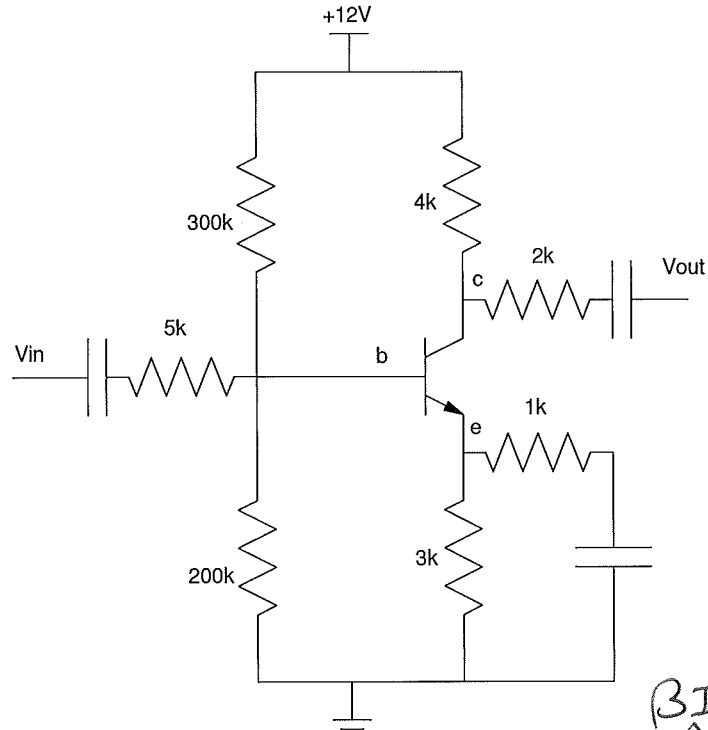5) Draw the small-signal model for the following common-emitter amplifier. Assume

- All capacitors are large ($\frac{1}{j\omega C} \approx 0$)
- $\beta = 200$
- $r_f = 2500\Omega$



Levi (one) two +

Bernie Sanders vs. Godzilla Bonus!!! Who has more kids: Bernie Sanders or Godzilla?

- note: Clones count as kids

Baby Godzilla (in Godzilla vs Destroyer)

Biollante: Clone of Godzilla, Rose Bush, mad Scientist's daughter

Space Godzilla: Godzilla DNA exposed to radiation from a black hole

Son of Godzilla: (he was adopted... doesn't count)