

ECE 321 - Homework #1



Push-Pull Amplifiers, Instrumentation Amplifiers, Active Filters. Due Wednesday, April 4th, 2018

For all circuits, assume TIP112 (NPN) and TIP117 (PNP) transistors

- $|V_{be}| = 1.4V$
- $|V_{ce(sat)}| = 0.9V$
- $\beta = 1000$


Push-Pull Amplifiers

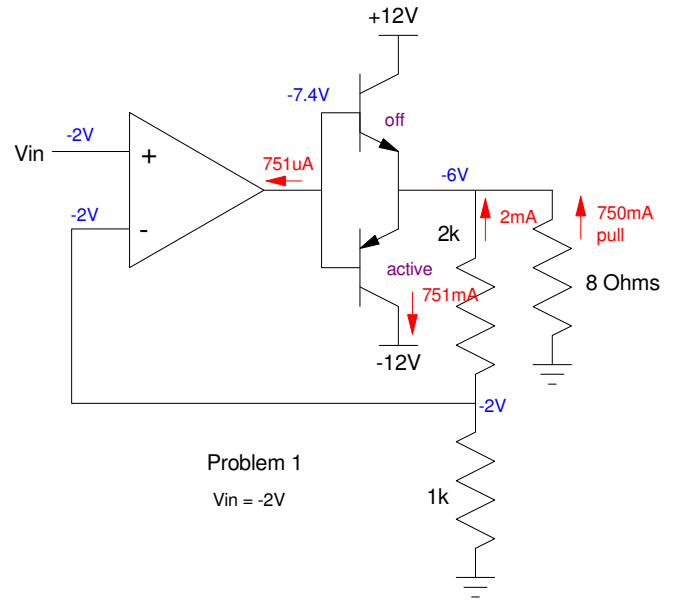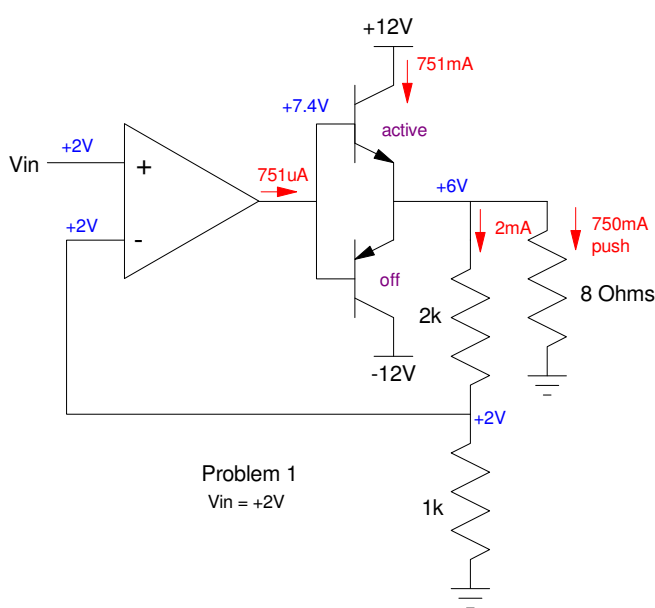1) Determine the voltages and current for the following push-pull amplifier with $V_{in} = 2V$




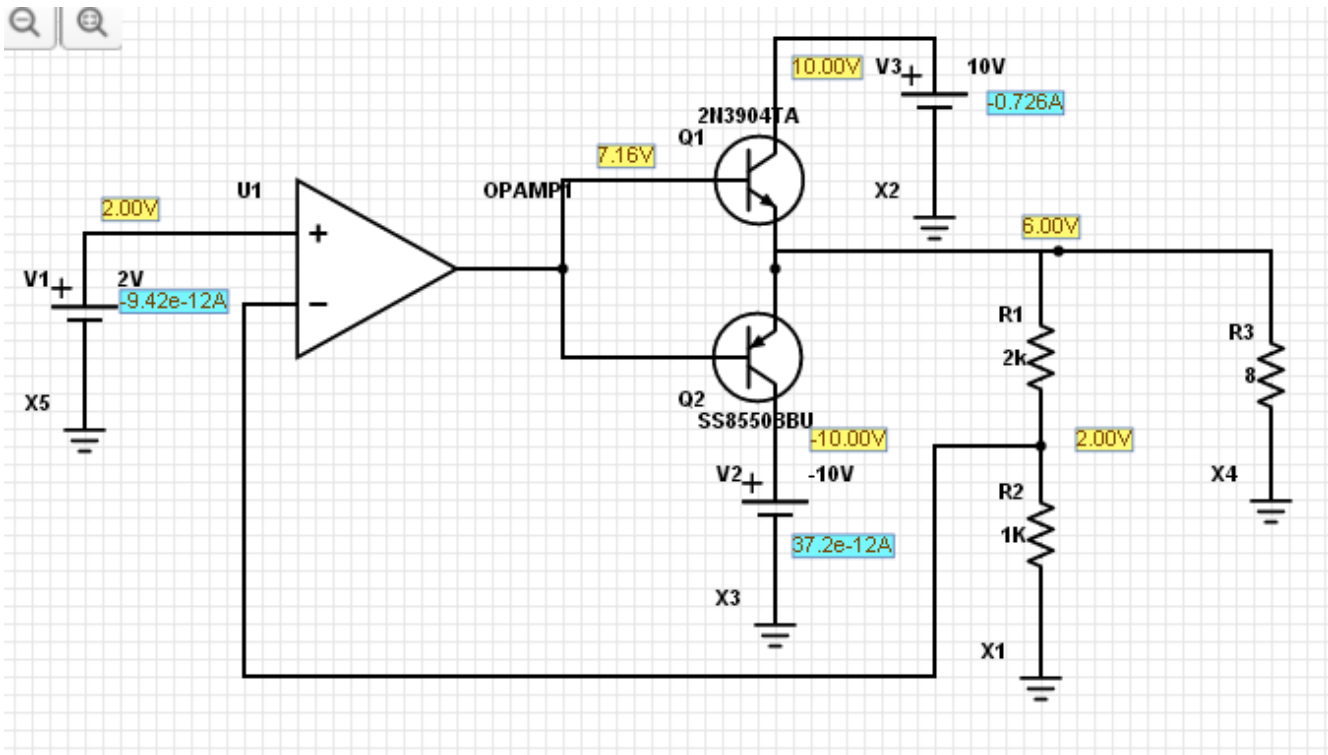2) Verify your design in PartSim

Push: At +2V, the NPN does almost all of the work (provides 726mA)





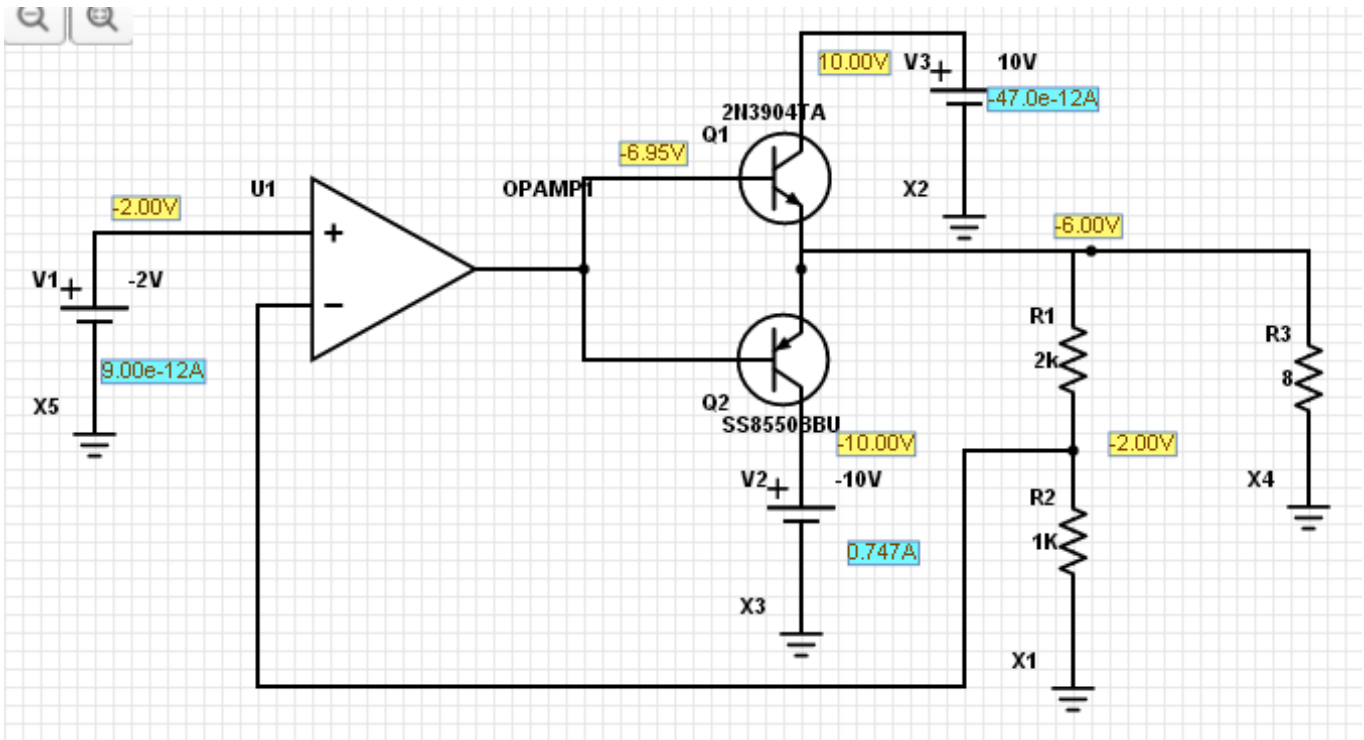Pull: At -2V, the PNP does almost all of the work (747mA)



3) Determine the voltages and current for the following push-pull amplifier with


- $V_{in} = 2V$
- $V_{in} = -2V$

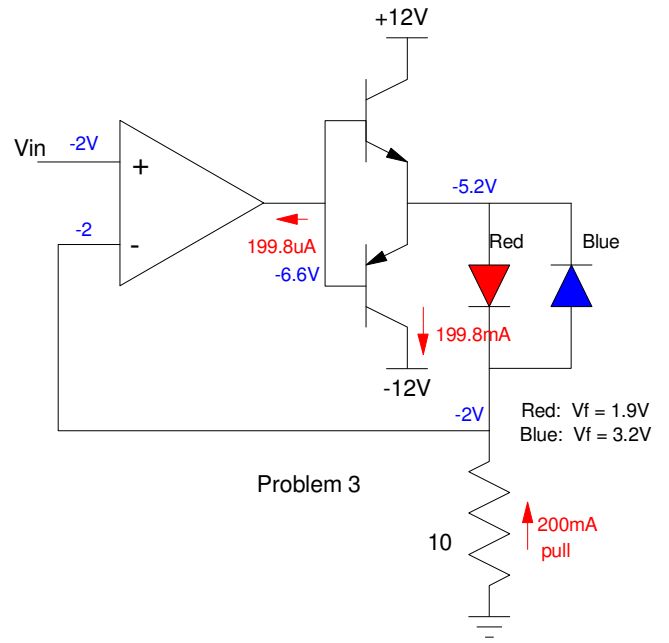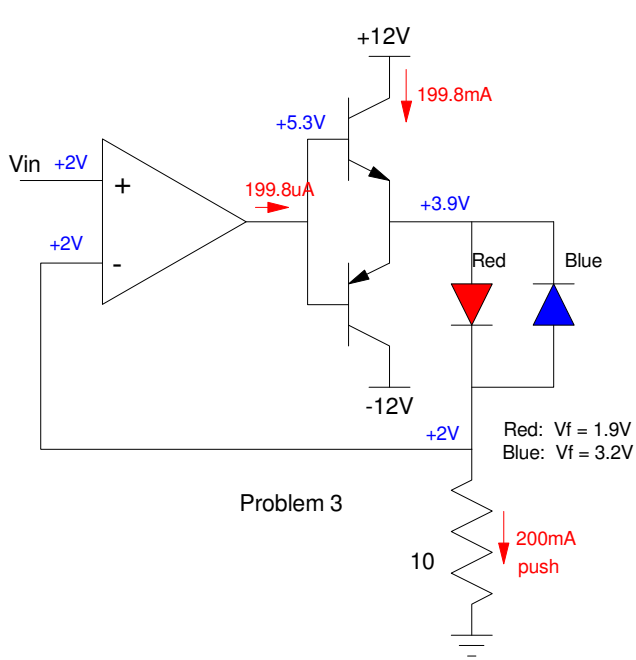


Op-Amp Circuits:

4) Design an op-amp circuit to implement the function


$$Y = 4X$$

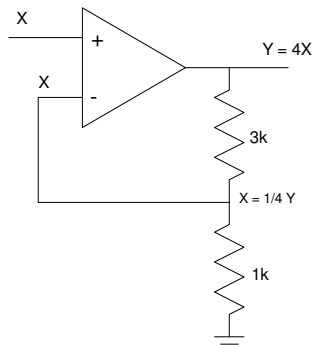

$$Y = -4X$$

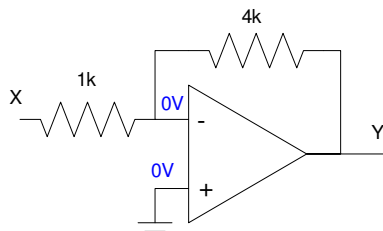

$$Y = 4X - 12 = 4(X - 3)$$

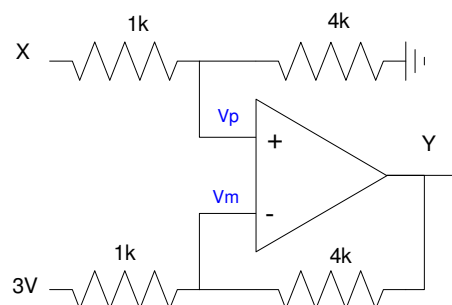

A light sensor has the following light / resistance relationship:

$$R = \frac{100,000}{Lux} \Omega$$

5) Design an instrumentation amplifier whose output is

- 0V when the light level is 50 Lux
- 10V when the light level is 100 Lux

Assume a voltage divider with a +10V input and a 1k resistor:

50 Lux

- $R = 2000 \text{ Ohms}$
- $V_a = 6.666V$
- $V_o = 0V$

100 Lux

- $R = 1000 \text{ Ohms}$
- $V_a = 5.00V$
- $V_o = +10V$


Since the output increases when the input decreases, connect to the - input

The output is 0V when the input is 6.666V. Set the offset to 6.666V

The gain is

$$gain = \left(\frac{\delta output}{\delta input} \right) = \left(\frac{10V-0V}{6.666V-5.00V} \right) = 6$$

Pick a 6:1 ratio for the resistors:

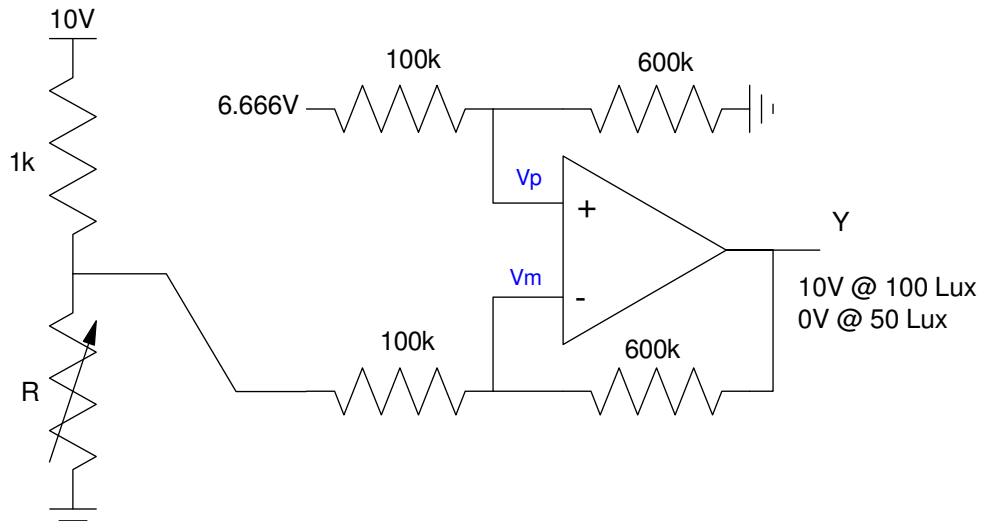

6) Design an instrumentation amplifier whose output is

- -10V when the light level is 50 Lux
- +10V when the light level is 100 Lux

Assume a voltage divider with a +10V input and a 1k resistor:

50 Lux

- $R = 2000 \text{ Ohms}$
- $V_a = 6.666\text{V}$
- $V_o = -10\text{V}$

100 Lux

- $R = 1000 \text{ Ohms}$
- $V_a = 5.00\text{V}$
- $V_o = +10\text{V}$

Since the output increases when the input decreases, connect to the - input

The gain is


$$\text{gain} = \left(\frac{10\text{V} - (-10\text{V})}{6.666\text{V} - 5.00\text{V}} \right) = 12$$

At 100 Lux

$$Y = \text{gain}(V_p - V_m)$$


$$10 = 12(V_p - 5)$$

$$V_p = 5.8333$$

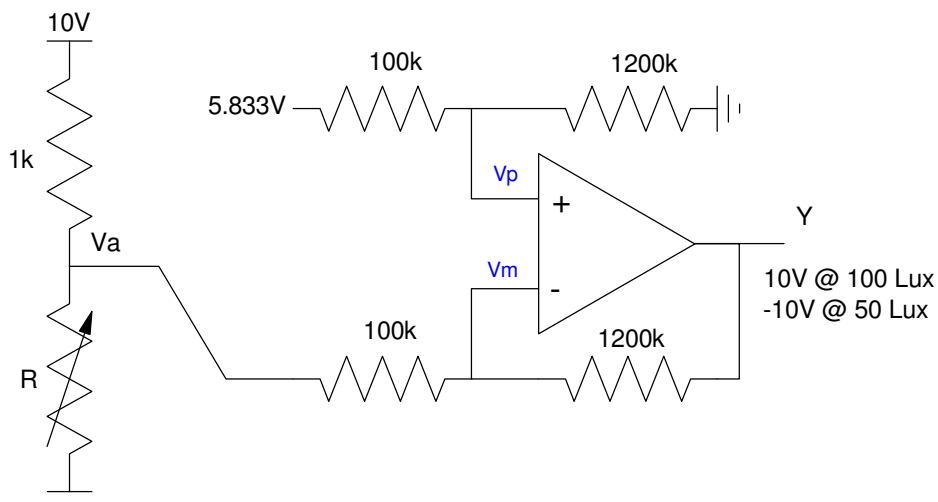

Op-Amp Circuits

7) Assume ideal op-amps

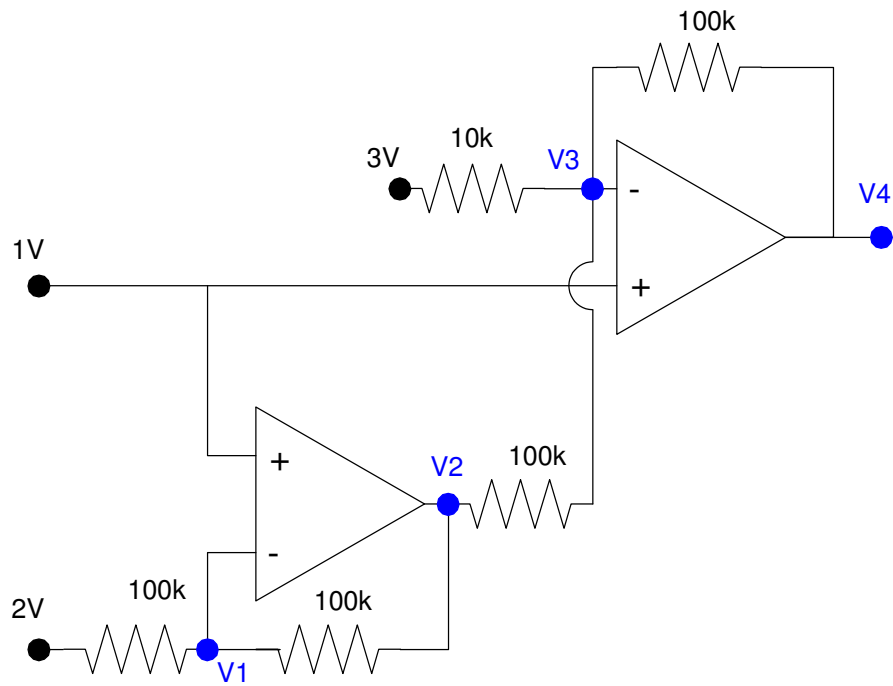

Write the voltage node equations for the following op-amp circuits

@ V2 $V_1 = 1$

@ V4 $V_3 = 1$

$$\left(\frac{V_1 - 2}{100k}\right) + \left(\frac{V_1 - V_2}{100k}\right) = 0$$

$$\left(\frac{V_3 - V_2}{100k}\right) + \left(\frac{V_3 - V_4}{100k}\right) + \left(\frac{V_3 - 3}{10k}\right) = 0$$

Solve for the voltages V1 .. V4

$$V_2 = 0V$$

$$V_4 = 9V$$