

## ECE 321 - Homework #2

Active Filters, Poles, Zeros, & Frequency Response. Due Monday, April 9th, 2018

1) Assume X and Y are related by the following transfer function:

$$Y = \left( \frac{2000}{(s+5)(s+6)(s+7)} \right) X = \left( \frac{2000}{s^3 + 18s^2 + 107s + 210} \right) X$$

1a) What is the differential equation relating X and Y?

Cross multiply

$$(s^3 + 18s^2 + 107s + 210)Y = (2000)X$$

'sY' means *the derivative of y*

$$y''' + 18y'' + 107y' + 210y = 2000x$$

1b) Determine y(t) assuming

$$x(t) = 2 + 3 \cos(10t)$$

Treat this as two separate problems

$$x(t) = 2$$

$$s = 0$$

$$Y = \left( \frac{2000}{(s+5)(s+6)(s+7)} \right)_{s=0} \cdot X$$

$$Y = (9.52) \cdot (2)$$

$$y(t) = 19.04$$

$$x(t) = 3 \cos(10t)$$

$$s = j10$$

$$X = 3 + j0$$

$$Y = \left( \frac{2000}{(s+5)(s+6)(s+7)} \right)_{s=j10} \cdot (3 + j0)$$

$$Y = (-1.25 - j0.055) \cdot (3 + j0)$$

$$Y = -3.76 - j0.16$$


$$y(t) = -3.76 \cos(10t) + 0.16 \sin(10t)$$

Put them together:


$$y(t) = 19.04 - 3.76 \cos(10t) + 0.16 \sin(10t)$$

1c) Plot the gain vs. frequency for this filter from  $0 < \omega < 20$  rad/sec
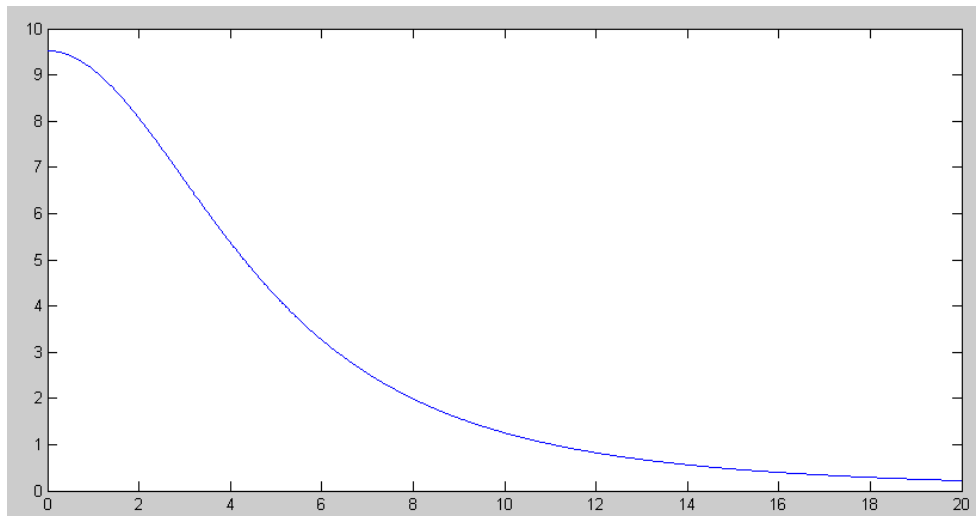
```
>> w = [0:0.01:20]';
>> s = j*w;
>> G = 2000 ./ ( (s+5).*(s+6).*(s+7) );
>> plot(w,abs(G))
```



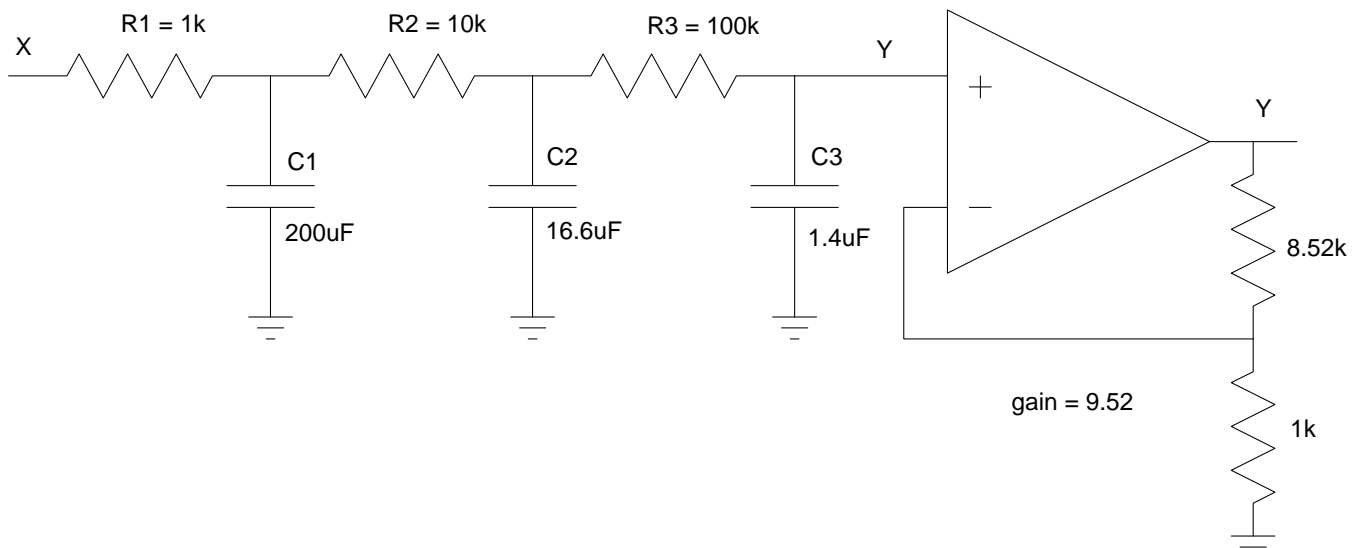1d) Design an op-amp circuit to implement this filter.



$$\frac{1}{R_1 C_1} = 5$$

$$\frac{1}{R_2 C_2} = 6$$

$$\frac{1}{R_3 C_3} = 7$$

2) Assume X and Y are related by the following transfer function:

$$Y = \left( \frac{2000}{(s+10)(s+5+j8.67)(s+5-j8.67)} \right) X = \left( \frac{2000}{s^3+20s^2+200s+1000} \right) X$$

2a) What is the differential equation relating X and Y?

Cross multiply

$$(s^3 + 20s^2 + 200s + 1000)Y = (2000)X$$

This means

$$y''' + 20y'' + 200y' + 1000y = 2000x$$

2b) Determine y(t) assuming

$$x(t) = 2 + 3 \cos(10t)$$

Treat this as two separate problems

$$x(t) = 2$$

$$s = 0$$

$$Y = \left( \frac{2000}{s^3+20s^2+200s+1000} \right)_{s=0} \cdot X$$

$$Y = (2) \cdot 2$$

$$y(t) = 4$$

$$x(t) = 3 \cos(10t)$$

$$s = j10$$

$$X = 3 + j0$$

$$Y = \left( \frac{2000}{s^3+20s^2+200s+1000} \right)_{s=j10} \cdot (3 + j0)$$

$$Y = (-1 - j) \cdot (3 + j0)$$

$$Y = -3 - j3$$


$$y(t) = -3 \cos(10t) + 3 \sin(10t)$$

Put it together

$$y(t) = 4 - 3 \cos(10t) + 3 \sin(10t)$$

2c) Plot the gain vs. frequency for this filter from  $0 < \omega < 20$  rad/sec
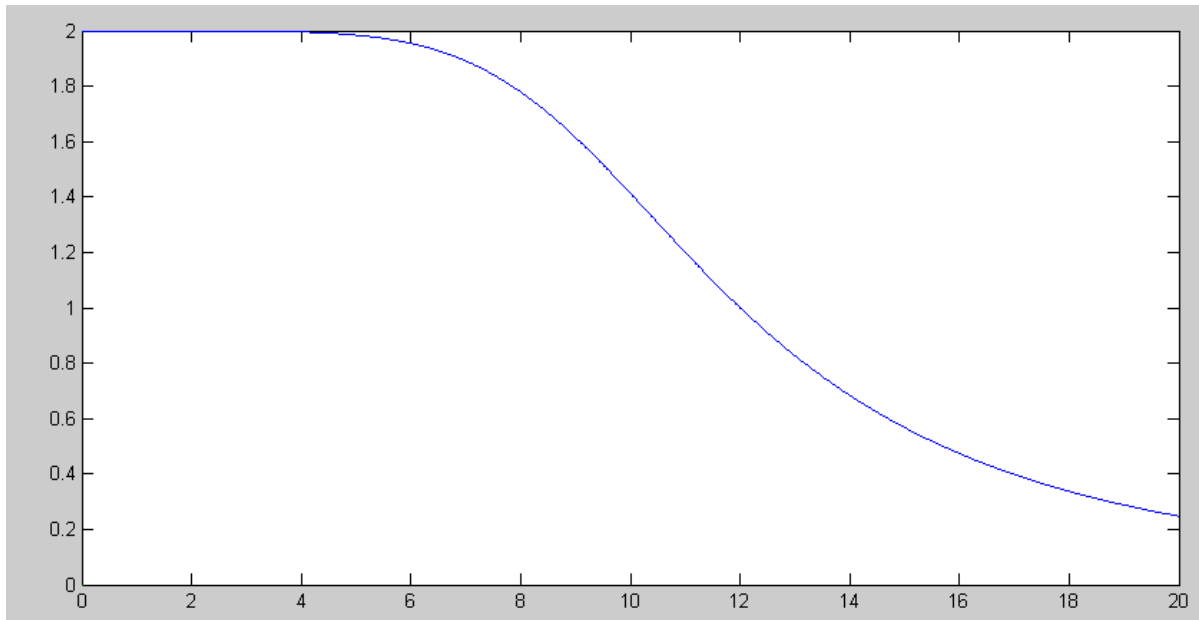
```
>> w = [0:0.01:20]';  
>> s = j*w;  
>> G = 2000 ./ ( s.^3 + 20*s.^2 + 200*s + 1000);  
>> plot(w,abs(G))
```



2d) Design an op-amp circuit to impliment this filter.

Rewrite this as two filters cascaded

$$Y = \left( \frac{10}{s+10} \right) \left( \frac{200}{(s+5+j8.67)(s+5-j8.67)} \right) X$$

$$Y = \left( \frac{10}{s+10} \right) \left( \frac{200}{(s+10\angle 60^\circ)(s+10\angle -60^\circ)} \right) X$$

This is an RC filter ( $1/RC = 10$ ) and a 2nd-order low-pass filter

$$\frac{1}{RC} = 10$$


Let  $R = 100k$ ,  $C = 1\mu F$

$$3 - k = 2 \cos \theta$$

$$3 - k = 2 \cos (60^\circ)$$

$$k = 2 = \left( 1 + \frac{R_2}{R_1} \right)$$

Let  $R_1 = R_2 = 100k$

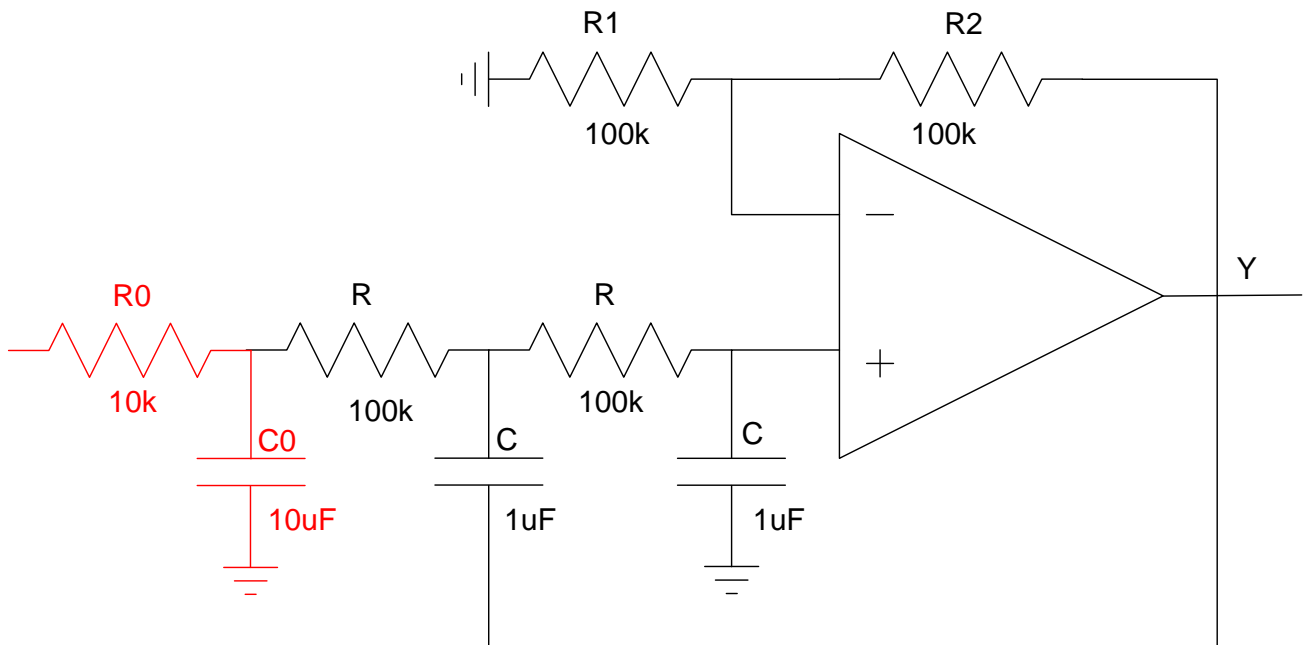

3) Assume X and Y are related by the following transfer function:

$$Y = \left( \frac{4s}{(s+2+j9.8)(s+2-j9.8)} \right) X = \left( \frac{4s}{s^2+4s+100} \right) X$$

3a) What is the differential equation relating X and Y?

Cross multiply

$$(s^2 + 4s + 100)Y = (4s)X$$

this means

$$y'' + 4y' + 100y = 4x'$$

3b) Determine y(t) assuming

$$x(t) = 2 + 3 \cos(10t)$$

Treat this as two separate problems

$$x(t) = 2$$

$$s = 0$$

$$X = 2$$

$$Y = \left( \frac{4s}{s^2+4s+100} \right)_{s=0} \cdot X$$

$$Y = (0) \cdot (2)$$

$$Y = 0$$

$$y(t) = 0$$

$$x(t) = 3 \cos(10t)$$

$$s = j10$$

$$X = 3 + j0$$

$$Y = \left( \frac{4s}{s^2+4s+100} \right)_{s=j10} \cdot X$$

$$Y = (1 + j0) \cdot (3 + j0)$$


$$Y = 3 + j0$$

$$y(t) = 3 \cos(10t)$$


Put it together

$$y(t) = 0 + 3 \cos(10t)$$

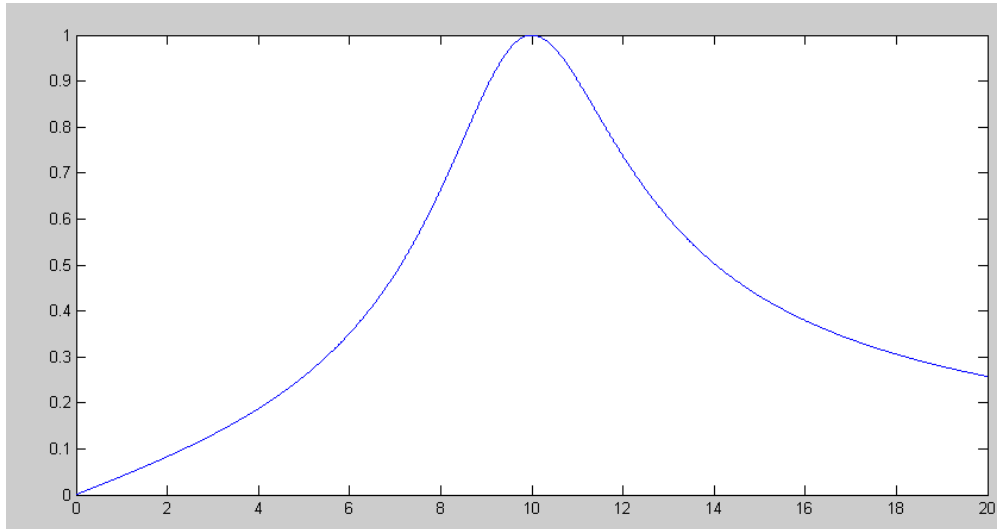3c) Plot the gain vs. frequency for this filter from  $0 < \omega < 20$  rad/sec



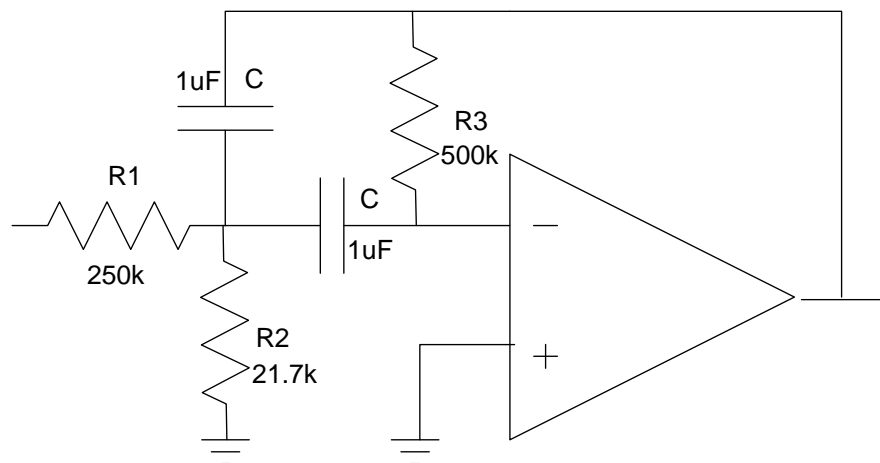3d) Design an op-amp circuit to implement this filter.



$$Y = \left( \frac{-\left(\frac{1}{R_1 C}\right)s}{s^2 + \left(\frac{2}{R_3 C}\right)s + \left(\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}\right)} \right) X = \left( \frac{4s}{s^2 + 4s + 100} \right) X$$

Let  $C = 1\mu\text{F}$

$$\left( \frac{1}{R_1 C} \right) = 4 \quad R_1 = 250\text{k}$$

$$\left( \frac{2}{R_3 C} \right) = 4 \quad R_3 = 500\text{k}$$

$$\left( \frac{R_1 + R_2}{R_1 R_2 R_3 C^2} \right) = 100 \quad R_2 = 21,739$$

**4) Lab:** Build a push-pull amplifier to meet the following requirements:

- Input: +/- 10V signal capable of driving 10mA ( 1 k Ohm )
- Output: 8 Ohm speaker
- Relationship:  $Y = X$  +/- 0.5 Volts from DC to 10kHz.

Collect data to verify your push-pull amplifier is working (save your circuit - we'll use it next week)