


# ECE 321 Final - Name \_\_\_\_\_

Closed-Book, Closed Notes, Calculators Permitted. - Spring 2019

1) Push Pull Amplifiers Determine the voltages and currents for the following push-pull amplifier. Assume TIP transistors:

- $\beta = 1000$
- $|V_{be}| = 1.4V$
- $\min(|V_{ce}|) = 0.9V$

I1	I2	V3	V4	V5
<b>1.32 mA</b>	<b>1.32 A</b>	<b>12V</b> <i>saturated at +Vcc</i>	<b>10.6V</b>	<b>1.77V</b>

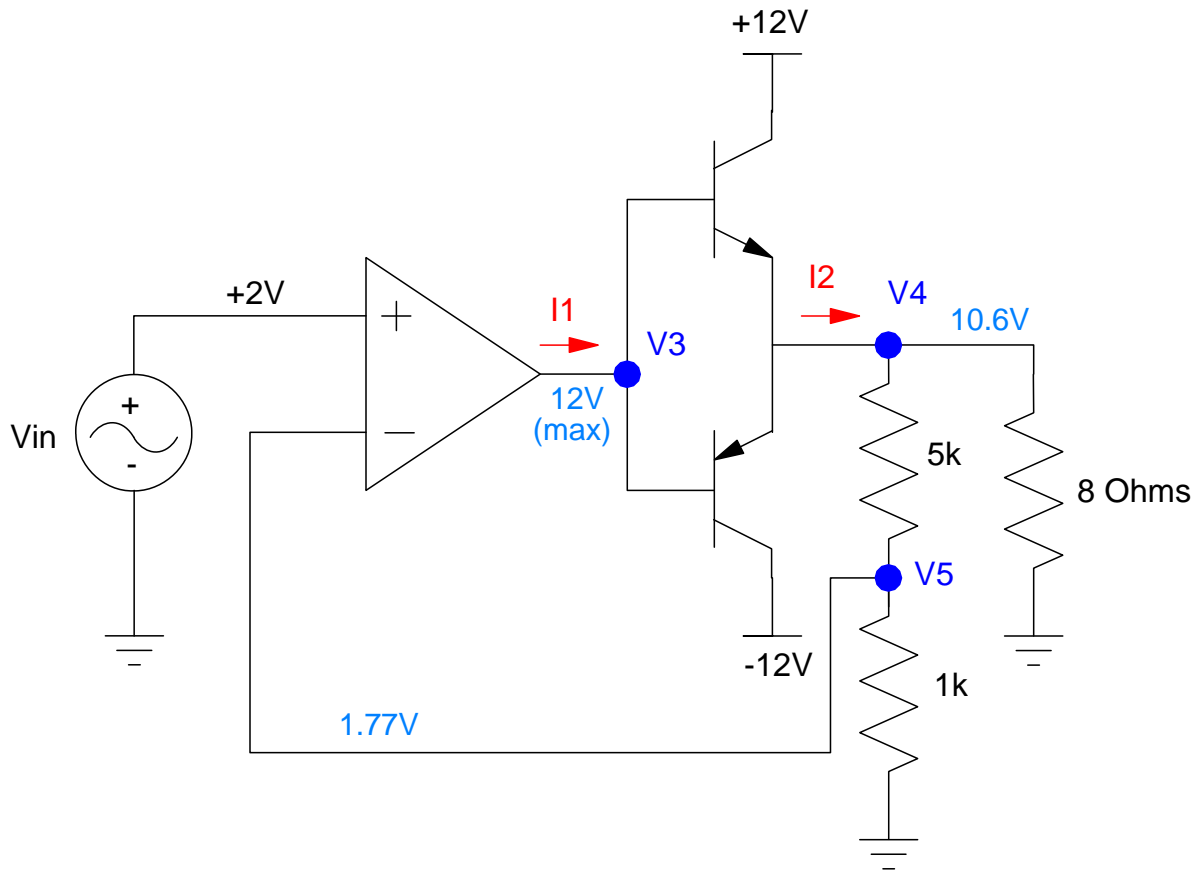


Assume  $V_p = V_m$ .

- $V5 = 2V$
- $V4 = 12V$  (can't happen with a 12V supply)

Assume the op-amp is maxed out at  $V_{cc}$  (+12V)

- $V3 = 12V$
- $V4 = V3 - 1.4V = 10.6V$
- $V5 = V4 / 6 = 1.77V$

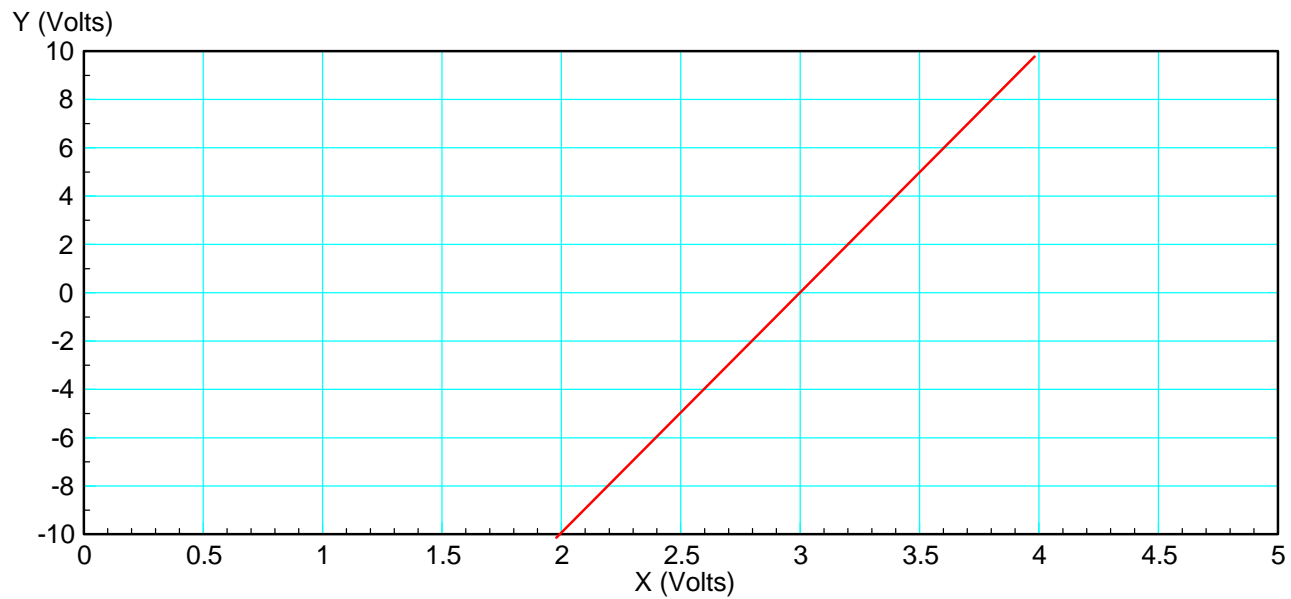
2a) Determine the relationship between X and Y from the following graph.



$$y = 10x - 30$$


2b) Design an op-amp circuit to match the following relationship between X and Y:

$$y = 10(x - 3)$$

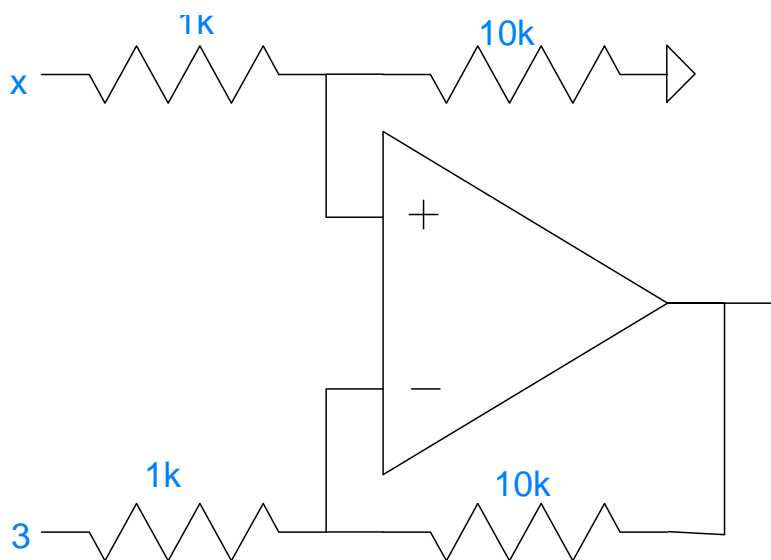

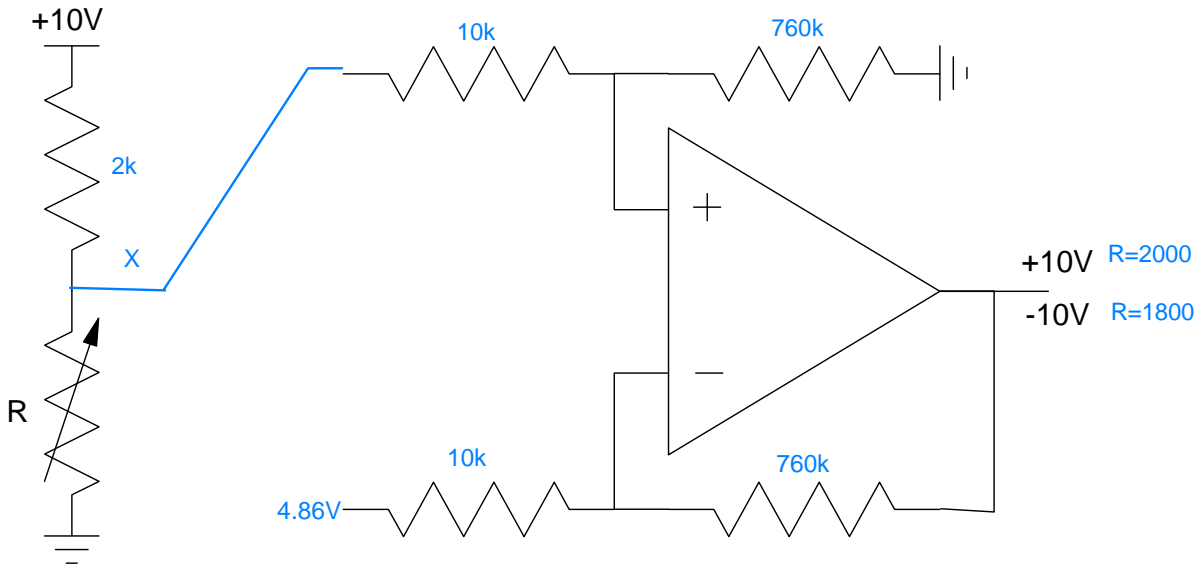3) Design a circuit which outputs

- -10V when R = 1800 Ohms
- +10V when R = 2000 Ohms



Assume a 2k resistor

When R = 1800

$$X = \left( \frac{1800}{1800+2000} \right) 10V = 4.7368V$$

When R = 2000


$$X = \left( \frac{2000}{2000+2000} \right) 10V = 5.00V$$

$$gain = \left( \frac{20V}{5.00V-4.7368V} \right) = 76.0$$

$$offset = \left( \frac{5.00V+4.7368V}{2} \right) = 4.86V$$

4) The following circuit uses a linearizing circuit with an instrumentation amplifier. Determine the voltages at V1..V4

V1	V2	V3	V4
<b>3.0805 V</b>	<b>4 V</b>	<b>4 V</b>	<b>7.68 V</b>

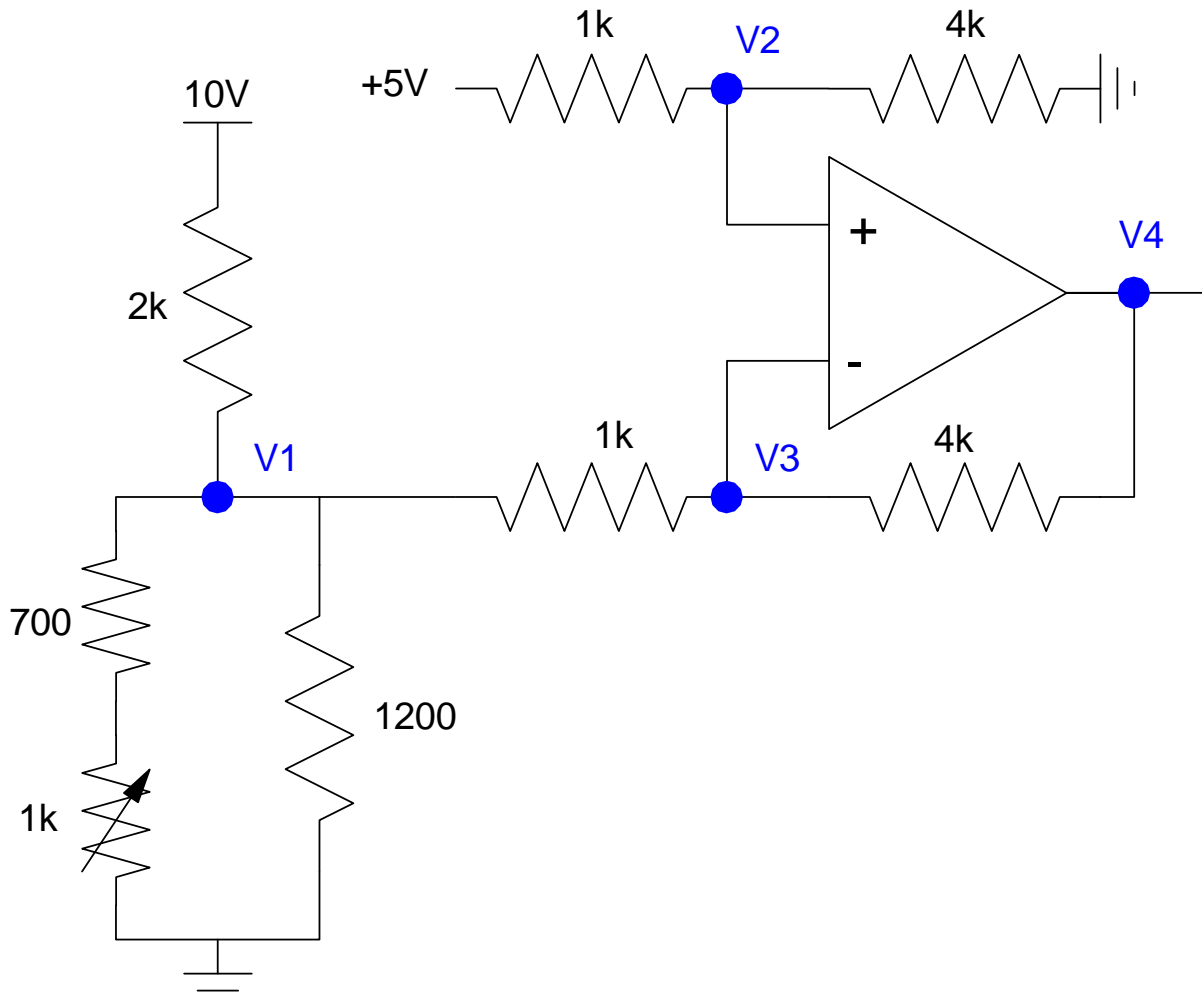

$$V_2 = \left( \frac{4k}{4k+1k} \right) 5V = 4V$$

$$V_3 = V_2 = 4V$$

$$\left( \frac{V_1}{1700} \right) + \left( \frac{V_1}{1200} \right) + \left( \frac{V_1-10}{2000} \right) + \left( \frac{V_1-4}{1000} \right) = 0 \quad \Rightarrow V_1 = 3.08V$$

$$V_4 = \left( \frac{4k}{1k} \right) (5 - V_1) = 7.68V$$

5) X and Y are related by the following filter

$$Y = \left( \frac{2s+7}{s^2+2s+17} \right) X = \left( \frac{2s+7}{(s+1+j4)(s+1-j4)} \right) X$$

a) What is the differential equation relating X and Y?

cross multiply

$$(s^2 + 2s + 17)Y = (2s + 7)X$$

'sY' means 'the derivative of Y'

$$y'' + 2y' + 17y = 2x' + 7x$$

b) Find y(t) assuming

$$x(t) = 5 + 6 \sin(10t)$$

Use superposition

$$x(t) = 5$$

$$X = 5$$

$$s = 0$$

$$Y = \left( \frac{2s+7}{s^2+2s+17} \right) X$$

$$Y = \left( \frac{2s+7}{s^2+2s+17} \right)_{s=0} \cdot (5)$$

$$Y = \left( \frac{7}{17} \right) \cdot 5$$

$$Y = 2.0588$$

$$x(t) = 6 \sin(10t)$$

$$X = 0 - j6$$

$$s = j10$$

$$Y = \left( \frac{2s+7}{s^2+2s+17} \right) X$$

$$Y = \left( \frac{2s+7}{s^2+2s+17} \right)_{s=j10} \cdot (0 - j6)$$

$$Y = -1.48 + j0.15$$

real means cosine, -imag means sine

$$y(t) = -1.48 \cos(10t) - 0.15 \sin(10t)$$

$$y(t) = 2.0588 - 1.48 \cos(10t) - 0.15 \sin(10t)$$

6) The transfer function for a 4th-order Butterworth low-pass filter with a corner at 100 rad/sec is

$$Y = \left( \frac{100^4}{(s+100\angle 22.5^\circ)(s+100\angle -22.5^\circ)(s+100\angle 67.5^\circ)(s+100\angle -67.5^\circ)} \right) X$$


Find R and C to implement this filter

C1	R1	C2	R2
<b>0.1 uF</b>	<b>15k</b>	<b>0.1 uF</b>	<b>123k</b>

Note: The transfer function for the first stage is

$$\left( \frac{k \left( \frac{1}{RC} \right)^2}{s^2 + \left( \frac{3-k}{RC} \right) s + \left( \frac{1}{RC} \right)^2} \right) \quad k = 1 + \frac{R_1}{100,000}$$

$$3 - k = 2 \cos \theta$$

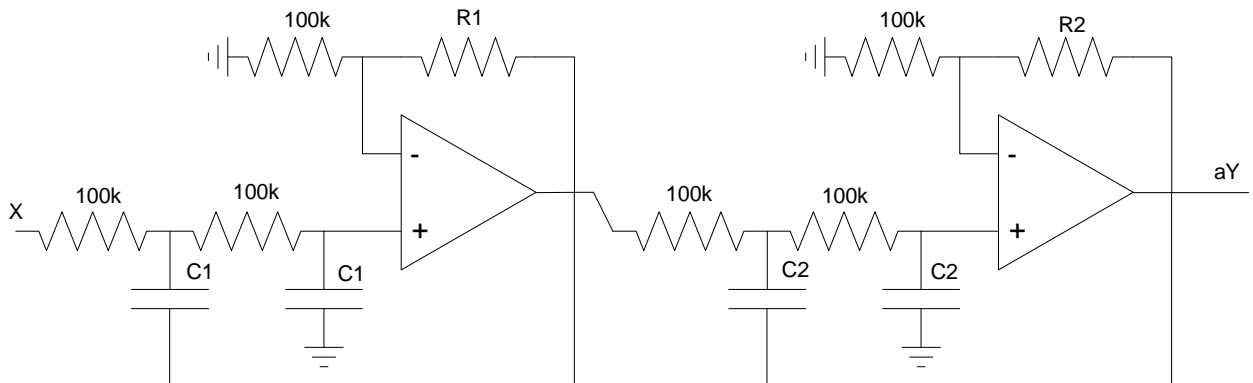

$$\left( \frac{1}{RC} \right) = 100$$

$$R = 100k$$

$$C1 = 0.1\mu F$$

$$\left( \frac{1}{RC} \right) = 100$$

$$R = 100k$$

$$C2 = 0.1\mu F$$

$$3 - k = 2 \cos \theta$$

$$\theta = 22.5^\circ$$

$$k = 1.15$$

$$k = 1 + \left( \frac{R_1}{100k} \right)$$

$$3 - k = 2 \cos \theta$$

$$\theta = 67.5^\circ$$


$$k = 2.2346$$

$$k = 1 + \left( \frac{R_2}{100k} \right)$$

7) Q-Point Analysis. Determine the Thevenin equivalent for R1 and R2 (Vb and Rb) and determine the Q-point for the following transistor circuit. Assume ideal silicon transistors:

- $V_{be} = 0.7V$
- $\beta = 200$

Vb	Rb	Vce	Ic
<b>2V</b>	<b>41.67k</b>	<b>8.767V</b>	<b>403.3uA</b>

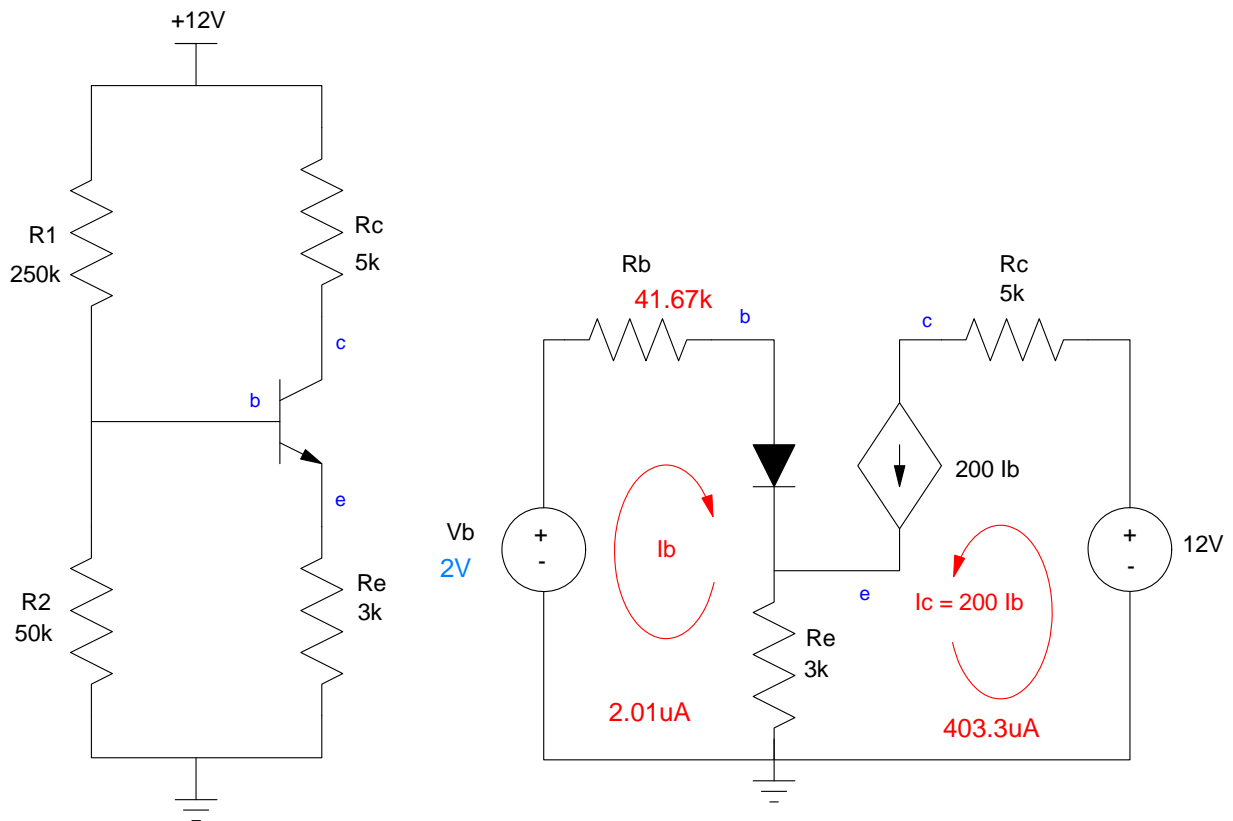

$$R_b = R_1 \parallel R_2 = 41.67k$$

$$V_b = \left( \frac{R_2}{R_1 + R_2} \right) 12V = 2V$$

$$I_b = \left( \frac{2V - 0.7V}{R_b + (1 + \beta)R_e} \right) = 2.01\mu A$$

$$I_c = 200I_b = 403.3\mu A$$

$$V_{ce} = 12 - 5k \cdot I_c - 3k \cdot (I_b + I_c) = 8.767V$$

8) Draw the small signal model for the following common emitter amplifier (with  $C_e$  removed) and determine the corresponding 2-port model



Small Signal Model	$R_{in}$	$A_o$	$R_{out}$
draw the AC model. Assume $Z_c = 0$	<b>106k</b>	<b>-1.94</b>	<b>2k</b>

Due to the current source the 1k resistor looks like a 201k resistor looking from the left

$$R_{in} = 400k \parallel 500k \parallel 4771 + 201k$$

$$R_{in} = 106k$$
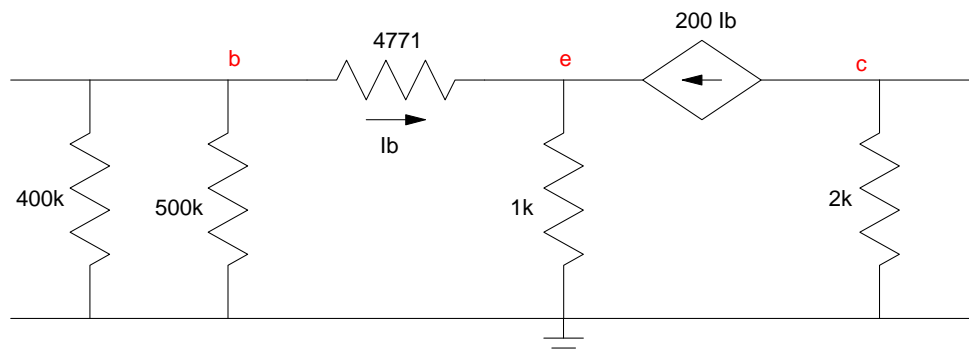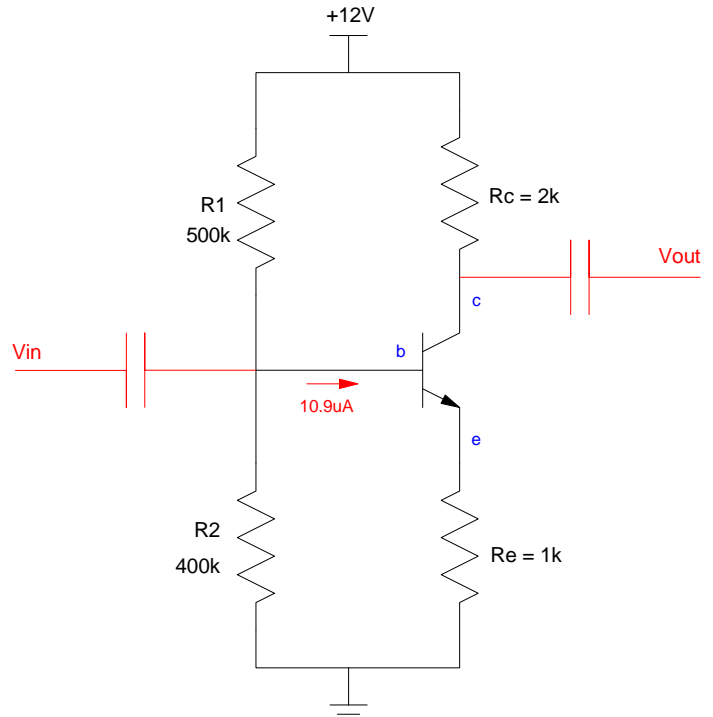
$$A_0 = -\left(\frac{200 \cdot 2k}{4771 + 201k}\right) = -1.944$$



Bonus! Four for the following are Democratic candidates running for President in 2020, four are Godzilla monsters. Circle the ones who are Democrats

Baragon - Buttigieg - Ebirah - Gabbard - Kamacuras - Messam - Orga - Swalwell