

ECE 321 - Quiz #2 - Name _____



Temperature, Strain, Instrumentation Amplifiers. April 11, 2019

1) Temperature Sensor: Assume a temperature sensor has the following characteristics:

$$R = 1000(1 + 0.0043 \cdot T) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- -10V at -40C and
- +10V at +40C

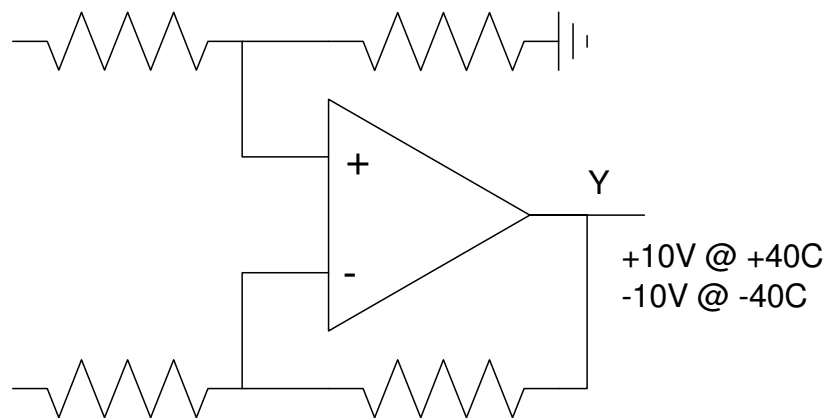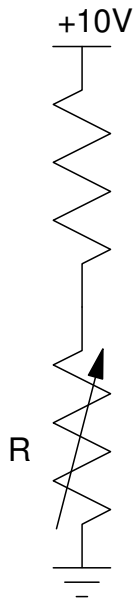


1b) For your circuit, what is the output voltage at 0C?

2) Strain Sensor (take 1). A pressure sensor uses a strain gage to measure the flex of a beam. Assume

- The length of the beam is 200mm
- The thickness of the beam is 2mm
- The beam deflects 10mm when the air pressure is 100 N/m²

Determine the strain on the inside edge and the outside edge. Assume the center line has no strain (free endpoints)

Radius (R)	Strain (inside edge)	Strain (outside edge)


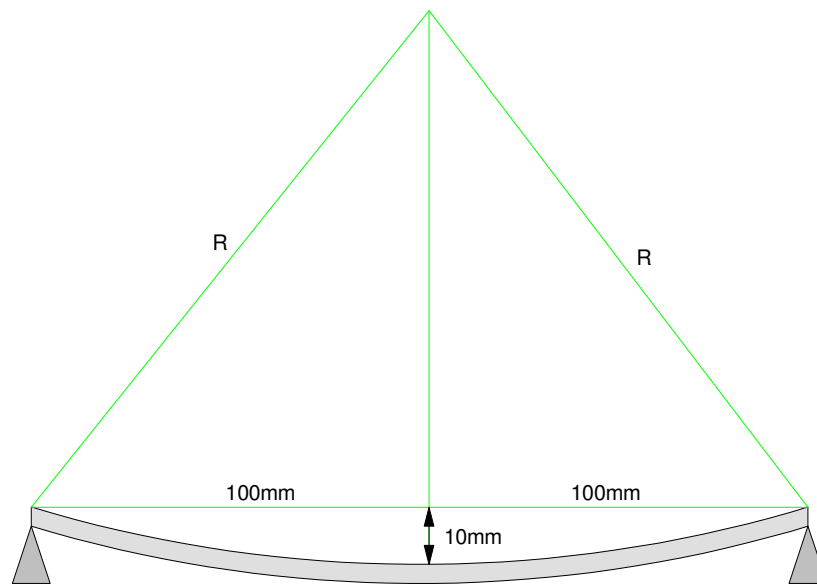


3) Strain Sensor (take 2). Assume a strain sensor has a resistance of

$$R = 120(1 + 2.14\epsilon)$$


where ϵ is the strain. Design a circuit which outputs

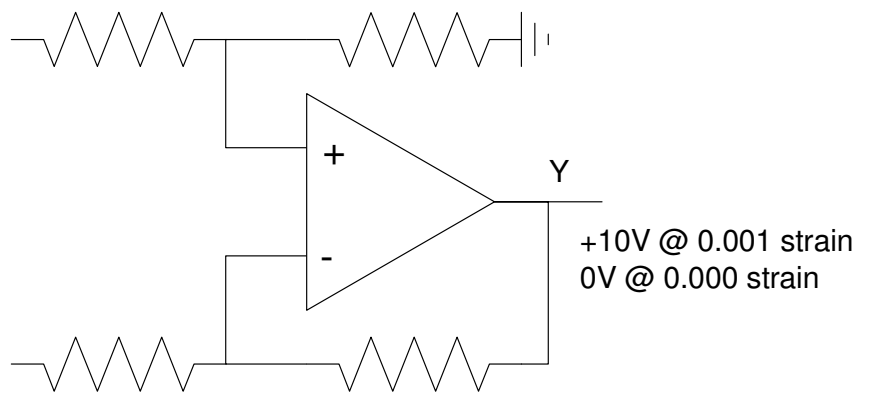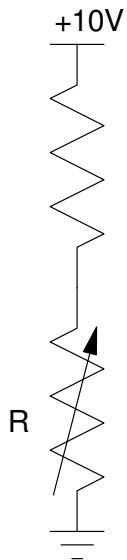- 0V when the strain is 0 and
- +10V when the strain is +0.001



4) The following circuit uses a linearizing circuit with an instrumentation amplifier. Determine the voltages at V1..V4

V1	V2	V3	V4

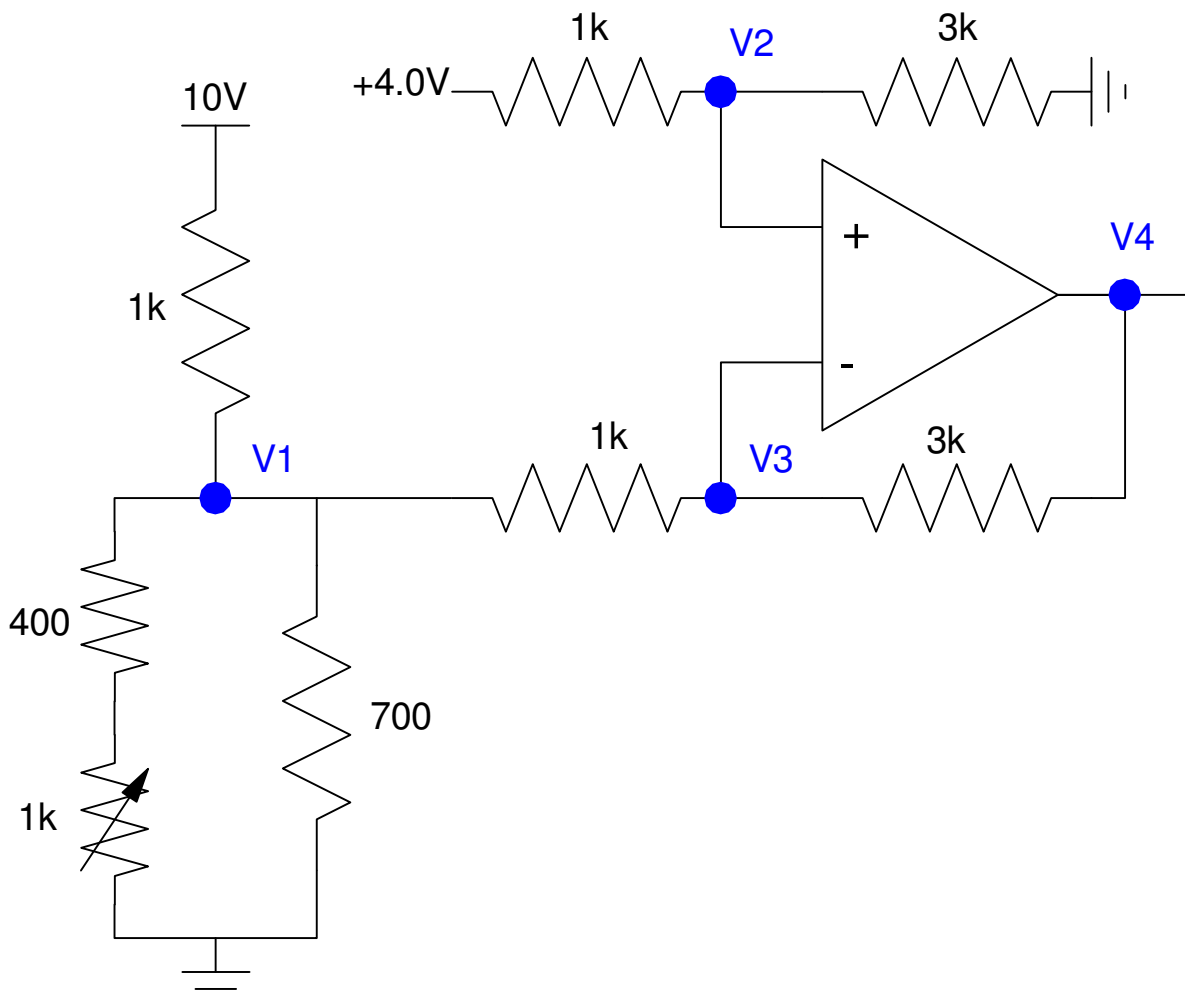

5) Let $\{A, B, C\}$ be -10V to $+10\text{V}$ analog voltages capable of driving 20mA (or less). Design a circuit to implement

$$Y = 2A + 3B - 4C$$

Bonus: All but three of the following countries have tuition-free college. Which three?

Brazil - Canada - Germany - Finland - France - Norway - Slovenia - Sweden - United States