## ECE 321 - Quiz #3 - Name \_\_\_\_

Filters, Common Emitter Amplifiers. April 25, 2019

1) Calibration. Assume a circuit is built which outputs -10V to +10V as light changes from 10 Lux to 100 Lux.

• Determine a calibration function of the form

 $Lux \approx aV + b$ 

• What is the light level (actual and estimated) when V = 5.0V?

Lux = aV + b		Lux when $V = 5.00V$	
a	b	Actual Lux	Estimated Lux from curve fit



2) X and Y are related by the following filter

$$Y = \left(\frac{5}{s^2 + 3s + 2}\right) X = \left(\frac{5}{(s+1)(s+2)}\right) X$$

a) What is the differential equation relating X and Y?

b) Find y(t) assuming

$$x(t) = 10 + 15\cos(3t)$$

## 3) A filter is to meet the following requirements



a) How many poles does this filter need?

b) Give the transfer function for a Butterworth low-pass filter which meets these requirements (note: the corner frequency might need adjusting)

4) Find R and C so that the following filter has the transfer function of

$$Y = \left(\frac{1000}{(s+4)(s+6)(s+8)}\right)X$$

C1	C2	C3	R



5) The transfer function for a 4th-order Chebychev low-pass filter with a corner at 100 rad/sec is

$$Y = \left(\frac{72^2 \cdot 111^2}{\left(s + 72 \angle 38.5^0\right)\left(s + 72 \angle -38.5^0\right)\left(s + 111 \angle 77.8^0\right)\left(s + 111 \angle 77.8^0\right)}\right)X$$

Find R and C to implement this filter

C1	R1	C2	R2

Note: The transfer function for the first stage is

$$\begin{pmatrix} \frac{k\left(\frac{1}{RC}\right)^2}{s^2 + \left(\frac{3-k}{RC}\right)s + \left(\frac{1}{RC}\right)^2} \end{pmatrix} \qquad k = 1 + \frac{R_1}{100,000}$$
$$3 - k = 2\cos\theta$$



Bonus: Which is more:

- The number of Democrats who have announced that they are running for President in 2020, or
- The number of Godzilla movies that have been made?