



ECE 321 - Quiz #4 - Name _____

Common Emitter - Common Base - Common Collector Amplifiers. May 2, 2019

1) Q-Point Analysis. Determine the Thevenin equivalent for R1 and R2 (V_b and R_b) and determine the Q-point for the following transistor circuit. Assume ideal silicon transistors:

- $V_{be} = 0.7V$
- $\beta = 200$



V_b	R_b	V_{ce}	I_c

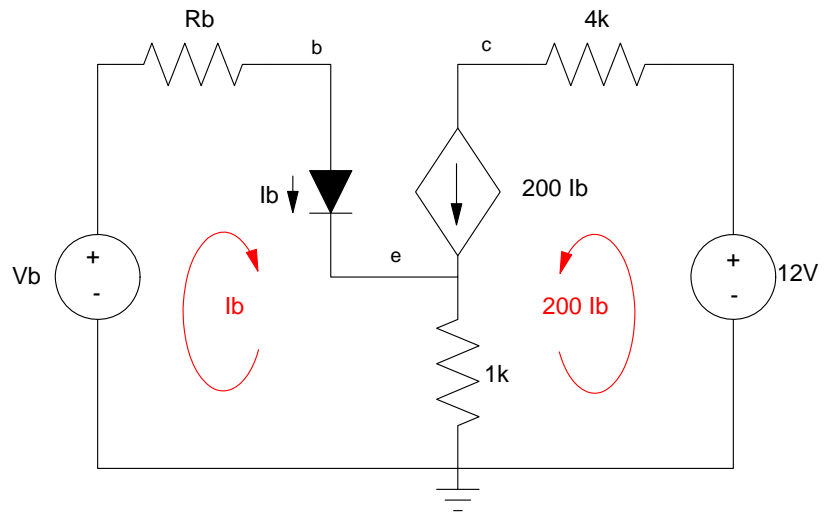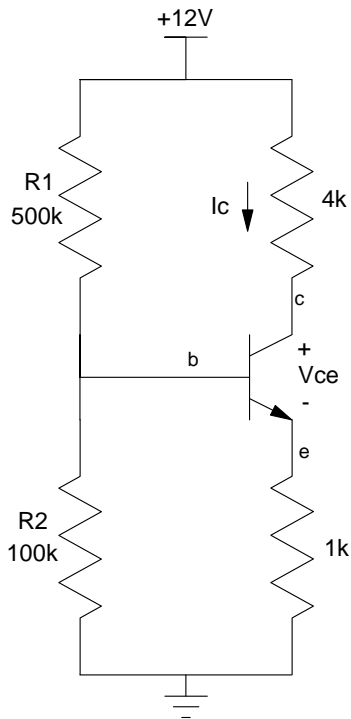

2) Q-Point Design. Find R_b and V_b and the corresponding R_1 and R_2 so that

- The Q-point is stabilized for variations in β (i.e. $(1 + \beta)R_e \gg R_b$)
- $V_{ce} = 6.0V$



R1	R2	Vb	Rb

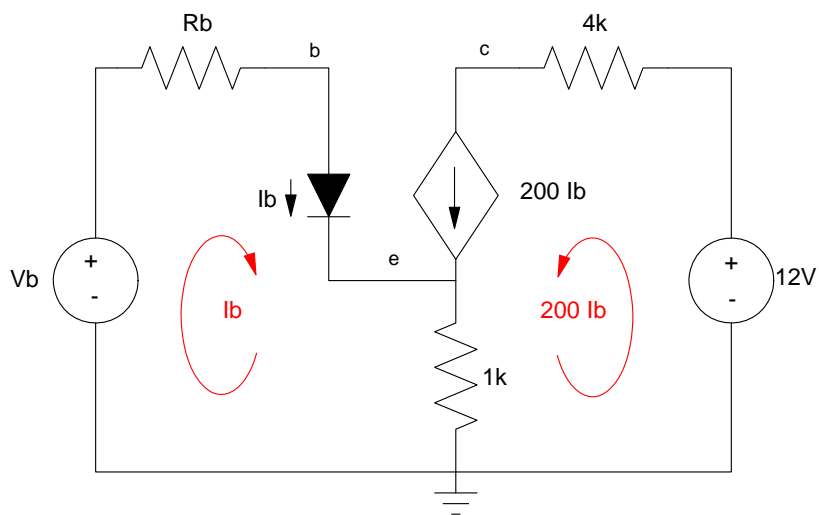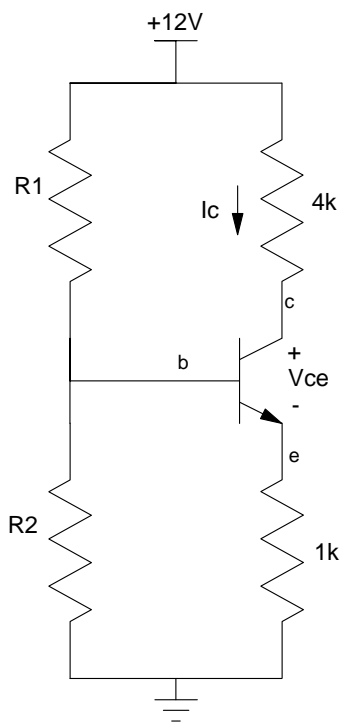

3) AC Analysis: Common Emitter.

- Draw the small signal model for the following common emitter amplifier. Assume $r_f = 17.3k$
- Determine the 2-port model for this common emitter amplifier



Small-Signal Model	R_{in}	A_o	R_{out}
draw			

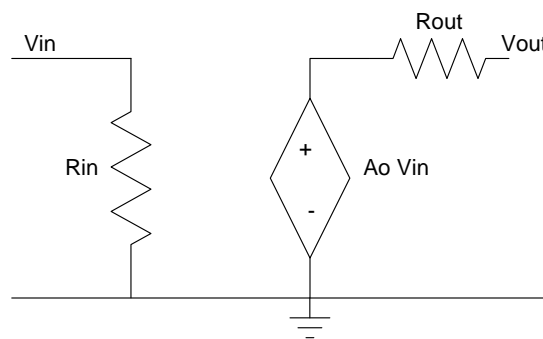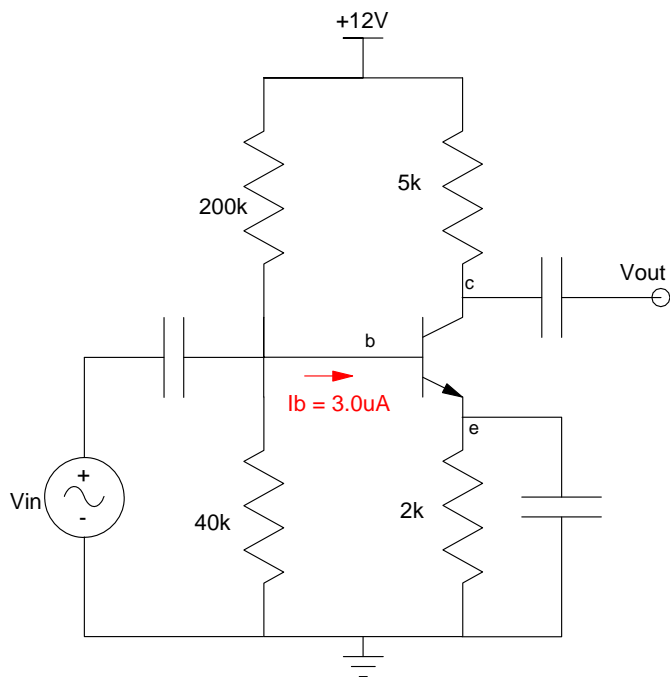

3) AC Analysis: Common Base.

- Draw the small signal model for the following common base amplifier. Assume $r_f = 17.3k$
- Determine the 2-port model for this common emitter amplifier


Small-Signal Model	R_{in}	A_o	R_{out}
draw			

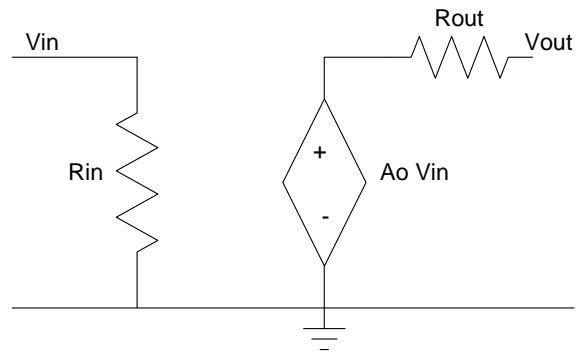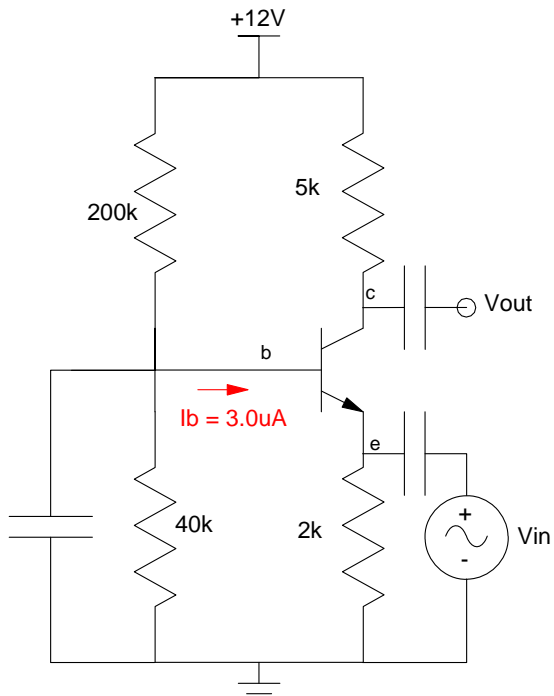

5) Multi-Stage Amplifier: Determine the 2-port model for the following 3-stage amplifier:

CB : CE : CE

Rin	Ai	Rout	Ao

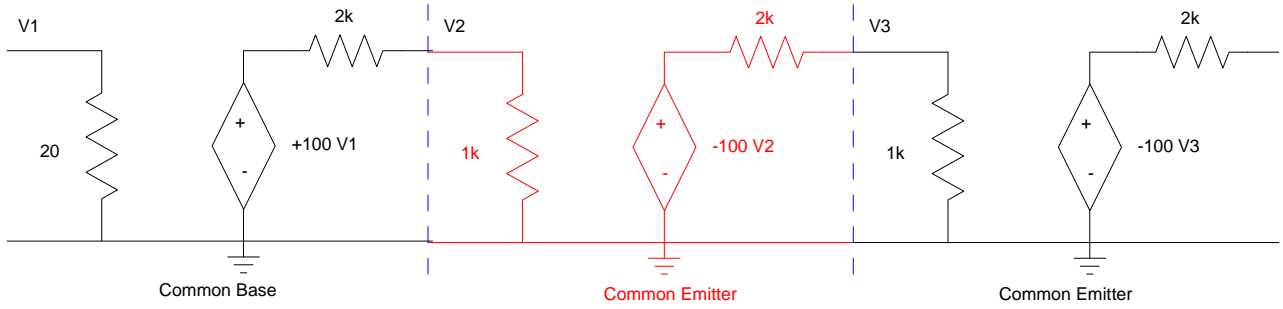

Socialism vs. Capitalism Bonus! What does capitalism say about how wealth is distributed?