

# ECE 321 - Homework #1

Push-Pull Amplifiers, Op-Amp Amplifiers. Due Monday, November 5th, 2018


For the following sections, assume TIP112 (NPN) and TIP117 (PNP) transistors:

- $\beta = 1000$
- $|V_{be}| = 1.4V$
- $\min(|V_{ce}|) = 0.9V$
- $\max(|I_c|) = 3A$

## Push-Pull Amplifiers


2) Specify the voltages and currents for the following voltage amplifier for

- $V_{in} = +2V$
- $V_{in} = -2V$

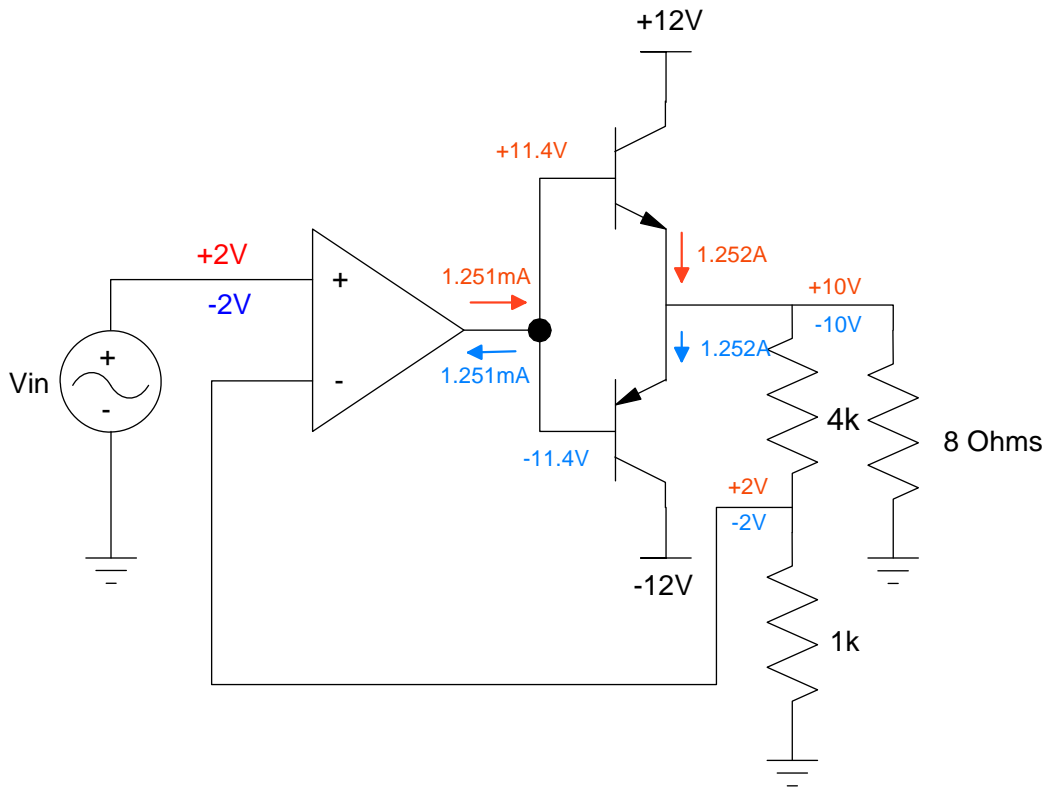

3) Specify the voltages and currents for the following current amplifier for

- $V_{in} = +5V$

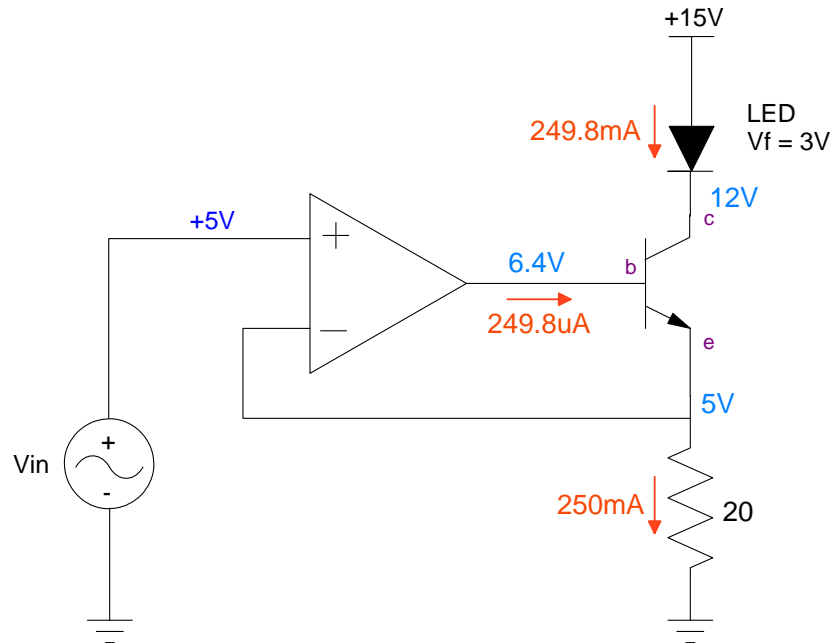

Note:


$$V_{ce} = 7V$$

The transistor is in the active region.

## Op-Amp Amplifiers


4) Design a circuit which implements the function

$$Y = 2X$$

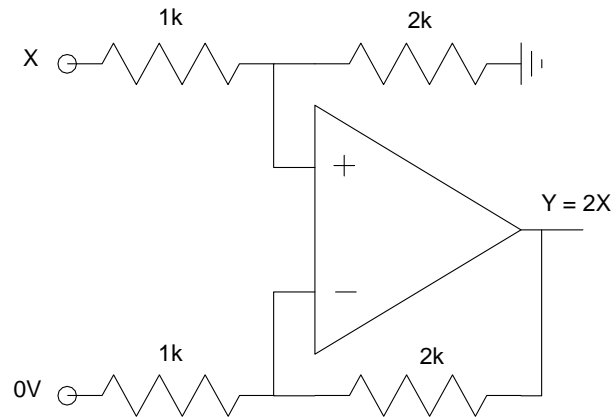

5) Design a circuit which implements the function

$$Y = -2X$$

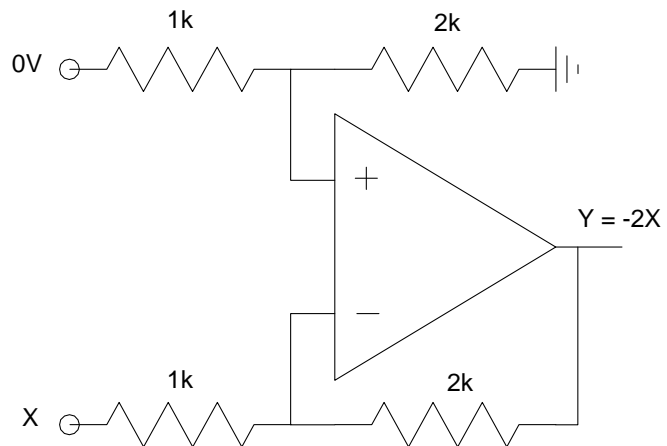

6) Design a circuit which implements the function

$$Y = 2X - 7$$

Rewrite as

$$Y = 2(X - 3.5)$$

