

ECE 321 - Homework #3

Calibration, Filter Circuits, and Frequency Response. Due Monday, April 20th

Please make the subject "ECE 321 HW#3" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

Calibration

Problem 1 & 2) Assume you are using a thermistor where the temperature - resistance relationship is

$$R = 1000 \exp\left(\frac{3905}{T} - \frac{3905}{298}\right) \Omega$$

along with a voltage divider (10V source, 2k resistor:

$$V = \left(\frac{R}{R+2000}\right) \cdot 10V$$

1) Determine a calibration function of the form

$$T \approx aV + b$$


to estimate temperature over the range of (0C, +30C). What is the maximum error in this calibration function?

```
T = [0:0.1:30]';
R = 1000 * exp(3905 ./ (T + 273) - 3905/298);
V = R ./ (R + 2000) * 10;
B = [V, V.^0];
A = inv(B'*B)*B'*T

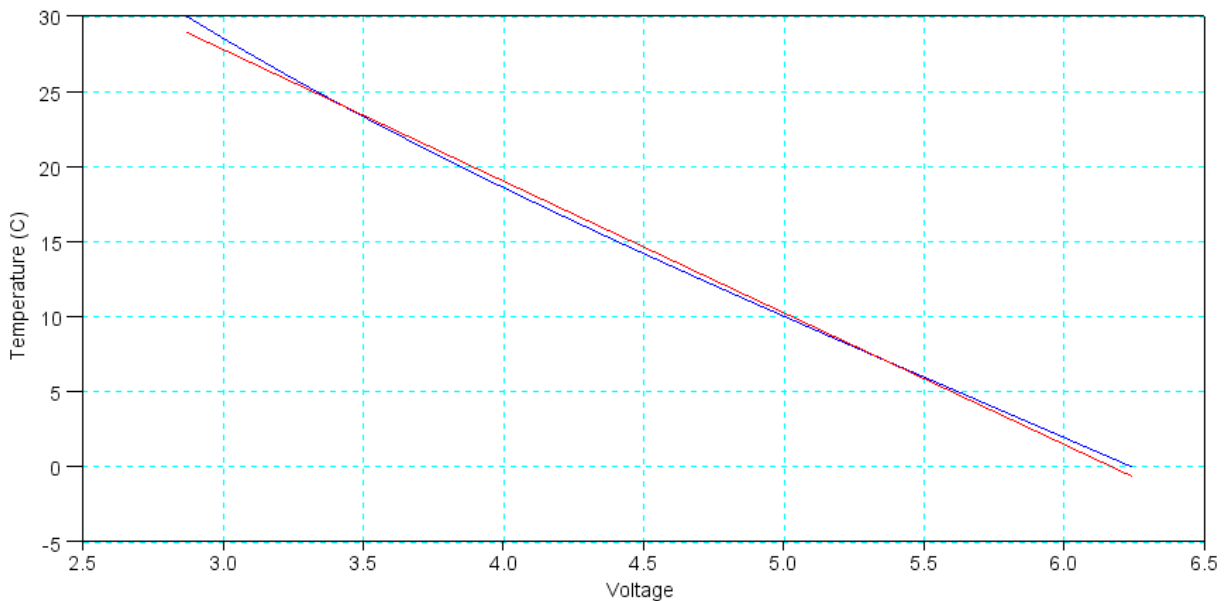- 8.7698745
 54.106726

max(T - B*A)
ans = 1.0738336 maximum error on the high side

min(T - B*A)
ans = - 0.4660400 maximum error on the low side
```



2) Determine a calibration function of the form

$$T \approx aV^3 + bV^2 + cV + d$$


to estimate temperature over the range of (0C, +30C). What is the maximum error in this calibration function?

```
B = [V.^3, V.^2, V, V.^0];  
A = inv(B'*B)*B'*T
```

```
- 0.1489113  
  2.4763568  
- 21.769242  
  75.579249
```

```
max(T - B*A)  
ans = 0.0353359
```

```
min(T - B*A)  
ans = - 0.0151326
```

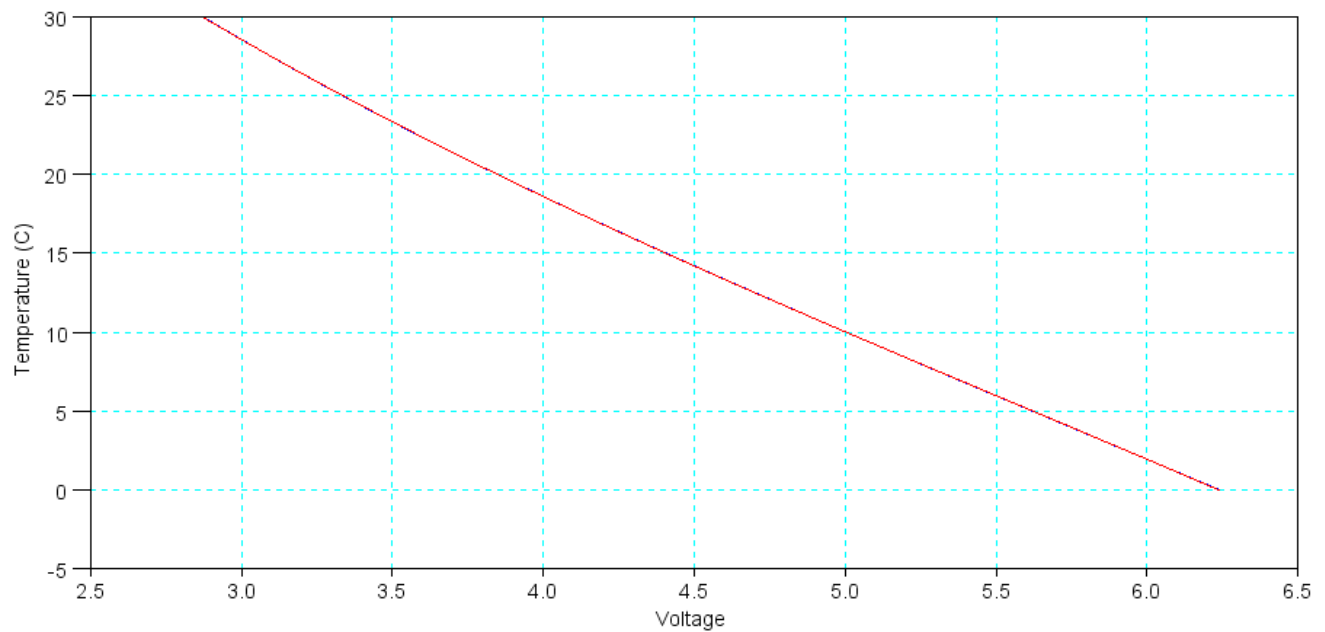

Filters

3) Assume X and Y are related by the following transfer function:

$$Y = \left(\frac{30}{(s+3)(s+8)} \right) X$$

a) What is the differential equation relating x and y?

$$(s^2 + 11s + 24)Y = 30X$$

$$\frac{d^2y}{dt^2} + 11\frac{dy}{dt} + 24y = 30x$$

b) Determine y(t) assuming

$$x(t) = 5 + 6 \cos(4t)$$

Use superposition

$$x(t) = 5$$

$$s = 0$$

$$X = 5 + j0$$

$$Y = \left(\frac{30}{(s+3)(s+8)} \right)_{s=0} (5 + j0)$$

$$Y = 6.25$$

$$y(t) = 6.25$$

$$x(t) = 6 \cos(4t)$$

$$s = j4$$

$$X = 6 + j0$$

$$Y = \left(\frac{30}{(s+3)(s+8)} \right)_{s=j4} (6 + j0)$$

$$Y = 0.720 - j3.960$$

$$y(t) = 0.720 \cos(4t) + 3.960 \sin(4t)$$

The total answer is then

$$y(t) = 6.25 + 0.720 \cos(4t) + 3.960 \sin(4t)$$

Filter Design using *fminsearch()*

4) Design a filter of the form

$$Y = \left(\frac{a}{(s^2+bs+c)(s^2+ds+e)} \right) X$$

to give a gain vs. frequency as close to $G_d(s)$ as possible over the range of (0, 10) rad/sec.

$$G_d(j\omega) = \begin{cases} 1 & 0 < \omega < 6 \\ 0 & \text{otherwise} \end{cases}$$

Plot your filter's actual frequency response vs. its ideal response (given by G_d).


```
Z, e] = fminsearch('costF', [130, 2, 5, 2, 26])
```

```
Z = 181.1933    3.2716    7.0623    1.2414    27.4180
```

```
e = 1.9369
```

meaning
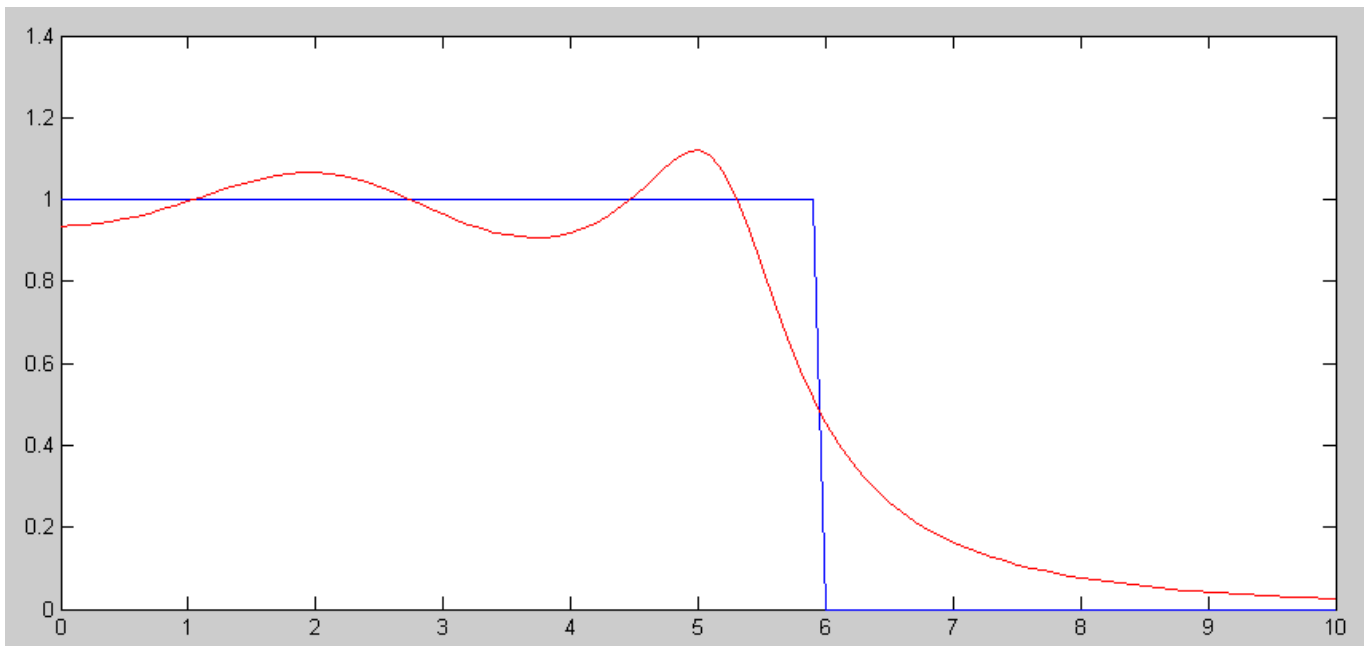
$$G(s) = \left(\frac{181.1933}{(s^2+3.2716s+7.0623)(s^2+1.2414s+27.4180)} \right)$$



Code:

```
function [ J ] = costF( z )

    a = z(1);
    b = z(2);
    c = z(3);
    d = z(4);
    e = z(5);

    w = [0:0.1:10]';
    s = j*w;

    Gd = 1 .* (w < 6);

    num = a;
    den = (s.^2 + b*s + c).*(s.^2 + d*s + e);

    Gs = num ./ den;

    e = abs(Gd) - abs(Gs);

    J = sum(e.^2);

    plot(w,abs(Gd),'b',w,abs(Gs),'r');
    pause(0.01);

end
```

5) Design circuit to implement the filter you designed in problem #4

$$G(s) = \left(\frac{181.1933}{(s^2 + 3.2716s + 7.0623)(s^2 + 1.2414s + 27.4180)} \right)$$

Put in polar form

$$G(s) = \left(\frac{181.1933}{(s + 2.657 \angle \pm 52.01^\circ)(s + 5.2362 \angle \pm 83.19^\circ)} \right)$$

Stage 1:

$$\left(\frac{1}{RC} \right) = 2.657$$

$$C = 1 \mu F$$

$$R = 376 k\Omega$$

$$3 - k = 2 \cos(52.01^\circ)$$

$$k = 1.769$$

Stage 2


$$\left(\frac{1}{RC} \right) = 5.2362$$

$$C = 1 \mu F$$

$$R = 191 k\Omega$$

$$3 - k = 2 \cos(83.19^\circ)$$

$$k = 2.763$$

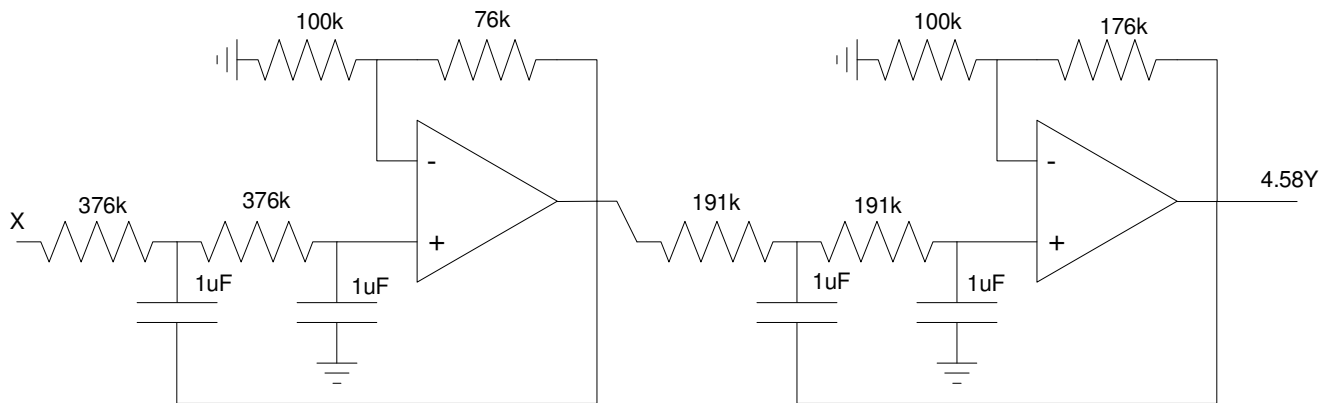

Note: The DC gain of this filter is 4.58.

- Reduce the gain (add a voltage divider) to make the DC gain match, or
- Label the output as 4.58Y

The latter is better: you're probably going to add gain somewhere. This filter provides a DC gain of 4.58. The rest of the circuit adds the rest.

6) Check your filter using CircuitLab

