

# ECE 321 - Homework #4

Butterworth & Chebychev filters, Analog Computers. Due Monday, April 27th

Please make the subject "ECE 321 HW#4" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## Butterworth and Chebychev Filters

1) Design a filter,  $G(s)$ , to meet the following specifications:

Input:

- 20 - 1 kHz audio signal
- 10Vpp, capable of driving 10mA @ 5V

Output:

- 20 - 1 kHz audio signal
- Capable of driving 10mA @ 5V

Relationship:

- $0.9 < \text{Gain} < 1.1$        $0 < \omega < 250 \text{ Hz}$
- $\text{Gain} < 0.1$        $\omega > 400 \text{ Hz}$

First, determine the number of poles you need:

$$\left(\frac{250\text{Hz}}{400\text{Hz}}\right)^2 < 0.1$$

$$n > 4.899$$

Let  $n = 5$  (kind of pushing it)

Assume a Chebychev filter. Pick the corner to be 250Hz (500 pi rad/sec). For a corner at 1 rad/sec

$$G(s) = \left( \frac{k}{(s+0.48)(s+0.76\angle\pm 59.3^\circ)(s+1.06\angle\pm 82.0^\circ)} \right):$$


For a corner at 500 pi

$$G(s) = \left( \frac{k}{(s+754)(s+1194\angle\pm 59.3^\circ)(s+1665\angle\pm 82.0^\circ)} \right)$$

Pick  $k$  to make the gain at DC equal to 1.000. Checking this filter in Matlab

```
f = [0:5:1000]';
w = 2*pi*f;
s = j*w;
p1 = 754;
p2 = 1194*exp(j*59.3*pi/180);
p3 = conj(p2);
p4 = 1665*exp(j*82*pi/180);
p5 = conj(p4);
num = abs(p1*p2*p3*p4*p5);
Gs = num ./ ( (s+p1).*(s+p2).*(s+p3).*(s+p4).*(s+p5) );
plot(f,abs(Gs),[250,400],[0.9,0.1],'x');
xlabel('frequency (Hz)');
ylabel('Gain');
```

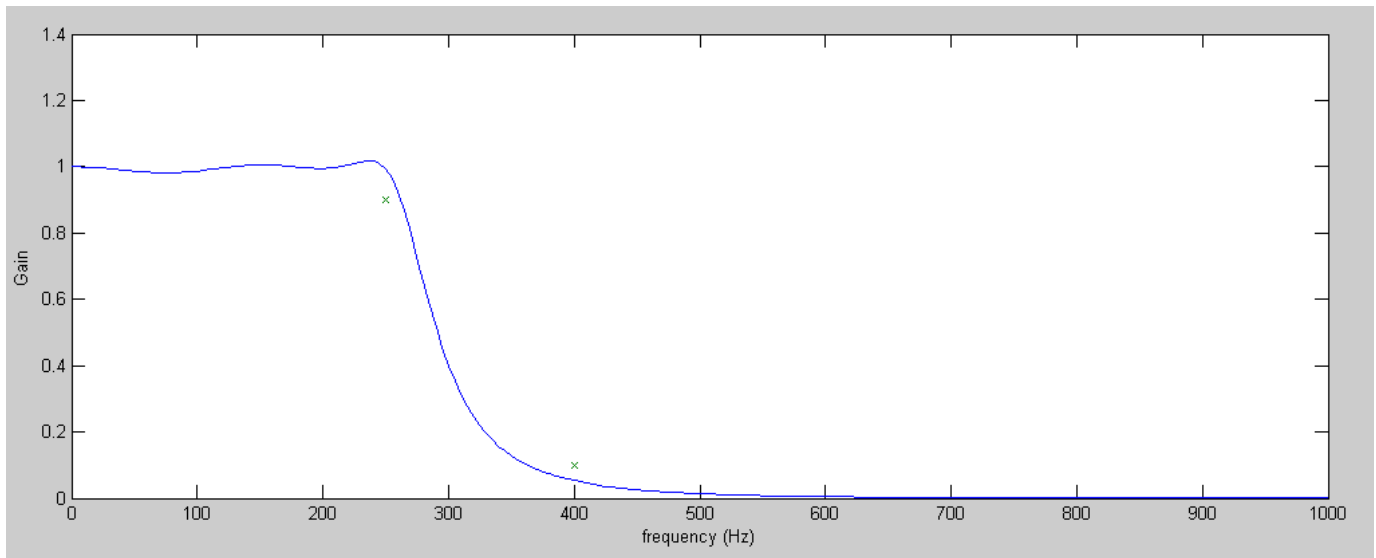Plot your filter's gain vs. frequency using Matlab (or similar program)



Kind of got lucky: this meets the specs with the first guess.

So...

$$G(s) = \left( \frac{k}{(s+754)(s+1194\angle\pm 59.3^\circ)(s+1665\angle\pm 82.0^\circ)} \right)$$

2) Design an op-amp circuit to implement your filter from problem #1

$$G(s) = \left( \frac{k}{(s+754)(s+1194\angle\pm 59.3^\circ)(s+1665\angle\pm 82.0^\circ)} \right)$$

Assume 10k - 100k - 100k resistors.

Stage 1: RC filter

$$\text{Pole} = 754$$

$$\left( \frac{1}{RC} \right) = 754$$

$$R = 10k$$

$$C = 132nF$$

Stage 2: Poles =  $1194\angle\pm 59.3^\circ$

$$\left( \frac{1}{RC} \right) = 1194$$

$$R = 100k$$

$$C = 8.37nF$$

$$3 - k = 2 \cos(59.3^\circ)$$

$$k = 1.98$$

$$R1 = 100k, R2 = 98k$$

Stage 3: Poles =  $1665\angle\pm 82.0^\circ$

$$\left( \frac{1}{RC} \right) = 1665$$

$$R = 100k$$

$$C = 6.01nF$$

$$3 - k = 2 \cos(82^\circ)$$



172.6k

$$k = 2.7216$$

$$R1 = 100k, R2 = 172.16k$$
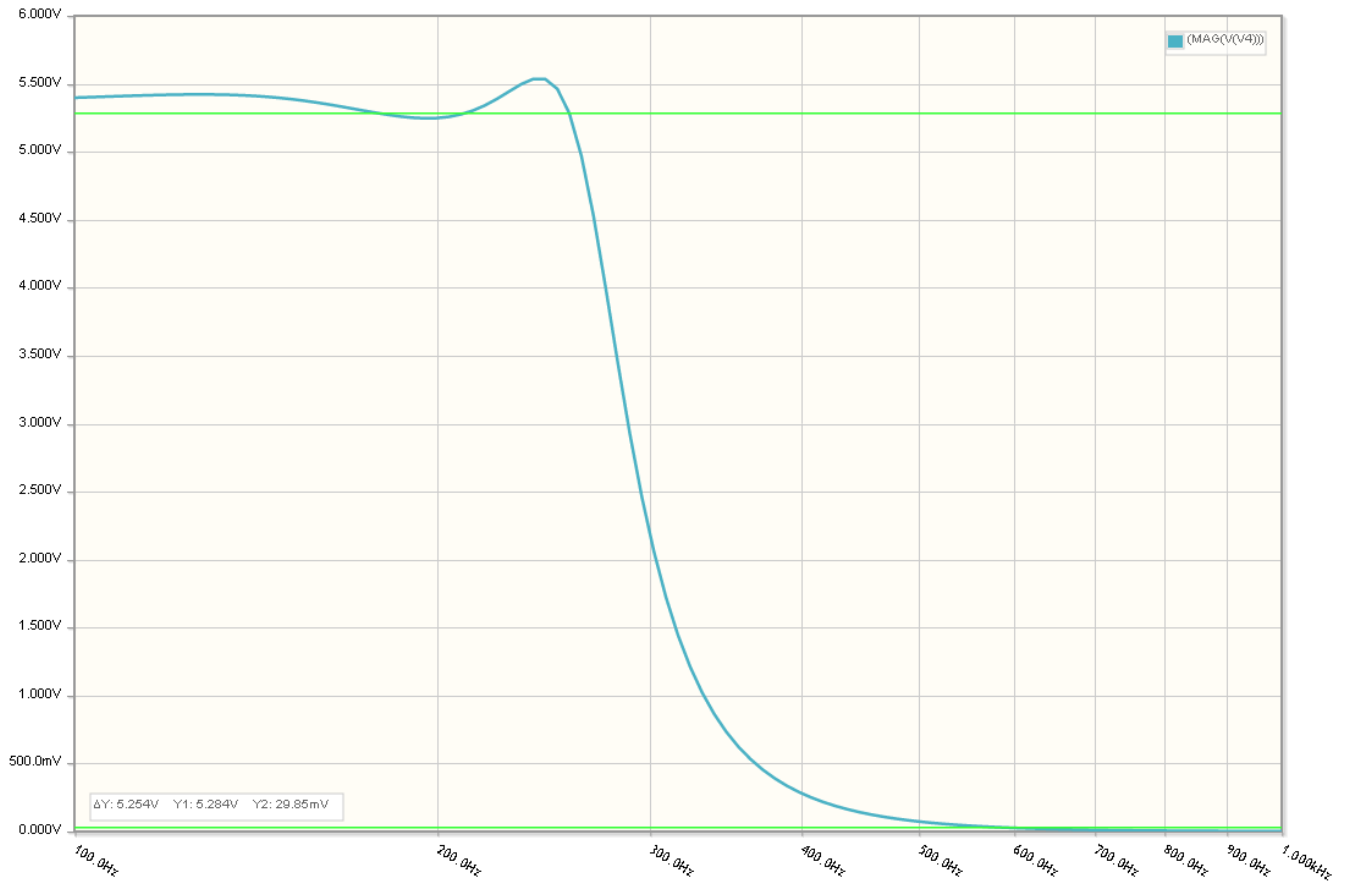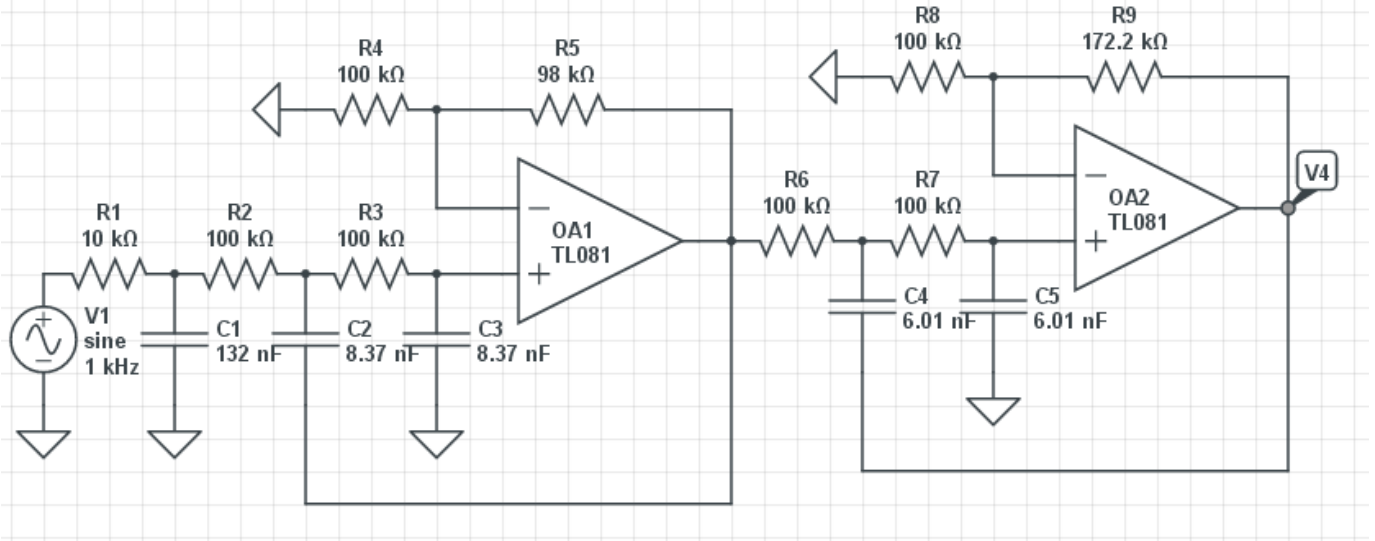
### 3) Verify your design in CircuitLab

- Check the gain at the design points ( 250Hz and 400Hz )
- Check the gain at two other points ( 100Hz and 1000Hz)



## Analog Computers


4) Design an analog computer to implement

$$Y = \left( \frac{10(s^2+9)}{(s+2)(s^2+2s+4)} \right) X$$


Multiply out

$$Y = \left( \frac{10s^2+90}{s^3+4s^2+8s+8} \right) X$$

Using analog computer notation

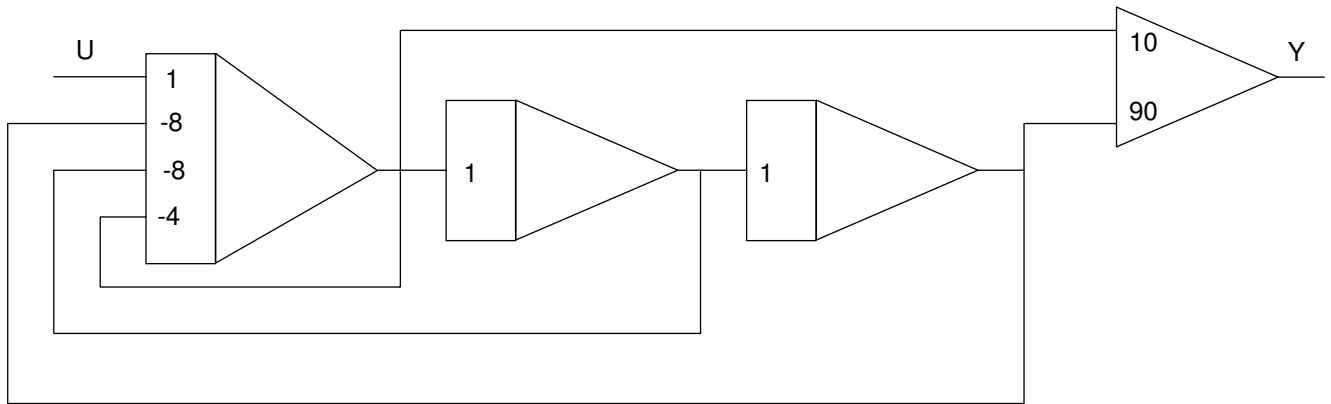

Make all gains negative

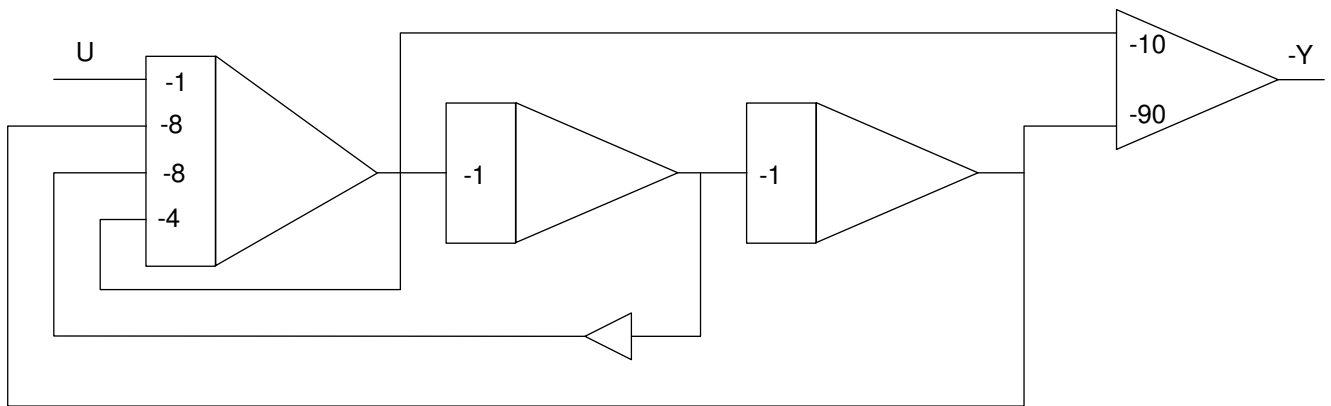

Replace with an op-amp circuit

