


# ECE 321 - Final Exam - Name \_\_\_\_\_

Spring 2022

**1. OpAmp Circuits:** Determine y as a function of A, B, C, and D. Assume

- Ideal op-amps
- $R = 900 + 100 * (\text{your birth month}) + (\text{your birth day})$ .

$R$ $900 + 100 * \text{mo} + \text{day}$	$Y = aA + bB + cC + dD$
<b>1414</b>	

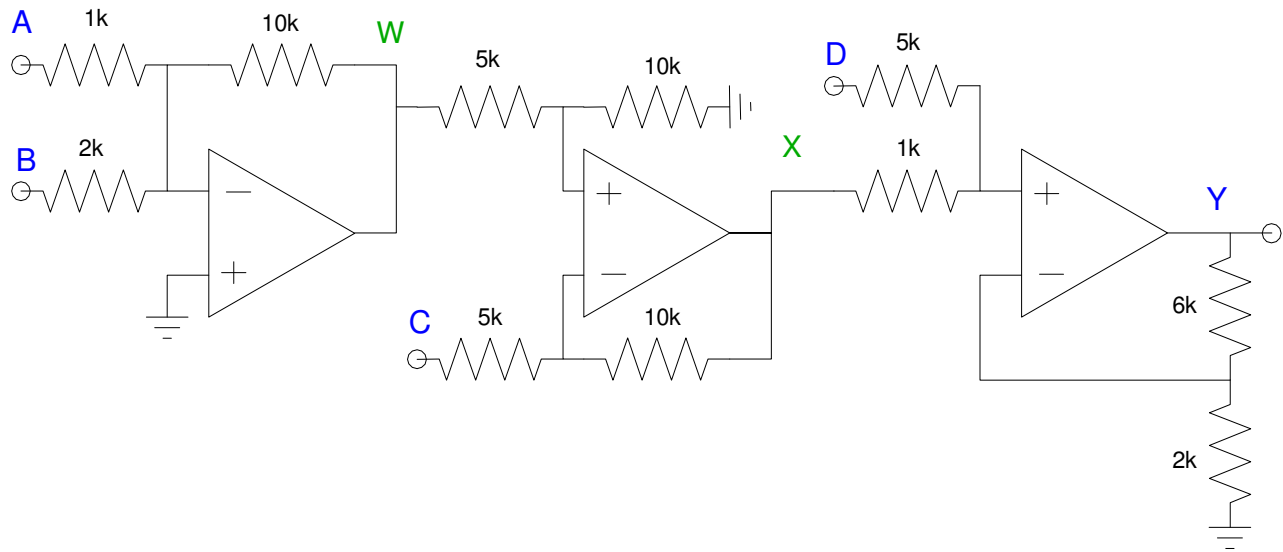

$$W = -10A - 5B$$

$$X = 2(W - C)$$

$$Y = 5 \left( \frac{5X + D}{6} \right)$$


net

$$Y = \left( \frac{5}{6} \right) D - \left( \frac{50}{6} \right) C - \left( \frac{100}{6} \right) A - \left( \frac{50}{6} \right) B$$

**2. Push-Pull:** Determine the voltages and currents for the following push-pull amplifier. Assume

- $R = 1100 + 100 * (\text{birth month}) + (\text{birth day})$ .
- $|V_{ce}| = 0.7V$  (ideal silicon diodes)
- $\beta = 30$

R	V1	V2	V3	I4	I5
900 + 100*mo + day					
<b>1414</b>	<b>4V</b>	<b>8.242V</b>	<b>7.542V</b>	<b>30.4mA</b>	<b>943mA</b>

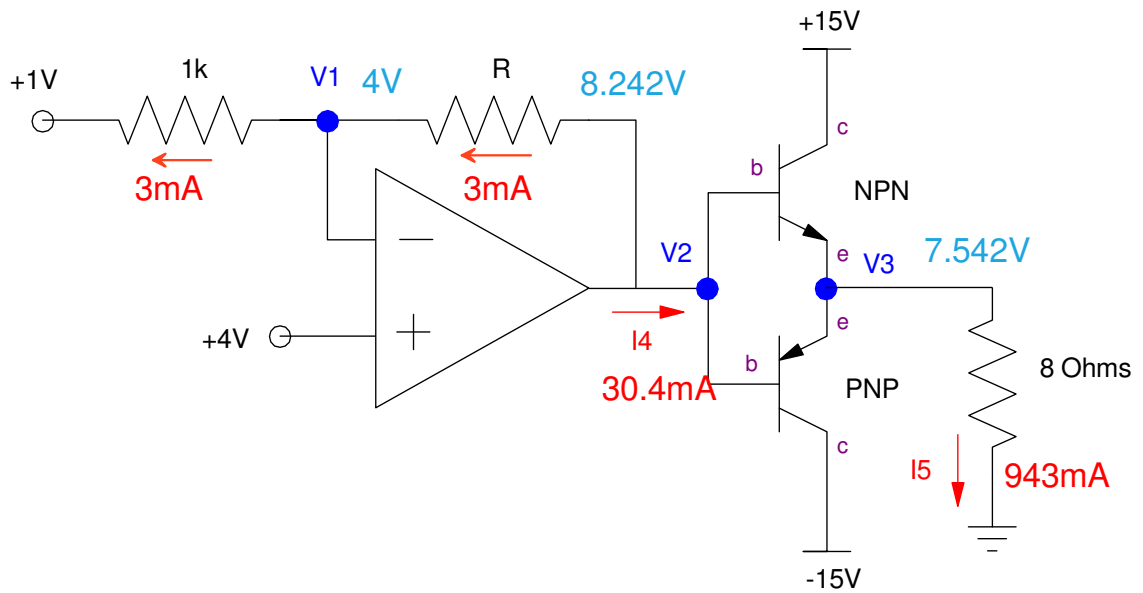

**3. Instrumentation Amplifier:** Assume an RTD has the temperature - resistance relationship of


$$R_t = 2000 \cdot (1 + 0.0043T)\Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- +15V at +150C, and
- -5V at -50C

Assume

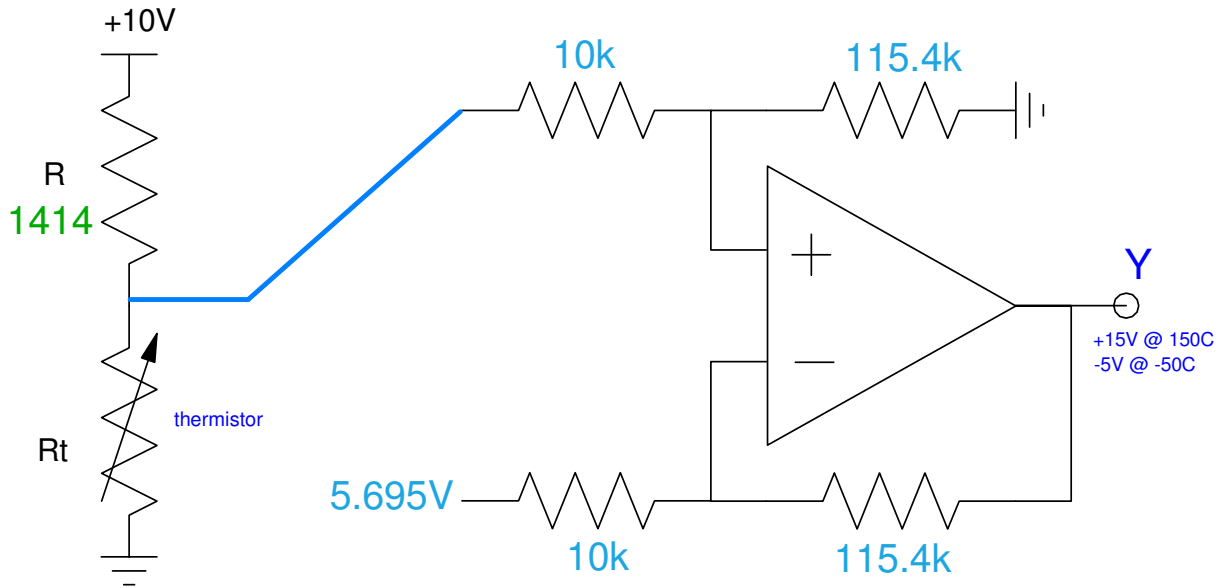- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$



-50C

- $R_t = 1570 \text{ Ohms}$
- $V_x = 5.261V$
- $V_y = -5V$

+150C

- $R_t = 3290 \text{ Ohms}$
- $V_x = 6.994V$
- $V_y = +10V$

Y goes up as X goes up. Connect to the + input

The gain needed is

$$gain = \left( \frac{+15V - (-5V)}{6.994V - 5.261V} \right) = 11.54$$

The offset needed comes from

$$Y = +15V = 11.543(6.994V - B)$$


$$B = 5.695V$$

#### 4. Filters: Let

- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$ . May 14th would give  $R = 1614$  Ohms

Find the transfer function from X to Y

R $900 + 100 \cdot \text{mo} + \text{day}$	Transfer Function $Y = G(s) \cdot X$
<b>1414</b>	

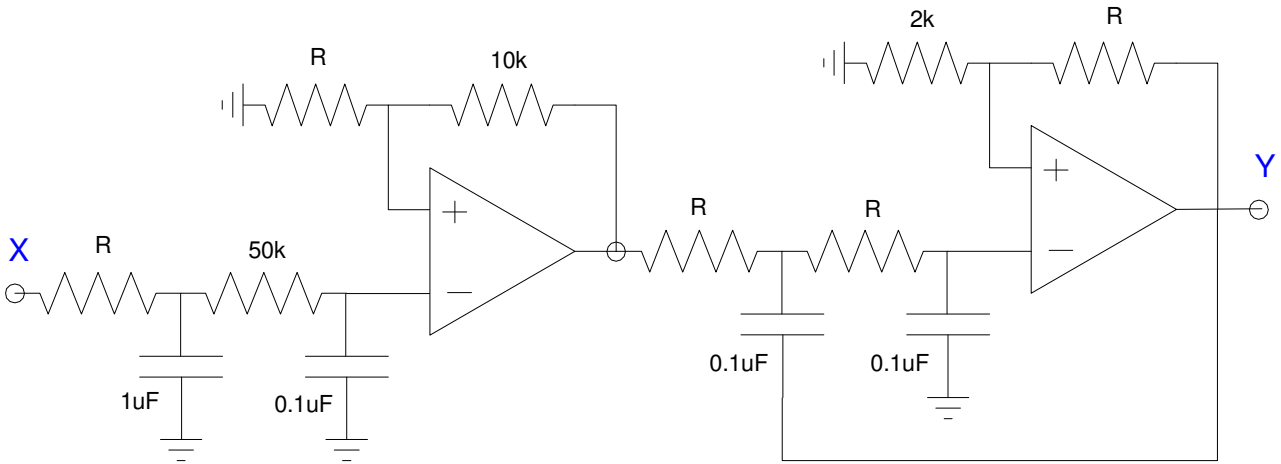

Stage 1: Low-pass filter with real poles

$$p_1 = \left( \frac{1}{R \cdot 1\mu F} \right) = 707.2$$

$$p_2 = \left( \frac{1}{50k \cdot 0.1\mu F} \right) = 200$$

$$k = 1 + \left( \frac{10k}{R} \right) = 8.072$$

$$G_1 = \left( \frac{707.2}{s+707.2} \right) \left( \frac{200}{s+200} \right) (8.072)$$

Stage 2: Low-pass filter with complex poles

$$p = \left( \frac{1}{R \cdot 0.1\mu F} \right) = 7072$$

$$k = 1 + \frac{R}{2k} = 1.707$$

$$3 - k = 2 \cos \theta$$

$$\theta = 49.7^\circ$$

$$G_2 = \left( \frac{1.707 \cdot 7072^2}{s+7072 \angle \pm 49.7^\circ} \right)$$

The total transfer function is then  $G_1 \cdot G_2$



**5. CE Amplifiers (DC design):** Determine R1 and R2 so that

- The Q-point is stabilized for variations in  $\beta$ , and
- $V_{ce} = 3.0V$

Assume

- $R_e = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- $\beta = 30$
- $|V_{be}| = 0.7V$  (ideal silicon diode)

$R_e$ 900 + 100*mo + day	R1	R2	$V_b$	$I_c$
<b>1414</b>	<b>5119</b>	<b>18.30k</b>	<b>2.623V</b>	<b>1.206mA</b>

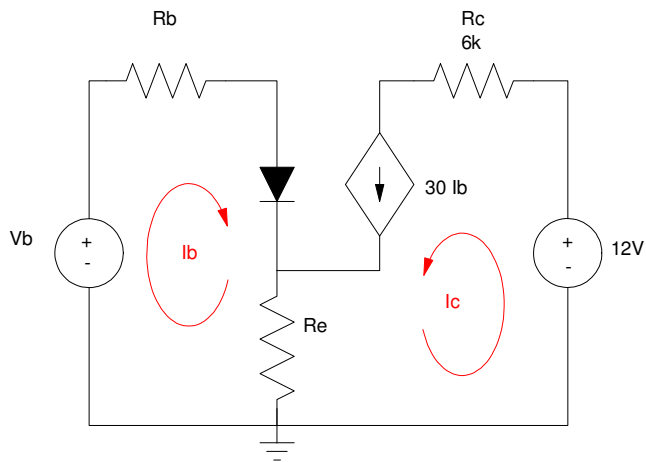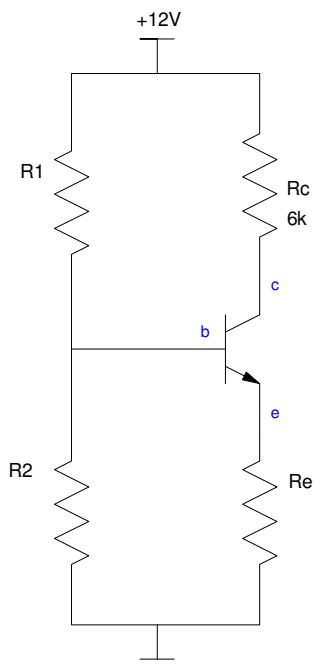

$$I_c = \left( \frac{9V}{6000 + R_e + \frac{1}{30}R_e} \right) = 1.206mA$$

$$I_b = \left( \frac{1}{30} \right) I_c = 40.21\mu A$$

To stabilize the Q-point

$$R_b \ll (1 + \beta)R_e = 43.83k$$

Let  $R_b = 4k$

$$V_b = R_e(I_b + I_c) + 0.7 + R_b I_b = 2.623V$$



$$R_1 = \left( \frac{12V}{2.623V} \right) 4k = 18.30k$$

$$R_2 = 5119\Omega$$

**6. 2-Port model:** Determine the 2-port parameters for the following circuit. Assume

- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$  Ohms

R	R <sub>in</sub>	A <sub>i</sub>	R <sub>out</sub>	A <sub>o</sub>
900 + 100*mo + day				
<b>1414</b>	<b>2586</b>	<b>0.5857</b>	<b>57.84</b>	<b>0.4062</b>

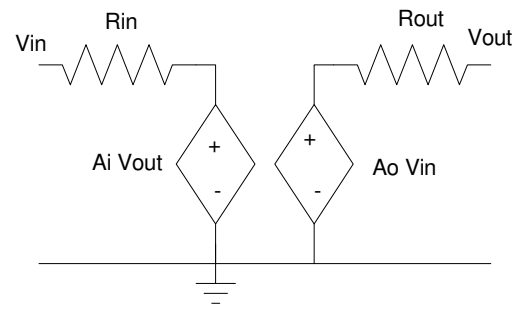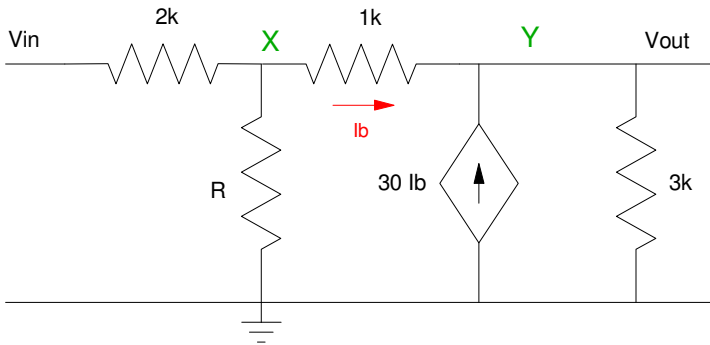

R<sub>in</sub>: Short V<sub>out</sub>

$$R_{in} = 2k + R \parallel 1k = 2586\Omega$$

A<sub>i</sub>: Apply 1V to V<sub>out</sub>, find V<sub>in</sub>

$$A_i = \left( \frac{1414}{1414+1000} \right) = 0.5857$$

R<sub>out</sub>: Short V<sub>in</sub>, Apply 1V to V<sub>out</sub> and find the current

$$\left( \frac{X}{2k} \right) + \left( \frac{X}{R} \right) + \left( \frac{X-1}{1k} \right) = 0$$

$$X = 0.4531V$$

$$I = \left( \frac{1V}{3k\Omega} \right) + \left( \frac{1V-0.4531V}{1k} \right) + 30 \left( \frac{1-0.4531}{1k} \right) = 17.29mA$$

$$R_{out} = \frac{1V}{17.29mA} = 57.84\Omega$$

A<sub>o</sub>: Apply 1V to V<sub>in</sub>, find V<sub>out</sub>

$$\left( \frac{X-1}{2k} \right) + \left( \frac{X}{R} \right) + \left( \frac{X-Y}{1k} \right) = 0$$

$$\left( \frac{Y-X}{1k} \right) + 30 \left( \frac{Y-X}{1k} \right) + \left( \frac{Y}{3k} \right) = 0$$

Solving 2 equations for 2 unknowns

$$X = 0.4106$$

$$Y = 0.4062 = A_o$$

**7. 2-Port model (experimental):** Determine the 2-port parameters for an unknown circuit (shown in blue) given the following experimental data:

Case 1:

- $V_{in} = 1\text{mV @ } 1\text{kHz}$
- $R_a = 0 \text{ Ohms}$
- $R_b = \text{infinity (open)}$
- $V_{out} = 96\text{mV @ } 1\text{kHz}$

Case 2:

- $V_{in} = 1\text{mV @ } 1\text{kHz}$
- $R_a = R \text{ Ohms}$
- $R_b = \text{infinity (open)}$
- $V_{out} = 63\text{mV @ } 1\text{kHz}$


Case 3:

- $V_{in} = 1\text{mV @ } 1\text{kHz}$
- $R_a = 0 \text{ Ohms}$
- $R_b = R \text{ Ohms}$
- $V_{out} = 28\text{mV @ } 1\text{kHz}$

Assume

- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date}) \text{ Ohms}$
- $A_i = 0$

R 900 + 100*mo + day	R <sub>in</sub>	A <sub>i</sub>	R <sub>out</sub>	A <sub>o</sub>
<b>1414</b>	<b>2699</b>	<b>0</b>	<b>3434</b>	<b>96</b>

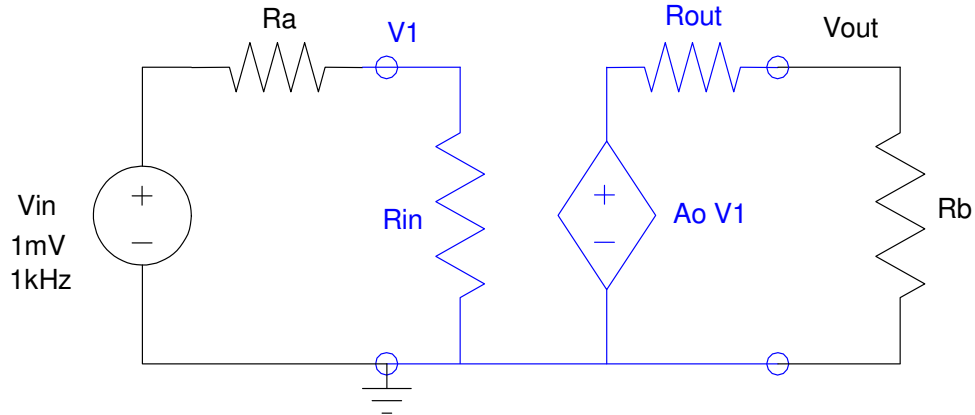

Ao: Case 1:

$$A_o = \left( \frac{96\text{mV}}{1\text{mV}} \right) = 96$$

Rin: Case 2

$$R_{in} = \left( \frac{63\text{mV}}{96\text{mV} - 63\text{mV}} \right) 1414\Omega = 2699\Omega$$

Rout: Case 3

$$R_{out} = \left( \frac{96\text{mV} - 28\text{mV}}{28\text{mV}} \right) 1414\Omega = 3434\Omega$$