

# ECE 321 - Quiz #2 - Name \_\_\_\_\_

## Temperature Sensors & Active Filters

1) A thermistor has a temperature-resistance relationship where T is the temperature in degrees C.

$$R_t = 2000 \cdot \exp\left(\frac{3000}{T+273} - \frac{3000}{298}\right) \Omega$$

Assume

$$R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$$


If X = 4.00V, determine the resistance, R, and the temperature, T

R 800 + 100*mo + day	X volts	R <sub>t</sub> Ohms	T degrees C
<b>1314</b>	<b>6.73V</b>	<b>2704.35</b>	<b>16.33C</b>

$$X = \left(\frac{R_t}{R_t + 1314}\right) 10V$$

$$R_t = \left(\frac{X}{10-X}\right) \cdot 1314\Omega = 2704.349\Omega$$

$$T = 16.329^{\circ}C$$

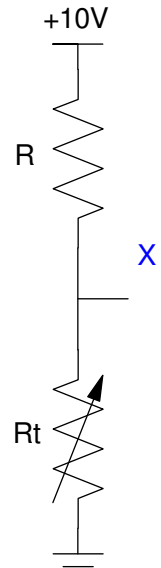

2) A thermistor has a temperature-resistance relationship where T is the temperature in degrees C.

$$R_t = 2000 \cdot \exp\left(\frac{3000}{T+273} - \frac{3000}{298}\right) \Omega$$


Design a circuit which outputs

- 0V at 0C and
- +10V at +40C

Assume

$$R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$$

note: A linearizing circuit isn't required.

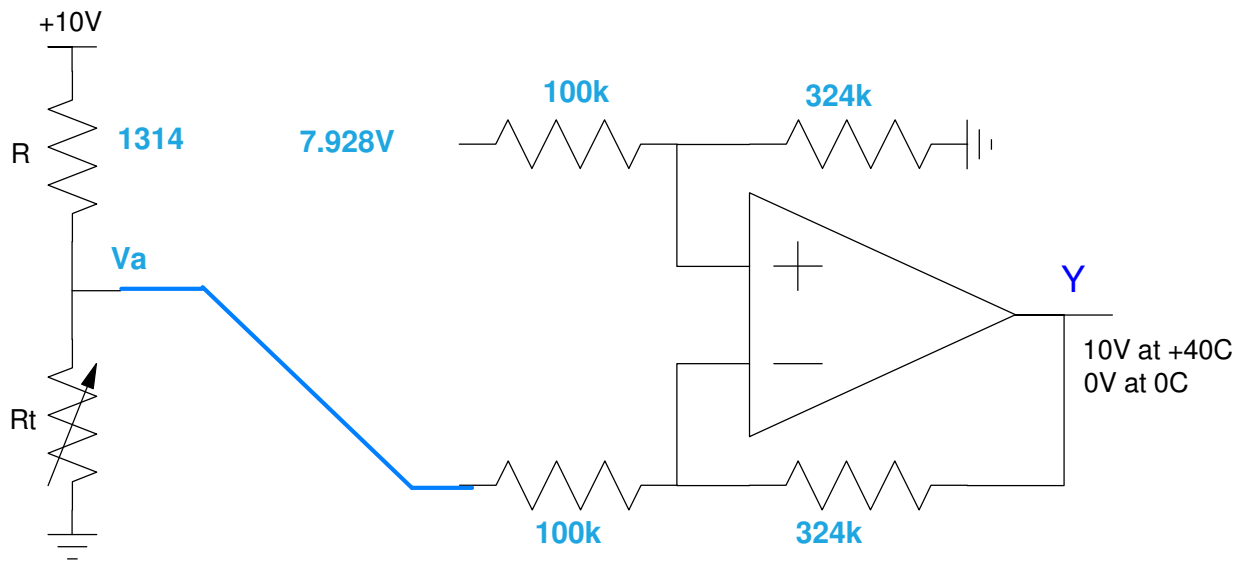

At 0C:  $Y = 0V$

$$R = 5028.11 \text{ Ohms}$$

$$V_a = \left(\frac{R}{R+1314}\right) 10V = 7.928V$$

At +40C,  $Y = 10V$

$$R = 1234.539 \text{ Ohms}$$

$$V_a = 4.844V$$

As  $V_a$  goes down,  $Y$  goes up. Connect to the plus input

When  $V_a = 7.92V$ ,  $Y = 0V$ . Make the offset 7.92V


$$gain = \left(\frac{10V-0V}{7.928V-4.844V}\right) = 3.243$$

3) Find C1, C2, C3, and R4 so that this circuit implements

$$Y = \left( \frac{10000}{(s+3)(s+m)(s+d)} \right) X$$

where

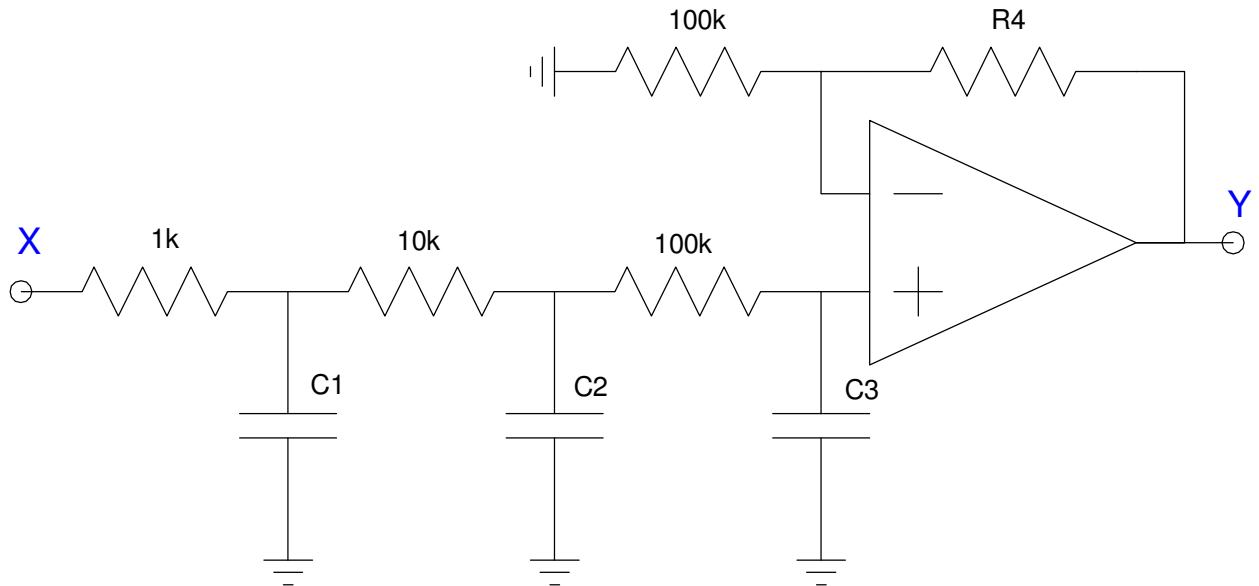- m is your birth month (1..12) and
- d is your birth date (1..31)



m month	d day	C1 uF	C2 uF	C3 uF	R4 Ohms
<b>5</b>	<b>14</b>	333.3uF	20.0uF	714nF	4.662M

DC gain is


$$\left( \frac{10000}{(s+3)(s+5)(s+14)} \right)_{s=0} = 47.62$$

4) Find R's and C's so that the following circuit implements

$$Y = \left( \frac{10,000}{(s+3)(s+m+jd)(s+m-jd)} \right)$$

where

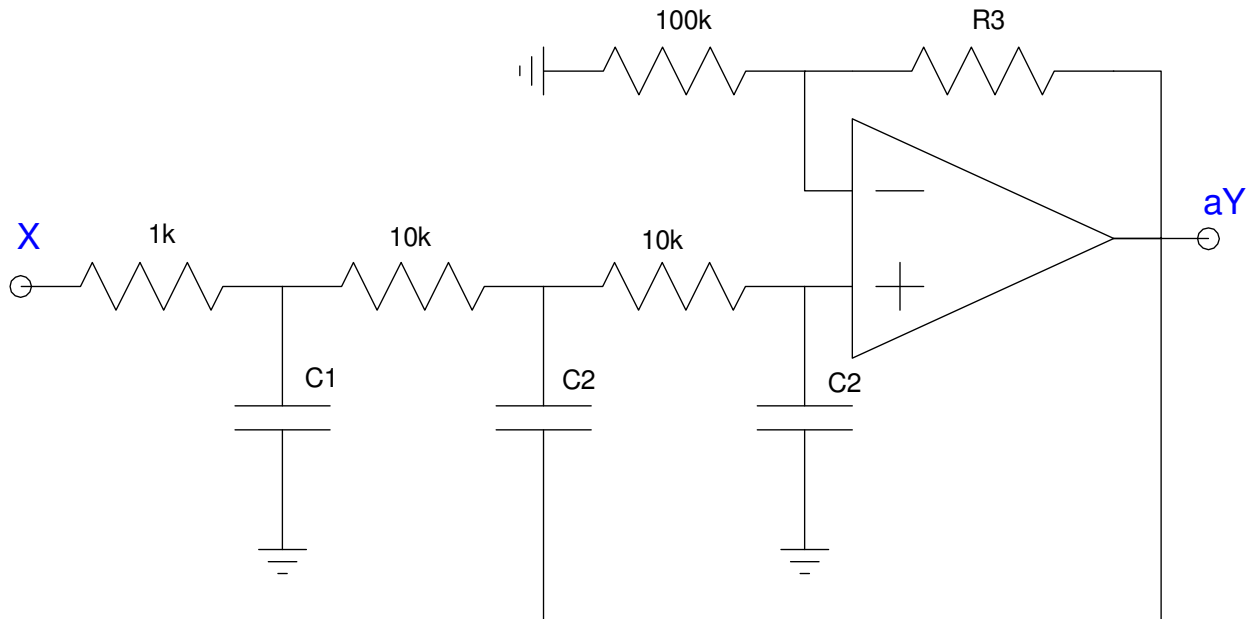- m is your birth month (1..12), and
- d is your birth date (1..31)



m month	d day	C1 uF	C2 uF	R3 k Ohms	a output is a*Y
<b>5</b>	<b>14</b>	<b>333uF</b>	<b>6.72uF</b>	<b>132.7k</b>	<b>0.15</b>

The pole is

$$s = -5 + j14 = -14.87 \angle 70.35^\circ$$

$$3 - k = 2 \cos \theta$$

$$k = 2.327$$

The DC gain should be

$$\left( \frac{10,000}{(s+3)(s+5+j14)(s+5-j14)} \right)_{s=0} = 15.08$$

so the output is scaled by

$$a = \frac{2.327}{15.08} = 0.154$$

5) Let X and Y be related by the following transfer function:

$$Y = \left( \frac{10000}{(s+3)(s+m)(s+d)} \right) X$$

where

- m is your birth month (1..12), and
- d is your birth date (1..31)

Assume

$$x(t) = 5 + 6 \cos(2t) + 7 \sin(2t)$$

Determine y(t) (i.e. find a, b, and c)

$$y(t) = a + b \cos(2t) + c \sin(2t)$$

DC:  $x(t) = 5$

$$Y = \left( \frac{10000}{(s+3)(s+5)(s+14)} \right)_{s=0} \cdot (5)$$

$$Y = 238.1$$

AC:  $x(t) = 6 \cos(2t) + 7 \sin(2t)$

$$Y = \left( \frac{10000}{(s+3)(s+5)(s+14)} \right)_{s=j2} \cdot (6 - j7)$$


$$Y = -131.4 - j309.01$$

$$y(t) = -131.4 \cos(2t) + 309.4 \sin(2t)$$

The total answer is DC + AC

$$y(t) = 238.1 - 131.4 \cos(2t) + 309.4 \sin(2t)$$

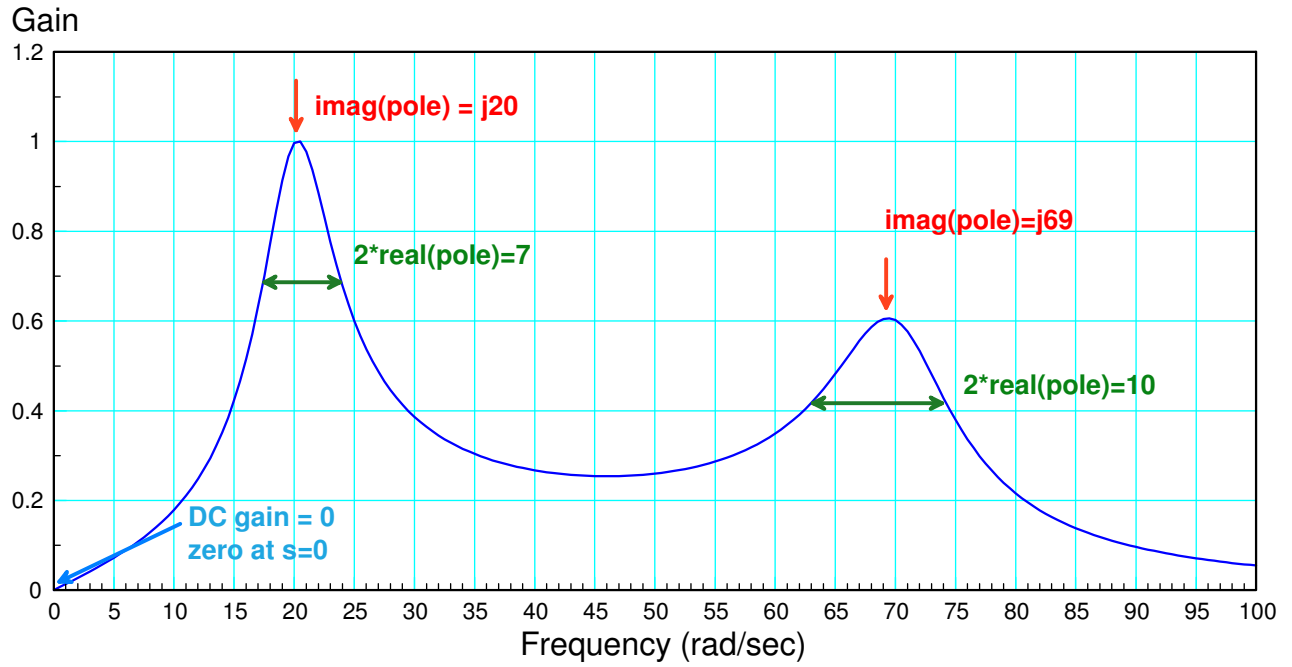6) Determine a filter,  $G(s)$ , with the following gain vs. frequency



$$G(s) \approx \left( \frac{ks}{(s+3.5+j20)(s+3.5-j20)(s+5+j69)(s+5-j69)} \right)$$