


# ECE 331 - Final Exam: Name \_\_\_\_\_

Closed Book. Closed Notes. Calculators permitted

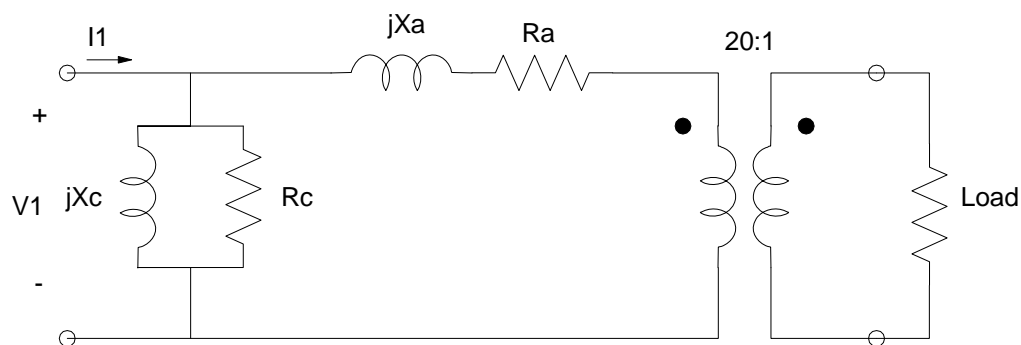
1) Transformers: Determine the parameters for a transformer with the following test data:

Open Circuit Test (Load = infinite):  $V_1 = 120V$ , 60Hz.  $I_1 = 2.4A$ ,  $pf = 0.3$  lagging

Short Circuit Test: (Load = 0 ohms):  $V_1 = 10V$ , 60Hz.  $I_1 = 3.8A$ ,  $pf = 0.9$  lagging.



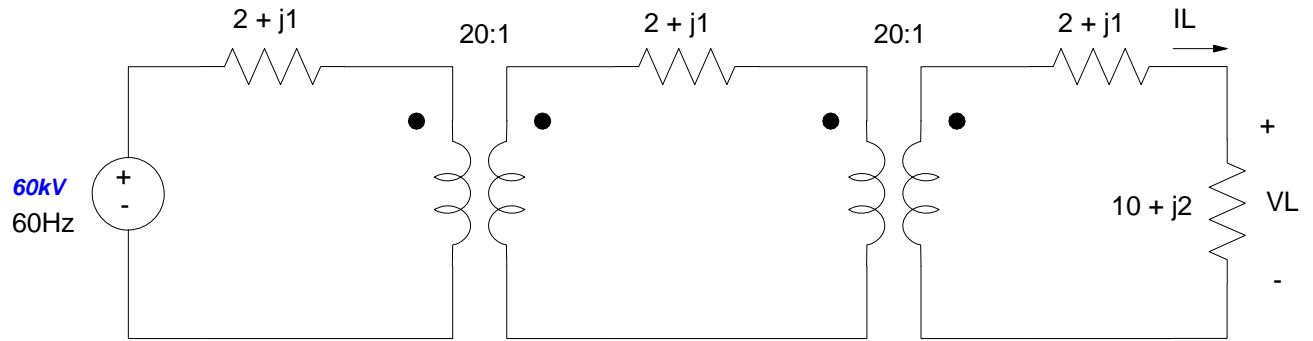2) Transformers. Two 20:1 step down transformers deliver 60kV to a customer as shown below. Determine the voltage, current, and power delivered to the load:




$V_L$	
$I_L$	
Power to the load	

3) AC Asynchronous Motors: Determine an electrical model for a 3-phase AC induction motor with the following measurements. All voltages are line-to-neutral

DC Test:  $V_a = 4V$ ,  $I_a = 1A$

Locked Rotor Test ( $s=1$ ):  $V_a = 60V$ ,  $I_a = 9A$ ,  $pf = 0.7$  lagging

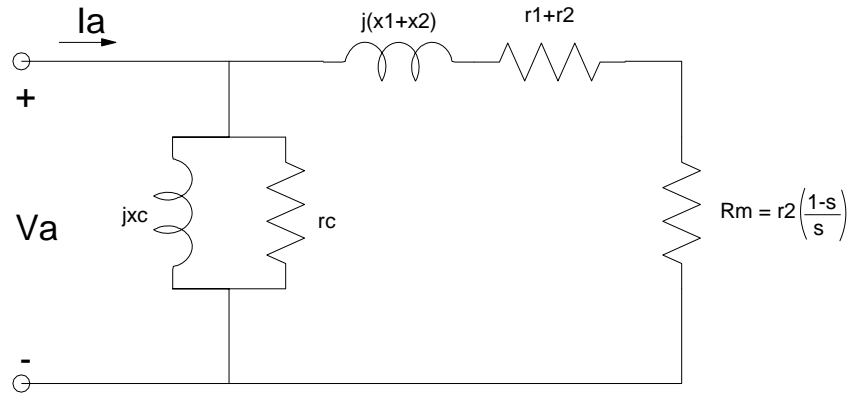
No-Load Test ( $s=0$ ):  $V_a = 200V$ ,  $I_a = 0.6A$ ,  $pf = 0.15$  lagging



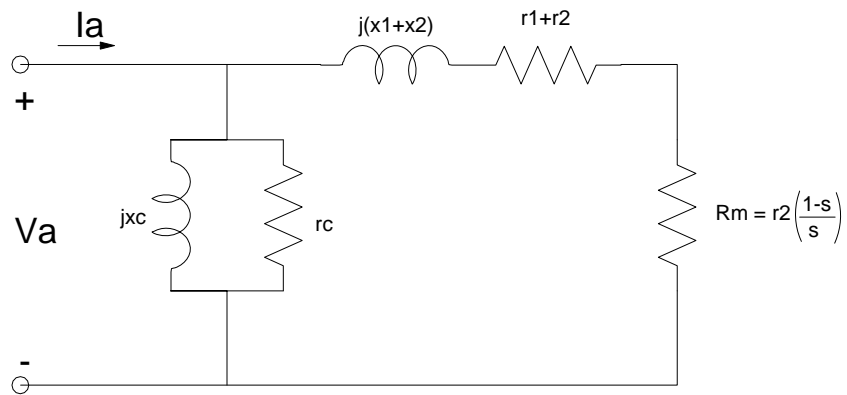4) 3 phase AC Induction Motor: Assume a 3-phase AC induction motor has the following parameters:

$$r_1 = 0.7 \text{ Ohms}, \quad jx_1 = j2.0 \text{ Ohms} \quad r_2 = 1.8 \text{ Ohms} \quad jx_2 = j2.8 \text{ Ohms}$$

$$r_c = 200 \text{ Ohms} \quad jx_c = j90 \text{ Ohms} \quad \text{slip} = 0.02$$




2a) Determine the electrical power in and the power factor assuming  $V_a = 120\text{VAC}$ .

2b) Determine the mechanical power out (power to  $R_m$ )

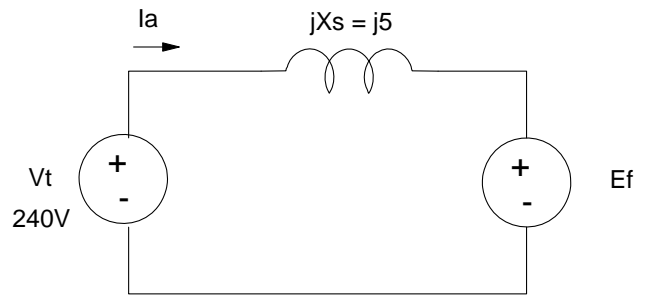5) AC Synchronous Motor: Assume a 3-phase AC synchronous motor with the following specifications:

- 3 phase
- 2 pole
- 60Hz
- $V_t = 300\text{V}$  line to neutral
- $X_s = 5$  Ohms
- $E_a = 350\text{V}$ .
- Load = 8kW



Find the slip angle, the input current,  $I_a$ , and the power factor:


Slip Angle ( $\delta$ )	
$I_a$ (Amps)	
Power Factor	

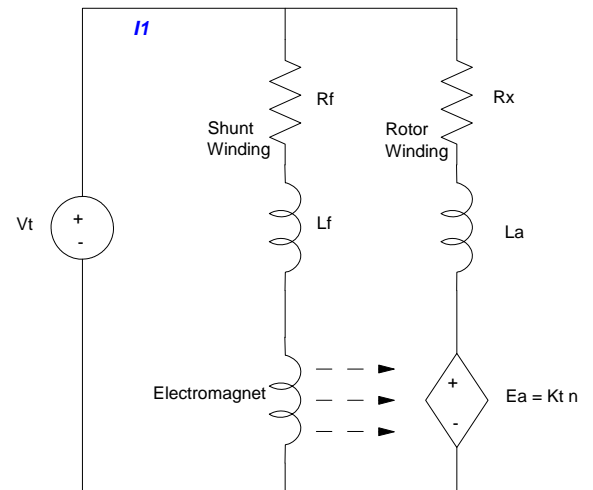6) DC Motor. Assume a DC shunt motor with  $R_f = 200$  Ohms,  $R_x = 1.5$  Ohms,  $V_t = 120$ V.

At no load,  $I_f = 1.00$ A and the motor spins at 1500 rpm.






Determine the following when the load is increased to  $T = 15$ Nm:

Torque Constant, $K_t$	
$I_f$	
Back EMF: $E_a$	
Speed (rad/sec)	
Power Out	
Efficiency	



# Godzilla Monster Bonus: Match the names with the following faces:

*Braaten, Gigan, Ghidorah, Hedorah, Megalon, Rodan*

--	--	--