

ECE 331 - Solution to Homework #8

DC Shunt Excited Motors:

1) Assume a DC motor with $V_t = 120\text{VDC}$, $R_f = 150\ \Omega$, $R_x = 3\ \Omega$, $N_f = 30$, $N_a = 30$, and a reluctance of 1000. Plot the speed vs. load torque relationship.

First, compute the torque constant:

$$I_f = \frac{120\text{V}}{150\ \Omega} = 0.8\text{A}$$

$$\Phi_P = \frac{N_f I_f}{\text{Rel}} = \frac{(30)(0.8)}{1000} = 0.024\text{Wb}$$

$$K_t = \frac{2N_a \Phi_P}{\pi} = 0.4584 \frac{\text{V}}{\text{rad/sec}}$$

The speed vs. load relationship is then...


$$E_a = K_t \omega$$


$$I_a = \frac{120\text{V} - E_a}{R_x}$$

$$T = K_t I_a$$

```
Vt = 120;
Rf = 150;
Rx = 3;
Kt = 0.4584;
Wmax = Vt / Kt;
```
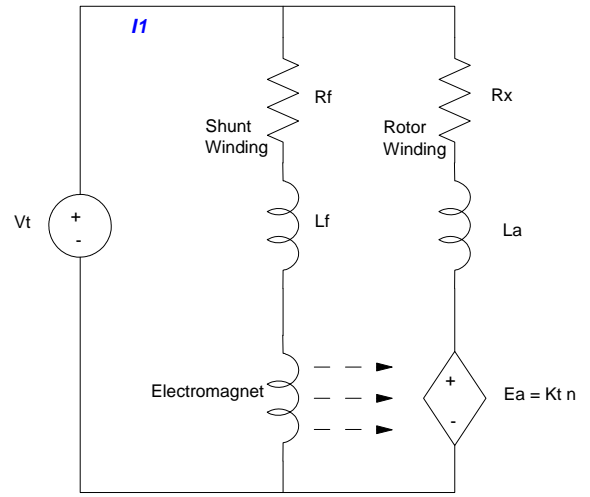
```
w = [0:0.01:1]' * Wmax;
Ea = Kt*w;
Ia = (Vt - Ea) / Rx;
T = Kt*Ia;
plot(w,T);
xlabel('Speed (rad/sec)');
ylabel('Torque');
xgrid(3)
```




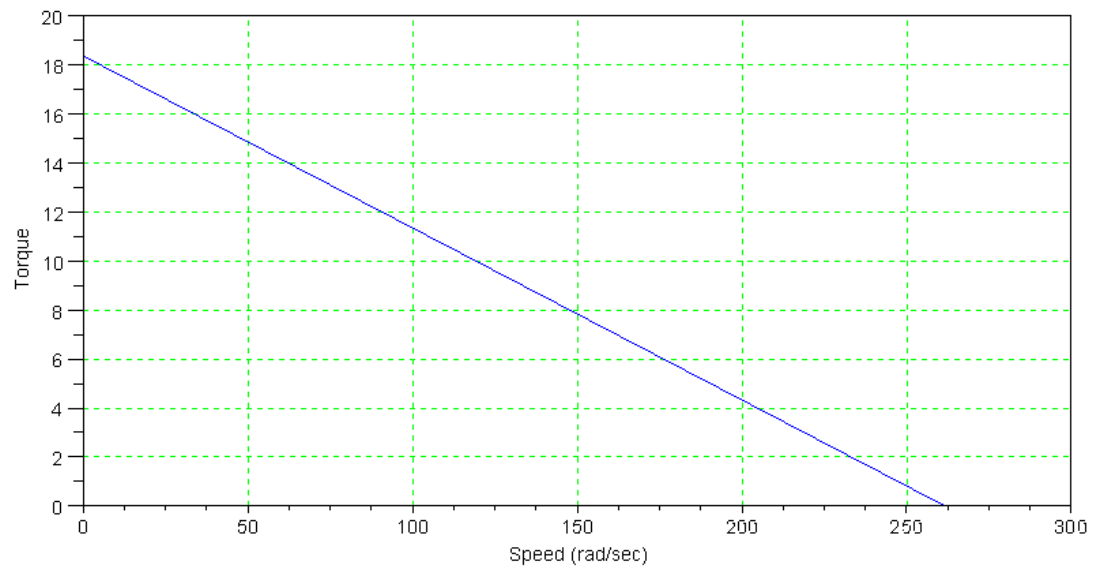

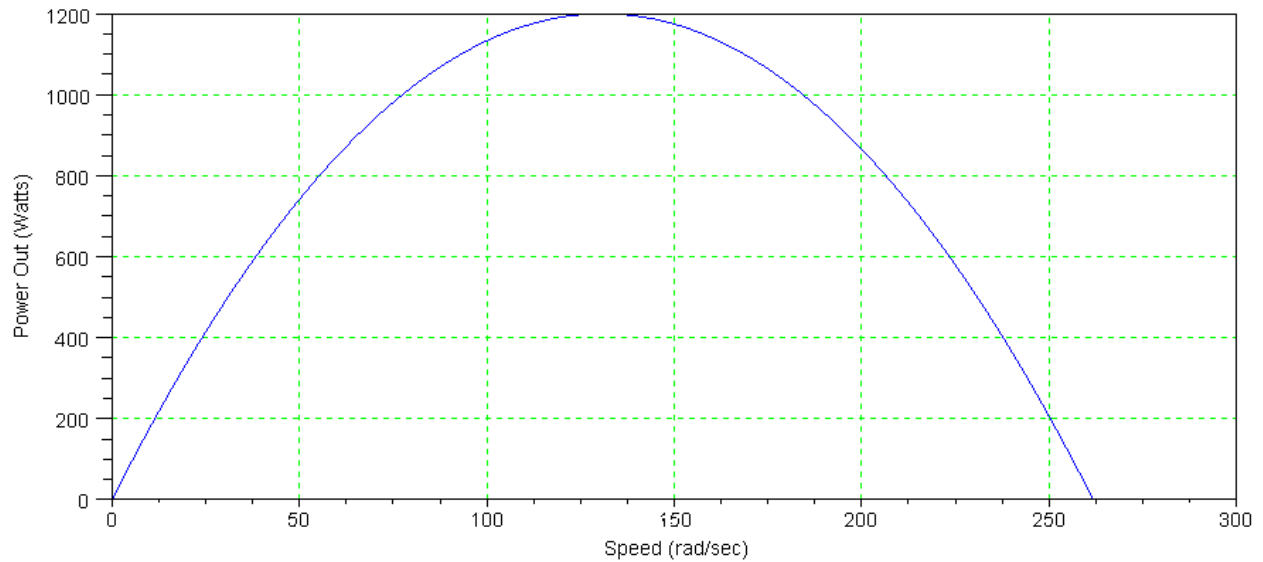
2) For the motor in problem #1, plot

- Speed vs. power out
- Speed vs. efficiency

```
-->Po = Ea .* Ia;  
-->plot(w,Po);  
-->xlabel('Speed (rad/sec)')  
-->ylabel('Power Out (Watts)')  
-->xgrid(3)
```



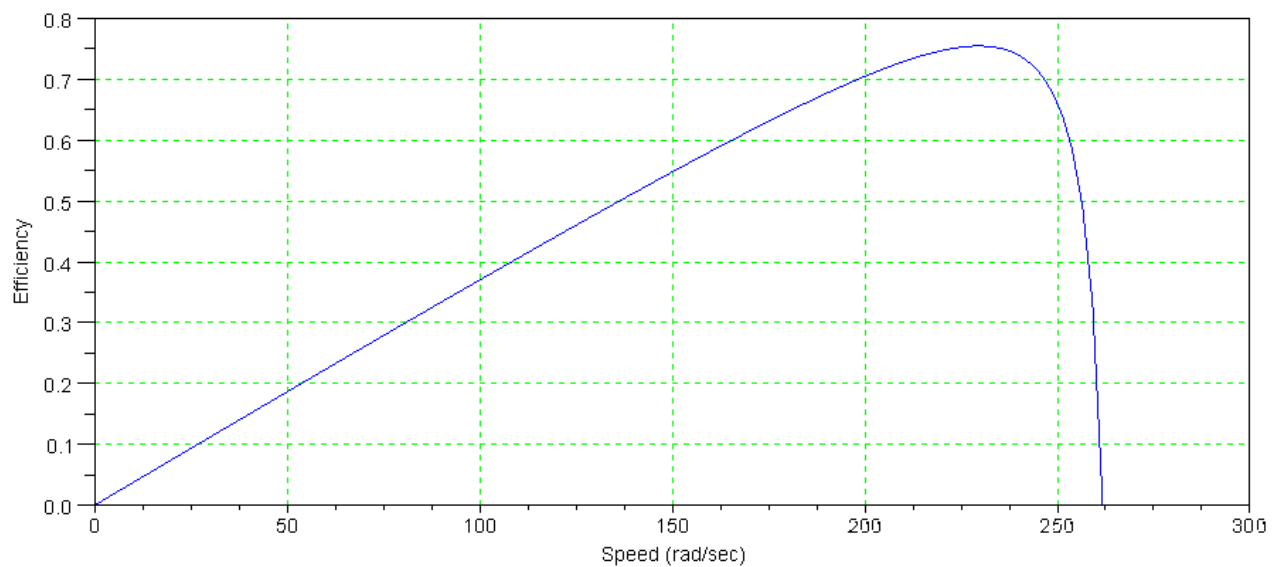
```
plot(w,(Ea.*Ia) ./ (Vt*(Ia + If)))  
xgrid(3)  
xlabel('Speed (rad/sec)')  
ylabel('Efficiency')
```



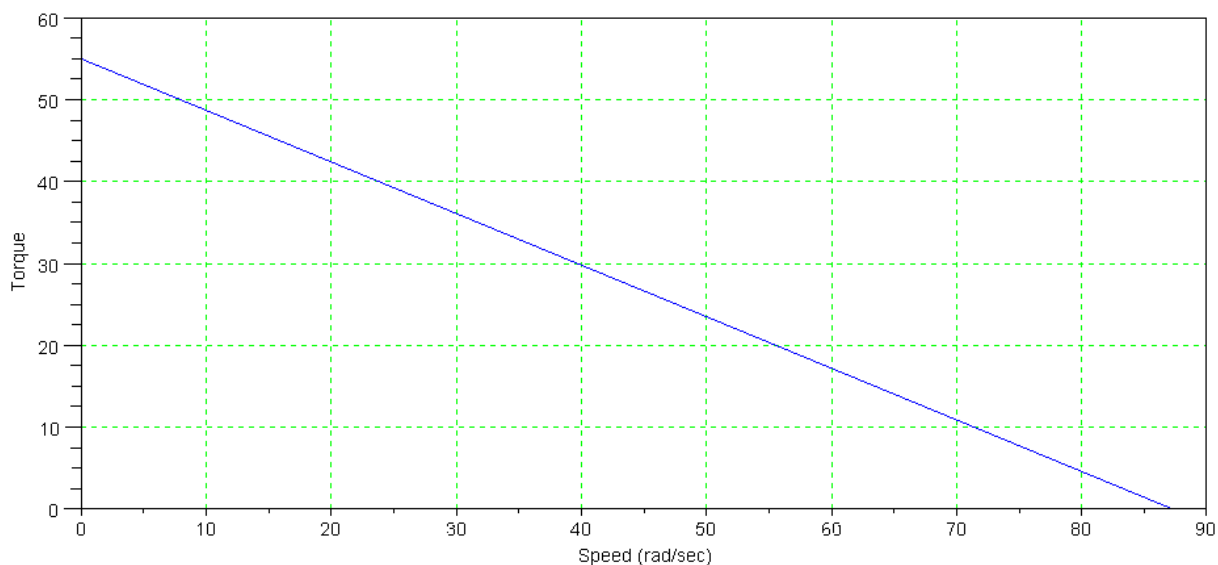3) Increase the field current by 3x (reduce R_f to 50 Ohms). Plot


- Load torque vs. speed

```
Vt = 120;  
Rf = 200;  
Rx = 2;  
Kt = 0.4297 * 3;  
Wmax = Vt / Kt;  
w = [0:0.01:1]' * Wmax;  
Ea = Kt*w;  
Ia = (Vt - Ea) / Rx;  
T = Kt*Ia;  
plot(w,T);  
xlabel('Speed (rad/sec)')  
ylabel('Torque');  
xgrid(3)
```




- Speed vs. power out
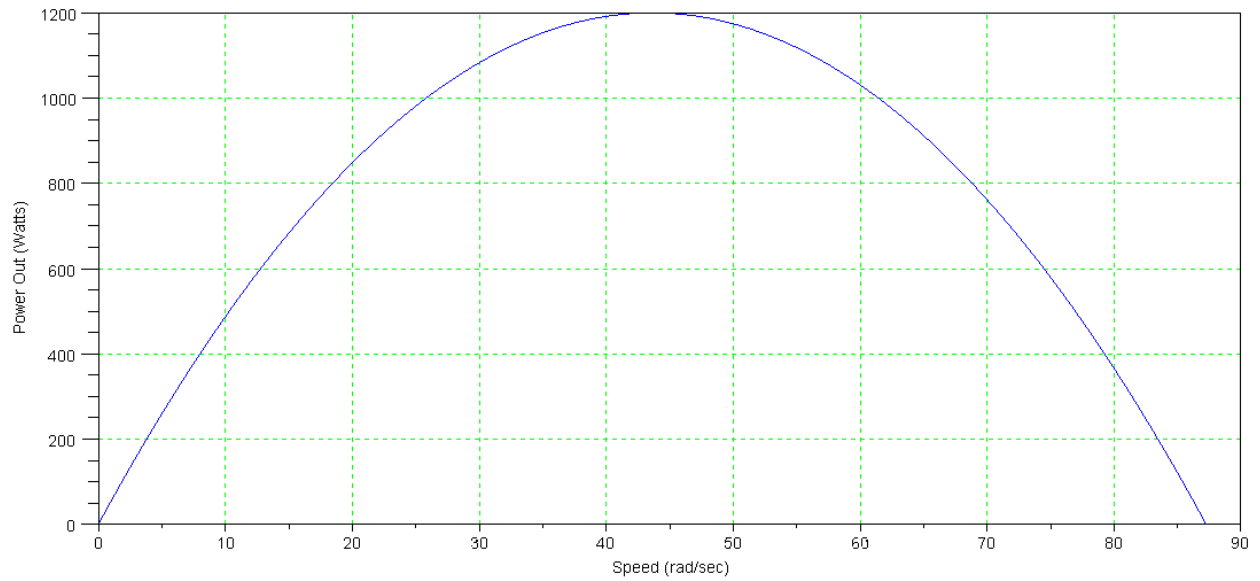
```
-->Po = Ea .* Ia;  
-->plot(w,Po);
```



- Speed vs. efficiency
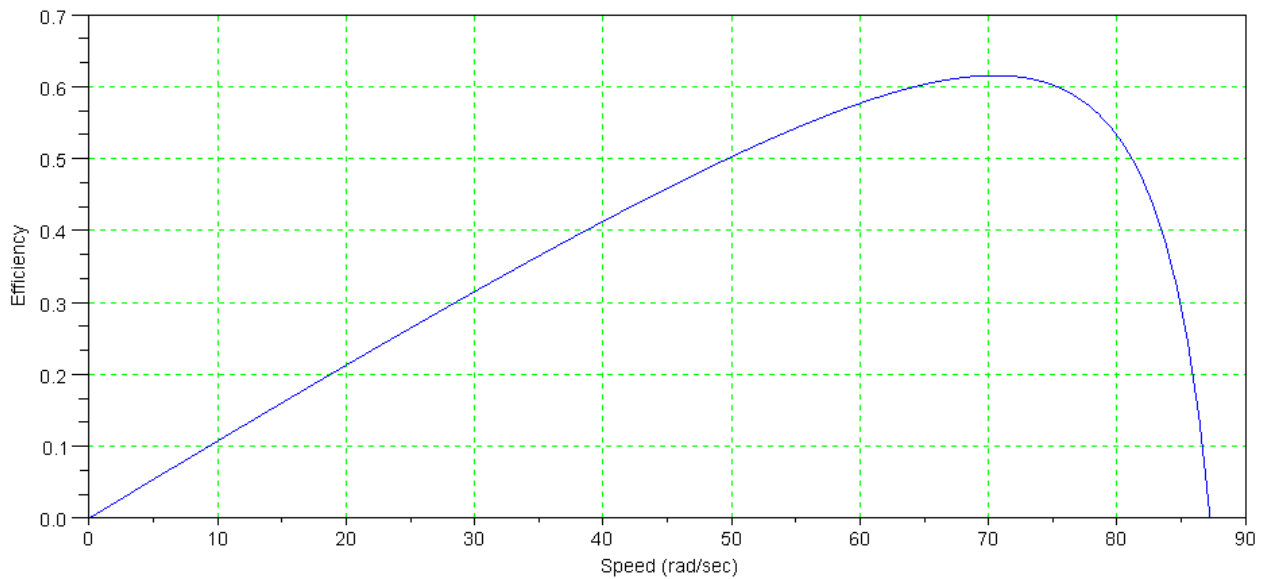
```
-->Pin = Vt*(Ia + If);
-->Eff = Po ./ (Pin + 0.00001);
-->plot(w, Eff)
-->xlabel('Speed (rad/sec)')
-->xgrid(3)
-->ylabel('Efficiency')
```



4) Design a DC shunt excited motor. The motor is to produce 15kW with $V_t = 120\text{VDC}$ at 3000 rpm. Specify R_f , R_x , K_t .

4) Design a DC shunt excited motor. The motor is to produce 10kW with $V_t = 120\text{VDC}$ at 3600 rpm. Specify R_f , R_x , K_t .

note: your designs will vary quite a bit.

One approach:

Assume your target is 85% efficient at the operating condition. Ignoring rotational losses, the efficiency is

$$0.85 = \frac{E_a}{V_t}$$

$$E_a = 102\text{V}$$

The torque constant is then

$$K_t = \frac{E_a}{\omega} = \frac{102\text{V}}{377\text{ rad/sec}} = 0.271 \frac{\text{V}}{\text{rad/sec}}$$

The torque is

$$T = \frac{P}{\omega} = \frac{15,000\text{W}}{377\text{ rad/sec}} = 39.79\text{Nm}$$

The armature current

$$I_a = \frac{T}{K_t} = \frac{39.79\text{Nm}}{0.271 \frac{\text{Nm}}{\text{A}}} = 146.8\text{A}$$

The armature resistance is

$$R_a = \frac{V_t - E_a}{I_a} = \frac{120\text{V} - 102\text{V}}{146.8\text{A}} = 0.1226\Omega$$

Let's use the same design as problem #1 with I_f adjusted. From problem #1,

- $I_f = 0.8\text{A}$ produced $K_t = 0.4584$
- To reduce the torque constant to $K_t = 0.271$, reduce I_f accordingly:

$$I_f = \left(\frac{0.271}{0.4584} \right) 0.8\text{A} = 0.4729\text{A}$$

Find R_f to get this current:

$$R_f = \left(\frac{120\text{V}}{0.4729\text{A}} \right) = 253.7\Omega$$

Note: There are other ways to do this. Once you specify the efficiency, the other parameters drop out one by one.

If you specify efficiencies closer to 100%, the armature resistance gets closer to zero.

5) Determine the efficiency of the DC motor you designed for problem #4 at this operating condition.

$$P_o = 15,000W$$

$$P_{in} = (I_a + I_f)V_t$$

$$P_{in} = (146.8A + 0.4729A)120V$$

$$P_{in} = 17,672W$$

$$\eta = \frac{P_o}{P_{in}} = \frac{15,000W}{17,672W} = 84.8\%$$

Note: I designed for 85% efficiency. This is a little lower since the 85% computations did not include the field losses.


(MATLAB - numerical integration)

6) Assume the inertia of the DC motor is 0.1 kg m² the the rotational losses are 1W/krpm.

Compute the speed vs. time using MATLAB as this motor accelerates from standstill to full speed.

Plot

- Speed vs. time
- Current vs. time

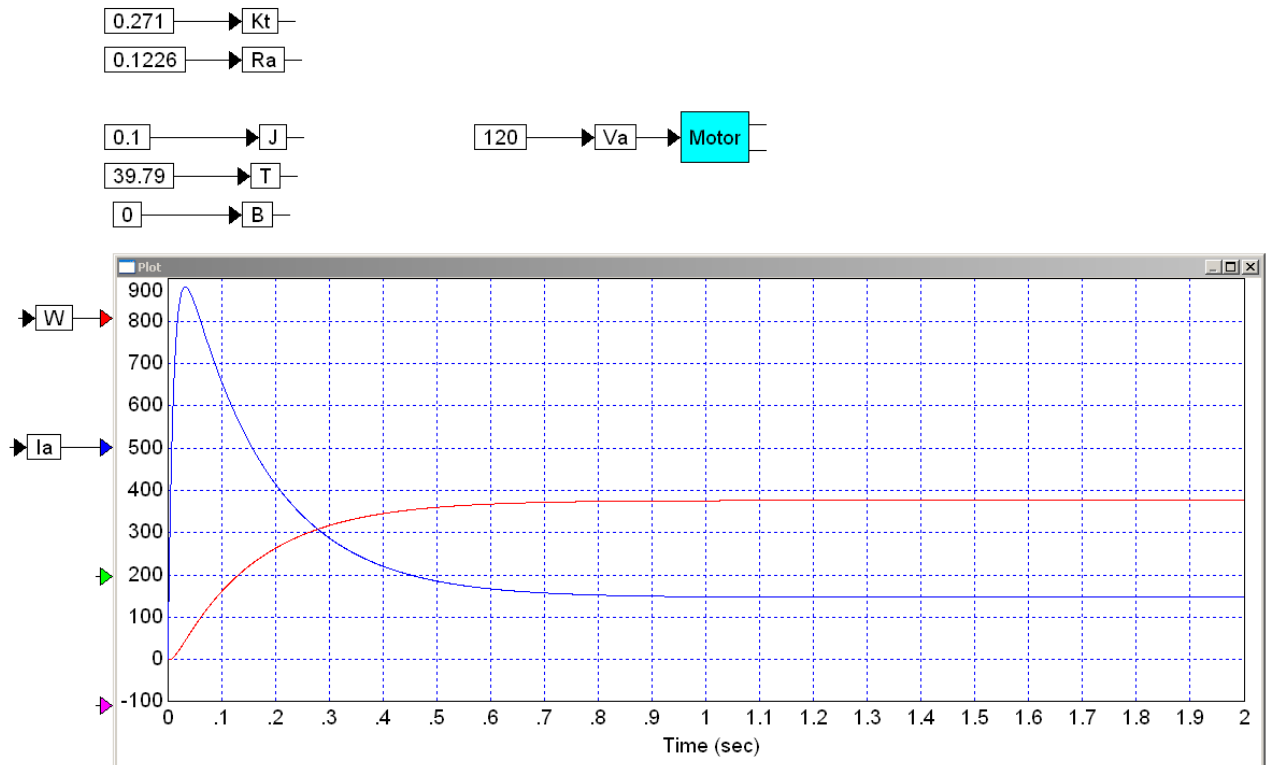

note: The in-rush current is about 6x the current required to output 15kW. If your motor isn't designed for that much current, you might burn it out on start-up.