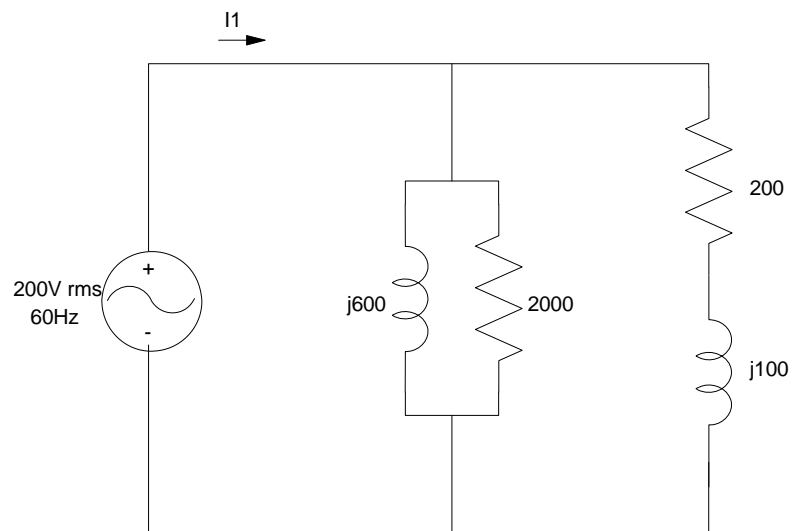


ECE 331: Test #1 Name _____

Closed Book, Closed Notes. Calculators Permitted


1) For the following circuit, find the current, I_1 , the power factor, and the total power delivered (real and complex).

I_1 (amps - rms)	
power factor	
power delivered (Watts)	



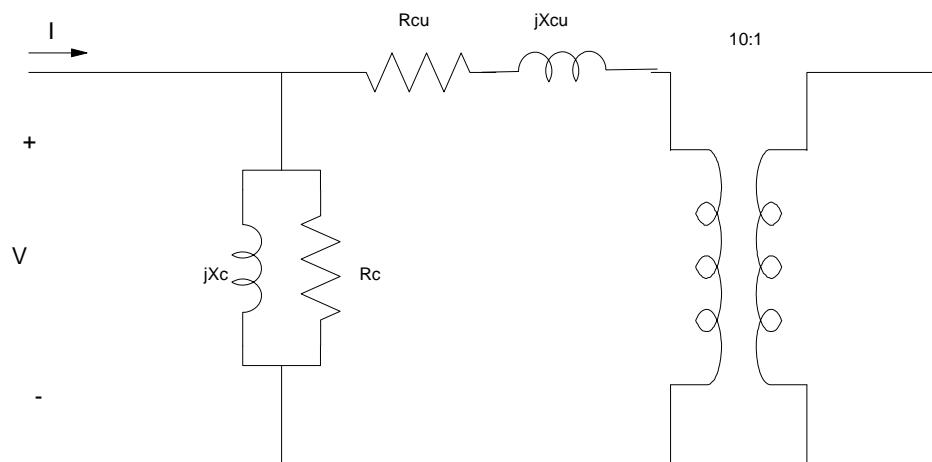
2) Find the core and copper impedances for a transformer with the following data:

- Open Circuit Test: $V = 3800V$, $I = 23A$, $pf = 0.2$
- Short Circuit Test: $V = 38V$, $I = 3A$, $pf = 0.8$




3) For the following transmission line, find the current at the load, the voltage at the load, and the efficiency of the transmission line.

V load	
I load	
Power to the load	
efficiency	

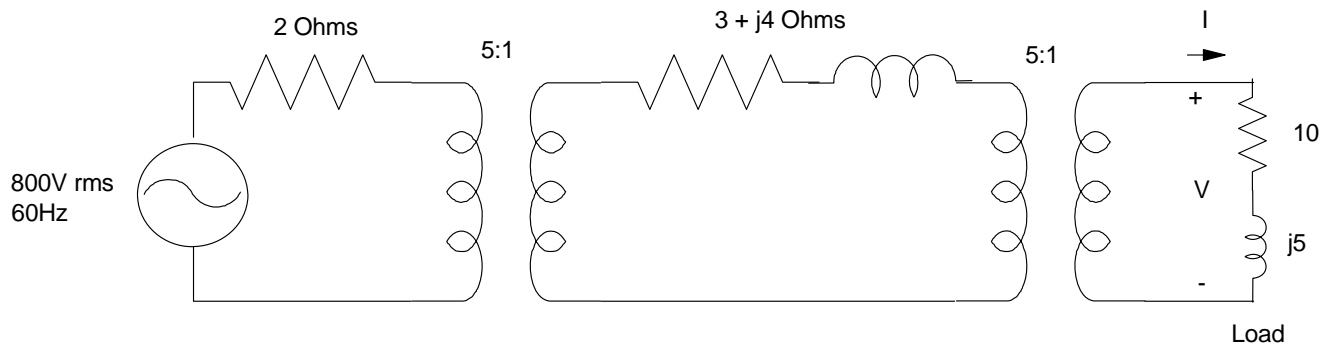

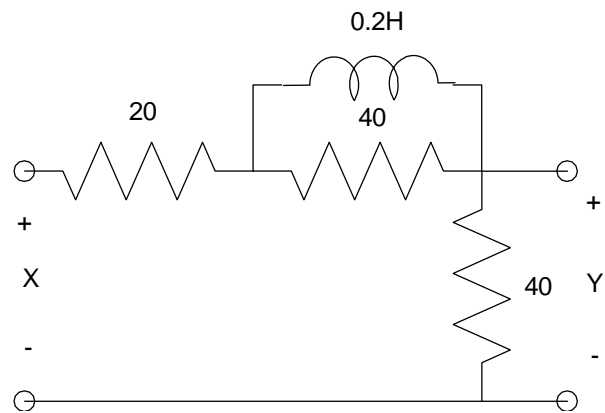4) Find the differential equation which relates voltages X and Y.



BONUS! According to the EERE, what is the approximate weight of a 138kV, 2000kVA transformer in pounds?