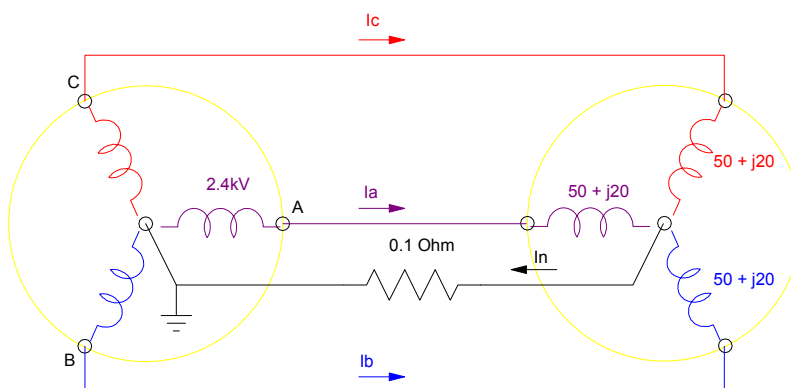


ECE 331 - Homework #5


Delta-Y Connections, Unbalanced Loads

Due Monday, February 24th, 4PM


1) A 3-phase transformer in Y configuration drives a 3-phase balanced load in Y configuration. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-neutral voltage for all three transformers is 2.4kV rms. $\{V_a, V_b, V_c\} = \{2.4kV\angle 0^\circ, 2.4kV\angle -120^\circ, 2.4kV\angle -240^\circ\}$



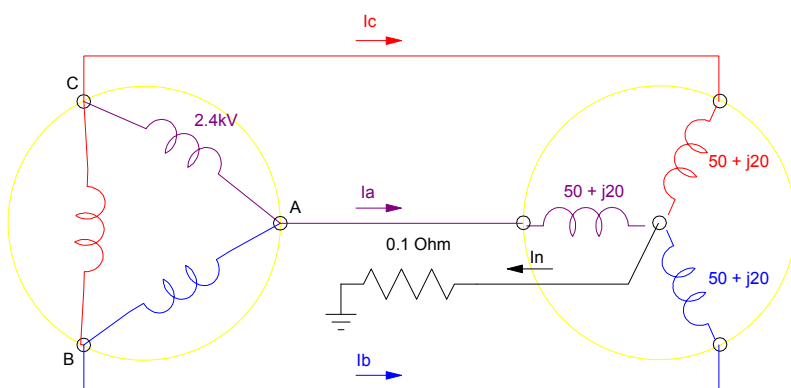
2) A 3-phase transformer in Delta configuration drives a 3-phase balanced load in Y configuration. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-line voltage at the transformer is 2.4kV.



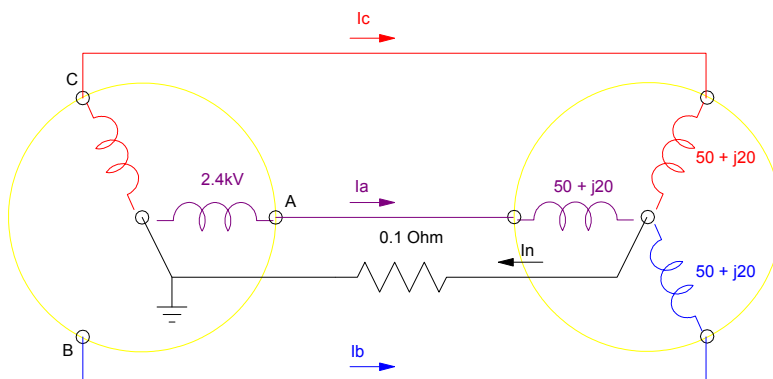3) A 3-phase transformer in Y configuration drives a 3-phase balanced load in Y configuration. Assume phase B transformer is removed. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-neutral voltage of each transformer is 2.4kV.



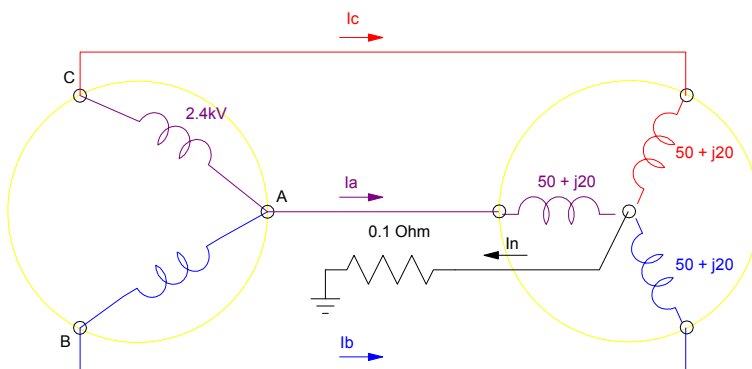4) A 3-phase transformer in Delta configuration drives a 3-phase balanced load in Y configuration. Assume the phase BC transformer is removed. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-line voltage of each transformer is 2.4kV.



5) A 3-phase transformer in Delta configuration drives a 3-phase unbalanced load in Y configuration. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-line voltage at the transformer is 2.4kV.

