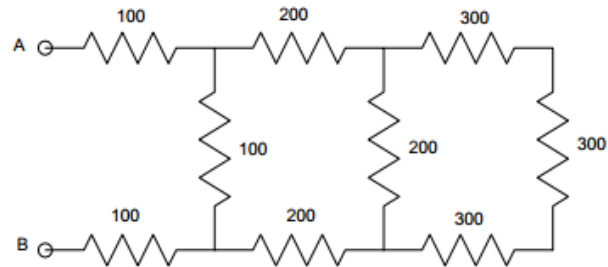


ECE 331 - Solution to Homework #1

Kirchoff's Laws, Complex Numbers. Due Wednesday, January 22nd, 4PM

1) Determine the resistance of the following circuit:



Starting from the right

$$300 + 300 + 300 = 1200 \quad (\text{series})$$

$$1200 \parallel 200 = 171$$


$$200 + 171 + 200 = 571$$

$$571 \parallel 100 = 85$$

$$100 + 85 + 100 = 285$$

answer: 285 Ohms

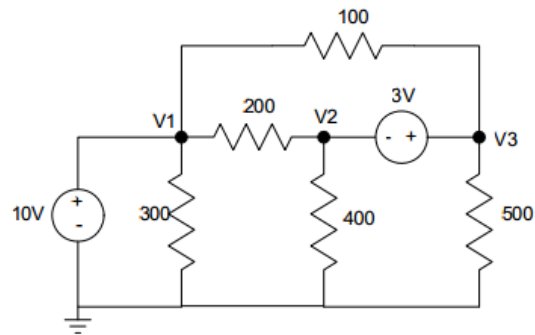2) For the following circuit, write N equations to solve for N unknown voltage nodes (KVN)



You need three equations for three unknown voltages. Start with the voltage sources:

$$V_1 = 10$$

$$V_3 - V_2 = 3$$

You need one more equation. Sum the currents to zero flowing away from the 3V source (super-node V2 and V3)

$$\left(\frac{V_2 - V_1}{200}\right) + \left(\frac{V_2}{400}\right) + \left(\frac{V_3 - V_1}{100}\right) + \left(\frac{V_3}{500}\right) = 0$$

Problem 3) Solve these N equations to find the voltages V1, V2, and V3

Group these three equations into common terms:

$$\left(\frac{-1}{200} + \frac{-1}{100}\right)V_1 + \left(\frac{1}{200} + \frac{1}{400}\right)V_2 + \left(\frac{1}{100} + \frac{1}{500}\right)V_3 = 0$$

Place in matrix form:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & 1 \\ \left(\frac{-1}{200} + \frac{-1}{100}\right) & \left(\frac{1}{200} + \frac{1}{400}\right) & \left(\frac{1}{100} + \frac{1}{500}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 3 \\ 0 \end{bmatrix}$$

Solve in MATLAB:

```
-->A = [1,0,0;0,-1,1;-1/100-1/200,1/200+1/400,1/100+1/500]
```

```
    1.    0.    0.
    0.   -1.    1.
   -0.015  0.0075  0.012
```

```
-->B = [10;3;0]
```

```
-->V = inv(A)*B
```

```
v1 =    10.
v2 =    5.8461538
v3 =    8.8461538
```

Complex Numbers: Determine the value of Y - showing the steps to find t

$$4) \quad Y = \left(\frac{10(s+3)}{(s+1)(s+5)} \right)_{s=j4}$$

$$Y = \left(\frac{10(j4+3)}{(j4+1)(j4+5)} \right)$$

$$\begin{aligned} \left(\frac{10(s+3)}{(s+1)(s+5)} \right)_{s=j4} &= 0.9039 - j1.6643 \\ &= 1.8939 \angle -61.49^\circ \end{aligned}$$

Either answer is correct.

$$5) \quad e^{(2+j3)} = (e^2)(e^{j3})$$

$$7.3891 \angle 3 \text{rad} = 7.3891 \angle 171.88^\circ \quad (\text{polar form})$$

$$\begin{aligned} e^{(2+j3)} &= 7.3891 \angle 171.88^\circ \\ &= -7.3151 + j1.0427 \end{aligned}$$

$$6) \quad Y = \ln(2 + j3)$$

$$Y = \ln(3.6056 \angle 56.31^\circ)$$

$$Y = \ln(e^{\ln(3.6056)} \angle 1.2825 \text{ rad})$$

$$Y = \ln(e^{0.9828} \cdot e^{j1.2825})$$

$$Y = \ln(e^{0.9828+j1.2825})$$

$$\begin{aligned} \ln(2 + j3) &= 0.9828 + j1.2825 \\ &= 1.6157 \angle 37.46^\circ \end{aligned}$$

$$7) \quad (2 + j3)^{(4+j5)}$$

$$= (e^{(0.9828+j1.2825)})^{(4+j5)}$$

$$= e^{(0.9828+j1.2825)(4+j5)}$$

$$= e^{0.2159+j10.3435}$$

$$= (e^{0.2159}) \angle 10.34 \text{ rad}$$

$$\begin{aligned} (2 + j3)^{(4+j5)} &= -0.7530 - j0.9864 \\ &= 1.2410 \angle 127.35^\circ \end{aligned}$$