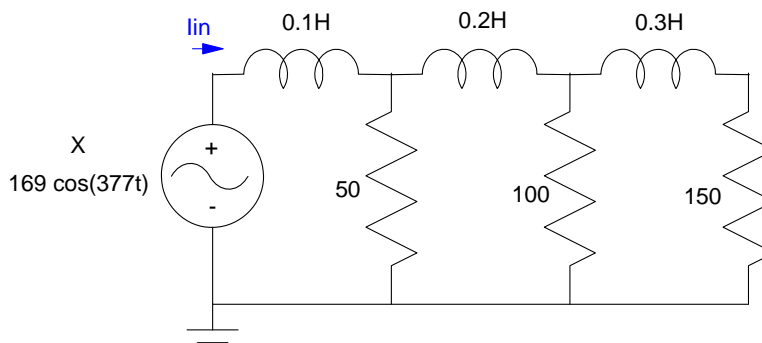


## ECE 331 - Homework #2

Phasors, RL Circuits, Power Factor - Due Monday, Jan 27th

- 1a) Determine the current,  $I_{in}$ :
- 1b) Determine the power factor:
- 1c) Determine the power consumed by this circuit



Step 1: Convert to impedance

$$0.1H \rightarrow j\omega L = j37.7\Omega$$

$$0.2H \rightarrow j75.4\Omega$$

$$0.3H \rightarrow j113.1\Omega$$

Step 2: Combine in series and parallel:

$$150 + j113.1 \parallel 100 = 66.79 + j15.02$$

parallel

$$(66.79 + j15.02) + (j75.4) = 66.79 + j90.42$$

series

$$(66.79 + j90.42) \parallel (50) = 36.51 + j10.36$$

parallel

$$(36.51 + j10.36) + (j37.7) = 36.61 + j48.06$$

$$Z_{in} = 36.61 + j48.06$$

1a): Compute the current

$$I_{in} = \frac{169/\sqrt{2} V_{rms}}{36.61 + j48.06\Omega} = 1.2036 - j1.5798$$

$$I_{in} = 1.2036 - j1.5798 \text{ Amps rms}$$

$$= 1.9861 \angle -52.69^\circ$$

1b) The power factor is

$$pf = \cos(-52.69^\circ) = 0.6060$$


1c) The power consumed is

$$P = V_{rms} \cdot I_{rms} \cdot pf$$

$$P = (120V_{rms})(1.9861A_{rms})(0.6060)$$

$$P = 144.43W$$

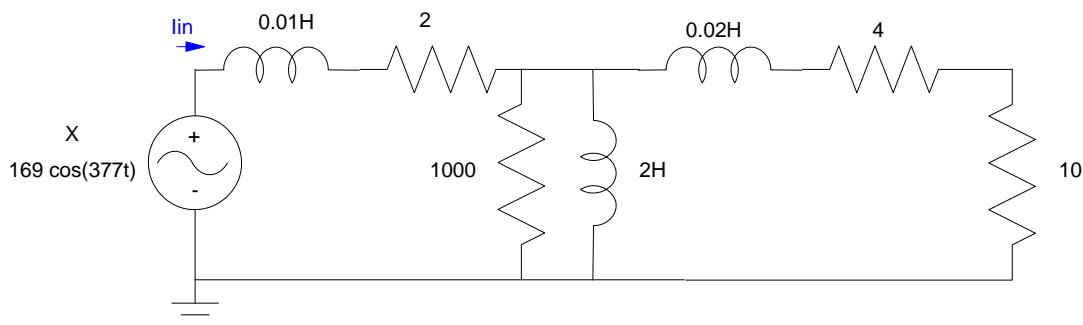- 2a) Determine the current,  $I_{in}$ :  
 2b) Determine the power factor:  
 2c) Determine the power consumed by this circuit



Step 1: Convert to impedance:

$$0.02H \rightarrow j7.54$$

$$2H \rightarrow j754$$

$$0.01H \rightarrow j3.77$$

Step 2: Combine:

$$(10) + (4) + (j7.54) = 14 + j7.54$$

$$(14 + j7.54) \parallel (j754) \parallel (1000) = (13.5910 + j7.5096)$$

$$(13.5910 + j7.5096) + (2) + (j3.77) = 15.5910 + j11.2796$$

$$Z_{in} = 15.5910 + j11.2796$$

Step 3: Determine the current

$$I = \frac{V}{Z} = \frac{120V_{rms}}{15.5910 + j11.2796\Omega}$$

2a)  $I = 5.5023 - j3.6552$  A rms  
 $= 6.2359 \angle -35.88^\circ$

$$pf = \cos(-35.88^\circ)$$

2b)  $pf = 0.8102$

$$P = V_{rms} \cdot I_{rms} \cdot pf$$

$$P = (120V)(6.2359A)(0.8102)$$

2c)  $P = 606W$

3) The following data is measured for a RL circuit:

- $V_{in} = 120V$  rms
- $I_{in} = 35A$  rms
- $P_{in} = 3000$  Watts
- $f = 60Hz$  ( $377$  rad/sec)

Determine the impedance and power factor.

$$|Z| = \frac{120V}{35A} = 3.4286\Omega$$

$$pf = \frac{P}{V \cdot I} = \frac{3000W}{(120V)(35A)}$$

$$pf = 0.7143$$

$$\theta = \arccos(0.7143) = 44.41^\circ$$

$$Z = 3.4286 \angle 44.41^\circ$$

4) Determine an RL series and RL parallel circuit to implement the impedance for problem #3 (at 60Hz):

In rectangular form

$$Z = 2.4490 + j2.3995$$

Series Model:

$$R_s = 2.4490$$

$$jX_s = j2.3995$$

Taking the inverse to find the parallel form

$$\frac{1}{Z} = \frac{1}{R_p} + \frac{1}{jX_p}$$

$$\frac{1}{Z} = 0.2083 - j0.2041$$

Parallel Model:

$$R_p = 4.8008$$

$$jX_p = j4.8996$$