

ECE 331 - Solution to Homework #4

Ideal Transformers, Transformer Testing, Transformer Design, Auto-Transformers
Due Wednesday, February 19th, 4PM

1) The following circuit uses a transformer to buffer a transistor amplifier to an 8 Ohm speaker.

1a) Determine the turns ratio for this amplifier to be 90% efficient.

The efficiency is

$$\eta = \frac{P_{out}}{P_{in}}$$

$$0.9 = \frac{I^2 \cdot 8\Omega}{I^2 \cdot (8\Omega + R)}$$

$$R = 0.8888$$

The 1000 Ohm resistor needs to look like an 0.8888 Ohm resistor at the load. To do this, you need a turns ratio of

$$0.8888\Omega = \left(\frac{1}{N}\right)^2 1000\Omega$$

$$N = 33.55$$

1b) For the turn ration of part a), determine the voltage, V_{in} , to drive the speaker at 10 Watts.

For 10 Watts at the load,

$$P = I^2 R$$

$$10W = I^2 \cdot 8\Omega$$

$$I = 1.118A$$

The voltage source is then


$$V_{in} = I \cdot (0.888 + 8) = 9.938V$$

This is on the right side of the transformer. Bringing it left by the turns ratio

$$V_{in} = (33.55)(9.938V)$$


$$V_{in} = 333V$$

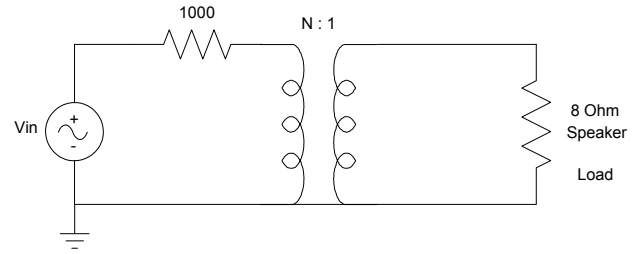You need fairly high voltages to drive an 8-Ohm speaker through a transformer.



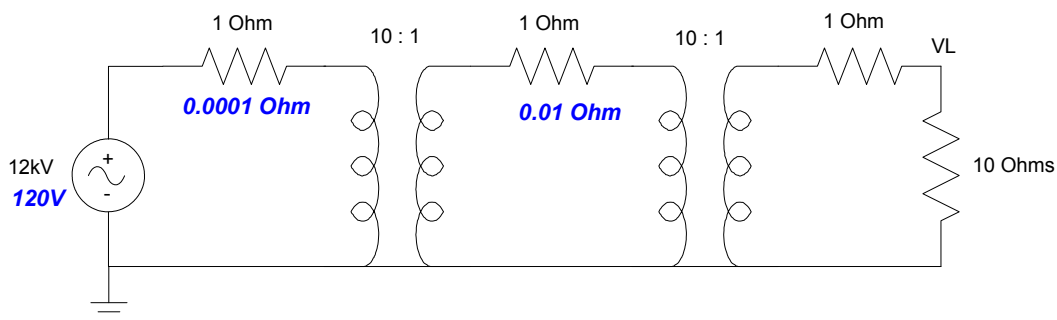2) The following circuit uses ideal transformers.

- Determine the voltage at the 10 Ohm load (V_L), and
- Determine the efficiency of this system.



Bringing everything to the load side (right) results in the voltages and impedances shown.

The voltage at the load by voltage division is then

$$V_L = \left(\frac{10}{10+1+0.01+0.0001} \right) 120V$$

$$V_L = 108.99V$$

The efficiency is


$$\eta = \frac{P_{out}}{P_{total}} = \frac{I^2 \cdot 10\Omega}{I^2 \cdot (10+1+0.01+0.0001)}$$

$$\eta = 0.9083$$

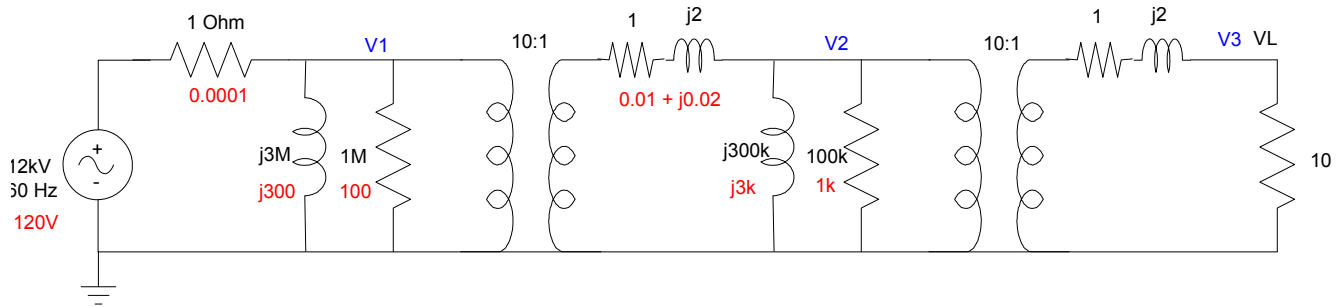3) The following circuit uses a more accurate model of a transformer:

- Determine the voltage at the 10 Ohm load (VL), and
- Determine the efficiency of this system.

Bring everything to the load side (right). This uses the values shown in red.



Writing 3 equations for 3 unknowns

$$\left(\frac{V_1-120}{0.0001}\right) + \left(\frac{V_1}{j300}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{V_1-V_2}{0.01+j0.02}\right) = 0$$

$$\left(\frac{V_2-V_1}{0.01+j0.02}\right) + \left(\frac{V_2}{j3000}\right) + \left(\frac{V_2}{1000}\right) + \left(\frac{V_2-V_3}{1+j2}\right) = 0$$

$$\left(\frac{V_3-V_2}{1+j2}\right) + \left(\frac{V_3}{10}\right) = 0$$

Putting this in MATLAB

```
a1 = [1/0.0001+1/(j*300)+1/100+1/(0.01+j*0.02), -1/(0.01+j*0.02), 0]
a2 = [-1/(0.01+j*0.02), 1/(0.01+j*0.02)+1/(j*3000)+1/1000+1/(1+j*2), -1/(1+j*2)]
a3 = [0, -1/(1+j*2), 1/(1+j*2)+1/10]
```

```
-->A = [a1;a2;a3]
```

```
10020.01 - 40.0033333i - 20. + 40.i 0
- 20. + 40.i 20.201 - 40.4003333i - 0.2 + 0.4i
0 - 0.2 + 0.4i 0.3 - 0.4i
```

```
-->B = [120/0.0001;0;0]
```

```
1200000.
0.
0.
```

```
-->V = inv(A)*B
```

```
119.99881 + 0.0002375i
119.85268 - 0.1932892i
105.43943 - 19.346523i
```

The voltage at the load is

$$V_L = 107.2V \angle -10^\circ$$

To find the efficiency, find the power out and power in. Power out is the power across the 10 Ohm resistor:

```
-->Pout = ( abs(V(3)) ) ^2 / 10  
1149.1762
```

Power (or total power) is a little harder to find. One way is to compute $V \cdot I$ at the source:

```
-->Iin = (120 - V(1))/0.0001  
Iin =  
11.86372 - 2.3747902i
```

```
-->Pin = real(120 * Iin)          actually you need the conjugate:  $P = V \cdot I^*$   
Pin =  
1423.6465
```

```
-->eff = Pout / Pin  
eff =  
0.8072062
```

The efficiency is 80.7%

This isn't very high - but you have only one customer. The efficiency goes up to 90.8% as the number of customers becomes large (meaning you can discount the core losses to zero).

4) A 10kVA transformer has the following open-circuit and short-circuit test results:

Open-Circuit Test

- $V_{in} = 12kV$
- $I_{in} = 1A$
- $P_{in} = 1 \text{ Watt}$

The core impedance is

$$Z_{core} = \left(\frac{12kV}{1A} \right) = 12k\Omega$$

$$P_{in} = \frac{V^2}{R}$$

$$1W = \frac{(12kV)^2}{R}$$

$$R_p = 144M\Omega$$

$$jX_p = j12k\Omega$$

Short-Circuit Test:

- $V_{in} = 24V$
- $I_{in} = 2A$
- $P_{in} = 40W$

Determine a model for this transformer.

$$Z_{Cu} = \left(\frac{24V}{2A} \right) = 12\Omega$$

$$pf = \frac{40W}{2A \cdot 24V} = 0.8333$$

$$Z_{Cu} = 12 \angle 33.5573^\circ$$

$$Z_{Cu} = 10 + j6.63$$


5) For problem #4, what current would you expect if you ran the short-circuit test at 12kV?

Assuming the short-circuit test was done on the high side, if you raise the voltage by a factor of 500, power goes up as 500 squared:

$$P_{in} = 10MW$$

You'll fry the transformer.

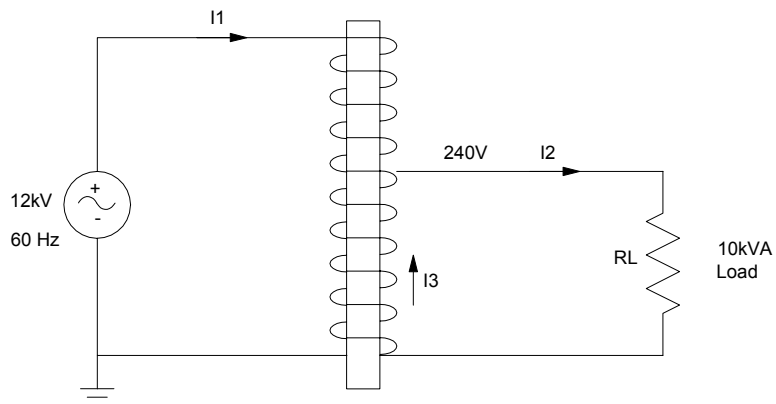6) The following auto-transformer steps 12kV down to 240V. Determine the currents I_1 , I_2 , and I_3



Power has to balance (and be 10kVA). At the left side

$$10kVA = (12kV)(I_1)$$

$$I_1 = 0.8333A$$

On the right side:

$$10kVA = (240V)(I_2)$$

$$I_2 = 41.6667A$$

Current has to balance:

$$I_1 + I_3 = I_2$$

$$I_3 = 40.83A$$