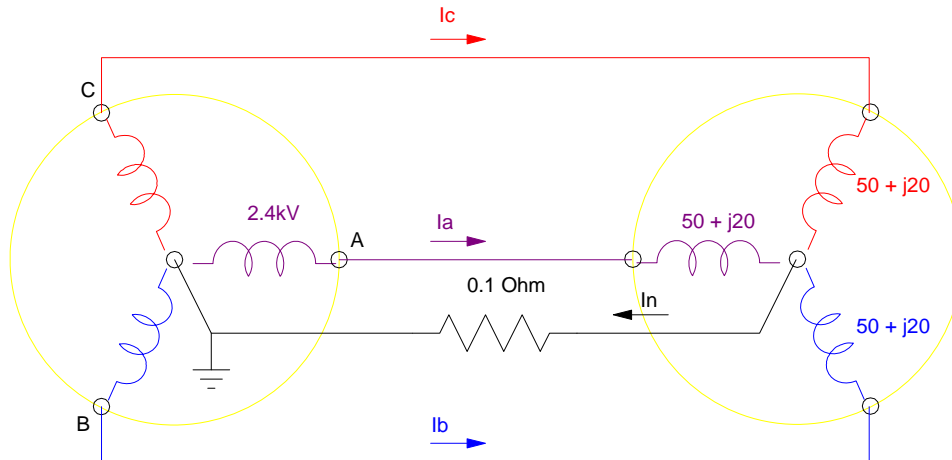


ECE 331 - Solutions to Homework #5

1) A 3-phase transformer in Y configuration drives a 3-phase balanced load in Y configuration. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-neutral voltage for all three transformers is 2.4kV rms.



Solution (from SciLab)

```
-->// Y source, Y load
-->Va = 2400;
-->Vb = 2400 * exp(-j*120*%pi/180);
-->Vc = 2400 * exp(-j*240*%pi/180);

-->Za = 50 + j*20;
-->Zb = 50 + j*20;
-->Zc = 50 + j*20;

-->// the voltage at the load neutral:
-->Vx = (Va/Za + Vb/Zb + Vc/Zc) / (1/Za + 1/Zb + 1/Zc + 10)

- 9.718D-14 - 6.008D-14i
```

Note that for a balanced load, the currents sum to zero, meaning the voltage at the neutral is zero.


```
-->// Line currents
-->Ia = (Va - Vx) / Za;
-->Ib = (Vb - Vx) / Zb;
-->Ic = (Vc - Vx) / Zc;
-->In = Vx / 0.1;

-->I = [Ia; Ib; Ic; In];
-->[abs(I), atan(imag(I),real(I))*180/%pi]
```

	Amps	Degrees
Ia	44.566881	- 21.801409
Ib	44.566881	- 141.80141
Ic	44.566881	98.198591
In	1.143D-12	- 148.27235

Again, the currents sum to zero ($I_n = 0$)

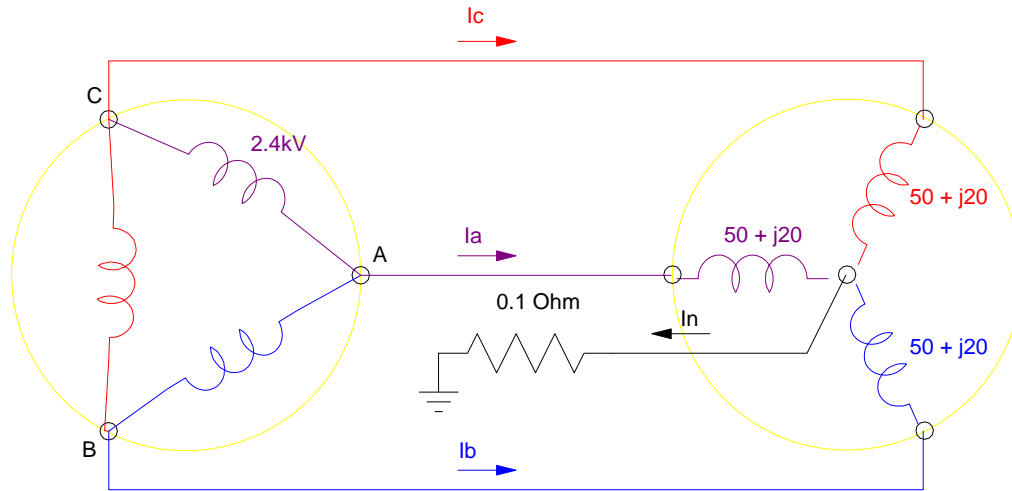Problem 2: A 3-phase transformer in Delta configuration drives a 3-phase balanced load in Y configuration. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-line voltage at the transformer is 2.4kV.



```

-->// Delta Source, Y Load
-->// Define the voltages and impedances:

-->Vab = 2400;
-->Vbc = 2400 * exp(-j*120*pi/180);
-->Vca = 2400 * exp(-j*240*pi/180);

-->Za = 50 + j*20;
-->Zb = 50 + j*20;
-->Zc = 50 + j*20;

-->// With 4 unknown voltages, write voltage node equations to solve for 4 unknowns:
-->// Writing the voltage node equations:

-->A = [1, 1, 1, 0; 0, 1, -1, 0; -1, 0, 1, 0; -1/Za, -1/Zb, -1/Zc,
1/Za+1/Zb+1/Zc+1/0.1]
-->B = [ 0; Vbc; Vca; 0]

```

$$\begin{bmatrix}
 1 & 1 & 1 & 0 \\
 0 & 1 & -1 & 0 \\
 -1 & 0 & 1 & 0 \\
 -0.0172 + j0.0068 & -0.0172 + j0.0069 & -0.01724 + j0.0069 & 10.0517 - j0.0207
 \end{bmatrix}
 \begin{bmatrix}
 V_a \\
 V_b \\
 V_c \\
 V_x
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 2400 \angle -120^\circ \\
 2400 \angle -240^\circ \\
 0
 \end{bmatrix}$$

```

-->//Solving for the line voltages:

-->V = inv(A)*B;
-->[ abs(V), atan(imag(V),real(V))*180/pi ]

```

	Volts	Degrees
Va	1385.6406	- 30.
Vb	1385.6406	- 150.
Vc	1385.6406	90.
Vx	0.	0.

Doesn't matter if the source is delta or Y. If you have a balanced load, the voltages and currents sum to zero. All that changes is line-to-line voltage is $\sqrt{3}$ times bigger than line-to-neutral.

Solving for currents:

```
-->Va = V(1);
-->Vb = V(2);
-->Vc = V(3);
-->Vx = V(4);


-->// Solving for the line currents

-->Ia = (Va - Vx) / Za;
-->Ib = (Vb - Vx) / Zb;
-->Ic = (Vc - Vx) / Zc;
-->In = Vx / 0.1;

-->I = [Ia; Ib; Ic; In];
-->[ abs(I), atan(imag(I),real(I))*180/%pi ]
```

	Amps	Degrees
Ia	25.730701	- 51.801409
Ib	25.730701	- 171.80141
Ic	25.730701	68.198591
In	0.	0.

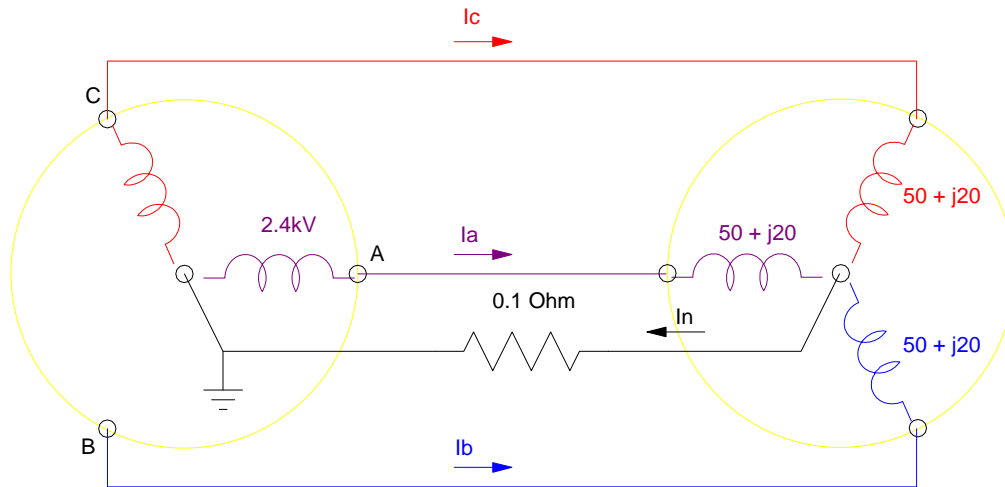Problem 3: A 3-phase transformer in Y configuration drives a 3-phase balanced load in Y configuration. Assume phase B transformer is removed. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-neutral voltage of each transformer is 2.4kV.



To model the loss of phase B, add 1G Ohm impedance to line B:

```
-->// Y source, Y load
-->Va = 2400;
-->Vb = 2400 * exp(-j*120*pi/180);
-->Vc = 2400 * exp(-j*240*pi/180);

-->Za = 50 + j*20;
-->Zb = 50 + j*20 + 1e9;           // open-circuit on line B
-->Zc = 50 + j*20;

-->// the voltage at the load neutral:
-->Vx = (Va/Za + Vb/Zb + Vc/Zc) / (1/Za + 1/Zb + 1/Zc + 1/0.1)
      3.4865692 + 2.7512888i
```

Note : In Y-Y configuration, if you lose one of the transformers,

- You lose that phase ($V_b = 3.48 + j2.75$ as well)
- The neutral is no longer zero volts

```
-->// Line currents
-->Ia = (Va - Vx) / Za;
-->Ib = (Vb - Vx) / Zb;
-->Ic = (Vc - Vx) / Zc;
-->In = Vx / 0.1;


-->I = [Ia; Ib; Ic; In];
-->[abs(I), atan(imag(I),real(I))*180/pi]
```

	Amps	Degrees	
Ia	44.502167	- 21.867187	
Ib	0.0000024	- 120.03918	// Ib = 0 due to a line loss
Ic	44.555083	98.303544	
In	44.413686	38.277346	

Likewise, if you lose a line with a Y-source,

- The line current in that phase becomes zero (duh)
- The neutral current becomes **large**. 44.4 Amps in this case

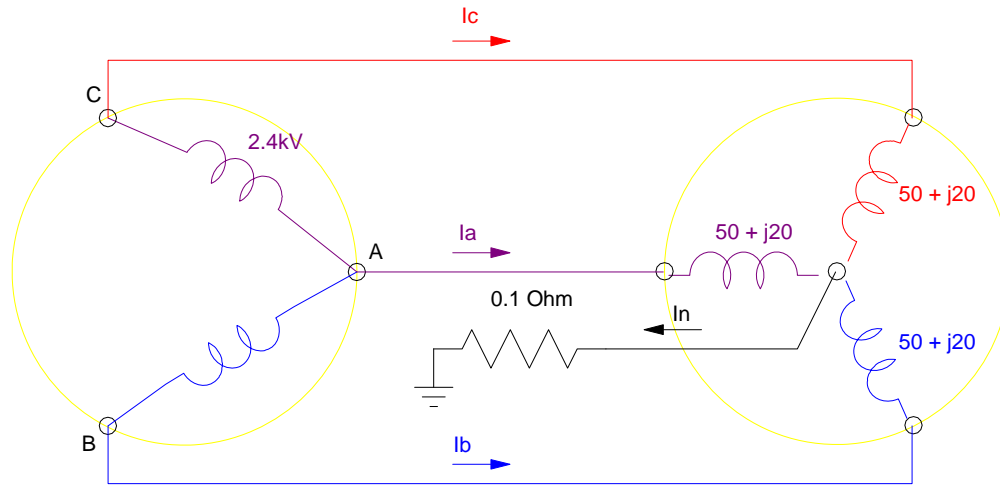Problem 4: A 3-phase transformer in Delta configuration drives a 3-phase balanced load in Y configuration. Assume the phase BC transformer is removed. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-line voltage of each transformer is 2.4kV.



```
-->// Delta Source, Y Load
-->// Define the voltages and impedances:
-->Vab = 2400;
-->Vbc = 2400 * exp(-j*120*%pi/180);
-->Vca = 2400 * exp(-j*240*%pi/180);
-->Za = 50 + j*20;
-->Zb = 50 + j*20;
-->Zc = 50 + j*20;
-->// With 4 unknown voltages, write voltage node equations to solve for 4 unknowns:
-->// Writing the voltage node equations:
-->A = [1, 1, 1, 0; 1, -1, 0, 0; -1, 0, 1, 0; -1/Za, -1/Zb, -1/Zc,
1/Za+1/Zb+1/Zc+1/0.1]
-->B = [ 0; Vab; Vca; 0]
-->//Solving for the line voltages:
-->V = inv(A)*B;
-->[ abs(V), atan(imag(V),real(V))*180/%pi ]
      Volts      Degrees
Va    1385.6406  - 30.
Vb    1385.6406  - 150.
Vc    1385.6406   90.
Vx     0.         0.
```

Note: In delta configuration,

- If you lose a source transformer, there is no affect on the system. The load still has the same voltages as before.

- The neutral voltage is still zero with a balanced load

Checking the currents:

```

-->Va = V(1);
-->Vb = V(2);
-->Vc = V(3);
-->Vx = V(4);

-->// Solving for the line currents

-->Ia = (Va - Vx) / Za;
-->Ib = (Vb - Vx) / Zb;
-->Ic = (Vc - Vx) / Zc;
-->In = Vx / 0.1;

-->I = [Ia; Ib; Ic; In];
-->[ abs(I), atan(imag(I),real(I))*180/%pi ]


```

	Amps	Degrees
Ia	25.730701	- 51.801409
Ib	25.730701	- 171.80141
Ic	25.730701	68.198591
In	0.	0.

The line currents are the same as problem #2.

Note that there is a slight difference: the power to the load is distributed between two transformers rather than three.

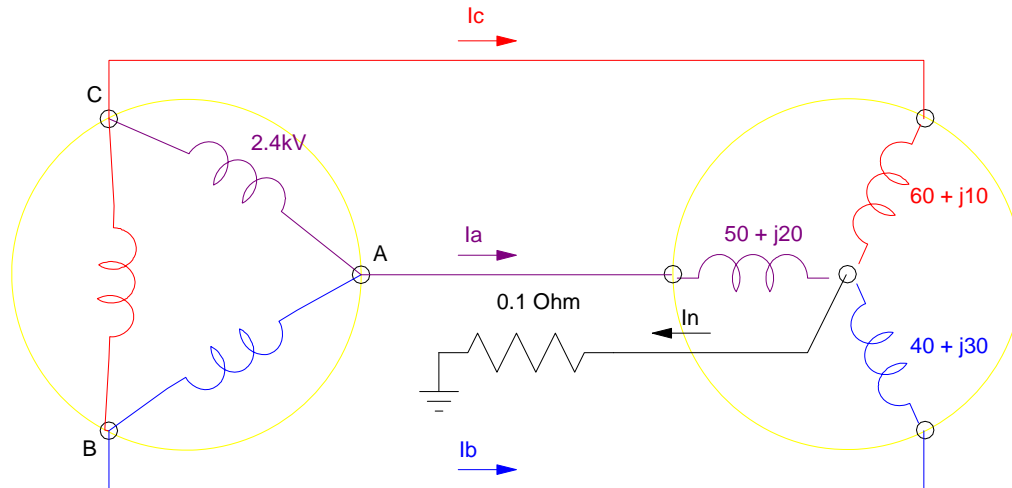Problem 5) A 3-phase transformer in Delta configuration drives a 3-phase unbalanced load in Y configuration. Determine the currents I_a , I_b , I_c and the current on the neutral line, I_n . Assume the line-to-line voltage at the transformer is 2.4kV.



```

-->// Delta Source, Y Load
-->// Define the voltages and impedances:
-->Vab = 2400;
-->Vbc = 2400 * exp(-j*120*pi/180);
-->Vca = 2400 * exp(-j*240*pi/180);

-->Za = 50 + j*20;
-->Zb = 30 + j*30;
-->Zc = 60 + j*10;

-->// With 4 unknown voltages, write voltage node equations to solve for 4 unknowns:
-->// Writing the voltage node equations:
-->A = [1, 1, 1, 0; 1, -1, 0, 0; -1, 0, 1, 0; -1/Za, -1/Zb, -1/Zc, 1/Za+1/Zb+1/Zc+10]
-->B = [ 0; Vab; Vca; 0]

// Solving for the line voltages:
-->V = inv(A)*B;
-->[ abs(V), atan(imag(V),real(V))*180/pi ]

      Volts      Degrees
Va    1385.6406  - 30.
Vb    1385.6406  - 150.
Vc    1385.6406   90.
Vx     1.5917389  138.16146

```

With an unbalanced load, the neutral (V_x) is no longer zero

Checking the line currents:

```

-->Va = V(1);
-->Vb = V(2);
-->Vc = V(3);
-->Vx = V(4);

-->// Solving for the line currents

-->Ia = (Va - Vx) / Za;
-->Ib = (Vb - Vx) / Zb;
-->Ic = (Vc - Vx) / Zc;
-->In = Vx / 0.1;

-->I = [Ia; Ib; Ic; In];
-->[ abs(I), atan(imag(I),real(I))*180/%pi ]

      Amps      Degrees
Ia    25.759631  - 51.814897
Ib    32.648189  165.06256
Ic    22.762345  80.488604
In    15.917389  138.16146

```

With an unbalanced load, the currents no longer match and the neutral current is no longer zero.