

# ECE 331 - Homework #7

3 Phase Induction Motors and Generators. Due March 24th 4PM  
Assume all units are rms.

1) A three-phase, two-pole, 30hp,  $120V_{LN}$ , 60Hz Y connected induction motor draws a current of 30A from the line source at a power factor of 0.9. At this condition, the motor losses are:

- Stator copper losses =  $P_{cu1} = 400W$
- Rotor copper losses =  $P_{cu2} = 200W$
- Stator core losses =  $P_c = 140W$
- Rotation losses =  $P_{rot} = 100W$

Calculations:

## a) The power transferred across the air gap

Analyze this on a per-phase basis. The total answer will be 3 times the result per phase.

The line-to-neutral voltage is  $120V_{LN}$ .

The electric power input and power across the gap are

$$P_{elec} = 3 \cdot 120V \cdot 30A \cdot 0.90 = 9,720W$$

$$P_g = P_{elec} - P_{Cu1} - P_c$$

$$P_g = 9,720W - 400W - 140W = 9,180W$$

## b) The internally developed torque in Nm

$$n_s = 2p \cdot 60Hz = 377 \text{ rad/sec}$$

$$T = \left( \frac{9180W}{377 \text{ rad/sec}} \right) = 24.35Nm$$

## c) the slip expressed in per unit and in rpm

$$P_{Cu2} = s \cdot P_g$$

$$s = \left( \frac{P_{Cu2}}{P_g} \right) = \left( \frac{200W}{9180W} \right) = 0.0218$$

## d) the mechanical power developed in watts

$$P_m = P_g - P_{Cu2} = 9180W - 200 = 8,980W$$

## e) the horsepower output

$$P_o = P_m - P_{rot} = 8,980W - 100W = 8,880W = 12.00 \text{ hp}$$

**f) the motor speed in rpm and radiands/second**

$$n = (1 - s)n_s = (1 - 0.0218)377 \text{ rad/aec}$$

$$n = 368.78 \text{ rad/sec} = 3,521 \text{ rpm}$$

**g) the torque at the output shaft**

$$T_o = \frac{P_o}{n} = \frac{8880W}{368.78 \text{ rad/sec}} = 24.08Nm$$

**h) the torque needed to overcome rotational losses**

$$T_{rot} = \frac{P_{rot}}{n} = \frac{100W}{377 \text{ rad/sec}}$$

$$T_{rot} = 0.2653 Nm$$

**i) the efficiency of the operation in the stated conditions**

$$\eta = \frac{P_o}{P_{elec}} = \frac{8880W}{9720W} = 0.9136$$

2) A three-phase, two pole, 20hp, 120V<sub>LN</sub>, 60Hz, Y connected induction motor has the following parameters per phase:

- $r_1 = 0.15 \text{ Ohm}$ ,  $x_1 = 0.25 \text{ Ohms}$
- $r_2 = 0.10 \text{ Ohms}$   $x_2 = 0.30 \text{ Ohms}$

The stator core losses are 400W and the rotational losses are 200W. At no-load, the motor draws 10A with a power factor of 0.1 lagging. When the motor operates at a slip of 3%, find

First, find the currents:

```
-->V1 = 120;

-->Im = 10.0 * exp(-j*84.26*pi/180)

1.0001441 - 9.9498599i

-->Rm = r2 * (1-s) / s

3.2333333

-->I2 = V1 / (r1 + r2 + Rm + j*(x1+x2) )

33.611794 - 5.3071253i

-->I1 = Im + I2

34.611938 - 15.256985i
```

Synchronous and actual speed:

```
-->ws = 2*pi*60;

-->w = (1-s)*ws;
```

Power across the air gap:

```
-->Pg = 3 * (abs(I2))^2 * r2/s

11579.182

-->Tg = Pg / w

31.664676

-->Pm = 3 * (abs(I2))^2 * Rm

11231.807

-->Prot = 200 * (w / 377)
Prot =

193.99543

-->Po = Pm - Prot

11037.812
```

$$\rightarrow T_o = P_o / \omega$$

$$30.184232$$

$$\rightarrow P_e = \text{real}(3 \cdot V_1 \cdot I_1)$$

$$P_e =$$

$$12460.298$$

$$\rightarrow \text{eff} = P_o / P_e$$

$$0.8858385$$

## Checking

$$\rightarrow [T_o, P_o, \text{eff}] = \text{slip}(0.03, 0.1)$$

$$\text{eff} =$$

$$0.8858385$$

$$P_o =$$

$$11037.812$$

$$T_o =$$

$$30.184232$$

## a) the input line current and power factor

$$V_1 = 120V_{LN}$$

$$I_1 = I_m + I_2$$

$$I_m = 10 \angle -84.26^\circ$$

$$R_m = r_2 \left( \frac{1-s}{s} \right) = (0.1 \Omega) \left( \frac{1-0.03}{0.03} \right) = 3.2333 \Omega$$

$$I_2 = \frac{120V}{3.2333 \Omega + (0.15 + j0.25) + (0.1 + j0.3)} = 34.03 \angle -8.97^\circ$$

so

$$I_1 = I_m + I_2 = 37.828 \angle -23.787^\circ$$

$$\text{power factor} = 0.915 \text{ lagging}$$

## b) the developed electromagnetic torque in Nm

$$n_s = 2\pi \cdot 60 \text{ Hz} = 377 \text{ rad/sec}$$

$$n = (1-s)n_s = 365.69 \text{ rad/sec}$$

$$P_m = 3 \cdot |I_2|^2 R_m = 7488 \text{ W}$$

$$T_m = \frac{P_m}{n} = \frac{7488 \text{ W}}{365.69 \text{ rad/sec}} = 20.478 \text{ Nm}$$

**c) the horsepower output**

$$P_o = P_m - P_{rot}$$

$$P_o = 7488W - 200W = 7288W$$

$$P_o = 9.848Hp$$

**d) the efficiency**

$$P_{elec} = 3 \cdot \text{real}(V_1 \cdot I_1^*)$$

$$P_{elec} = 3 \cdot 120V \cdot 37.828A \cdot \cos(-23.787^\circ)$$

$$P_{elec} = 12.461W$$

$$\eta = \frac{P_o}{P_{elec}} = \frac{7,288W}{12,461W} = 0.585$$

Note: Write a SciLab routine for this:

```
function [To, Po, eff] = slip(s, r2)

j = sqrt(-1);

r1 = 0.15;
r2 = 0.10;
x1 = 0.25;
x2 = 0.30;

Pc = 400; // stator core losses
Prot = 200; // rotational losses

V1 = 120;
Im = 10.0 * exp(-j*84.26*pi/180);

Rm = r2 * (1-s) / s;
I2 = V1 / (r1 + r2 + Rm + j*(x1+x2) );

I1 = Im + I2;

ws = 2*pi*60;
w = (1-s)*ws;

Pg = 3 * (abs(I2))^2 * r2/s;
Tg = Pg / w;

Pm = 3 * (abs(I2))^2 * Rm;
Prot = 200 * (w / 377);

Po = Pm - Prot;
To = Po / w;

Pe = real(3*V1 * I1);

eff = 0;
if (s > 0) eff = Po / Pe; end
if (s < 0) eff = Pe / Po; end

endfunction
```

## Checking

```
-->[To, Po, eff] = slip(0.03,0.1)
eff =


    0.8858385
Po =

    11037.812
To =

    30.184232
```

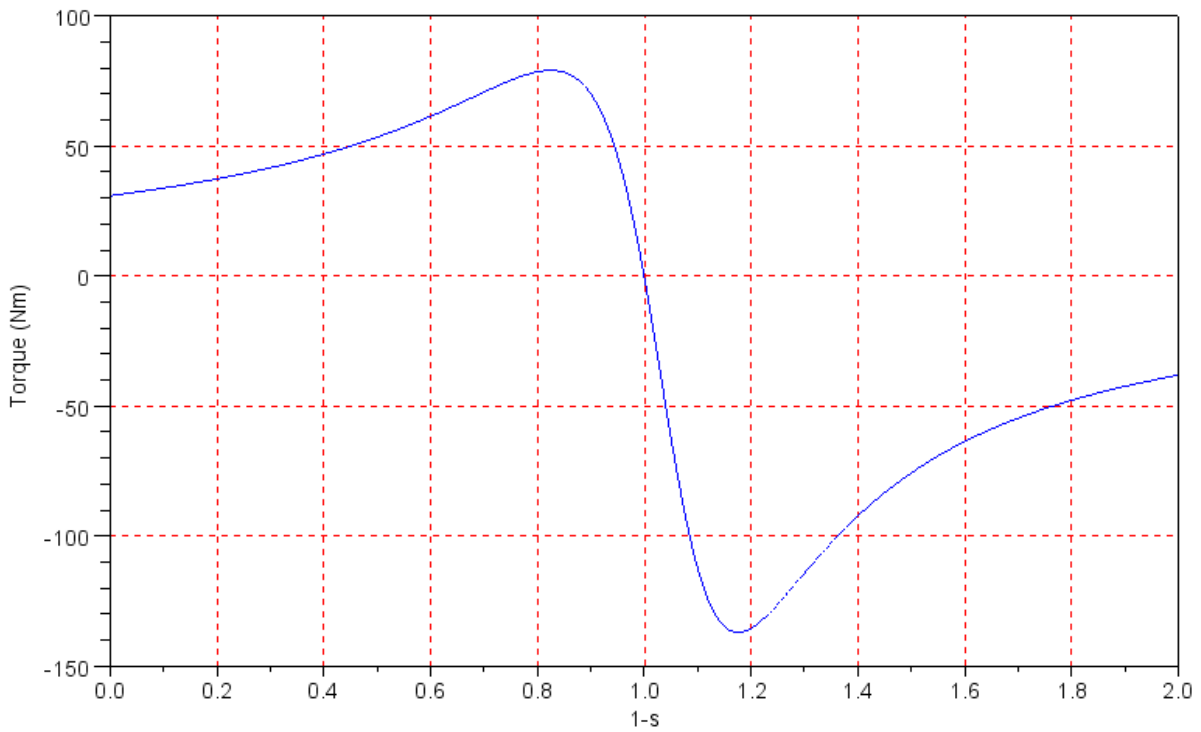3) Plot the torque-slip speed relationship for the motor in problem 2.


```
T = 0*s;  
P = 0*s;  
eff = 0*s;  
  
s = [-0.999:0.001:0.999]' + 1e-6;  
  
for i=1:length(s)  
    [T(i),P(i),eff(i)] = slip(s(i), 0.1);  
end  
  
plot(1-s,T)  
xlabel('1-s')  
ylabel('Torque (Nm)')  
xgrid(5)
```



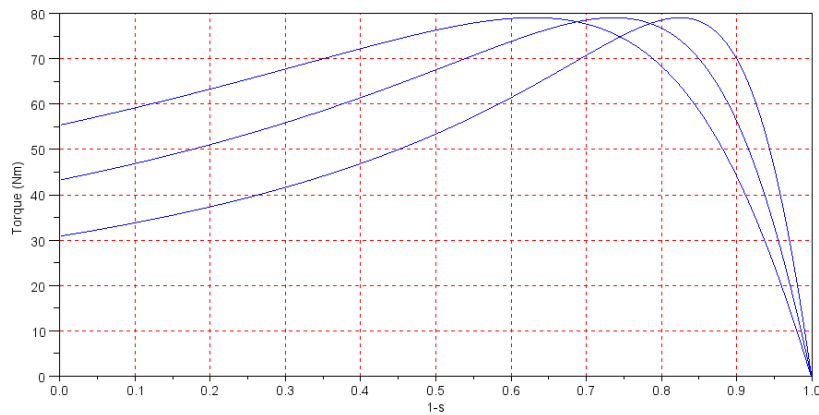4) Find  $r_2$  so that the starting torque is 70% of the peak torque.

Using trial and error

```
T = 0*s;  
P = 0*s;  
eff = 0*s;  
  
s = [0.001:0.001:0.999]';  
  
for i=1:length(s)  
    [T(i),P(i),eff(i)] = slip(s(i), 0.2112);  
end  
  
plot(1-s,T)  
xlabel('1-s')  
ylabel('Torque (Nm)')  
xgrid(5)  
  
T(999) / max(T)
```



$r_2 = 0.1$  (bottom curve),  $0.15$ ,  $0.2112$  (top curve)

Starting torque = 70% of the peak torque for  $r_2 = 0.2112$  Ohms

$r_2$	%
0.1	39%