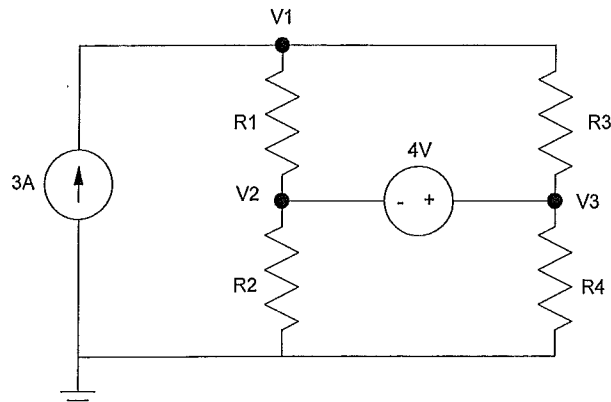


ECE 331 Test 1: Name _____

February 5, 2014. Magnetic Circuits

1) KVN. Write 3 equations to solve for the 3 unknown voltages




$$-3 + \frac{V_1 - V_2}{R_1} + \frac{V_1 - V_3}{R_3} = 0$$

$$V_3 - V_2 = 4$$

$$\frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3 - V_1}{R_3} + \frac{V_3}{R_4} = 0$$

Super-node

2) Determine the impedance, Z_{in} :

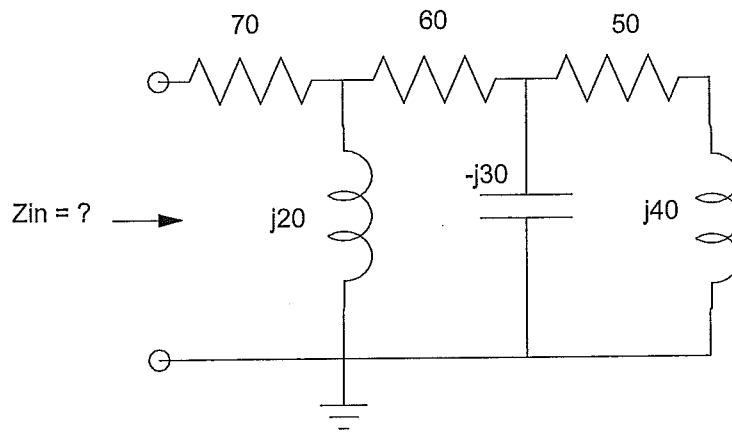

$Z_{in} =$	$75 + j20.8$
------------	--------------

$$\begin{aligned}
 &= 50 + j40 && 4 \\
 (50 + j40) \parallel (-j30) &= 17.30 - j33.46 && 4 \\
 +60 &= 77.3 - j33.4 && 4 \\
 \parallel j20 &= 5.02 + j20.8 && 4 \\
 +70 &= 75 + j20.8 && 4
 \end{aligned}$$


3) Assume the input to the following circuit is a 120V rms sine wave at 60Hz (377 rad/sec).

3a) Determine the phasor impedances for the two inductors,

0.1H	0.3H
$j37.7$	$j113.1$

3b) Determine the current, I_n , in phasor notation

I_n (rms)
$3.92 \angle -68^\circ$

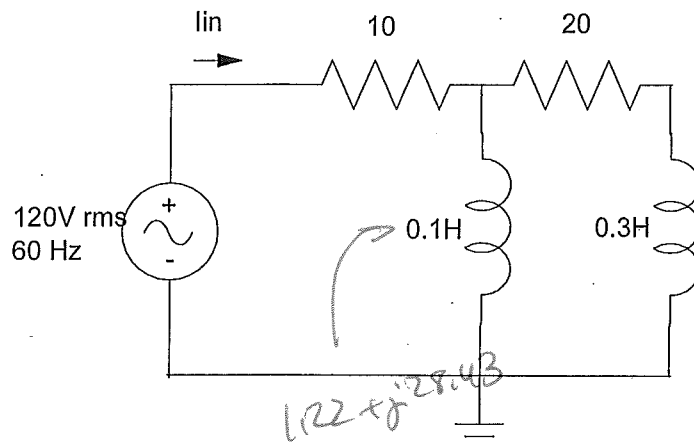

$$Z = 11.22 + j28.43 \quad (10)$$

$$I = 1.44 - j3.65$$

$$= 3.92 \angle -68^\circ \quad (5)$$

-1.18 radians

4) Determine the complex impedance as well as a series and parallel RL circuit to model a load with the following characteristics:


- $V_L = 120V$ rms
- $I_L = 6A$ rms
- Power 100 Watts

Impedance: Z_L	$20 \angle 82.01^\circ$ 1.43rad
Series Resistance: R_s	2.78
Series Reactance: jX_s	$j19.8$
Parallel Resistance: R_p	143
Parallel Reactance: jX_p	$j20.19$

$$pf = \frac{100}{120.6} = 0.8388$$

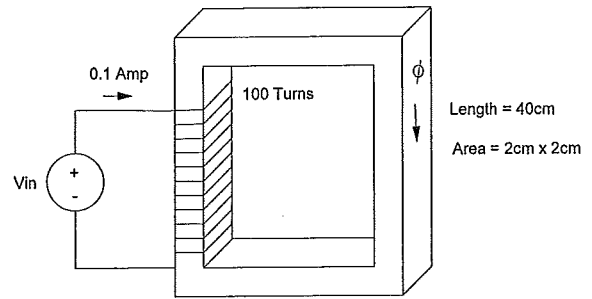5) An inductor is composed of an iron core with

- A cross sectional area of 2cm x 2cm.
- A total length around the inductor of 40cm
- A relative permittivity of 5000
- A saturation of B = 2 Teslas



Note:

$$\phi = \frac{F}{R} \quad \text{Flux (Webers)}$$

$$F = NI \quad \text{MMF (amp-turns)}$$

$$R = \frac{\text{length}}{\mu_r \mu_0 \text{Area}} \quad \text{Reluctance } (\mu_0 = 4\pi \cdot 10^{-7})$$

$$B = \frac{\phi}{\text{Area}} \quad \text{Flux Density (Webers) } \quad \text{Teslas}$$

5a) Determine the reluctance of the iron core, the flux (ϕ) in Webers, and the flux density, B, in Teslas.

Reluctance (R)	$= \frac{.4m}{(5000)(4\pi \cdot 10^{-7})(.02)(.02)} = 159,154$
Flux (Webers)	62.8 μ Wb
Flux Density (Teslas)	.157 Teslas

5b) If the frequency of the input is increased, will the flux density (B) go up or down? Why?

flux goes down

the impedance

the current = $\frac{V}{jX}$ goes down

flux is proportional to current

