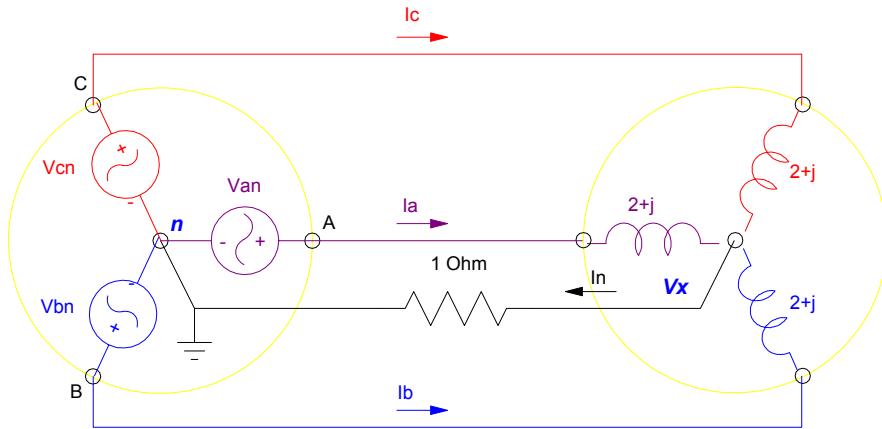


Analysis of 3-Phase Loads

Y Source, Y Load, Balanced Load



Define the voltages and impedances:

```
-->Va = 120;
-->Vb = 120 * exp(-j*120*%pi/180);
-->Vc = 120 * exp(-j*240*%pi/180);

-->Za = 2 + j;
-->Zb = 2 + j;
-->Zc = 2 + j;
```

Here you have just one unknown: V_n . Write one equation to solve for one unknown.

```
-->Vx = (Va/Za + Vb/Zb + Vc/Zc) / (1/Za + 1/Zb + 1/Zc + 1)

Vx = 0
```

Note: With a balanced load, the three phase voltages sum to zero. Solving for the line currents:

```
-->Ia = (Va - Vn) / Za;
-->Ib = (Vb - Vn) / Zb;
-->Ic = (Vc - Vn) / Zc;
-->In = Vn / 1;

-->I = [Ia; Ib; Ic; In];
-->[abs(I), atan(imag(I), real(I))*180/%pi]
```


	Amps	degrees
Ia	53.665631	-26.565051
Ib	53.665631	-146.56505
Ic	53.665631	93.434949
In	0.000000	-164.74488

Note: With a balanced load, the three phase currents sum to zero. You can get the same result using per-phase analysis:

$$I_a = \frac{V_{an}}{Z_a} = 53.665 \angle -26.565^0$$

Y Source, Y Load, Unbalanced Load

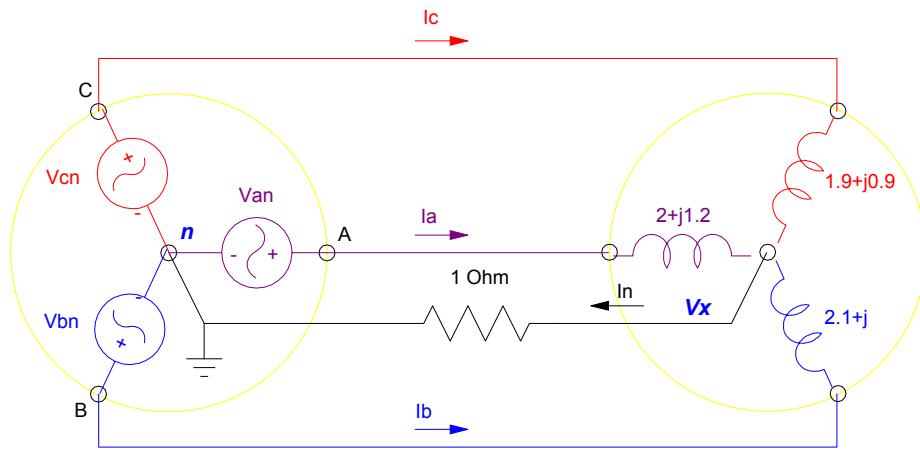If the load is not balanced, you can't use per-phase analysis. Circuits I and II techniques always work, however. Just use voltage nodes.



```
-->Va = 120;
-->Vb = 120 * exp(-j*120*%pi/180);
-->Vc = 120 * exp(-j*240*%pi/180);

-->Za = 2 + j*1.2;
-->Zb = 2.1 + j;
-->Zc = 1.9 + j*0.9;
```

With only one unknown (V_n), write one equation for one unknown:

$$-->Vx = (Va/Za + Vb/Zb + Vc/Zc) / (1/Za + 1/Zb + 1/Zc + 1)$$

$$- 1.4176461 + 0.1403446i$$

Note that the voltage at the load's ground is no longer 0V.

```
-->Ia = (Va - Vn) / Za;
-->Ib = (Vb - Vn) / Zb;
-->Ic = (Vc - Vn) / Zc;
-->In = Vn / 1;


-->I = [Ia; Ib; Ic; In];

-->[ abs(I), atan(imag(I), real(I))*180/%pi]

          Amps      degrees
Ia      52.057421   -31.029984
Ib      51.34257    -144.84063
Ic      56.685889    94.097303
In      1.4245761   174.34623
```

Note also that unbalanced loads result in currents that don't sum to zero. You have current on the ground line.

Delta Source, Y Load, Balanced Load

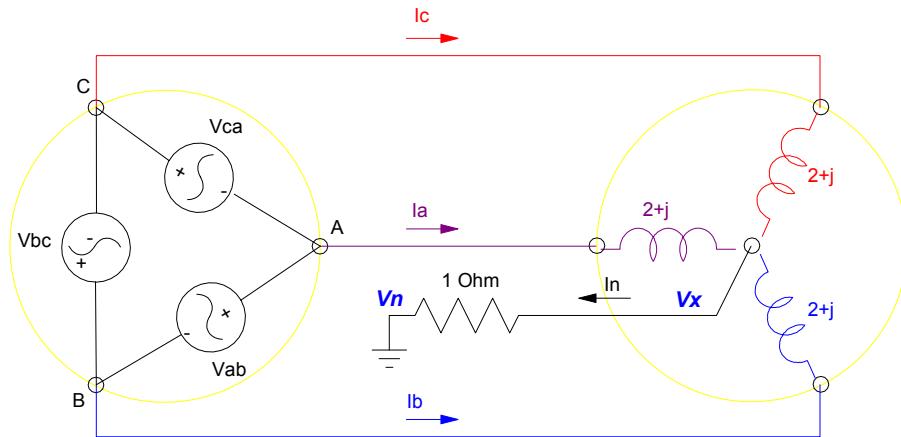

Define the voltages and impedances:

```
-->Vab = 120;
-->Vbc = 120 * exp(-j*120*pi/180);
-->Vca = 120 * exp(-j*240*pi/180);

-->Za = 2 + j;
-->Zb = 2 + j;
-->Zc = 2 + j;
```

With 4 unknown voltages, write voltage node equations to solve for 4 unknowns:

$$A \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_x \end{bmatrix} = B$$

Writing the voltage node equations:

```
-->A = [1, -1, 0, 0; 0, 1, -1, 0; -1, 0, 1, 0; -1/za, -1/zb, -1/zc,
1/za+1/zb+1/zc+1]

1.          - 1.          0          0
0           1.          - 1.          0
- 1.          0           1.          0
- 0.4 + 0.2i - 0.4 + 0.2i - 0.4 + 0.2i   2.2 - 0.6i

-->B = [Vab; Vbc; Vca; 0]

120.
- 60. - 103.92305i
- 60. + 103.92305i
0
```


Solving

```
-->V = inv(A)*B;
!--error 19
Problem is singular.
```

The A-matrix is singular - meaning the three transformers are redundant.

Delta Source, Y Load, Balanced Load

(take 2)

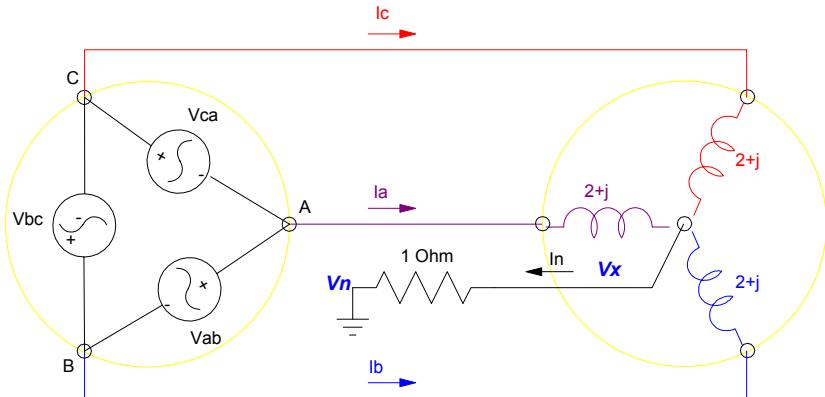

One way to fix the problem is to replace one transformer equation with

$$V_a + V_b + V_c = 0$$

```
-->A = [1, 1, 1, 0; 0, 1, -1, 0; -1, 0, 1, 0; -1/z_a, -1/z_b, -1/z_c,
1/z_a+1/z_b+1/z_c+1]
```

$$\begin{array}{cccc} 1. & 1. & 1. & 0 \\ 0 & 1. & -1. & 0 \\ -1. & 0 & 1. & 0 \\ -0.4 + 0.2i & -0.4 + 0.2i & -0.4 + 0.2i & 2.2 - 0.6i \end{array}$$

```
-->B = [0; Vbc; Vca; 0]
```

$$\begin{array}{l} 0 \\ -60. - 103.92305i \\ -60. + 103.92305i \\ 0 \end{array}$$

Solving for the line voltages:

```
-->V = inv(A)*B;
-->[ abs(V), atan(imag(V),real(V))*180/%pi ]
```

	Volts	degrees
V_a	69.282032	-30.
V_b	69.282032	-150.
V_c	69.282032	90.
V_x	0.	0.

Delta configuration is just like Y configuration, except

- The line-to-line voltages are $\sqrt{3}$ times larger than the line-to-neutral voltages, and
- There is a 30 degree phase shift between V_{an} and V_{bn} .

Solving for the line currents:


```
-->Ia = (Va - Vn) / Za;
-->Ib = (Vb - Vn) / Zb;
-->Ic = (Vc - Vn) / Zc;
-->In = Vn / 1;

-->I = [Ia; Ib; Ic; In];
-->[ abs(I), atan(imag(I),real(I))*180/%pi ]
```

Ia	30.983867	-56.565051
Ib	30.983867	-176.56505
Ic	30.983867	63.434949
In	0.	0.

With a balanced load, delta configuration still winds up with no current on the neutral line.

Delta Source, Y Load, Unbalanced Load

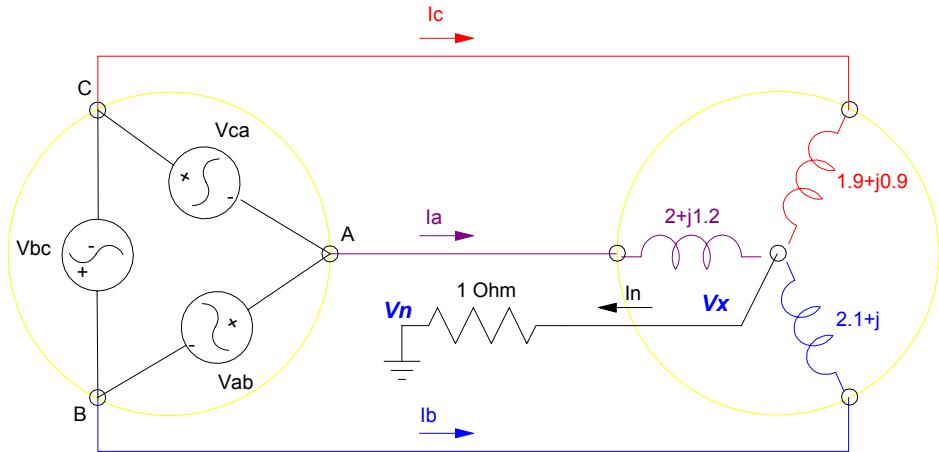

Define the voltages and impedances:

```
-->Vab = 120;
-->Vbc = 120 * exp(-j*120*pi/180);
-->Vca = 120 * exp(-j*240*pi/180);

-->Za = 2 + j;
-->Zb = 1.9 + j*1.1;
-->Zc = 2.1 + j*0.9;
```

Write 4 equations for 4 unknowns as

$$A \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_x \end{bmatrix} = B$$

```
-->A = [1, 1, 1, 0; 0, 1, -1, 0; -1, 0, 1, 0; -1/Za, -1/Zb, -1/Zc,
1/Za+1/Zb+1/Zc+1]
```

$$\begin{array}{cccc} 1. & 1. & 1. & 0 \\ 0 & 1. & -1. & 0 \\ -1. & 0 & 1. & 0 \\ -0.4 + 0.2i & -0.394 + 0.228i & -0.402 + 0.172i & 2.196 - 0.600i \end{array}$$

```
-->B = [0; Vbc; Vca; 0]
```

$$\begin{array}{c} 0 \\ -60. - 103.92305i \\ -60. + 103.92305i \\ 0 \end{array}$$

Solving:

```
-->V = inv(A) *B;  
-->[abs(V), atan(imag(V),real(V))*180/%pi]
```

	Volts	Degrees
Va	69.282032	-30.
Vb	69.282032	-150.
Vc	69.282032	90.
Vx	1.4343974	156.34116

Note that with an unbalanced load, the voltages don't sum to zero.

Solving for the line currents:

```
-->Va = V(1);  
-->Vb = V(2);  
-->Vc = V(3);  
-->Vx = V(4);  
  
-->Ia = (Va - Vx) / Za;  
-->Ib = (Vb - Vx) / Zb;  
-->Ic = (Vc - Vx) / Zc;  
-->In = Vx / 1;  
  
-->I = [Ia; Ib; Ic; In];  
  
-->[abs(I), atan(imag(I),real(I))*180/%pi]
```

	Amps	Degrees
Ia	31.621503	- 56.436675
Ib	31.174373	- 179.10129
Ic	30.077482	65.705905
In	1.4343974	156.34116

Note that with an unbalanced load, there is current on the neutral line