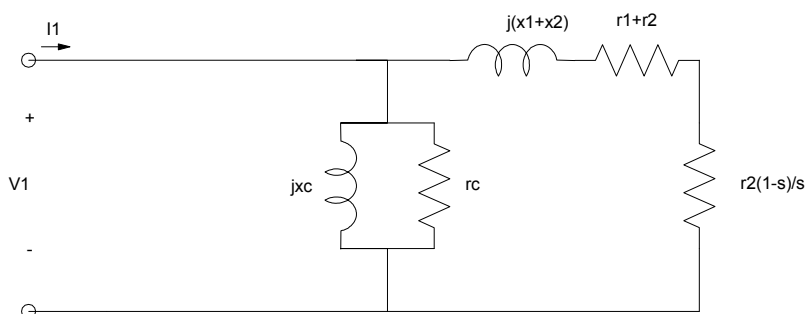


Testing Induction Motors

Problem: Determine the parameters for a 3-phase induction motor experimentally.



Per-phase model for a 3-phase induction motor. $R_m = r_2 \left(\frac{1-s}{s} \right)$

Solution: An induction is essentially an N:1 transformer.

- The stator (primary side) sees 60Hz like it or not (it's connected to the power grid) ($r_1 + jx_1$)
- The rotor (secondary side) sees a frequency related to the slip speed: $f = s \cdot 60\text{Hz}$

Just like a transformer you use a no-load and short-circuit test

No-Load Test: Let the motor spin freely with no load. The slip speed should be close to zero. Measure V_{in} , I_{in} , P_{in} to compute a parallel RL model for the core.

Short-Circuit Test (Locked Rotor Test): Lock the rotor. Apply a smaller voltage to the motor and measure V_{in} , I_{in} , P_{in} to compute the series RL model for the copper: $r_1 + r_2 + j(x_1 + x_2)$

DC Test: You really need to know r_2 to model the transformer. You can't measure r_2 directly since it's in the rotor and not electrically connected to anything at DC. You can measure the DC resistance of the stator, however. This tells you r_1 , which in turns lets you find r_2 .

Example: Typical numbers from the lab are:

No-Load Test:

- $V_{LL} = 100.41\text{V}$
- $I_L = 0.29\text{A}$
- $P_{total} = 18.47\text{W}$

The model is a per-phase model, so convert everything to line-to-neutral

$$V_{LN} = \frac{100.41V}{\sqrt{3}} = 57.97V$$

The core impedance is

$$Z_c = \frac{57.97V}{0.29A} = 199.9\Omega$$

The power factor is

$$pf = \frac{18.47W}{3 \cdot 57.97V \cdot 0.29A} = 0.3662$$

(the 3 comes from the power out being mechanical (total) power. The power in has a '3' since this is a 3-phase circuit and V and I are per-phase.) The total core impedance is then

$$Z_c = 199.9 \angle 68.517^\circ$$

The parallel RL model for the core is then

$$Z_c = 545.8\Omega \parallel j214.8\Omega$$

Note: The no-load test has the motor running at full speed. The 545.8 Ohms lumps the rotational, eddy, and hysteresis losses all together. You can

- Include 545.8 Ohms in the core and say the rotational losses are zero, or
- Exclude the 545.8 Ohms in the core and say the rotational losses are 18.47W.

Just don't do both.

Locked Rotor Test: (slip = 1. Also same as the short-circuit test for a transformer)

Lock the rotor, reduce the input voltage, and measure the voltage, current, and power. This tells you the windings:

Data:

- $V_{LL} = 32.13V$
- $I_L = 0.38A$
- $P_{total} = 8.82W$

Like before, find the impedance.

$$V_{LN} = \frac{32.13}{\sqrt{3}} = 18.55V$$

$$Z_{cu} = \frac{18.55V}{0.38A} = 48.816\Omega$$

The power factor is

$$pf = \frac{8.82W}{3 \cdot 18.55V \cdot 0.38A} = 0.4171$$

so

$$Z_{cu} = 48.816 \angle 65.35^\circ$$

or in rectangular form

$$Z_{Cu} = 20.36 + j44.36$$

$$R1 + R2 = 20.36$$

$$jX1 + jX2 = j44.36$$

It doesn't really matter how the $j44.36$ Ohms is allocated to $jX1$ and $jX2$. Just for simplicity, half is assigned to each term:

$$jX1 = jX2 = 22.1837$$

It *does* matter how the resistance is allocated to $R1$ and $R2$, however since $R2$ determines R_m . To separate these terms, measure the DC resistance of the stator. This tells you $R1$

DC Test:

- The DC resistance line-to-line is 24.709 Ohms..

This actually measures $2R1$ since it is the resistance from one line to the other. Hence

$$R1 = 12.3547 \text{ Ohms}$$

and

$$R2 = 20.36 - 12.35 = 8.01 \text{ Ohms}$$