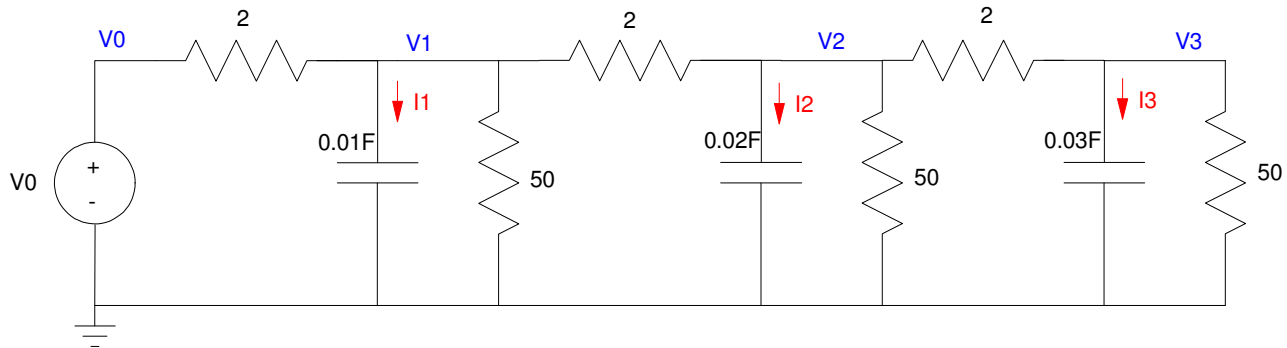


ECE 343 - Homework #16

Circuit Analysis using LaPlace Transforms - Summer 2018

Problem 1 -3) Assume $V_o(t) = 0$.



Problem 1: Assume $v_1(0) = v_2(0) = v_3(0) = 10V$.

- Write the dynamics for this system (i.e. the voltage node equations using LaPlace notation)
- Place in matrix form
- Find $v_3(t)$ (Matlab graph of v_3 vs. time)


Problem 2: Assume $v_3(0) = 10$.

- What initial conditions on $v_1(0)$ and $v_2(0)$ result in $v_3(t)$ decaying as slow as possible?
- Find $V_3(t)$ for these initial conditions.

Problem 3: Assume $v_3(0) = 10$.

- What initial conditions on $v_1(0)$ and $v_2(0)$ result in $v_3(t)$ decaying as fast as possible?
- Find $v_3(t)$ for these initial conditions.

Problem 4-6: Assume $v_{in}(t) = 0$.

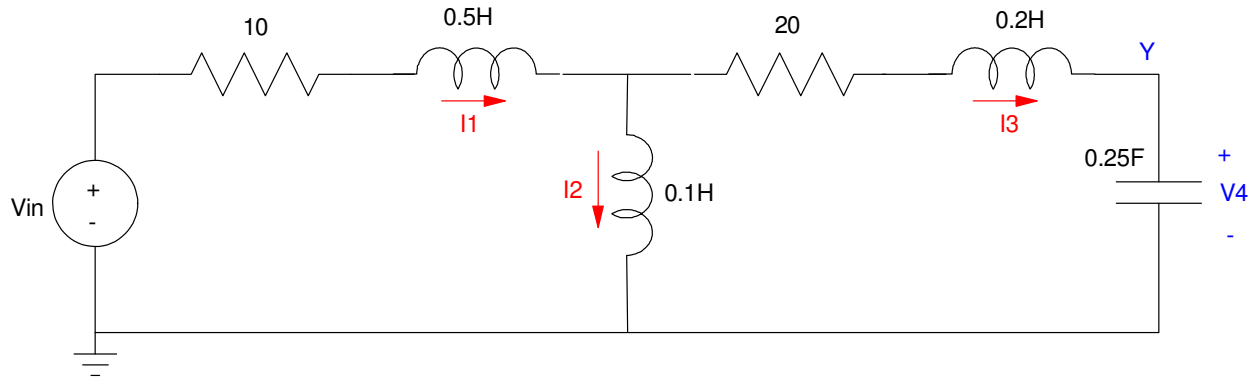

Problem 4: Assume

- $i_1(0) = i_2(0) = i_3(0) = 2A$.
- $v_4(0) = 10V$.

i) Write the dynamics for this system (i.e. the voltage node equations using LaPlace notation)

ii) Place in matrix form

iii) Find $v_4(t)$ (Matlab graph of v_4 vs. time)

Problem 5: Assume $v_4(0) = 10$.

- What initial conditions on $i_1(0)$, $i_2(0)$, and $i_3(0)$ result in $v_4(t)$ decaying as slow as possible?
- Find $v_4(t)$ for these initial conditions.

Problem 6: Assume $v_4(0) = 10$.

- What initial conditions on $i_1(0)$, $i_2(0)$, and $i_3(0)$ result in $v_4(t)$ decaying as fast as possible?
- Find $v_4(t)$ for these initial conditions.